

Special Singularity Integrals
Encountered
in Electric Circuits

Aziz S. Inan & Peter M. Osterberg
School of Engineering
University of Portland

ISCAS 2005 (Kobe, Japan)

Impulse Function:

$$\mathbf{d}(t) = 0 \quad \text{for } t \neq 0$$

and

$$\int_{-\infty}^{\infty} \mathbf{d}(t) dt = \int_{0^-}^{0^+} \mathbf{d}(t) dt = 1.$$

$\mathbf{d}(0)$ is undefined.

Unit Step Function:

$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0. \end{cases}$$

$u(0)$ is undefined.

Impulse-Step Relationship:

$$\mathbf{d}(t) = \frac{du(t)}{dt}$$

or

$$u(t) = \int_{-\infty}^t \mathbf{d}(t) dt$$

Doublet-Impulse Relationship:

$$\mathbf{d}'(t) = \frac{d\mathbf{d}(t)}{dt}$$

or

$$\mathbf{d}(t) = \int_{-\infty}^t \mathbf{d}'(t) dt.$$

Special Singularity Integral # 1
Involving $d(t)$ and $u(t)$ Product:

$$\int_{0^-}^{0^+} u(t) \underbrace{d(t)}_{du(t)} = \int_{u(0^-)}^{u(0^+)} u(t) du(t)$$
$$= \frac{u^2(t)}{2} \Big|_{u(0^-)}^{u(0^+)} = \frac{1-0}{2} = \frac{1}{2}.$$

Special Singularity Integral # 2
Involving $d(t)$ and $d'(t)$ Product:

$$\int_{0^-}^{0^+} \mathbf{d}(t) \underbrace{\mathbf{d}'(t) dt}_{d\mathbf{d}(t)} = \int_{d(0^-)}^{d(0^+)} \mathbf{d}(t) d\mathbf{d}(t)$$
$$= \frac{\mathbf{d}^2(t)}{2} \Bigg|_{d(0^-)}^{d(0^+)} = \frac{0 - 0}{2} = 0.$$

Special Singularity Integral # 3:

$$\int_{0^-}^{0^+} \mathbf{d}^2(t) dt = \lim_{t \rightarrow 0} \int_{-t/2}^{t/2} \left(\frac{1}{\mathbf{t}^2} \right) dt$$
$$= \lim_{t \rightarrow 0} \frac{1}{\mathbf{t}} \rightarrow \infty.$$

Special Singularity Integral # 4:

$$\begin{aligned}\int_{0^-}^{0^+} u^2(t) dt &= \lim_{t \rightarrow 0} \int_{-t/2}^{t/2} \left(\frac{t + t/2}{t} \right)^2 dt \\ &= \lim_{t \rightarrow 0} \frac{(t + t/2)^3}{3t^2} \Bigg|_{-t/2}^{t/2} \\ &= \lim_{t \rightarrow 0} \frac{t}{3} = 0.\end{aligned}$$

Example # 1:

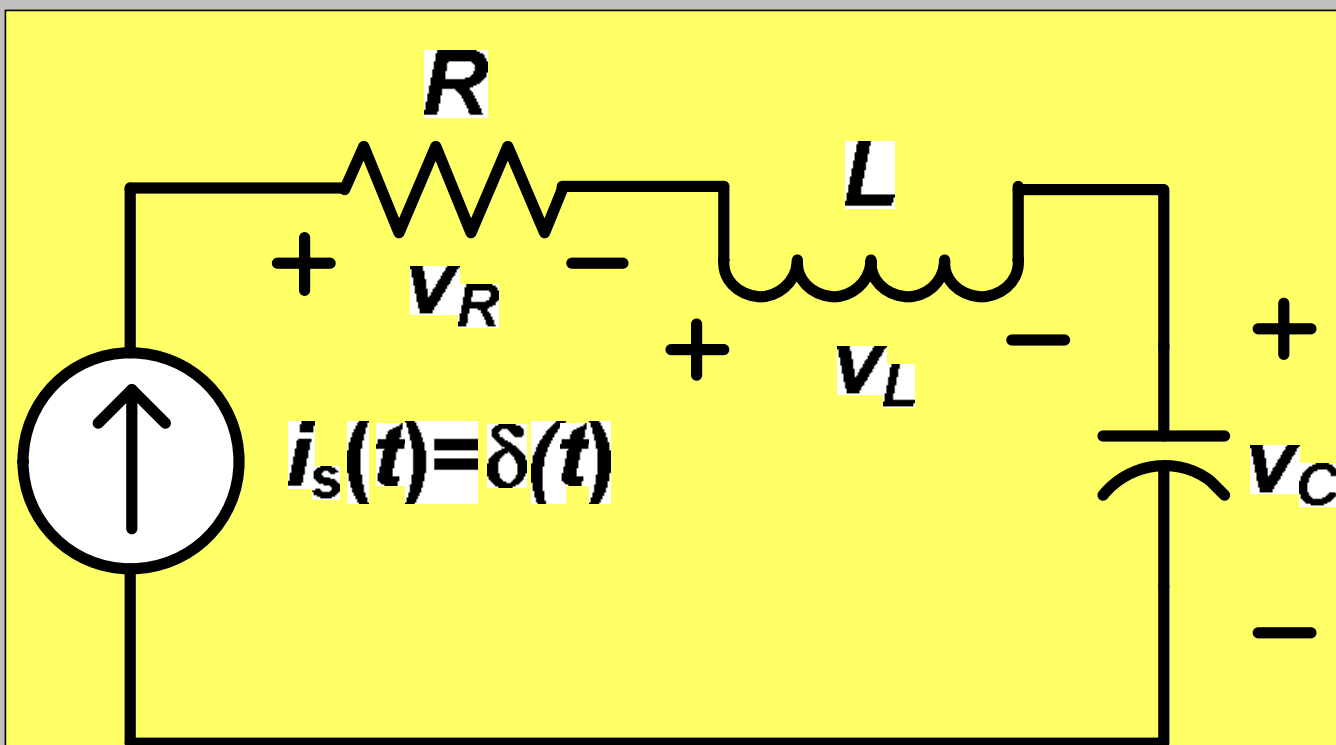


Fig. 1. Series RLC circuit excited by an impulse current source.

Voltage Across Each Element:

$$v_R(t) = Ri_S(t) = R\mathbf{d}(t)$$

$$v_L(t) = L \frac{di_S(t)}{dt} = L \frac{d\mathbf{d}(t)}{dt} = L\mathbf{d}'(t)$$

$$v_C(t) = \frac{1}{C} \int_{0^-}^t i_S(\mathbf{t}) d\mathbf{t} = \frac{1}{C} \int_{0^-}^t \mathbf{d}(\mathbf{t}) d\mathbf{t} = \frac{u(t)}{C}.$$


Energy of Each Element:

$$W_R = \int_{0^-}^{\infty} v_R(t) i_S(t) dt = R \int_{0^-}^{0^+} \mathbf{d}^2(t) dt = \infty$$

$$W_L = \int_{0^-}^{\infty} v_L(t) i_S(t) dt = L \int_{0^-}^{0^+} \mathbf{d}(t) \mathbf{d}'(t) dt = 0$$

$$W_C = \int_{0^-}^{\infty} v_C(t) i_S(t) dt = \frac{1}{C} \int_{0^-}^{0^+} u(t) \mathbf{d}(t) dt = \frac{1}{2C}.$$

Example # 2:

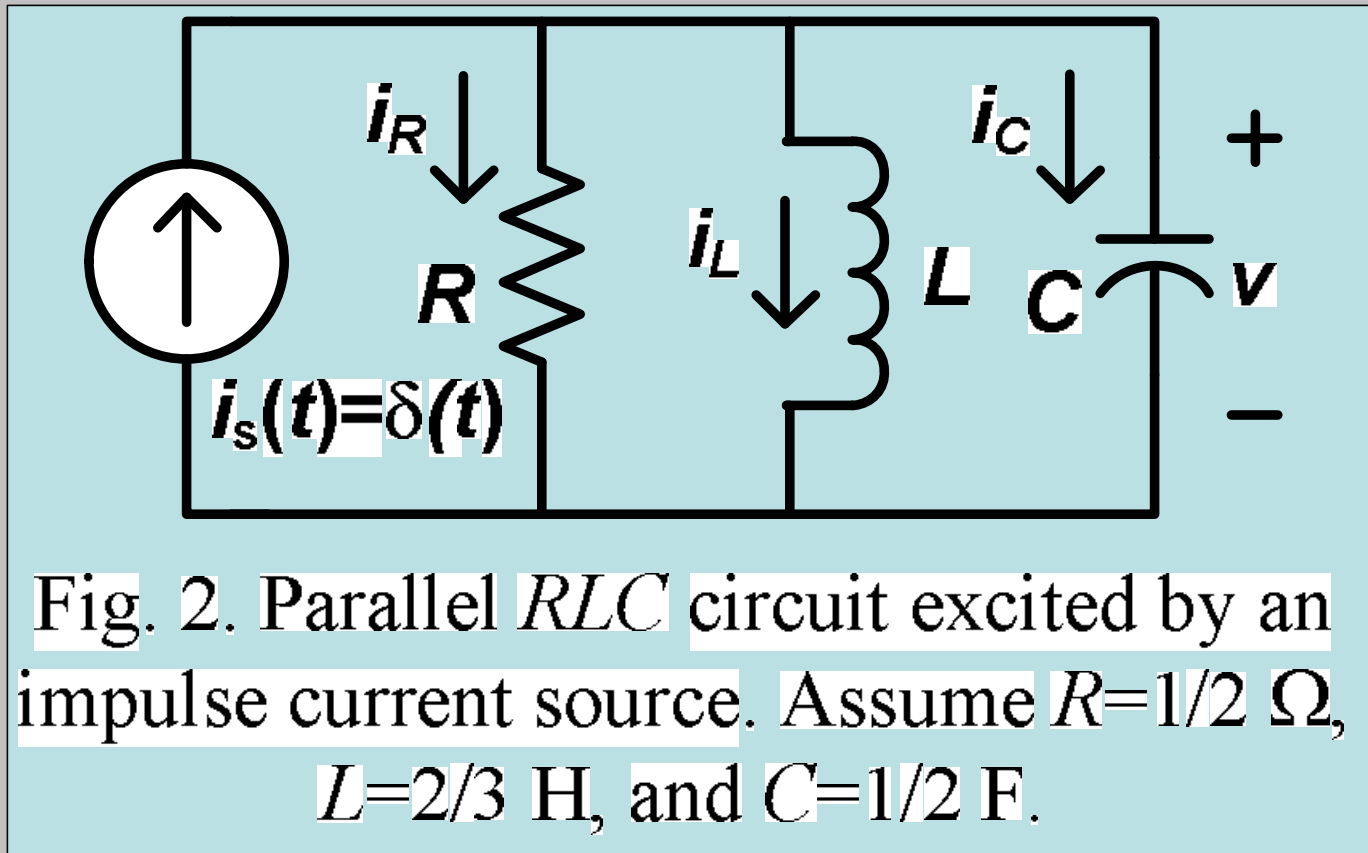

Governing Differential Equation:

$$\frac{d^2 v}{dt^2} + 4 \frac{dv}{dt} + 3v = 2d'(t).$$

Voltage of Each Element:

$$v(t) = \left(3e^{-3t} - e^{-t} \right) u(t).$$

Current of Each Element:

$$i_R(t) = \frac{v(t)}{R} = (6e^{-3t} - 2e^{-t})u(t)$$

$$i_L(t) = \frac{1}{L} \int_{0^-}^t v(t) dt = \left(\frac{3e^{-t}}{2} - \frac{3e^{-3t}}{2} \right) u(t)$$

$$i_C(t) = C \frac{dv(t)}{dt} = \left(-\frac{9e^{-3t}}{2} + \frac{e^{-t}}{2} \right) u(t) + \mathbf{d}(t).$$

Total Energy Dissipated in the Resistor:

$$\begin{aligned} W_R &= \int_{0^-}^{\infty} v(t) i_R(t) dt \\ &= \underbrace{\int_{0^-}^{0^+} 8u^2(t) dt}_0 + \underbrace{\int_{0^+}^{\infty} 2(3e^{-3t} - e^{-t})^2 dt}_1 = 1. \end{aligned}$$

Total Energy Stored in the Inductor:

$$\begin{aligned}W_L &= \int_{0^-}^{\infty} v(t) i_L(t) dt \\&= \underbrace{\int_{0^-}^{0^+} v(t) i_L(t) dt}_0 \\&\quad + \underbrace{\int_{0^+}^{\infty} \left(6e^{-4t} - \frac{3}{2}e^{-2t} - \frac{9}{2}e^{-6t} \right) dt}_0 = 0.\end{aligned}$$


Total Energy Stored in the Capacitor:

$$\begin{aligned}W_C &= \int_{0^-}^{\infty} v(t) i_C(t) dt \\&= \underbrace{\int_{0^-}^{0^+} 2[u(t) \mathbf{d}(t) - 4u^2(t)] dt}_1 \\&\quad + \underbrace{\int_{0^+}^{\infty} \left(6e^{-4t} - \frac{1}{2}e^{-2t} - \frac{27}{2}e^{-6t} \right) dt}_{-1} = 0.\end{aligned}$$

Conclusions:

- Four special singularity integrals and their proofs are provided;
- Applications of these integrals are demonstrated in two circuit examples;
- Coverage of these integrals in the educational literature is recommended.

Any
questions?

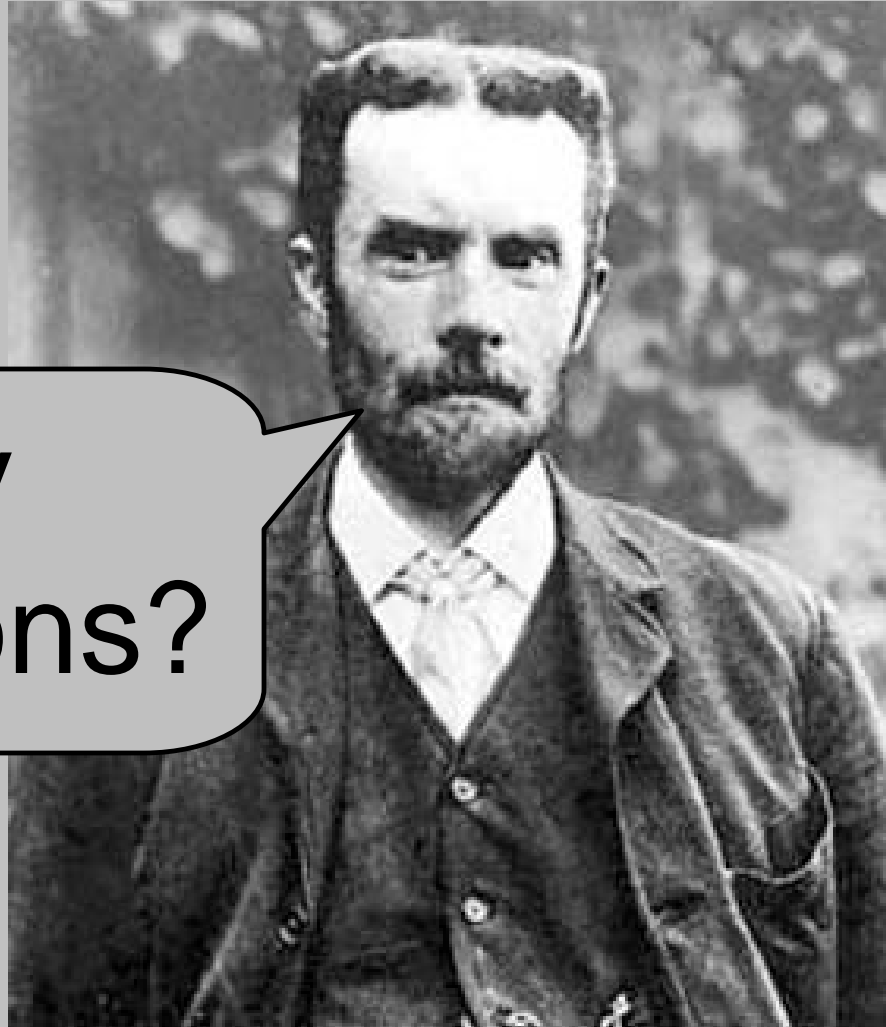

ISCAS 2005 (Kobe, Japan)