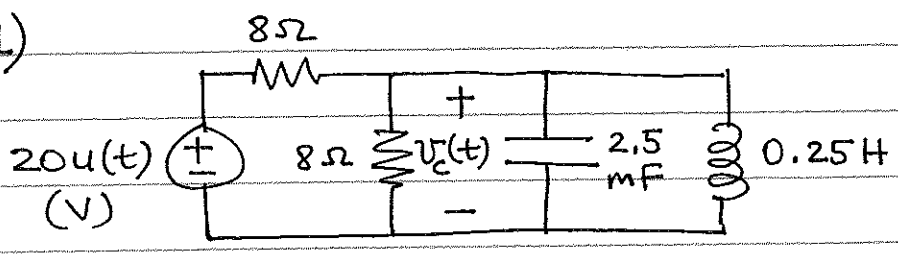


SECOND-ORDER RLC CIRCUITS
STEP EXCITATION PROBLEMS DONE DURING CLASS


(#1)




Find $v_c(t)$
 for $t \geq 0$.

Solution:

At $t=0^-$ (Steady state holds):

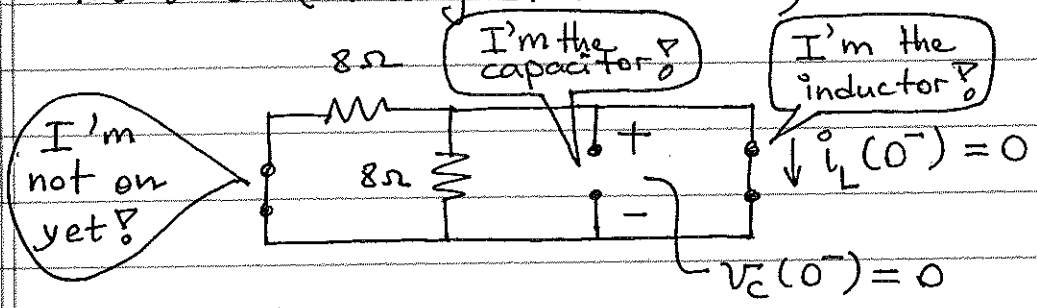

After $t=0$:

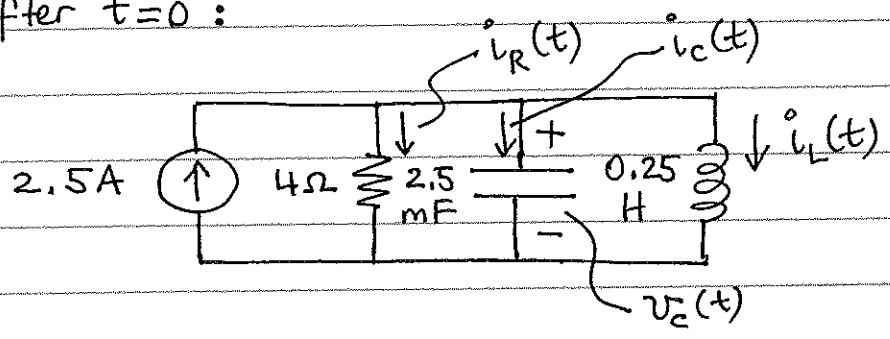

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \rightarrow \frac{s^2 + 100s + 1600}{(s+20)(s+80)} = 0$$

\therefore Overdamped response $\rightarrow v_c(t) = A_1 e^{-20t} + A_2 e^{-80t} + A_3$

$$v_c(0^+) = \boxed{A_1 + A_2 + A_3 = 0} \leftarrow (I)$$


Using KCL:

$$\begin{aligned} \dot{i}_L(t) &= 2.5 - \dot{i}_C(t) - \dot{i}_R(t) \\ &= 2.5 - C \frac{dv_C(t)}{dt} - \frac{v_C(t)}{R} \\ &= 2.5 - 2.5 \times 10^{-3} \left[-20A_1 e^{-20t} - 80A_2 e^{-80t} \right] \\ &\quad - \frac{[A_1 e^{-20t} + A_2 e^{-80t} + A_3]}{4} \end{aligned}$$

$$\begin{aligned} \therefore \dot{i}_L(0^+) &= 2.5 + \cancel{0.05A_1} + \cancel{0.2A_2} - \cancel{0.25A_1} - \cancel{0.25A_2} - 0.25A_3 \\ &= 2.5 - 0.2A_1 - 0.05A_2 - 0.25A_3 = 0 \end{aligned}$$

$$\text{or } \boxed{4A_1 + A_2 + 5A_3 = 50} \leftarrow \text{(II)}$$

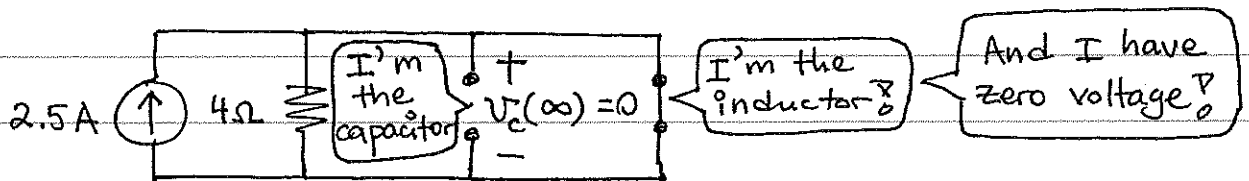
At $t \rightarrow \infty$ (steady state holds):



$$v_C(t \rightarrow \infty) = \boxed{A_3 = 0} \leftarrow \text{(III)}$$

Solving (I), (II) & (III) simultaneously yields:
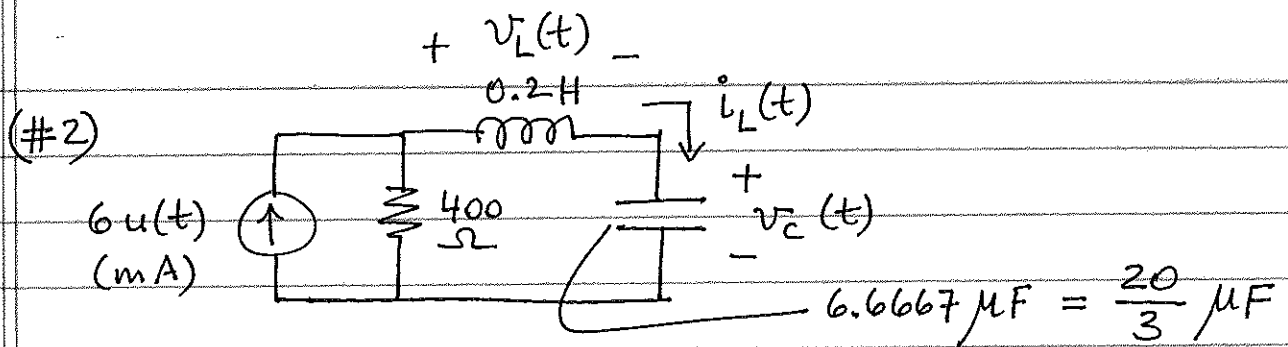
$$\boxed{v_C(t) = \frac{50}{3} e^{-20t} - \frac{50}{3} e^{-80t} \text{ (V)}, \text{ for } t \geq 0}$$




Given $v_c(0^-) = 2 \text{ V}$ & $i_L(0^-) = 8 \text{ mA}$, find

(a) $v_c(t)$ for $t \geq 0$

(b) $v_L(t)$ for $t > 0$

Solution: After $t=0$:

Using Norton
to Thevenin
transformations

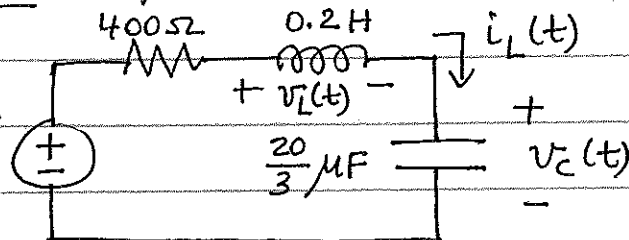

Second-order series RLC circuit, so using table:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \leftarrow \text{Characteristic equation}$$

$$s^2 + \frac{400}{0.2}s + \frac{1}{(0.2)(6.6667 \mu)} = 0 \rightarrow s^2 + 2000s + 750,000 = 0$$

$$\rightarrow (s+500)(s+1500) = 0 \rightarrow s_1, s_2 = -500, -1500$$

\therefore Overdamped response since real and different characteristic roots, therefore:

$$v_c(t) = A_1 e^{-500t} + A_2 e^{-1500t} + A_3$$

Using the first initial condition:

$$v_c(0^+) = \boxed{A_1 + A_2 + A_3 = 2} \quad \leftarrow \text{(I)}$$

4


$$i_L(t) = i_c(t) = C \frac{dv_c(t)}{dt} = \frac{20 \times 10^{-6}}{3} \left[-500A_1 e^{-500t} - 1500A_2 e^{-1500t} \right]$$

6.6667 MF

$$i_L(0^+) = \frac{20}{3} \times 10^{-6} \left[-500A_1 - 1500A_2 \right] = 8 \times 10^{-3}$$

$$\rightarrow \boxed{A_1 + 3A_2 = -12} \leftarrow \text{(II)}$$

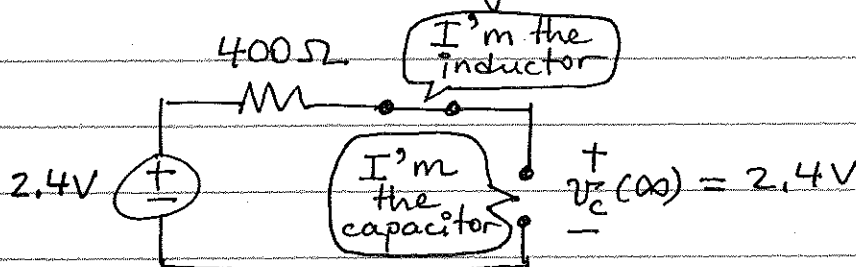At $t \rightarrow \infty$ (steady state holds):



$$v_c(t \rightarrow \infty) = \boxed{A_3 = 2.4V} \leftarrow \text{(III)}$$

Then, solving (I), (II) and (III) simultaneously:

$$\left. \begin{array}{l} A_1 + A_2 = -0.4 \\ A_1 + 3A_2 = -12 \end{array} \right\} \rightarrow A_1 = 5.4 \text{ \& } A_2 = -5.8$$

$$\therefore v_c(t) = 5.4 e^{-500t} - 5.8 e^{-1500t} + 2.4 \text{ (V), for } t \geq 0$$

Next, to find $v_L(t) = L \frac{di_L(t)}{dt}$ where $i_L(t) = i_c(t)$,

we first find $i_c(t) = C \frac{dv_c(t)}{dt}$:

$$i_c(t) = \frac{20}{3} \times 10^{-6} \left[-2700 e^{-500t} + 8700 e^{-1500t} \right]$$


$$i_c(t) = -0.018 e^{-500t} + 0.058 e^{-1500t} \quad (\text{A})$$

Next, we find $v_L(t) = L \frac{di_c(t)}{dt}$:


$$v_L(t) = 0.2 \left[9 e^{-500t} - 87 e^{-1500t} \right]$$

$$\therefore v_L(t) = 1.8 e^{-500t} - 17.4 e^{-1500t}, \text{ for } t > 0$$

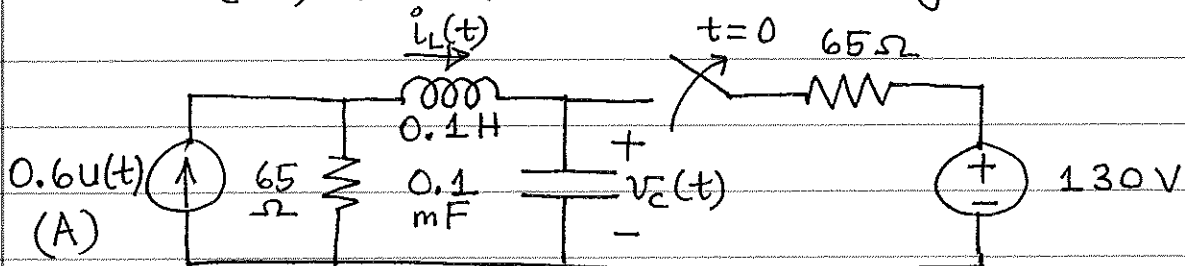(#3) For the electric circuit shown, find $v_c(t)$ for $t \geq 0$. Assume steady state at $t = 0^-$.



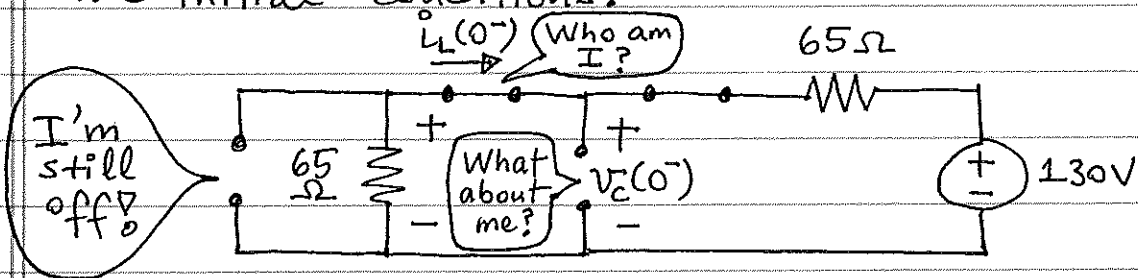
Solution: Draw the circuit at $t = 0^-$ to obtain the initial conditions:



$$\text{Using VDP} \rightarrow v_c(0^-) = \frac{65}{65+65} (130) = 65 \text{ V}$$

$$i_L(0^-) = -\frac{65 \text{ V}}{65 \Omega} = -1 \text{ A}$$

} initial conditions!

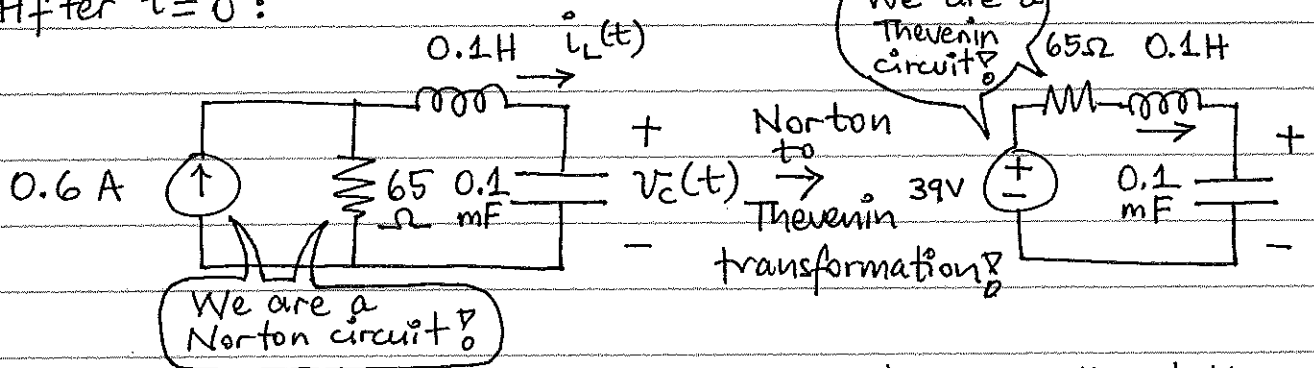After $t=0$:

Since second-order series RLC circuit, using the table, characteristic equation can be obtained as

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \rightarrow s^2 + \frac{65}{0.1}s + \frac{1}{(0.1)(0.1m)} = 0$$

$$\rightarrow \underbrace{s^2 + 650s + 100,000}_{(s+250)(s+400)} = 0$$

\therefore Overdamped response:

$$v_c(t) = A_1 e^{-250t} + A_2 e^{-400t} + A_3, \text{ for } t \geq 0$$

Using the initial conditions:


$$v_c(0^+) = \boxed{A_1 + A_2 + A_3 = 65} \leftarrow \text{(I)}$$

Since $\text{---} \text{---}$ and $\frac{1}{\text{---}}$ are connected in series:

$$i_L(t) = i_c(t) = C \frac{dv_c(t)}{dt}$$

$$= 10^{-4} \left[-250A_1 e^{-250t} - 400A_2 e^{-400t} \right] \leftarrow \text{(II)}$$
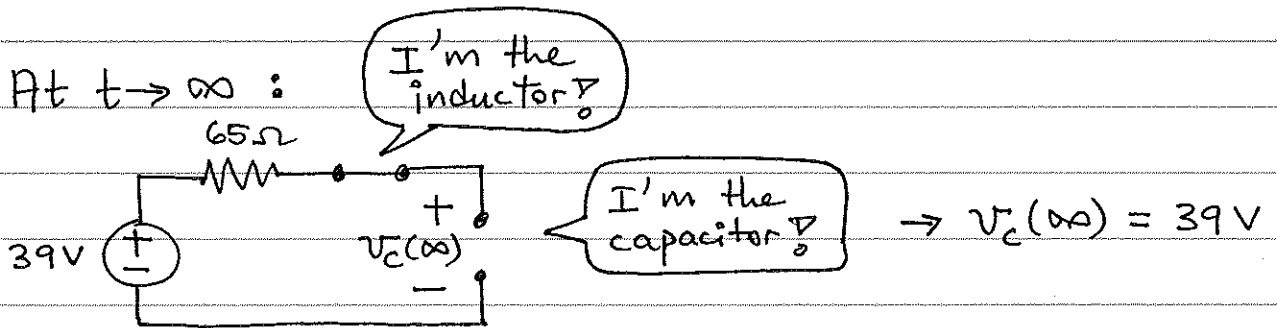
$$i_L(0^+) = -0.025A_1 - 0.04A_2 = -1 \rightarrow \boxed{5A_1 + 8A_2 = 200}$$



$$\therefore v_c(\infty) = \boxed{A_3 = 39V} \leftarrow \text{(III)}$$

Solving (I), (II) and (III) simultaneously yields:

$$\left. \begin{array}{l} A_1 + A_2 = 26 \\ 5A_1 + 8A_2 = 200 \end{array} \right\} \begin{array}{l} \downarrow \\ 5(26 - A_2) + 8A_2 = 200 \\ \downarrow \\ 3A_2 = 70 \rightarrow \boxed{A_2 = \frac{70}{3}} \\ \downarrow \\ \boxed{A_1 = \frac{8}{3}} \end{array}$$

$$\therefore v_c(t) = \frac{8}{3} e^{-250t} + \frac{70}{3} e^{-400t} + 39 \text{ (V)}, \text{ for } t \geq 0$$