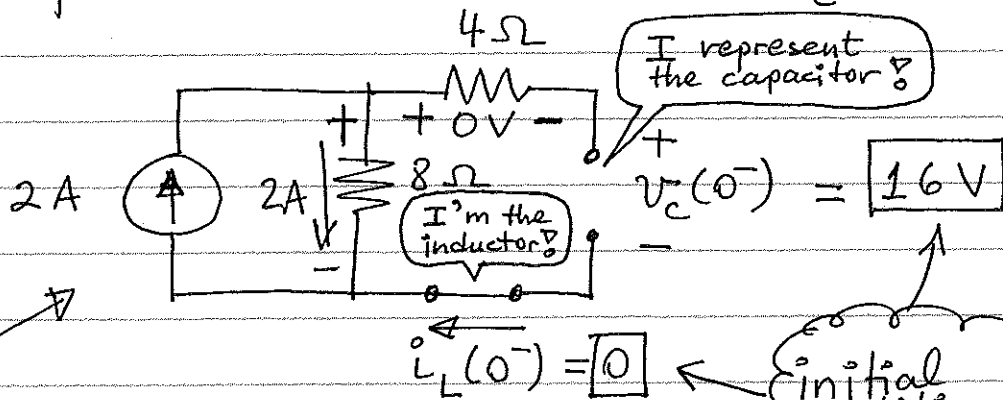


Find $v_C(t)$ for $t \geq 0$ for three cases:

- (a) $C = 0.1 \text{ F}$ (b) $C = 0.05 \text{ F}$ (c) $C = 1/18 \text{ F}$

Solution: We start with the $t = 0^-$ circuit to find the initial conditions $v_C(0^-)$ and $i_L(0^-)$:



Steady state


initial conditions

Next, we analyze the circuit after $t = 0$:

We meant we together are

I'm a Norton circuit

We are a Thevenin circuit

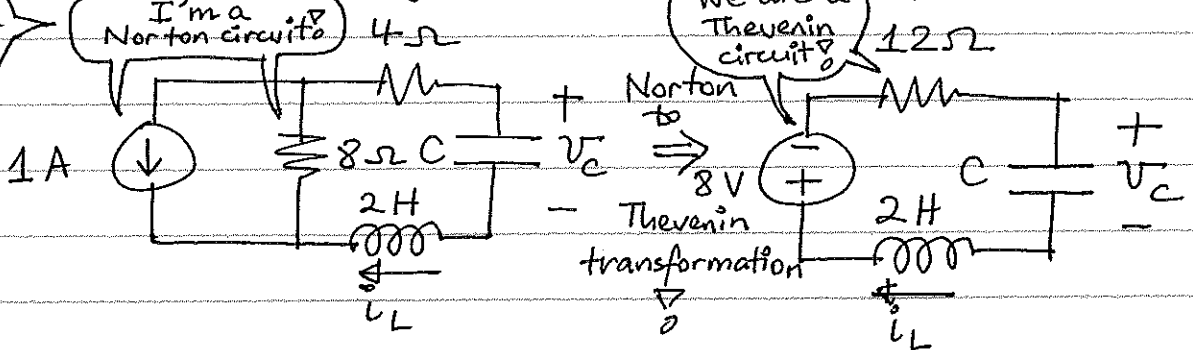

Since this is a second-order series RLC circuit, its characteristic equation is given by

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \leftarrow \text{(From table)}$$

(a) Substituting $R = 12\Omega$, $L = 2H$ and $C = 0.1F$:

$$s^2 + 6s + 5 = 0 \rightarrow s_1, s_2 = -1, -5$$


Therefore the solution is an overdamped response given by

$$v_c(t) = A_1 e^{-t} + A_2 e^{-5t} + A_3, \text{ for } t \geq 0$$


Since $v_c(0^+) = v_c(0^-) = 16V$, we can write

$$v_c(0^+) = \boxed{A_1 + A_2 + A_3 = 16} \quad \leftarrow \text{(I)}$$

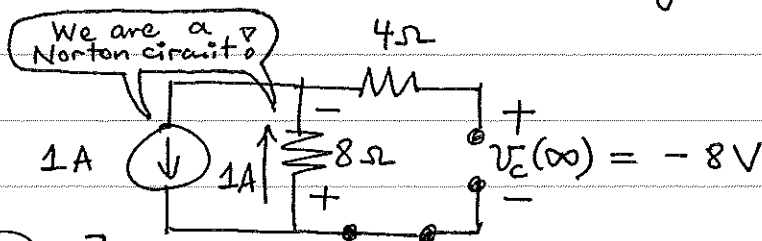Note that at $t = \infty$ (steady state holds), we have



Either is acceptable!

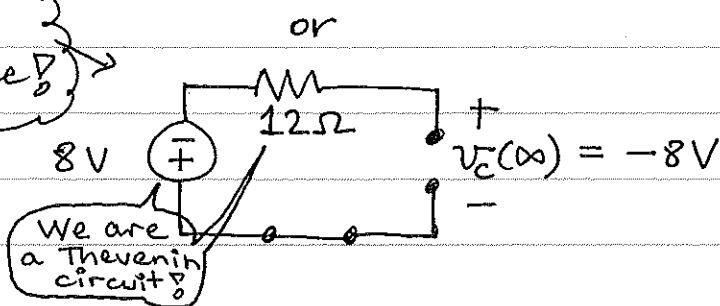

Final condition!

$$\text{So, } v_c(t \rightarrow \infty) = A_3 = \boxed{-8V} \leftarrow (\text{II})$$

Next, we find $i_L(t) = i_c(t) = C \frac{dv_c(t)}{dt}$:

$$i_L(t) = 0.1 \left[-A_1 e^{-t} - 5A_2 e^{-5t} \right]$$

Since $i_L(0^+) = i_L(0^-) = 0$, we can write

$$i_L(0^+) = -0.1A_1 - 0.5A_2 = 0 \rightarrow \boxed{A_1 = -5A_2} \leftarrow (\text{III})$$

Substituting (II) and (III) into (I) yields:

$$-5A_2 + A_2 - 8 = 16 \rightarrow A_2 = \boxed{-6} \rightarrow A_1 = -5A_2 = \boxed{30}$$

Therefore, the capacitor voltage expression is given by

$$\boxed{v_c(t) = 30e^{-t} - 6e^{-5t} - 8 \text{ (V), for } t \geq 0}$$

(b) For $C = 0.05 \text{ F}$, the characteristic equation is given by

$$s^2 + 6s + 10 = 0 \rightarrow s_1, s_2 = -3 \pm j$$

Therefore the solution is an underdamped response given by

$$v_c(t) = A_1 e^{-3t} \cos t + A_2 e^{-3t} \sin t + A_3$$

The initial & final conditions are still the same, so, following the same steps:

$$v_c(0^+) = \boxed{A_1 + A_3 = 16} \leftarrow \text{(I)}$$

$$v_c(t \rightarrow \infty) = A_3 = \boxed{-8 \text{ V}} \leftarrow \text{(II)}$$

$$i_L(t=0^+) = 0.05 \left[-3A_1 e^{-3t} \cos t - A_1 e^{-3t} \sin t - 3A_2 e^{-3t} \sin t + A_2 e^{-3t} \cos t \right]_{t=0^+}$$

$$= -0.15A_1 + 0.05A_2 = 0 \rightarrow \boxed{A_2 = 3A_1} \leftarrow \text{(III)}$$

Substituting (II) into (I) yields:

$$A_1 = 16 - A_3 = 16 + 8 = \boxed{24}$$

$$\text{Then, using (III)} \rightarrow A_2 = \boxed{72}$$

$$\therefore v_c(t) = 24e^{-3t} \cos t + 72e^{-3t} \sin t - 8 \text{ (V)}, \text{ for } t \geq 0$$

$$(c) \quad s^2 + 6s + 9 = 0 \rightarrow s_1 = s_2 = -3$$

Therefore, the solution is critically damped response given by

$$v_c(t) = (A_1 + A_2 t) e^{-3t} + A_3$$

$$v_c(0^+) = \boxed{A_1 + A_3 = 16} \leftarrow \text{(I)}$$

$$v_c(t \rightarrow \infty) = A_3 = \boxed{-8 \text{ V}} \leftarrow \text{(II)}$$

$$i_L(t=0^+) = \frac{4}{18} \left[A_2 e^{-3t} - 3(A_1 + A_2 t) e^{-3t} \right]_{t=0^+}$$


$$= \frac{1}{18} [A_2 - 3A_1] = 0 \leftarrow \text{(III)}$$

Solving, we find out that $A_1 = \boxed{24}$ & $A_2 = \boxed{72}$

$$\therefore v_c(t) = 24(1+3t)e^{-3t} - 8 \text{ (V), for } t \geq 0$$

Practice Problem:

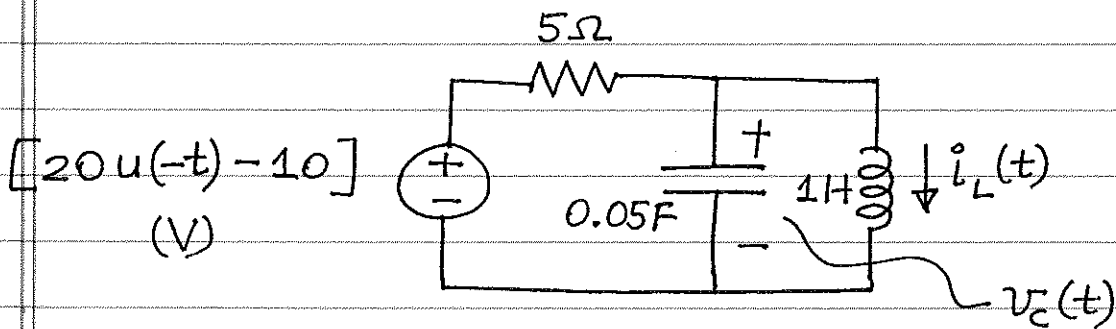For the circuit shown, find $i_L(t)$ for $t \geq 0$.



Using $i_L(t)$ expression, find $v_c(t)$ for $t \geq 0$.

Partial answer:

$$i_L(t) = 4e^{-2t} \cos(4t) + 2e^{-2t} \sin(4t) - 2 \text{ (A), for } t \geq 0$$

— THE END —