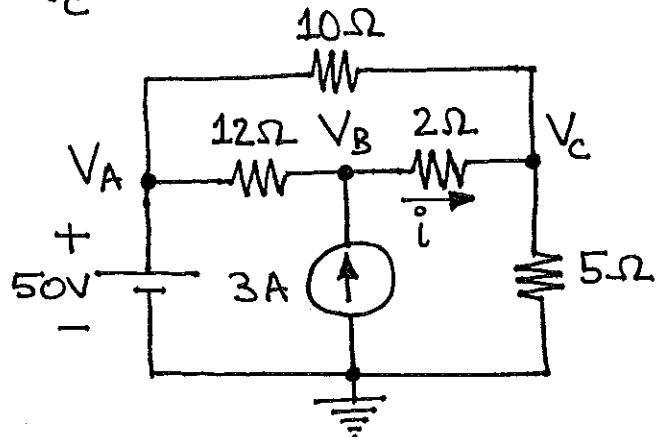


EE 261
FALL 2011
A. INAN


9/21/2011

HOMEWORK #3

1. In the circuit shown, find the node voltages V_B and V_C and use them to determine current i .



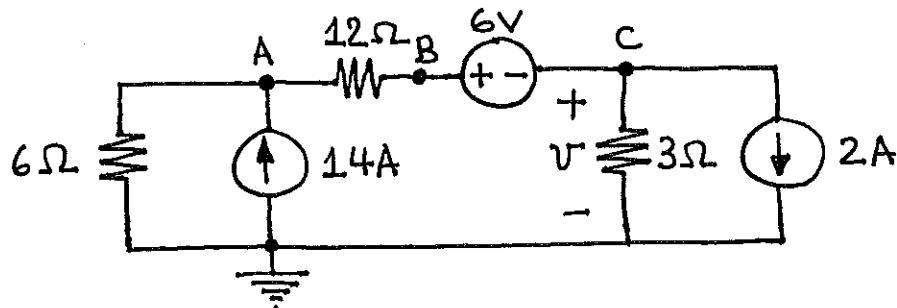2. In the circuit shown, find the voltage V .



3. For the circuit shown, find the voltage of the 1Ω resistor and the current of the 4Ω resistor.

