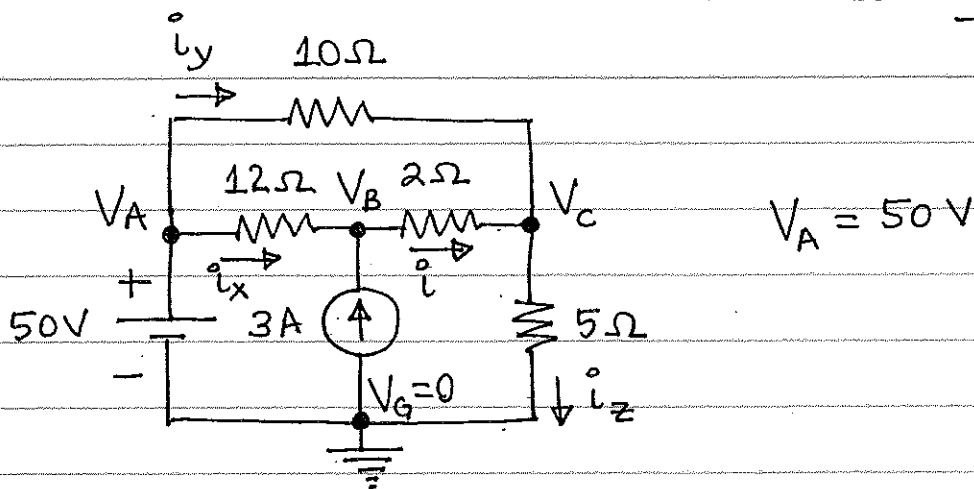


1.



Note that the currents  $i$ ,  $i_x$ ,  $i_y$  and  $i_z$  are arbitrarily assigned. Find  $i$ .

$$i_x = \frac{V_A - V_B}{12} = \frac{50 - V_B}{12}, \quad i_y = \frac{V_A - V_C}{10} = \frac{50 - V_C}{10}$$

$$i = \frac{V_B - V_C}{2}, \quad i_z = \frac{V_C - V_G}{5} = \frac{V_C}{5}$$

Using KCL at node B:

$$i_x + 3 = i \rightarrow \frac{50 - V_B}{12} + 3 = \frac{V_B - V_C}{2} \rightarrow \boxed{7V_B - 6V_C = 86}$$

(4)      (12)      (6)

Using KCL at node C:

$$i_y + i = i_z \rightarrow \frac{50 - V_C}{10} + \frac{V_B - V_C}{2} = \frac{V_C - V_G}{5} \rightarrow \boxed{-5V_B + 8V_C = 50}$$

(4)      (5)      (2)

$$7V_B - 6V_C = 86 \quad \xrightarrow{\times 5} \quad 35V_B - 30V_C = 430$$

$$-5V_B + 8V_C = 50 \quad \xrightarrow{\times 7} \quad -35V_B + 56V_C = 350$$

$$26V_C = 780 \rightarrow V_C = 30V$$


$$\downarrow V_B = 38V$$

$$\therefore i = \frac{V_B - V_C}{2} = \frac{38 - 30}{2}$$

$$= \boxed{4A}$$

9/28/2011

p#2

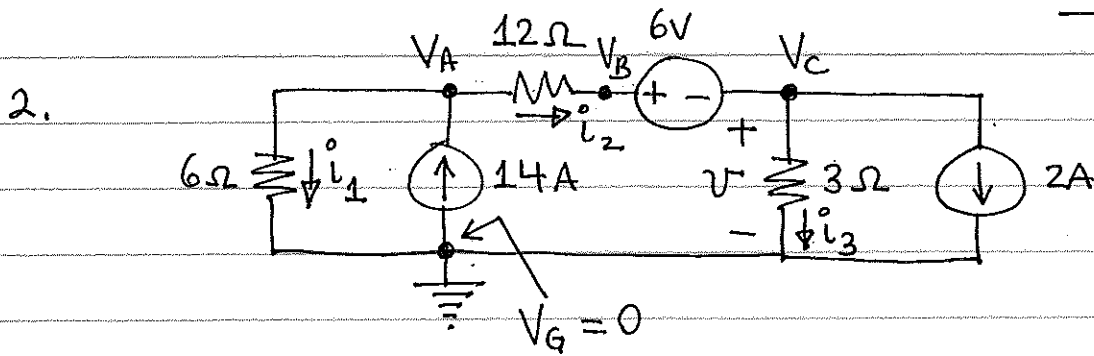

Again, currents  $i_1$ ,  $i_2$  and  $i_3$  are assigned arbitrarily.

$$i_1 = \frac{V_A - V_G}{6} = \frac{V_A}{6}$$

$$i_2 = \frac{V_A - V_B}{12}$$

$$i_3 = \frac{V_C - V_G}{3} = \frac{V_C}{3}$$

KCL at node A:

$$14 = i_1 + i_2 \rightarrow 14 = \frac{V_A}{6} + \frac{V_A - V_B}{12} \rightarrow \boxed{3V_A - V_B = 168}$$

(12)    (2)    (1)

KCL at node C:

$$i_2 = i_3 + 2 \rightarrow \frac{V_A - V_B}{12} = \frac{V_C}{3} + 2 \rightarrow \boxed{V_A - V_B - 4V_C = 24}$$

(1)    (4)    (12)

Also, we know that  $V_B - V_C = 6 \rightarrow V_B = 6 + V_C$

Substituting into first and second equations yield:


$$\left. \begin{array}{l} 3V_A - V_C = 174 \\ V_A - 5V_C = 30 \end{array} \right\} \rightarrow \begin{array}{l} -3V_A - V_C = 174 \\ +3V_A - 15V_C = 90 \end{array}$$

$$14V_C = 84 \rightarrow V_C = 6V$$

$$\therefore V = V_C = \boxed{6V}$$

9/28/2011

p#3

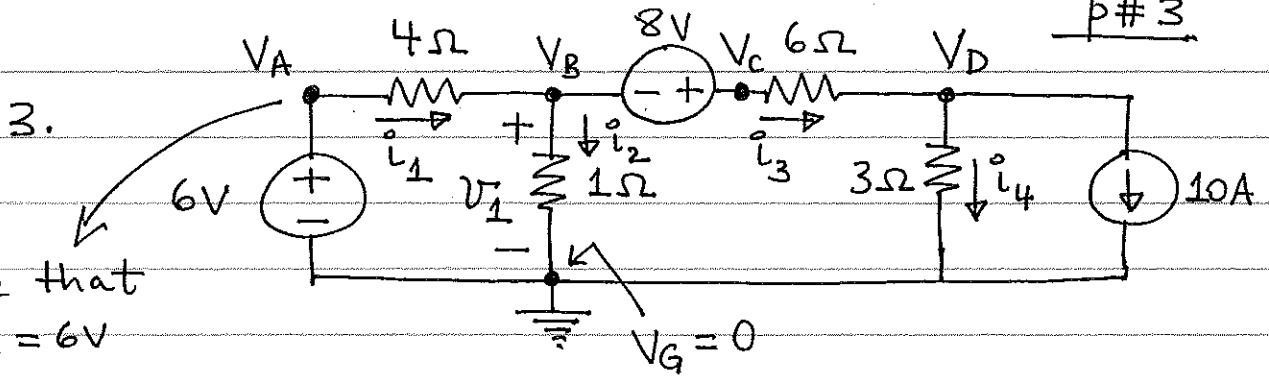

3.  
Note that  $V_A = 6V$

Currents  $i_1, i_2, i_3$  and  $i_4$  assigned. Their directions are chosen arbitrarily.

$$i_1 = \frac{V_A - V_B}{4} = \frac{6 - V_B}{4}$$

$$i_2 = \frac{V_B - \cancel{V_G}^0}{1} = V_B$$

$$i_3 = \frac{V_C - V_D}{6}, \quad i_4 = \frac{V_D - \cancel{V_G}^0}{3} = \frac{V_D}{3}$$

KCL at node B:

$$i_1 = i_2 + i_3 \rightarrow \frac{6 - V_B}{4} = V_B + \frac{V_C - V_D}{6}$$

$$\rightarrow \boxed{15V_B + 2V_C - 2V_D = 18} \quad (\#1)$$

KCL at node D:

$$i_3 = i_4 + 10 \rightarrow \frac{V_C - V_D}{6} = \frac{V_D - \cancel{V_G}^0}{3} + 10$$

$$\rightarrow \boxed{V_C - 3V_D = 60} \quad (\#2)$$

Also,  $\boxed{V_C - V_B = 8V} \rightarrow V_C = 8 + V_B$

Substituting into equations #1 & #2 yield:

$$\left. \begin{array}{l} 17V_B - 2V_D = 2 \\ V_B - 3V_D = 52 \end{array} \right\} \rightarrow \begin{array}{l} 51V_B - 6V_D = 6 \\ + \quad +2V_B - 6V_D = +104 \\ \hline 49V_B = -98 \rightarrow V_B = -2V \end{array}$$

$\boxed{2A}$   
 $= \frac{6 - (-2)}{4}$   
 $i_1 =$   
 $\&$   
 $\boxed{-2V}$   
 $= V_B =$   
 $V_1 =$