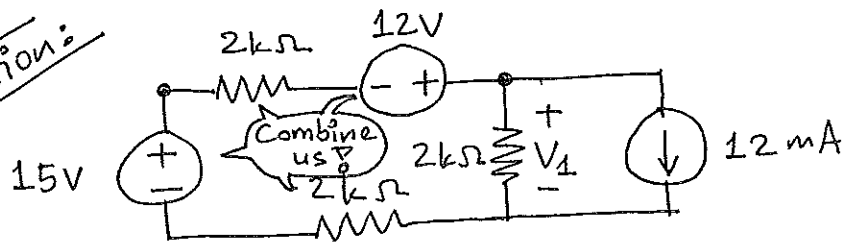


11/05/2011


EE 261 - FALL 2011 - SOLUTIONS TO MIDTERM #2
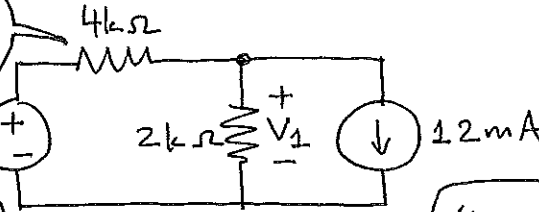
#1  
Using source transformation:




$15 + 12 = 27V$  &  $2k\Omega + 2k\Omega = 4k\Omega$


Transform us to a Norton circuit  
 $(15+12)V$



Thevenin to Norton

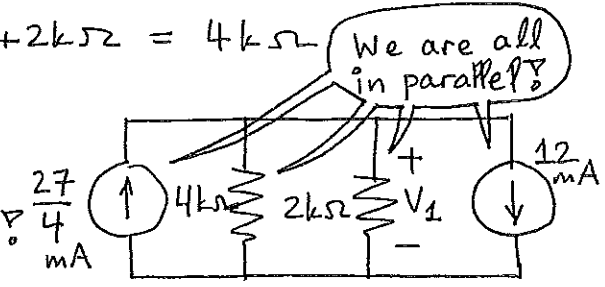


We are all in parallel

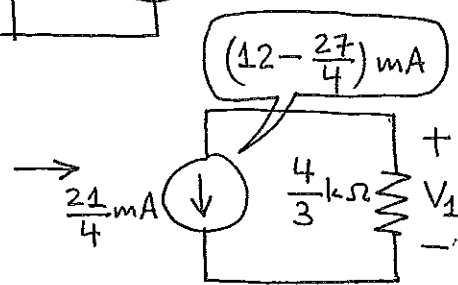

$\therefore V_1 = -\left(\frac{4}{3}k\Omega\right)\left(\frac{21}{4}mA\right) = \boxed{-7V}$

11/05/2011

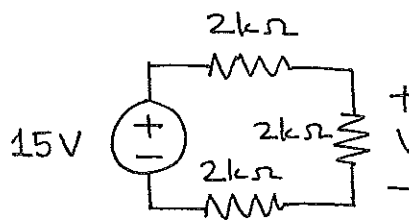
#1 Second approach: Superposition principle:



Using VDP

$V_1' = \frac{2k\Omega}{6k\Omega} (15V) = \boxed{5V}$

I'm the other resistor

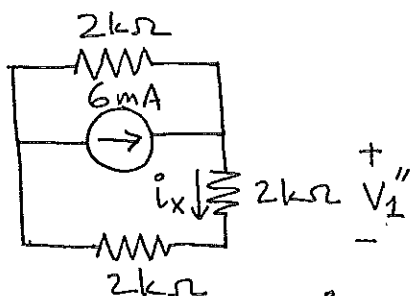


Using CDP

$i_x = \frac{2k\Omega}{6k\Omega} (6mA) = 2mA$

$\therefore V_1'' = (2k\Omega)(2mA) = \boxed{4V}$

2kΩ + 2kΩ

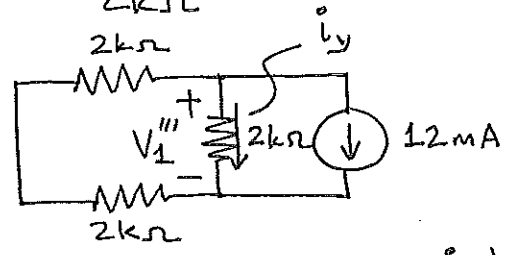

CDP


$i_y = -\frac{4k\Omega}{6k\Omega} (12mA) = -8mA$

$\therefore V_1''' = -(2k\Omega)(8mA) = \boxed{-16V}$

$\therefore V_1 = V_1' + V_1'' + V_1''' = 5 + 4 - 16 = \boxed{-7V}$



11/05/2011

#2 Using superposition principle:

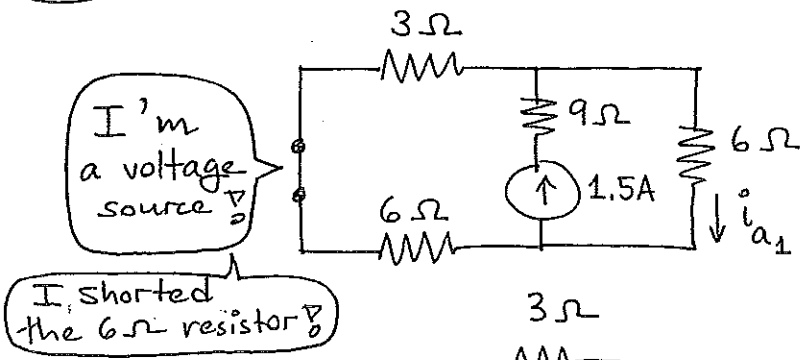

Using CDP:
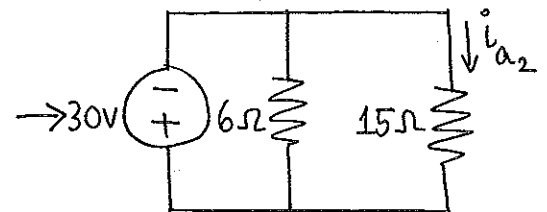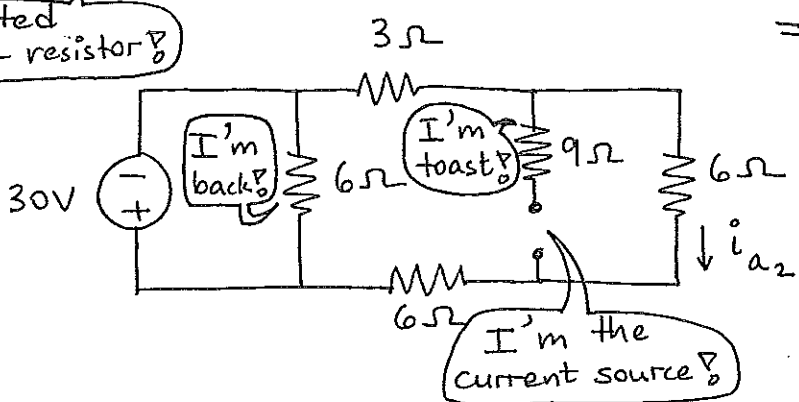
$$i_{a1} = \frac{(3+6)}{(3+6)+6} (1.5A) = 0.9A$$





$$i_{a2} = -\frac{30V}{15\Omega} = -2A$$

$$i_a = i_{a1} + i_{a2} = 0.9 - 2 = -1.1A$$


11/05/2011

#3 Find the Thevenin equivalent circuit:

To find  $R_T$ :

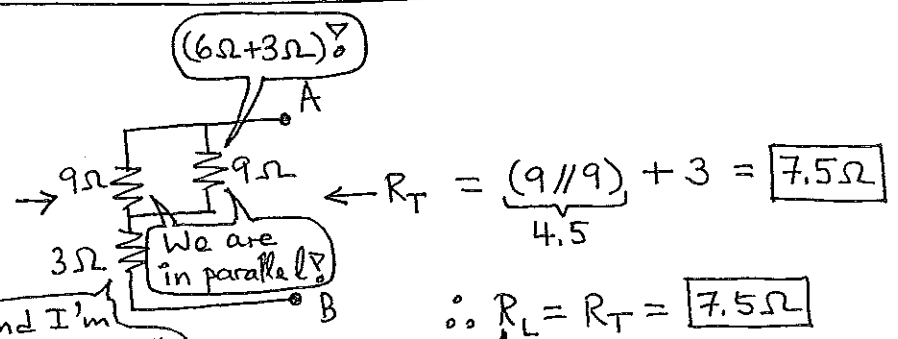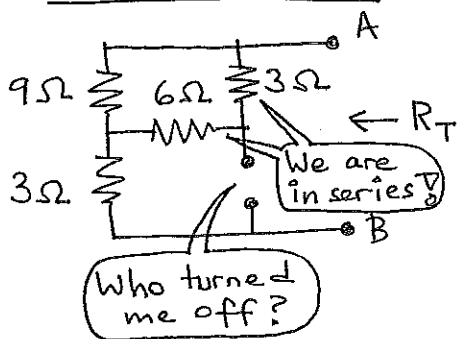

To find  $V_T$ :

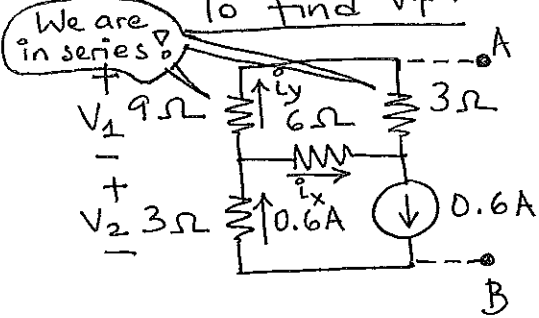

$V_T = V_{oc} = V_1 + V_2$

The other resistor

CDP:  $i_y = \frac{6}{6+12} (0.6) = 0.2A \rightarrow i_x = 0.6 - i_y = 0.4A$

We are both in Amperes

$V_T = -(9\Omega)(0.2) - (3\Omega)(0.6) = -3.6V$

$P_{Lmax} = \frac{V_T^2}{4R_T} = \frac{(3.6)^2}{4(7.5)} = 0.432W$

11/05/2011


#4  $C_{eq1} = C // C = \frac{(C)(C)}{C+C} = \frac{C}{2}$

$$C_{eq2} = C_{eq1} + C = \frac{3C}{2}$$

$$C_{eq3} = C_{eq2} // C = \frac{(3C/2)(C)}{5C/2} = \frac{3C}{5}$$

$$C_{eq4} = C_{eq3} + C = \frac{8C}{5}$$
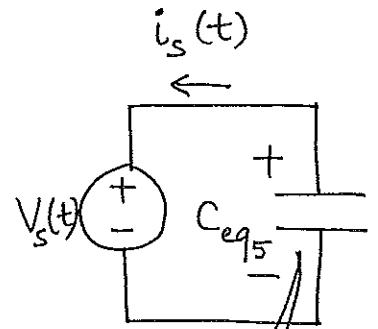
$$C_{eq5} = C_{eq4} // C = \frac{(8C/5)(C)}{(13C/5)} = \boxed{\frac{8C}{13}}$$



I represent all the capacitors

$$i_s(t) = -C_{eq5} \frac{dV_s(t)}{dt}$$

$$\rightarrow 4 \sin(2.6 \times 10^6 t) \times 10^{-3} = -\left(\frac{8C}{13}\right) \left[ -2.6 \times 10^7 \sin(2.6 \times 10^6 t) \right]$$

$$\rightarrow C = \frac{4 \times 10^{-3}}{8 \times 0.2 \times 10^7} = 2.5 \times 10^{-10} \text{ F} = \boxed{0.25 \text{ nF}}$$