

*University of Portland
School of Engineering*

EE 261-Electrical Circuits-3 cr. hrs.
Fall 2013

Midterm Exam # 2

(Wednesday, October 30, 2013)

(Closed Book Exam, Two Formula Sheets Allowed)

(Total Time: 55 minutes)

Name: SOLUTIONS! ☺


Signature: _____ ☺

"An honest mind possesses a kingdom."

Lucius Annaeus Seneca (4B.C.-65A.D.)


"Honest people are the true winners of the universe."

Anonymous

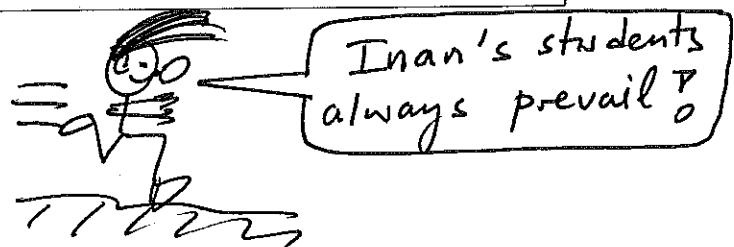


NOTE: You are expected to do Problems #1 to #4 in class. Problem #5 is take-home, due beginning of the class time on Monday, November 4, 2013.

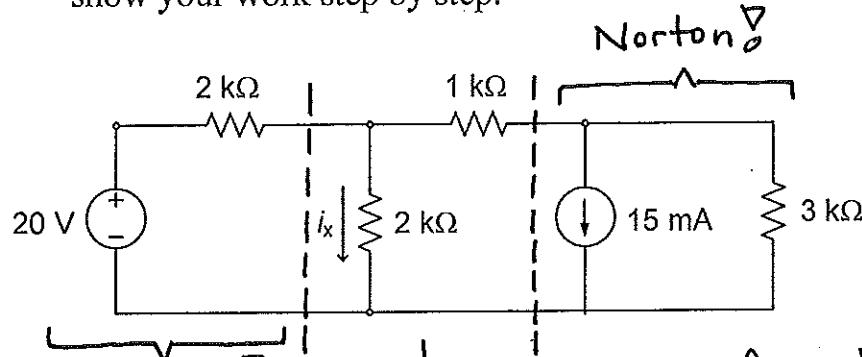1. (20 points) For the electric circuit shown, find the current i_x . Please show your work step by step.




Problem	Score
#1	
#2	
#3	
#4	
#5	
Total	

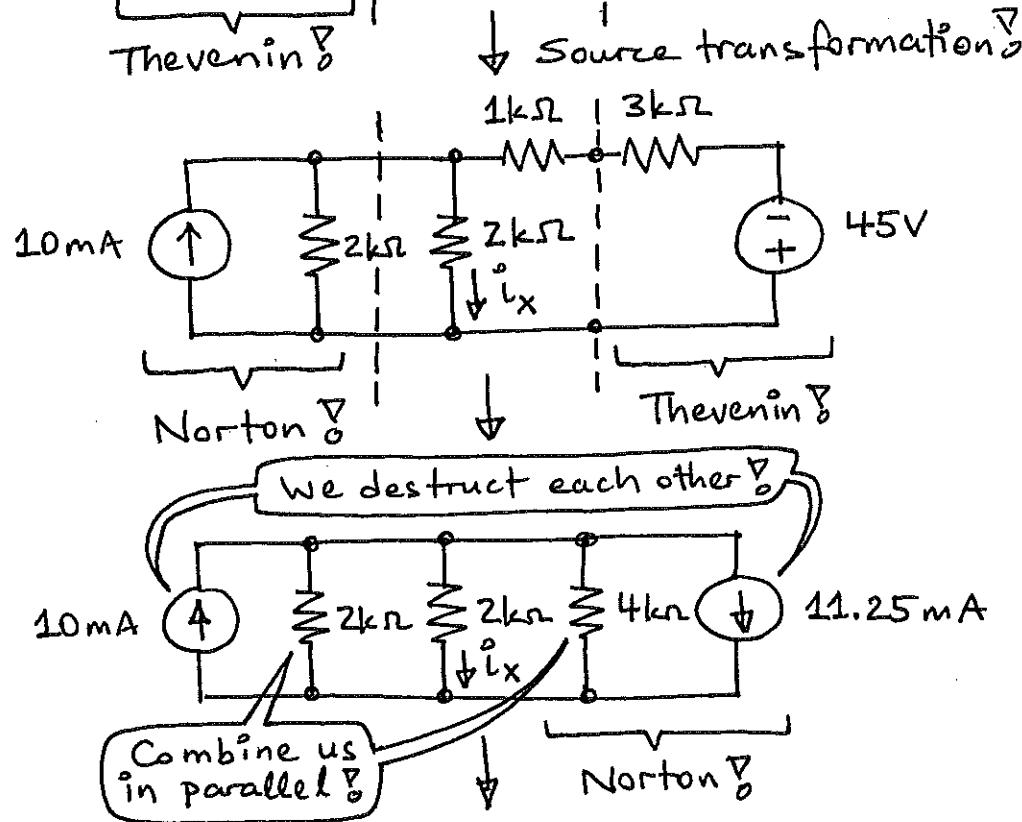

$$\frac{(2k\Omega)(4k\Omega)}{6k\Omega} = \frac{4}{3} k\Omega$$


$$CDP \rightarrow i_x = -\frac{\frac{4}{3} k\Omega}{(\frac{4}{3} + 2) k\Omega} (1.25 \text{ mA}) = -0.5 \text{ mA}$$

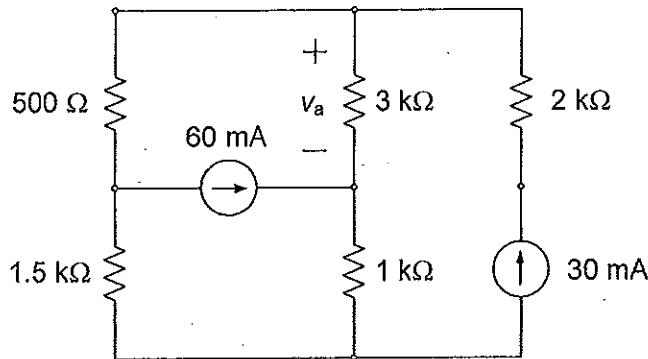2. (20 Points) In the electric circuit shown, determine the value of the voltage v_a across the $3\text{ k}\Omega$ resistor. (Again, please show your work clearly and provide brief justifications for the steps you take. Provide units.)



Using superposition principle:


We are in series ∇

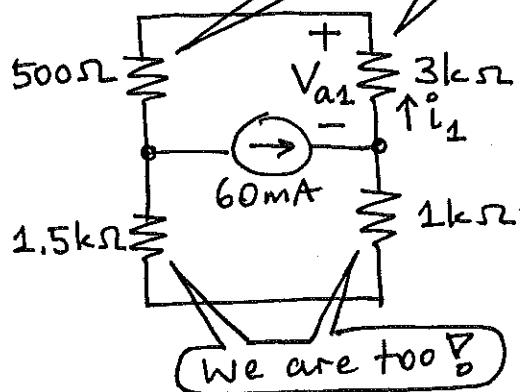

$$\text{CDP} \rightarrow i_1 = \frac{2.5\text{k}\Omega}{(2.5+3.5)\text{k}\Omega} (60\text{mA}) \\ = 25\text{mA}$$

$$V_{a1} = -(3\text{k}\Omega)i_1 = -75\text{V}$$

We are too ∇

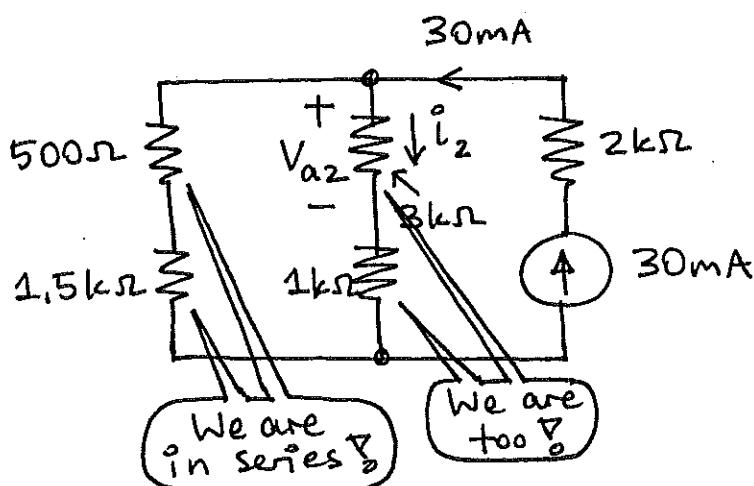

$$\text{CDP} \rightarrow i_2 = \frac{2\text{k}\Omega}{(2+4)\text{k}\Omega} (30\text{mA}) \\ = 10\text{mA}$$


$$V_{a2} = (3\text{k}\Omega)(10\text{mA}) \\ = 30\text{V}$$

$$\therefore V_a = V_{a1} + V_{a2} = -75 + 30$$

$$= -45\text{V}$$



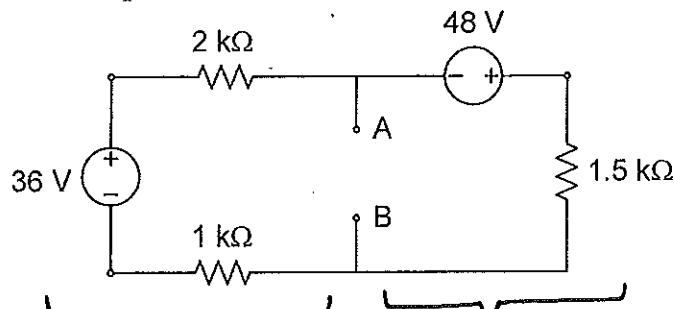
3. (20 Points) Consider the electric circuit shown. Determine the value of the external load resistor R_L to be connected between A-B terminals so that it receives maximum power from this circuit. What is the maximum power delivered to the load resistor chosen? Please provide your work step by step with justifications. Don't forget to calculate the power value!



Thevenin ∇


Thevenin ∇

Source transformation ∇

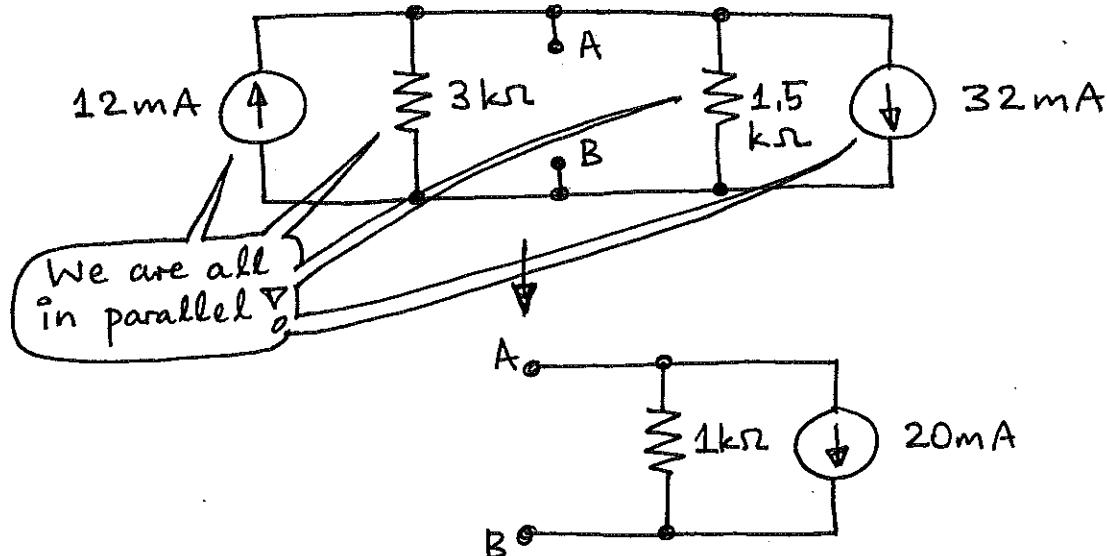


Based on Maximum Power Transfer Theorem:

$$R_L = R_N = 1\text{k}\Omega$$

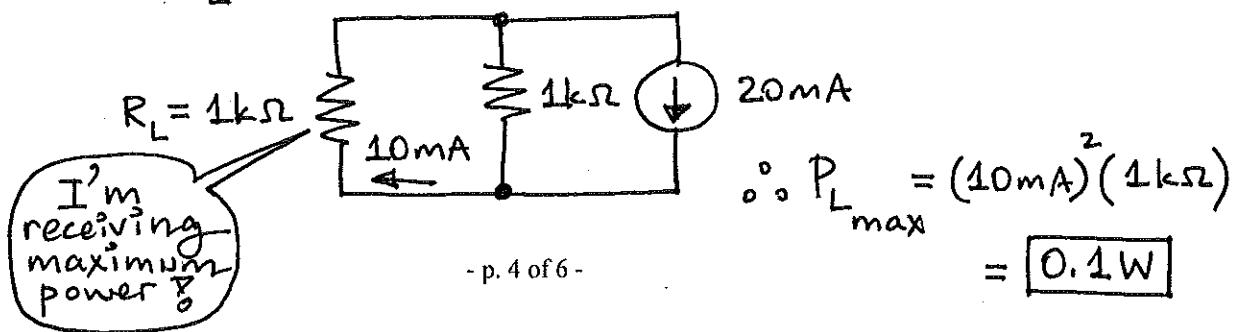

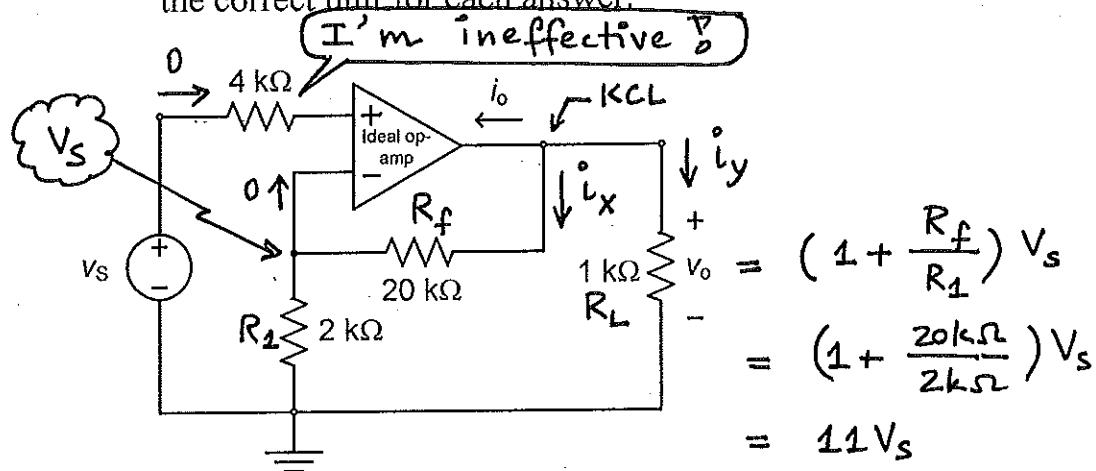4. (20 Points) For the op-amp circuit shown, determine the values of voltage v_o and current i_o for two cases: (a) $v_s = \frac{1}{2}$ V; (b) $v_s = 2$ V. Show your work step by step and provide justifications. Also provide the correct unit for each answer.




$$(a) \quad v_s = \frac{1}{2} \text{ V} \rightarrow v_o = \frac{11}{2} = \boxed{5.5 \text{ V}}$$

$$\text{KCL} \rightarrow i_o = -i_x - i_y = -\frac{v_o}{R_1 + R_f} - \frac{v_o}{R_L}$$

$$= -\frac{5.5 \text{ V}}{22 \text{ k}\Omega} - \frac{5.5 \text{ V}}{1 \text{ k}\Omega} = \boxed{-5.75 \text{ mA}}$$


$$(b) \quad v_s = 2 \text{ V} \rightarrow v_o = (11)(2) = \boxed{22 \text{ V}}$$
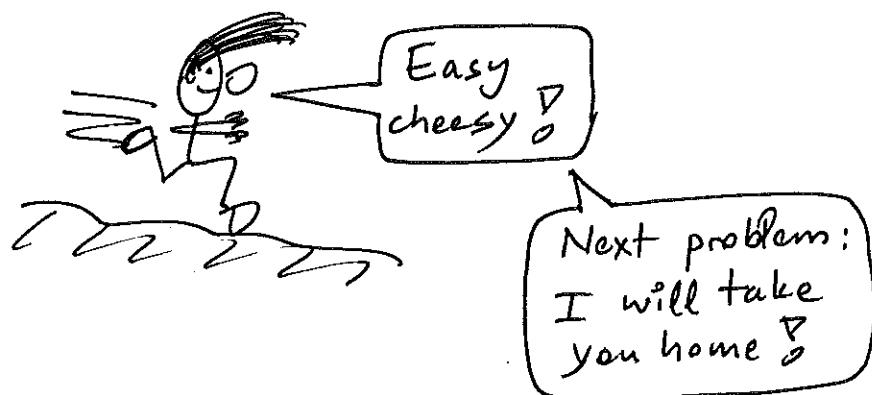
$$i_o = -\frac{22 \text{ V}}{22 \text{ k}\Omega} - \frac{22 \text{ V}}{1 \text{ k}\Omega} = \boxed{-23 \text{ mA}}$$



5. (Take-home; Total: 20 points) For the op-amp circuit shown:

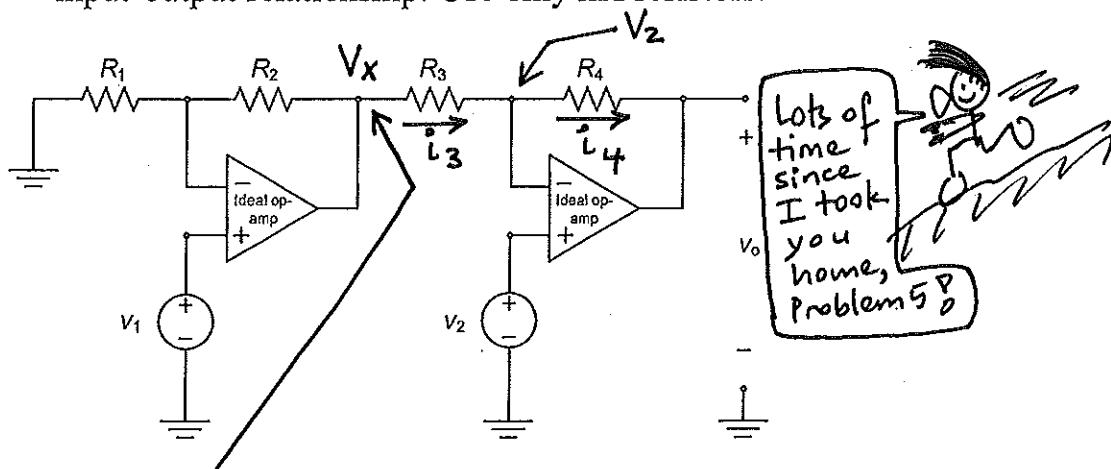- (a) (10 points) Find a general simplified expression for the output voltage v_o in terms of the two input voltages, v_1 and v_2 . Show your work step by step. What does this circuit do?
- (b) (10 points) Design this circuit so that $v_o = 6v_2 - 20v_1$. Note that design means you determine the values of the four resistors to achieve this input-output relationship. Use only $k\Omega$ resistors.



(a)

Noninverting amplifier:

$$V_x = \left(1 + \frac{R_2}{R_1}\right) V_1$$

$$\overset{\circ}{i}_3 = \frac{V_x - V_2}{R_3} = \overset{\circ}{i}_4$$

$$V_o = -R_4 \overset{\circ}{i}_4 + V_2$$


$$= -R_4 \left[\frac{\left(1 + \frac{R_2}{R_1}\right) V_1 - V_2}{R_3} \right] + V_2$$

$$V_o = -\frac{R_4(R_1 + R_2)}{R_1 R_3} V_1 + \left(1 + \frac{R_4}{R_3}\right) V_2$$

(b) $V_o = 6V_2 - 20V_1 \rightarrow 1 + \frac{R_4}{R_3} = 6$

Let $R_3 = 1k\Omega \rightarrow R_4 = 5k\Omega$

\downarrow $\rightarrow -\frac{R_4(R_1 + R_2)}{R_1 R_3} = -20$

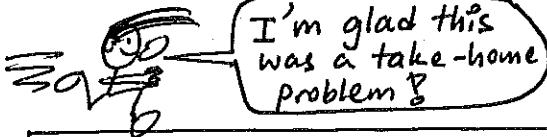 Let $R_1 = 1k\Omega \rightarrow R_2 = 3k\Omega$

$\therefore R_1 = R_3 = 1k\Omega, R_2 = 3k\Omega, R_4 = 5k\Omega$