

From "In Memory of JFK,"
by A. S. Inan:

1. How do you express
JFK's birthday by using
three consecutive primes?

Answer: $(23 \times 23) 1917$
529



John F. Kennedy

(May 29, 1917-November 22, 1963)

2. What is the unique
numerical connection
between JFK's and
RFK's birthdays?

Answer:

JFK's birthday $\boxed{5291917}$
RFK's birthday $1120\boxed{1925}$

University of Portland
School of Engineering

EE 261-Electrical Circuits-3 cr. hrs.

Fall 2013

Midterm Exam # 3

(Friday, November 22, 2013)

President JFK was killed 50 years ago, on this day.

(Closed Book Exam, Three Formula Sheet are Allowed)

(Total Time: 55 minutes)

Name: SOLUTIONS! 😊

Signature: _____ 😊


"An honest mind possesses a kingdom."
Lucius Annaeus Seneca (4B.C.-65A.D.)

"Honest people are the true winners of the universe."
Anonymous

NOTE: Problem # 4 is take-home, due Monday. On all the problems, please show your work clearly, and provide the appropriate units for your answers. Also mark on the schematic to show any current or voltage that you define in your solution.

P # 1 (25 pts.)	P # 2 (25 pts.)	P # 3 (25 pts.)	P # 4 (25 pts.)	Total (100 pts.)

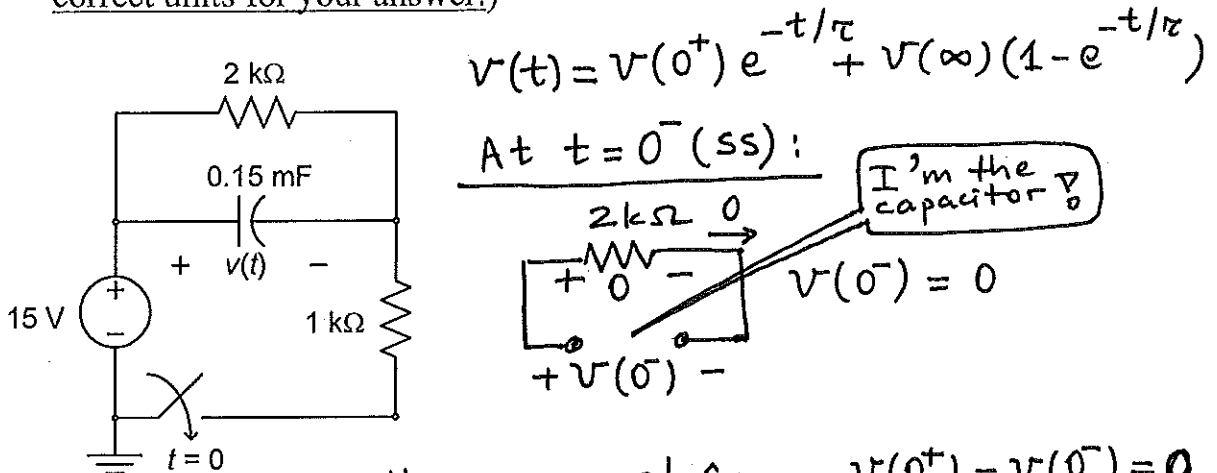
1. (15 mins., 25 points) In the electric circuit shown, the switch closes at $t = 0$, after being open for a long time. Find the complete mathematical expression for the voltage $v(t)$ across the 0.15 mF capacitor for $t \geq 0$. (Please show your work clearly and provide brief justifications for the steps you take. Also, don't forget to provide the correct units for your answer.)




Since capacitor voltage can not jump, $v(0^+) = v(0^-) = 0$

At $t = \infty$ (SS):

To find $\tau = R_T C$:

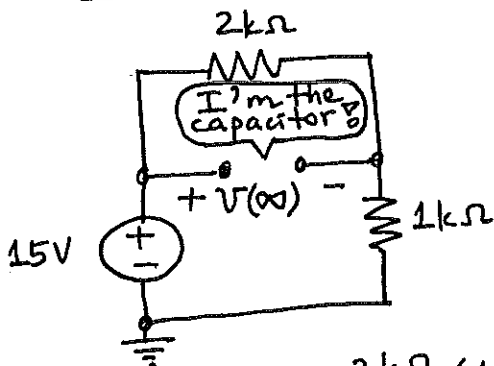
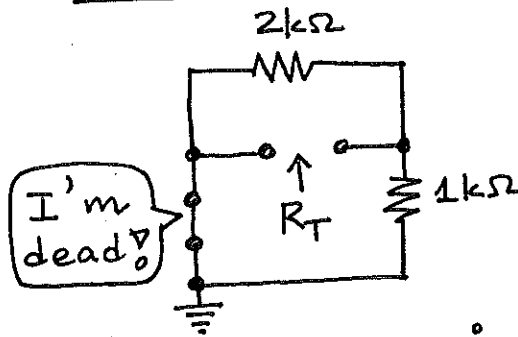
$$VDP \rightarrow v(\infty) = \frac{2k\Omega}{3k\Omega} (15V) = 10V$$







$$R_T = 2k\Omega // 1k\Omega = \frac{(2k\Omega)(1k\Omega)}{(2+1)k\Omega} = \frac{2}{3} k\Omega$$


$$\therefore \tau = \left(\frac{2}{3} k\Omega\right)(0.15mF) = 0.1s$$

$$\therefore v(t) = 10(1 - e^{-10t}) V, \text{ for } t \geq 0$$

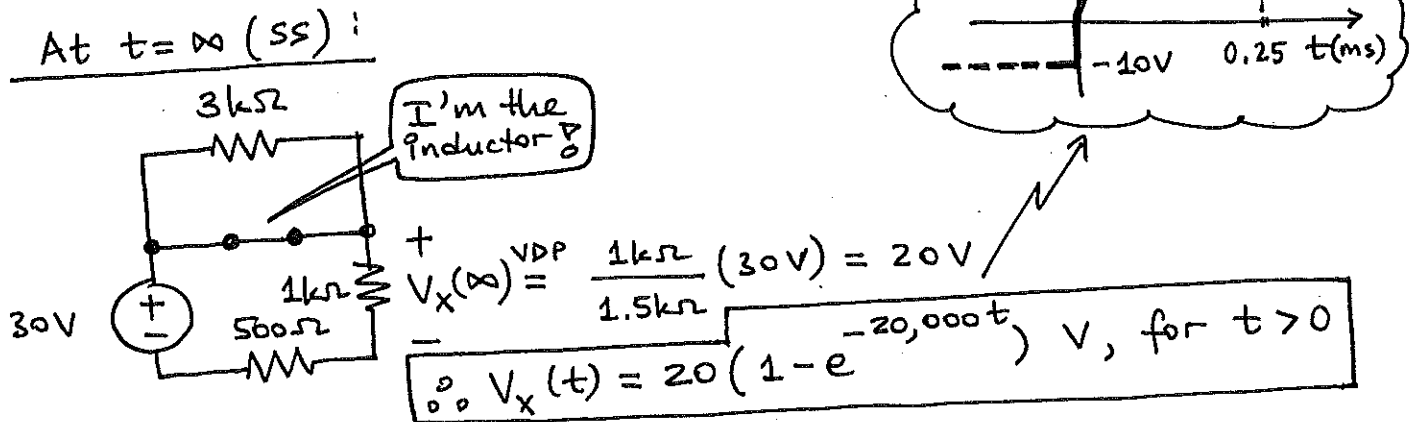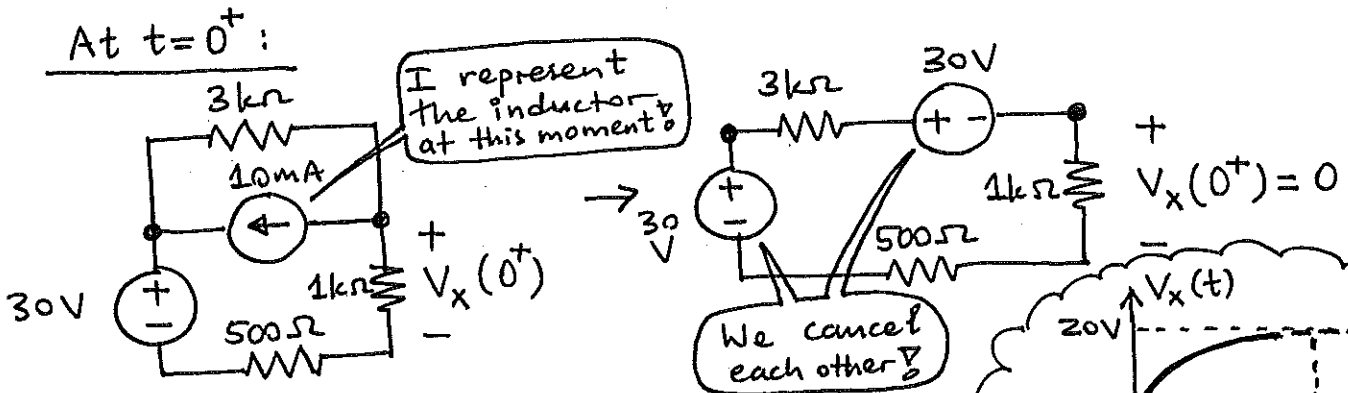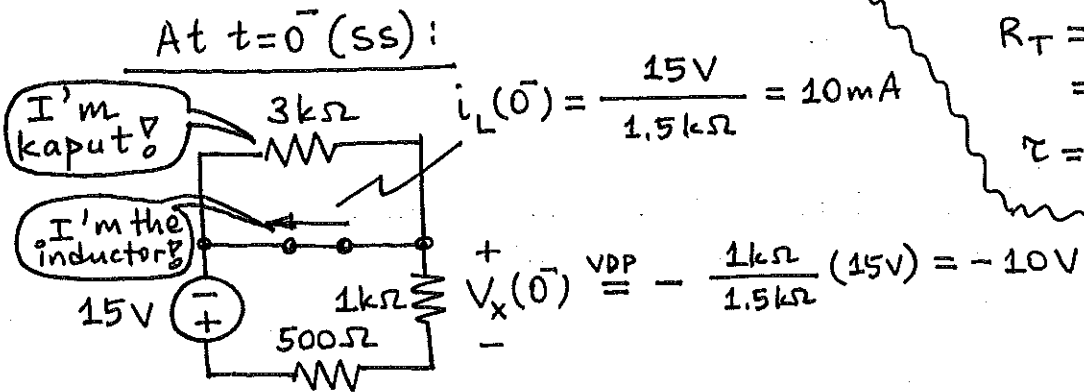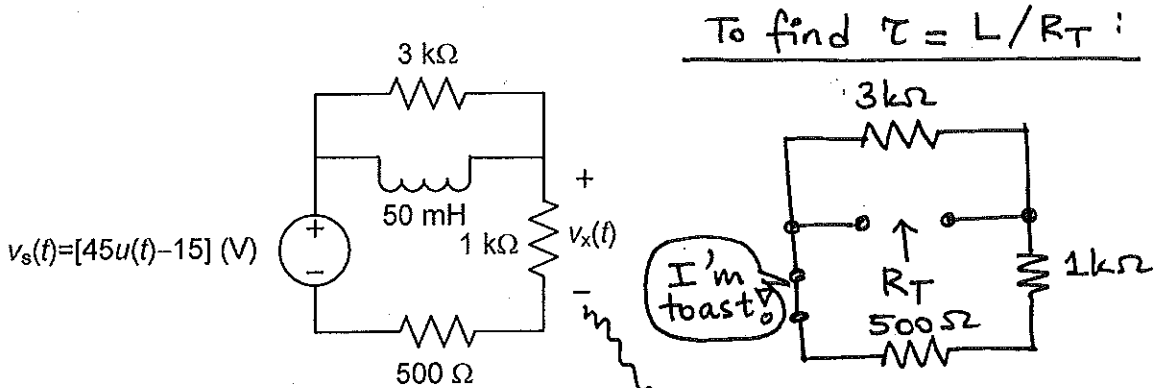2. (15 mins., 25 points) In the electric circuit shown, find the complete mathematical expression and sketch the voltage $v_x(t)$ across the $1\text{ k}\Omega$ resistor for $t > 0$. (Please show your work step by step.)



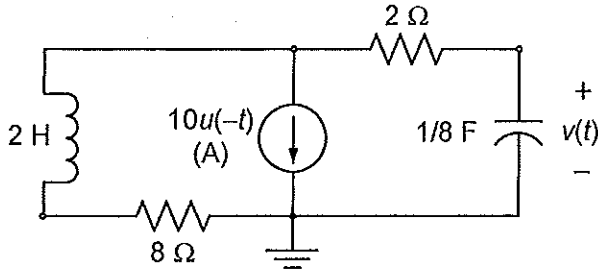3. (20 mins., 25 points) Consider the electric circuit shown. Solve for the complete mathematical expression for the capacitor voltage $v(t)$ for $t \geq 0$. Show your work step by step including justifications.



I'm an initial condition


At $t = 0^-$ (SS):

I represent the capacitor


Me too

$i_L(0^-) = 10A = i_L(0^+)$

I'm the inductor

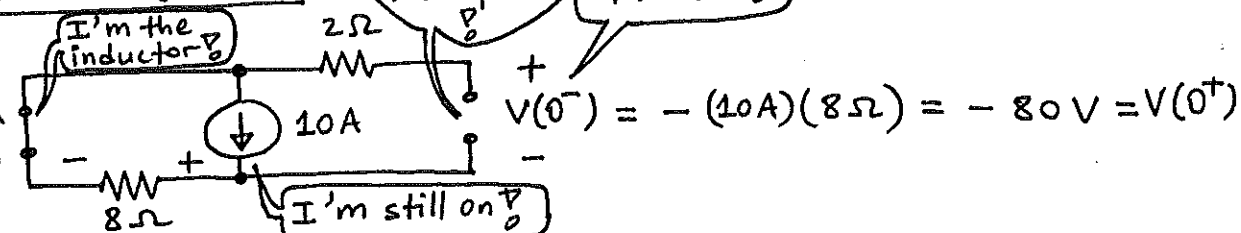

For $t > 0$:

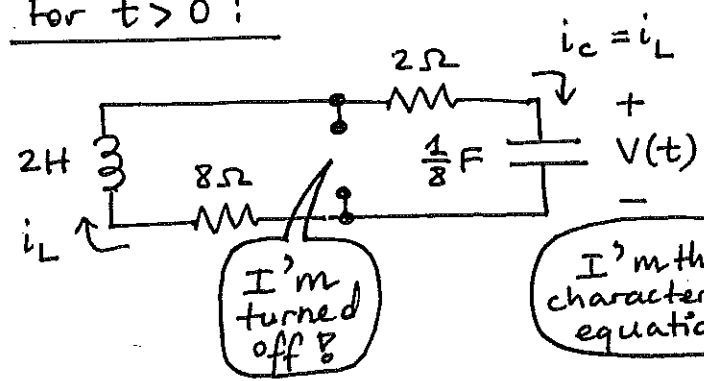

I'm turned off

I'm the characteristic equation

Series RLC circuit:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + \frac{10}{2}s + \frac{8}{2} = 0$$

$$s^2 + 5s + 4 = 0 \rightarrow s_1, s_2 = -1, -4$$

We are the characteristic roots

Since real and distinct roots \rightarrow Overdamped response.

$$\therefore V(t) = A_1 e^{-t} + A_2 e^{-4t} + A_3$$

Since $V(\infty) = A_3$ and $V(\infty) = 0 \rightarrow A_3 = 0$

$$V(0^+) = A_1 + A_2 = -80 \quad \text{Eqn. (I)}$$

$$i_c(t) = C \frac{dV(t)}{dt} = \frac{1}{8} [-A_1 e^{-t} - 4A_2 e^{-4t}] = i_L(t)$$


$$i_L(0^+) = -\frac{A_1}{8} - \frac{A_2}{2} = 10 \rightarrow A_1 + 4A_2 = -80 \quad \text{Eqn. (II)}$$

Solving Eqns. (I) and (II) simultaneously: $A_1 = -80$ & $A_2 = 0$.


$$\therefore V(t) = -80e^{-t} \text{ V, for } t \geq 0$$

(4) (Take-home: Total: 25 points)

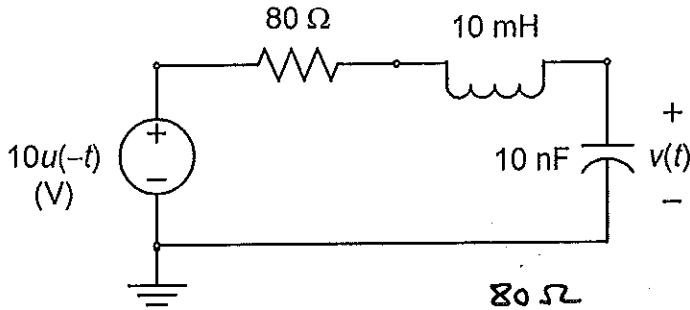(a) (15 points) For the electric circuit shown, find the complete mathematical expression for voltage $v(t)$ across the 10 nF capacitor for $t \geq 0$. Show your work including justifications step by step.



At $t=0^-$ (ss):

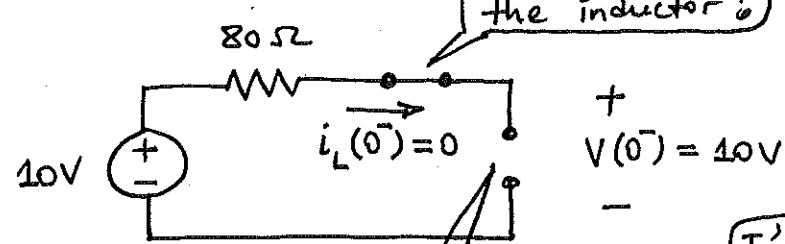


I represent the inductor

I represent the capacitor

I've 0.5 μJ of energy

For $t \geq 0$:

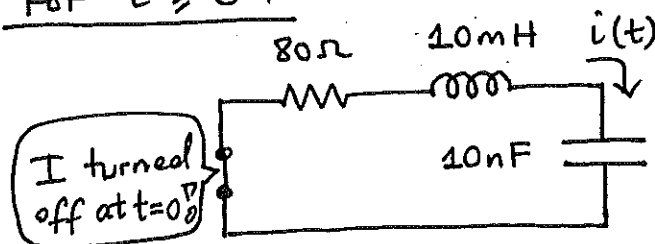

I turned off at $t=0$

Note that $V(0^+) = V(0^-) = 10V$
 $i_L(0^+) = i_L(0^-) = 0$

Series RLC circuit \rightarrow Characteristic equation $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

$$\rightarrow s^2 + \frac{80}{0.01}s + \frac{1}{(0.01)(10^{-8})} = 0 \rightarrow s^2 + 8,000s + 10^{10} = 0$$

Characteristic roots $\rightarrow s_1, s_2 = \frac{-8,000 \pm \sqrt{(8,000)^2 - 4 \times 10^{10}}}{2}$

$\approx -4000 \pm j99,920$ (Underdamped response)

$$\therefore v(t) = A_1 e^{-4,000t} \cos(99,920t) + A_2 e^{-4,000t} \sin(99,920t) + A_3$$

$$v(0^+) = A_1 = 10$$



$$i(t) \Big|_{t=0^+} = C \frac{dv(t)}{dt} \Big|_{t=0^+} = 0$$

$$10^{-8} [-4,000A_1 + 99,920A_2] = i_L(0^+) = 0$$

$$\rightarrow A_2 = \frac{4,000A_1}{99,920} \approx 0.4003$$

$$\therefore v(t) \approx 10e^{-4,000t} \cos(99,920t) + 0.4e^{-4,000t} \sin(99,920t)$$

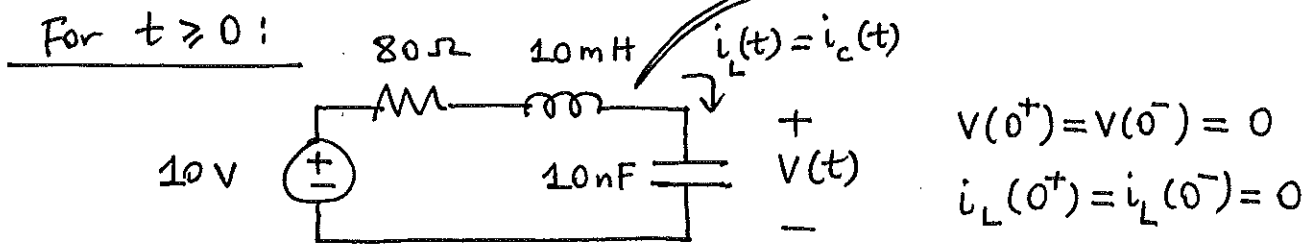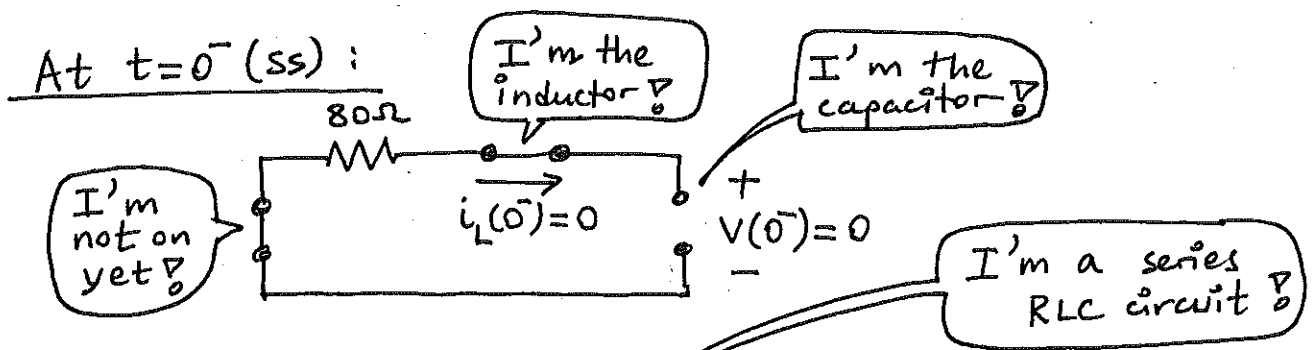(b)(10 points) Repeat part (a) if the source voltage is changed from $10u(-t)$ to $10u(t)$.



Same characteristic roots found in part (a) apply.

$$\therefore V(t) = A_1 e^{-4,000t} \cos(99,920t) + A_2 e^{-4,000t} \sin(99,920t) + A_3$$

$$V(0^+) = A_1 + A_3 = 0$$

$$i_L(0^+) = C \left. \frac{dV(t)}{dt} \right|_{t=0^+} = 10^{-8} [-4,000A_1 + 99,920A_2] = 0 \rightarrow A_1 \approx 24.98A_2$$

$$V(\infty) = A_3 = 10V \text{ since } t \rightarrow \infty \text{ circuit}$$

$V(\infty) = 10V$

I'm the inductor!

I'm the capacitor!

$$\rightarrow A_1 = -A_3 = -10V$$

$$\rightarrow A_2 \approx \frac{A_1}{24.98} \approx -0.4003$$

$$\therefore V(t) \approx -10 e^{-4,000t} \cos(99,920t) - 0.4003 e^{-4,000t} \sin(99,920t) + 10V, \text{ for } t \geq 0$$

