

*University ☺ Portland*  
*School ☺☺ of Engineering*

**EE 261-Electrical Circuits-3 cr. hrs.**  
**Fall 2015**

**Midterm Exam # 2**

(Friday, November 13, 2015)

*Happy Sequential Calendar Date*

*11/13/15!*

(Closed Book Exam, Two Formula Sheets Allowed)

(Total Time: 55 minutes)


**Name:** \_\_\_\_\_ ☺

**Signature:** \_\_\_\_\_ ☺

*“An honest mind possesses a kingdom.”*  
Lucius Annaeus Seneca (4B.C.–65A.D.)


*“Honest people are the true winners of the universe.”*  
Anonymous

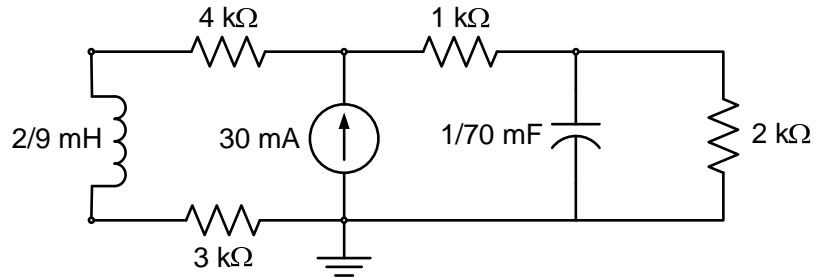1. (25 points) The electric circuit shown below is at DC steady state. Find the energies stored in the capacitor and the inductor. Provide units for your answers. Box your answers.




1	
2	
3	
4	
Total	

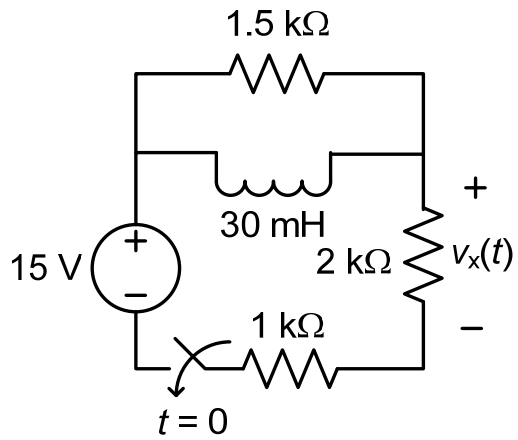2. (25 Points) For the electric circuit shown, find the voltage  $v_x(t)$  across the  $2\text{ k}\Omega$  resistor for  $t > 0$ . Assume the switch to be open for a long time before it closes at  $t = 0$ .



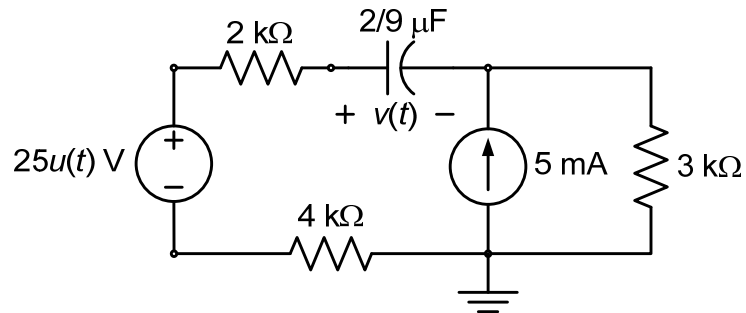3. (25 Points) For the electric circuit shown, find the voltage waveform  $v(t)$  across the capacitor for  $t \geq 0$ . (Hint: Note that the capacitor voltage is not zero at  $t = 0^-$ !)



4. (25 Points) For the op-amp circuit shown, given the source voltage to be  $v_s = 0.21$  V, determine the values of the current  $i_o$  and the voltage  $v_o$ . Provide the correct unit for each answer. Please box your answers.

