

*University of Portland
School of Engineering*

EE 261-Electrical Circuits-3 cr. hrs.
Fall 2015

Midterm Exam # 2

(Friday, November 13, 2015)

Happy Sequential Calendar Date
11/13/15!

(Closed Book Exam, Two Formula Sheets Allowed)
(Total Time: 55 minutes)

Name: SOLUTIONS ☺


Signature: *Synitulos* ☺

Read me
backwards!


*"An honest mind possesses a kingdom."
Lucius Annaeus Seneca (4B.C.-65A.D.)*

*"Honest people are the true winners of the universe."
Anonymous*

A sequential
calendar date?
Wow!

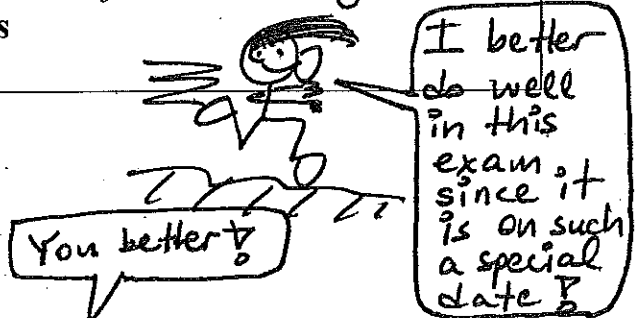

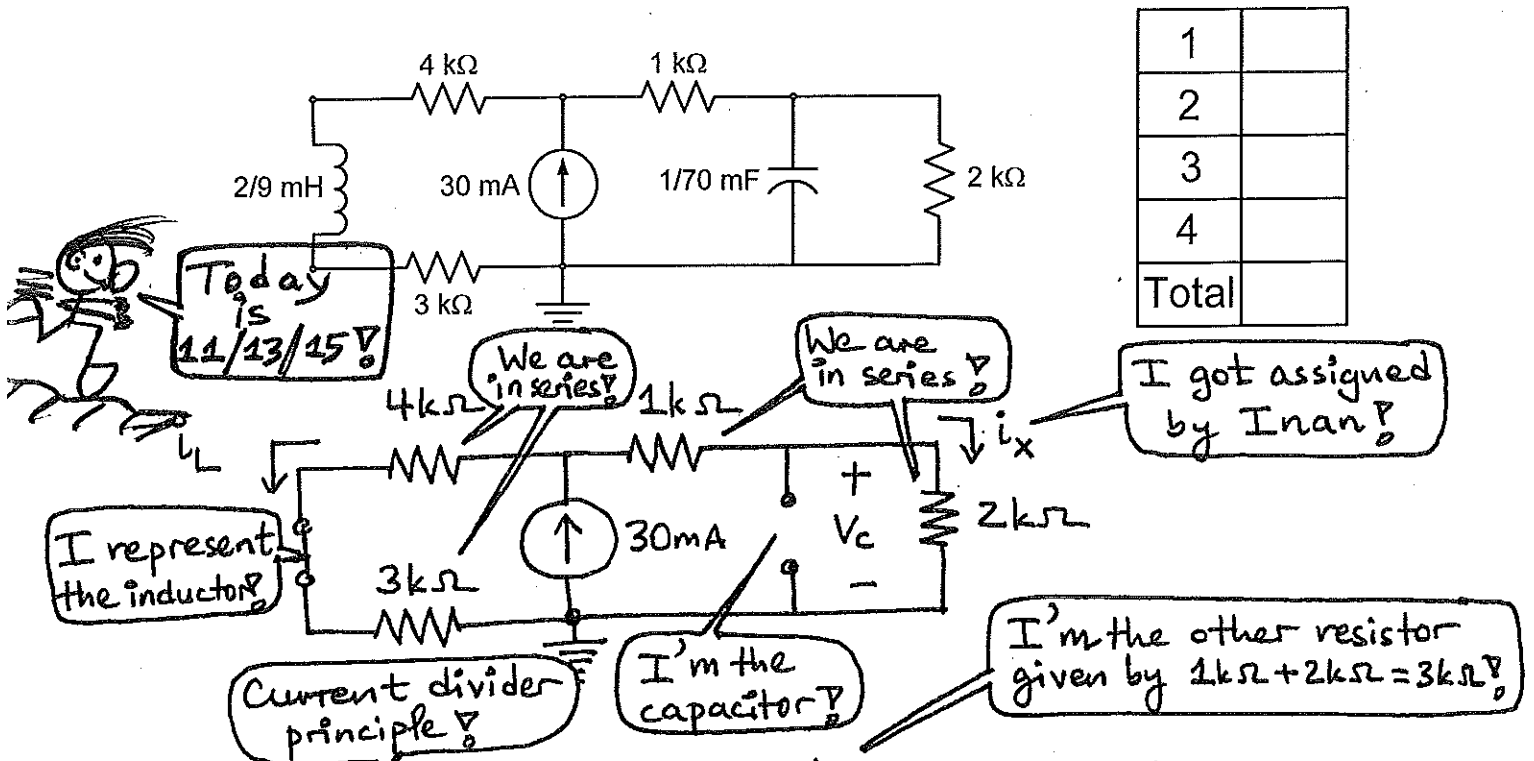1. (25 points) The electric circuit shown below is at DC steady state. Find the energies stored in the capacitor and the inductor. Provide units for your answers. Box your answers.



Using CDP: $i_L = \frac{3k\Omega}{7k\Omega + 3k\Omega} (30mA) = 9mA$

Kirchhoff's current law: $i_x = 30mA - i_L = 21mA$

Energies stored in the capacitor and inductor can be calculated as

I represent capacitor energy: $W_C = \frac{1}{2} C V_C^2 = \frac{1}{2} \left(\frac{1}{70} \times 10^{-3} \right) \left[\underbrace{(2k\Omega) i_x}_{42V} \right]^2$
 $= 0.0126 J = \boxed{12.6 mJ}$

I'm the inductor energy: $W_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \left(\frac{2}{9} \times 10^{-3} \right) (9 \times 10^{-3})^2$
 $= 9 \times 10^{-9} J = \boxed{9 nJ}$


Since 13/15/17 is not a date?

Last odd-numbered sequence calendar date of this century?

I agree!

A sequence of even numbers...

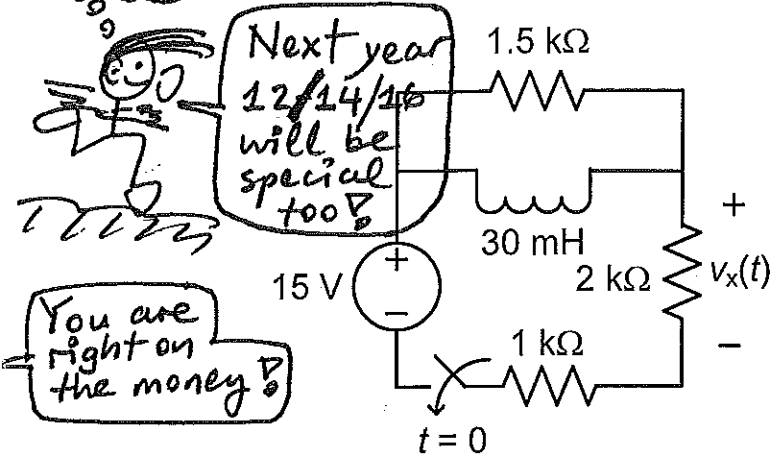
(25 Points) For the electric circuit shown, find the voltage $v_x(t)$ across the $2\text{ k}\Omega$ resistor for $t > 0$. Assume the switch to be open for a long time before it closes at $t = 0$.



Since 1st-order, switching, DC circuit, $v_x(t)$ has the general form:

$$v_x(t) = v_x(0^+) e^{-t/\tau} + v_x(\infty) (1 - e^{-t/\tau}), \text{ for } t > 0.$$


At $t = 0^-$ (steady state):

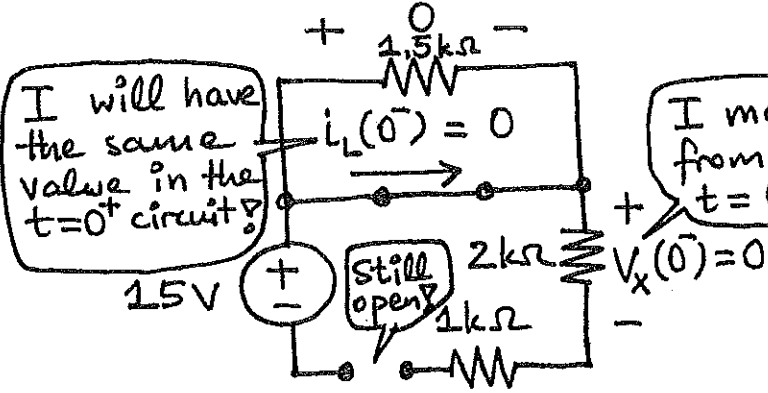

I will have the same value in the $t = 0^+$ circuit?

I may jump from $t = 0^-$ to $t = 0^+$?

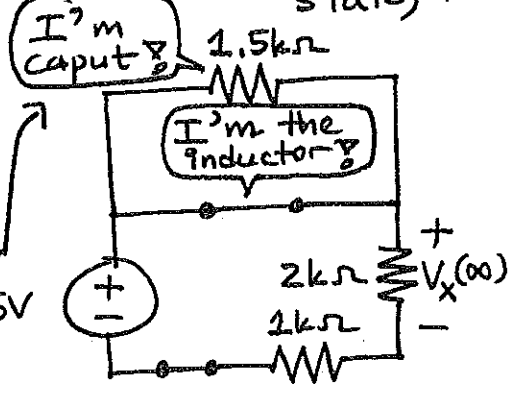
At $t \rightarrow \infty$ (steady state):



I'm a capacitor?

I'm the inductor?

At $t = 0^+$ (not steady state):

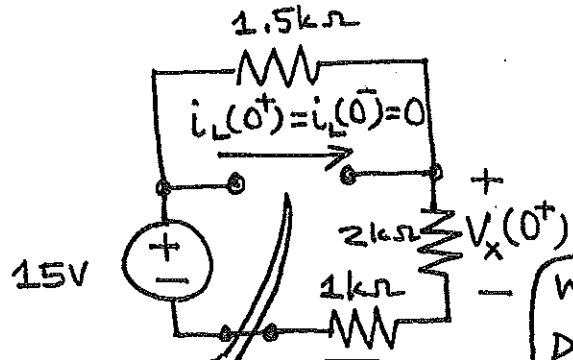

Voltage divider principle?


I represent the inductor with zero current?

Who am I? Do you recognize me?

I got removed?

VDP: $v_x(\infty) = \frac{2\text{ k}\Omega}{3\text{ k}\Omega} (15\text{ V}) = 10\text{ V}$

To find $\tau = \frac{L}{R_T}$

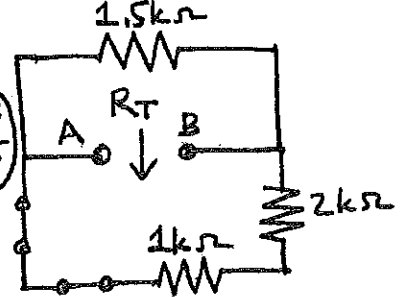

$R_{T\text{ A-B}} = 3\text{ k}\Omega // 1.5\text{ k}\Omega = 1\text{ k}\Omega$

$\tau = \frac{30\text{ mH}}{1\text{ k}\Omega} = 30\text{ }\mu\text{s}$

VDP: $v_x(0^+) = \frac{2\text{ k}\Omega}{4.5\text{ k}\Omega} (15\text{ V}) = \frac{20}{3}\text{ V}$

$v_x(t) = \frac{20}{3} e^{-t/30\text{ }\mu\text{s}} + 10 (1 - e^{-t/30\text{ }\mu\text{s}}) \text{ V, for } t > 0$

3. (25 Points) For the electric circuit shown, find the voltage waveform $v(t)$ across the capacitor for $t \geq 0$. (Hint: Note that the capacitor voltage is not zero at $t = 0^-$)



11/13/17 in 2017 will be a sequence of prime numbers!

Any more?

Yes, keep thinking!

Good job!

Since 1st-order, switching, DC circuit!

$$v(t) = V(0^+) e^{-t/\tau} + V(\infty)(1 - e^{-t/\tau}), \text{ for } t \geq 0$$

At $t = 0^-$ (steady state applies):

I'm still off!

Kirchhoff's voltage law!

$$KVL: V(0^-) = V_{2k\Omega} + V_{4k\Omega} + V_{3k\Omega} = -15V \rightarrow V(0^+) = V(0^-) = -15V$$

I got my value from Ohm's law!

At $t \rightarrow \infty$ (steady state):

I've been on for a long time!

I'm the time constant!

Note that I can't jump!

$$KVL: V(\infty) = 25 - 15 = 10V$$

To find $\tau = R_T C$:

I got eliminated!




How about 4/3/21? 5/4/32? 6/5/43, 7/6/54, and so on?

Now you are talking!

01/23/45! Wow!

1/2/34, 2/3/45, 3/4/56...?

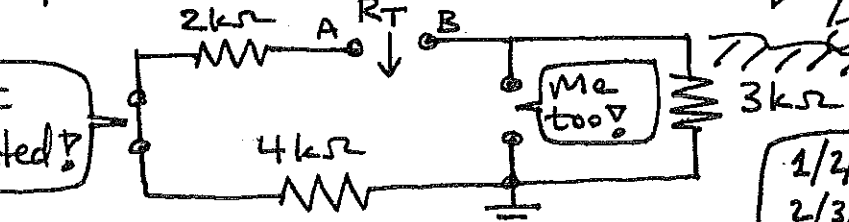


$$R_{T A-B} = (2 + 4 + 3) k\Omega = 9 k\Omega$$

$$\tau = (9 k\Omega) \left(\frac{2}{9} \mu F \right) = 2 \text{ ms}$$

$$\therefore v(t) = -15 e^{-500t} + 10(1 - e^{-500t}) \text{ V, for } t \geq 0$$

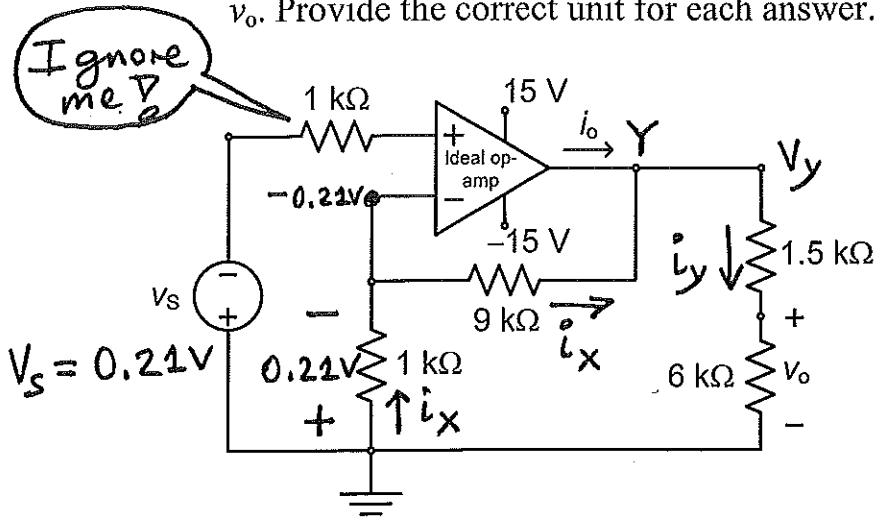4. (25 Points) For the op-amp circuit shown, given the source voltage to be $v_s = 0.21$ V, determine the values of the current i_o and the voltage v_o . Provide the correct unit for each answer. Please box your answers.



$$\text{Ohm} \rightarrow i_x = \frac{0.21\text{V}}{1\text{k}\Omega} = 0.21\text{mA}$$

$$\text{KVL} \rightarrow v_y = -(9\text{k}\Omega)i_x - 0.21 = -1.89 - 0.21 = -2.1\text{V}$$

$$\text{Ohm} \rightarrow i_y = \frac{v_y}{7.5\text{k}\Omega} = -0.28\text{mA}$$

$$\text{VDP} \rightarrow v_o = \frac{6\text{k}\Omega}{7.5\text{k}\Omega}(v_y) = \boxed{-1.68\text{V}}$$

$$\text{KCL at node Y} \rightarrow i_x + i_o = i_y \rightarrow i_o = i_y - i_x$$

$$= -0.28\text{mA} - 0.21\text{mA}$$

$$= \boxed{-0.49\text{mA}}$$



Also 8/13/21 consisting of three consecutive Fibonacci numbers?

Wow! You are in full control!

And thanks for your curiosity and interest in sequential calendar dates!



You are most welcome & thanks for making us aware of these fun dates Inan!