

University of Portland
School of Engineering

EE 261-Electrical Circuits-3 cr. hrs.
Spring 2006

Midterm Exam # 2

(Monday, March 27, 2006)

(Closed Book Exam, Two Formula Sheets Allowed)

(Total Time: 55 minutes)

Name: _____ 😊

Signature :
_____ 😊

“An honest mind possesses a kingdom.”
Lucius Annaeus Seneca (4B.C.–65A.D.)


“Honest people are the true winners of the universe.”
Anonymous

This table will be used by Inan for recording the grades!


Problem #	Points gained
#1	
#2	
#3	
#4	
Total	

NOTE: On all the problems, please show all your work, and provide the appropriate units for your answers. Also mark on the schematic to show any currents or voltages that you define in your solution.

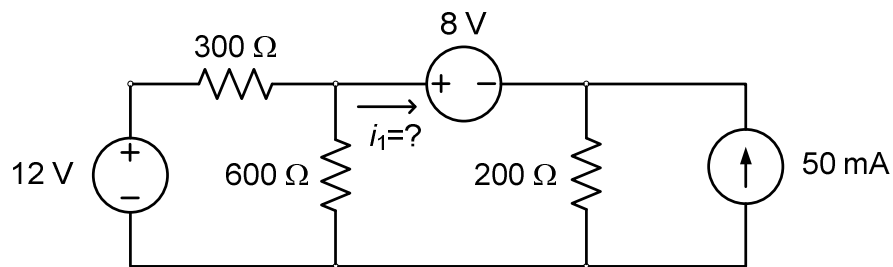1. (25 Points) For the resistive circuit shown, find the current i_1 that flows through the 8 V voltage source as indicated.




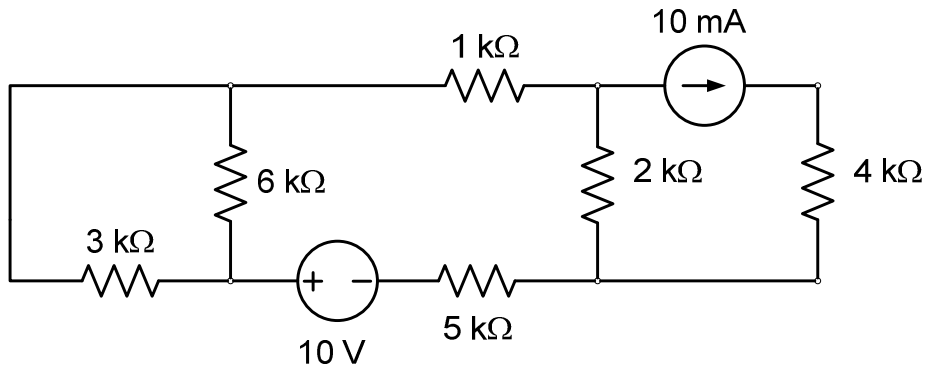2. (25 points) Find the power absorbed by the $2\text{ k}\Omega$ in the circuit shown.



3. (Total: 25 points) Consider the circuit shown below.

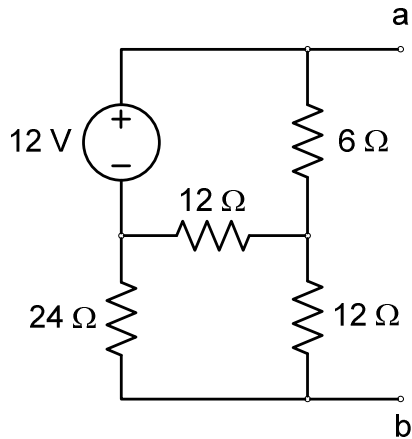(a) (15 Points) Find the value of the load resistance R_L to be connected externally between terminals “a” and “b” such that the power absorbed by R_L is maximized.



(b) (10 Points) Find the maximum value of the power absorbed by R_L .

4. (25 points) In the circuit shown, given the initial condition $i_L(t = 0) = 15$ mA, find the source voltage $v_S(t)$ for $t > 0$. Note that the current through the 50Ω resistor is also given.

