

3/6/2007

*University of Portland  
School of Engineering*

**EE 261-Electrical Circuits-3 cr. hrs.**  
**Spring 2007**

**Midterm Exam # 1**


(Friday, February 16, 2007)  
(Closed Book Exam, One Formula Sheet Allowed)  
(Total Time: 55 minutes)

**Name:** SOLUTIONS! ☺

**Signature:** *Solutions* ☺

*"An honest mind possesses a kingdom."  
Lucius Annaeus Seneca (4B.C.-65A.D.)*

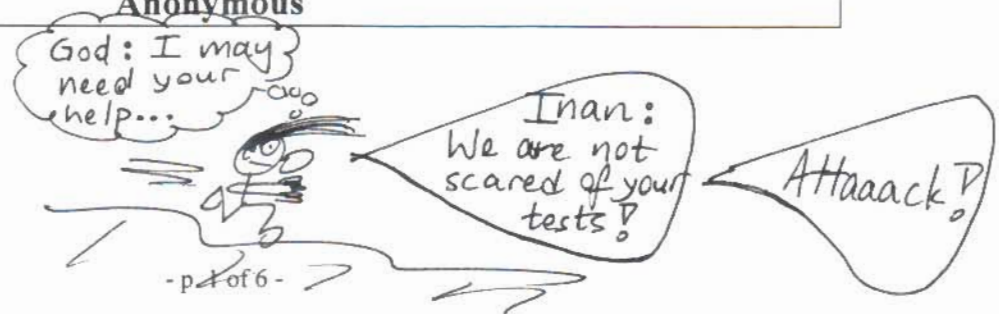*"Honest people are the true winners of the universe."  
Anonymous*




3/6/2007

**NOTE:** On all the problems, please show your work clearly, and provide the appropriate units for your answers. Also mark on the schematic to show any current or voltage that you define in your solution.

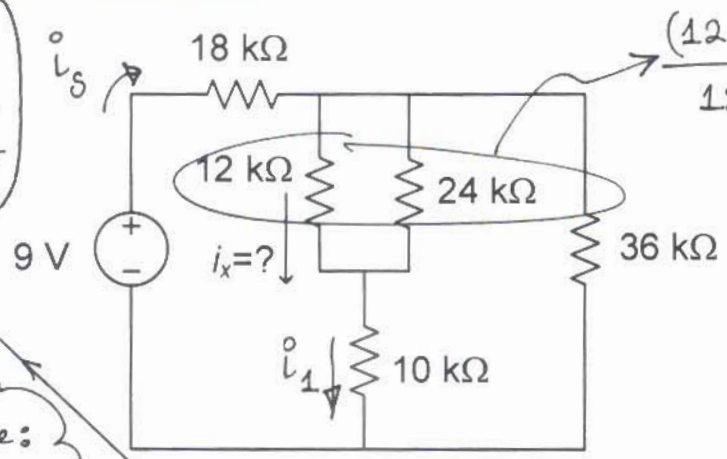1. (25 points) In the circuit shown, find the value of the current  $i_x$  through the 12 kΩ resistor. (Please show your work clearly and provide brief justifications for the steps you take. Also, don't forget to provide the correct units for your answers.)



Come out you coward problems I will get you one by one



$$\frac{(12k)(24k)}{12k+24k} = 8k\Omega$$


Using CDP twice:

$$i_1 = \frac{36k}{18k+36k} (0.3mA) = 0.2mA$$

$$i_x = \frac{24k}{12k+24k} (0.2mA)$$


$$= \frac{0.4}{3} mA$$

$$\approx 0.13 mA$$

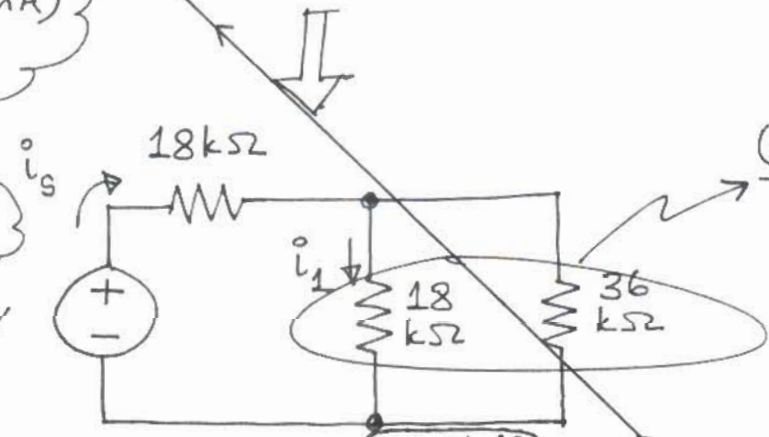

$$\frac{(18k)(36k)}{54k} = 12k\Omega$$

This stuff is a piece of cake

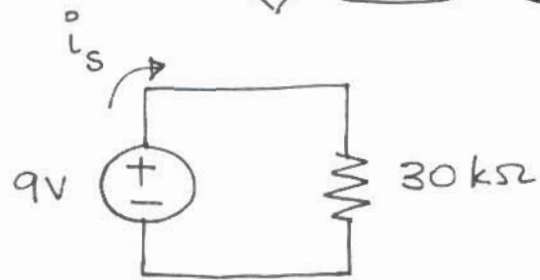


Using Ohm's law,

$$i_s = \frac{9V}{30k\Omega}$$


$$= 0.3 mA$$

3/6/2007

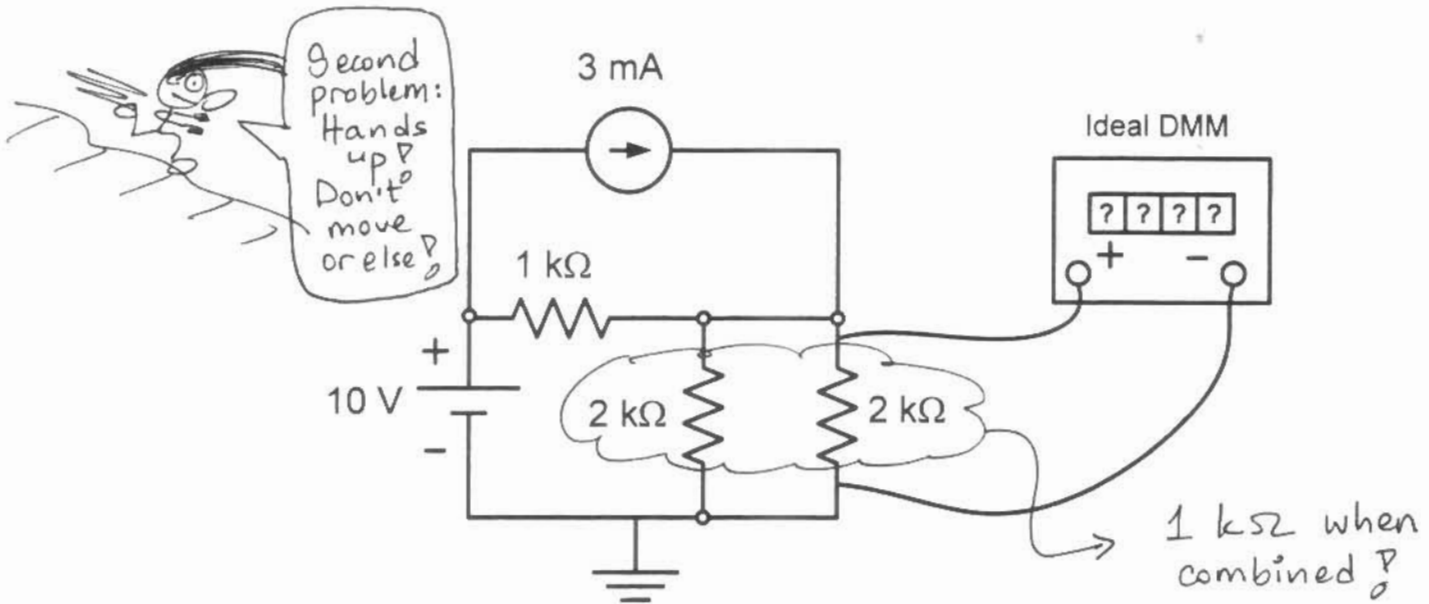2. (Total: 25 Points) Consider the circuit with the ideal DMM connected as shown.



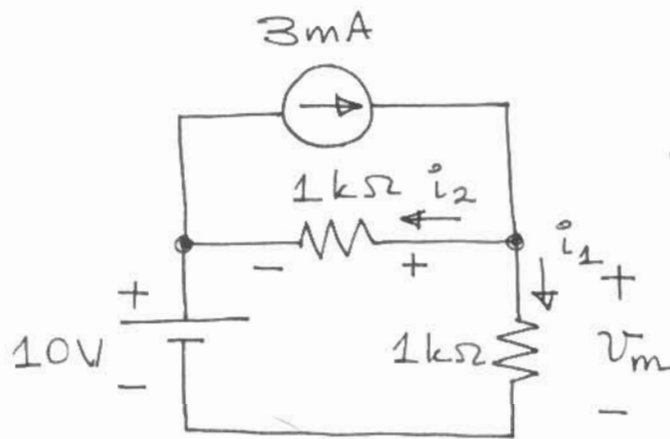(a) (12.5 points) Find the DMM reading if it's set to measure voltage. Please indicate the appropriate units.



voltmeter which acts like an open circuit (or infinite resistance)?

I hope I'm right...

Third problem: You will never forget this moment?

Ohm's law  $\rightarrow i_1 = \frac{V_m}{1k\Omega}$


KCL  $\rightarrow i_2 = 3mA - i_1 = 3mA - \frac{V_m}{1k\Omega}$   
Ohm's law?

KVL  $\rightarrow (1k\Omega) \left( 3mA - \frac{V_m}{1k\Omega} \right) + 10 - V_m = 0$



$\rightarrow 3 - V_m + 10 - V_m = 0 \rightarrow V_m = \frac{13}{2} = \boxed{6.5V}$

3/6/2007

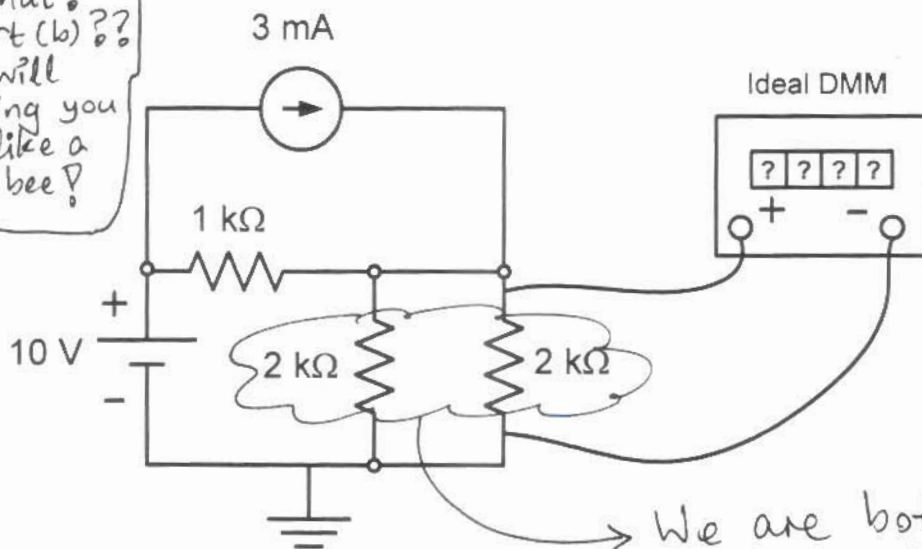(b) (12.5 points) Find the DMM reading if it's set to measure current. Again, indicate your units.



We are both doomed!  
(shorted!)

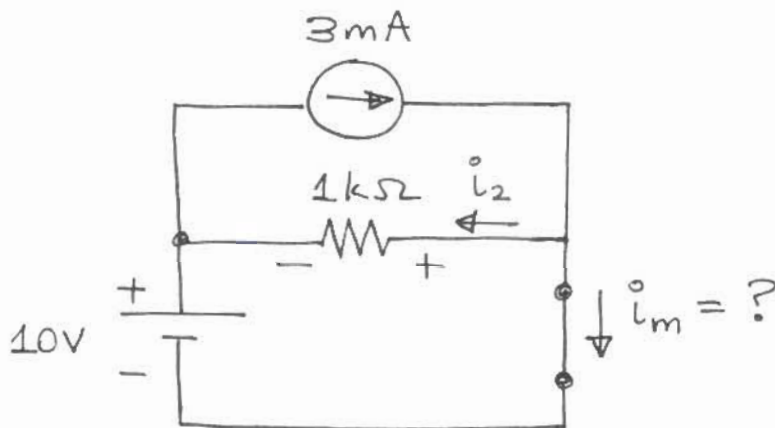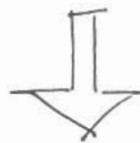

KCL  $\rightarrow i_2 = 3\text{mA} - i_m$

KVL  $\rightarrow (1\text{k}\Omega)(3\text{mA} - i_m) + 10 = 0$   
Ohm's law!

$\rightarrow i_m = \frac{13\text{V}}{1\text{k}\Omega} = \boxed{13\text{mA}}$

-p. 4 of 6-



Call for help because you will need it!

Dependent sources bother me a bit but I shouldn't cave in!


3/6/2007

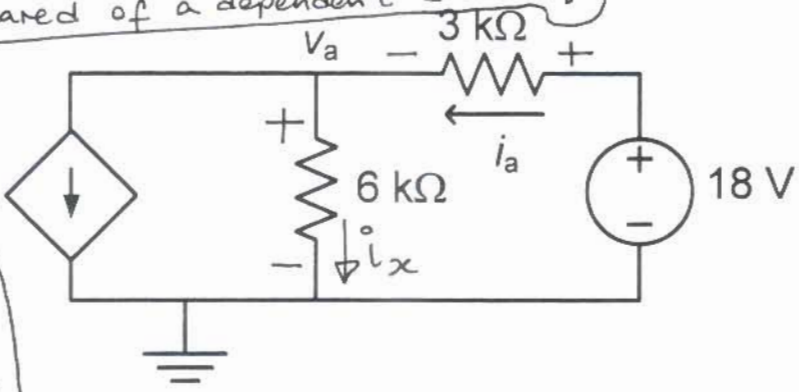3. (25 Points) Consider the circuit shown. Determine the node voltage  $v_a$ . Also, determine the power delivered by the voltage source. Please show your work step by step.



Aha! You think that I will be scared of a dependent source?

You are dead wrong! I will make depend on me for the rest of your life!



KCL  $\rightarrow i_x = i_a - 0.3i_a = 0.7i_a$

KVL  $\rightarrow 18 = (3k\Omega)i_a + (6k\Omega)(0.7i_a) = (7.2k\Omega)i_a$   
Ohm's law!

$\therefore i_a = \frac{18V}{7.2k\Omega} = 2.5\text{ mA}$

$\therefore v_a = (6k\Omega)(0.7i_a) = \boxed{10.5\text{ V}}$

$\therefore P_{18\text{ V source}} = (18\text{ V})(-i_a)$   
 $= (18\text{ V})(-2.5\text{ mA})$   
 $= \boxed{-45\text{ mW}}$

Due to passive convention!

Whew!

I indicate supplied power!

Where are you last problem? I will bust you in your cave!


3/6/2007

God help!  
How much time left?

4. (25 Points) In the circuit shown, find the power of each voltage source. Indicate the type of each power (i.e., supplied or absorbed). Please show your work step by step.

You are under house arrest until I solve you!

Thanks for your help supernode!

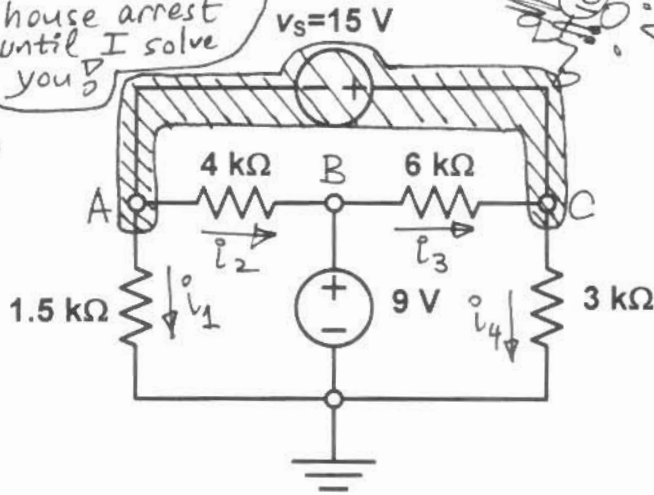

Note that  $v_C - v_A = 15V$

KCL at supernode  $\rightarrow i_1 + i_2 + i_4 = i_3$

$$\rightarrow \frac{v_A}{1.5k} + \frac{v_A - 9}{4k} + \frac{v_C}{3k} = \frac{9 - v_C}{6k} \rightarrow 11v_A + 6v_C = 45$$

$$\rightarrow 11v_A + 6(15 + v_A) = 45 \rightarrow v_A = -\frac{45}{17} V \approx \boxed{-2.65 V}$$

$$\rightarrow v_C = 15 + v_A = 15 - \frac{45}{17} = \frac{210}{17} V \approx \boxed{12.35 V}$$

$$\begin{aligned} \therefore P_{9V \text{ source}} &= (9)(i_2 - i_3) = (9) \left[ \frac{-2.65 - 9}{4k} - \frac{9 - 12.35}{6k} \right] \\ &\approx \boxed{-21.2 \text{ mW}} \end{aligned}$$

$$\begin{aligned} P_{15V \text{ source}} &= (15)(i_3 - i_4) = (15) \left[ \frac{9 - 12.35}{6k} - \frac{12.35}{3k} \right] \\ &\approx \boxed{-70.1 \text{ mW}} \end{aligned}$$

Hurraay!

Done, done, done!

Inan now knows that we are tougher than his tests!