

University of Portland
School of Engineering

EE 261-Electrical Circuits-3 cr. hrs.
Spring 2015

Midterm Exam # 2

(Friday, April 10, 2015)

(Closed Book Exam, Two Formula Sheets Allowed)

(Total Time: 55 minutes)


Name: SOLUTIONS ☺

Signature: *SOLUTIONS* ☺

"An honest mind possesses a kingdom."
Lucius Annaeus Seneca (4B.C.-65A.D.)

"Honest people are the true winners of the universe."
Anonymous

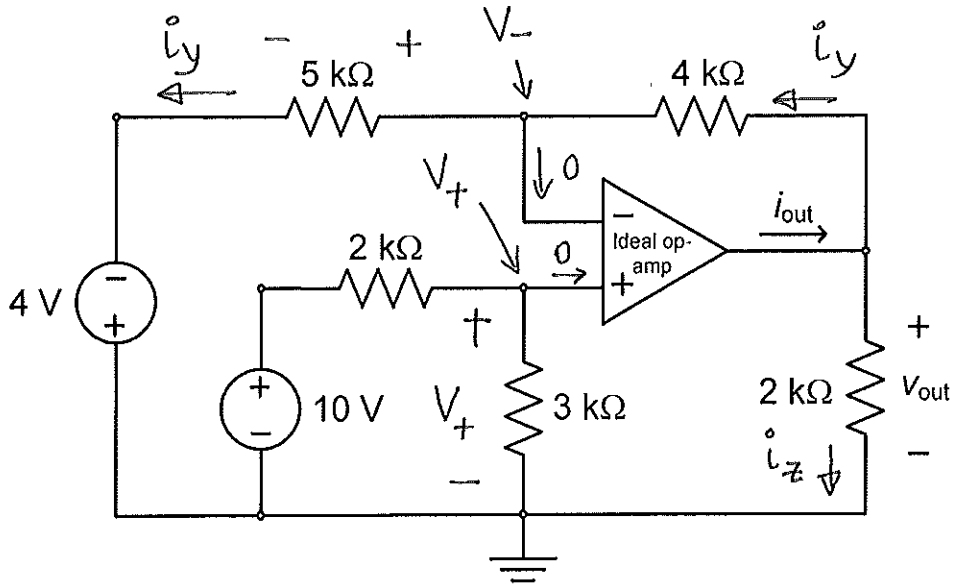1. (15 mins., 30 Points) For the op-amp circuit shown, find the values of the output voltage v_o and the current i_o . Show your work and box your answers with the appropriate units.



$$V_+ \stackrel{\text{VDP}}{=} \frac{3 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} (10 \text{ V}) = 6 \text{ V} = V_-$$

$$i_y = \frac{6 - (-4)}{5 \text{ k}\Omega} = 2 \text{ mA}$$

$$V_{\text{out}} = (4 \text{ k}\Omega) i_y + V_+ = 8 + 6 = \boxed{14 \text{ V}}$$

$$i_z = \frac{V_{\text{out}}}{2 \text{ k}\Omega} = \frac{14 \text{ V}}{2 \text{ k}\Omega} = 7 \text{ mA} \rightarrow i_{\text{out}} \stackrel{\text{KCL}}{=} i_y + i_z$$


$$= (2 + 7) \text{ mA}$$

$$= \boxed{9 \text{ mA}}$$


Inan's table!

Problem # 1	
Problem # 2	
Problem # 3	
Total Score	

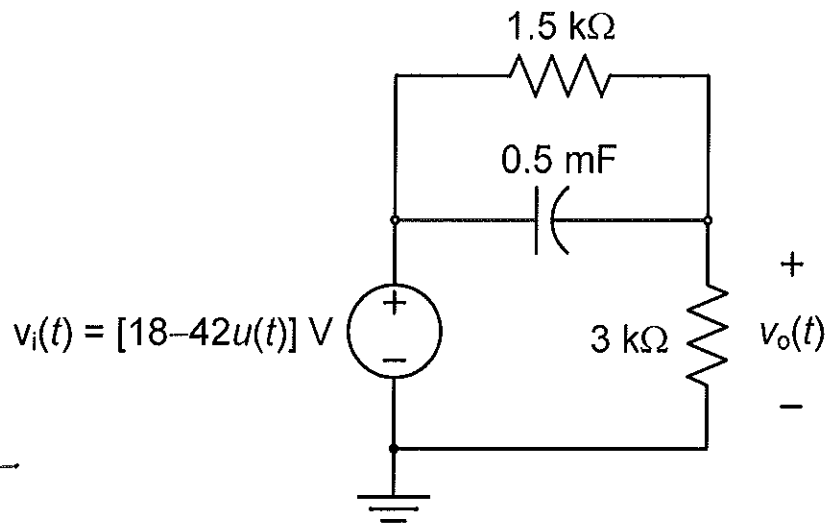2. (15 mins., 30 points) For the circuit shown, find the complete mathematical expression for the voltage $v_o(t)$. Provide your steps and box your answer with the appropriate unit.




At $t = 0^-$ (ss):

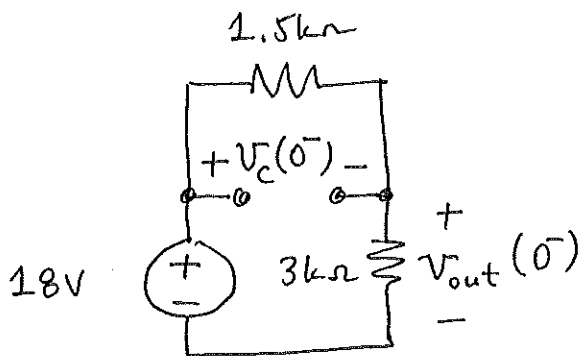

$$V_C(0^-) = \frac{1.5 \text{ k}\Omega}{4.5 \text{ k}\Omega} (18 \text{ V}) = 6 \text{ V}$$


$$V_{\text{out}}(0^-) = 18 - 6 = 12 \text{ V}$$

At $t = 0^+$ (not ss):

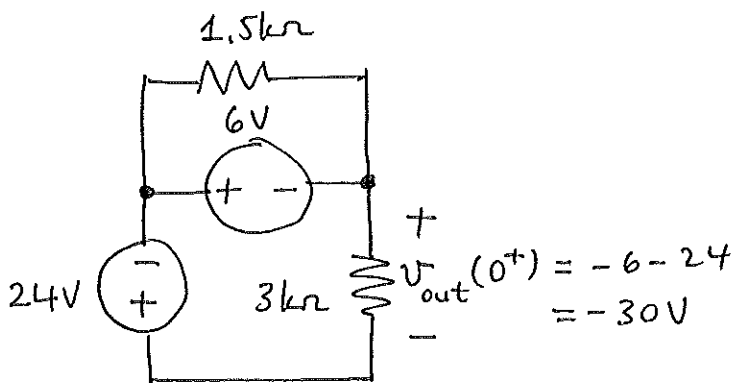


$$V_{\text{out}}(0^+) = -6 - 24 = -30 \text{ V}$$

At $t \rightarrow \infty$ (ss):

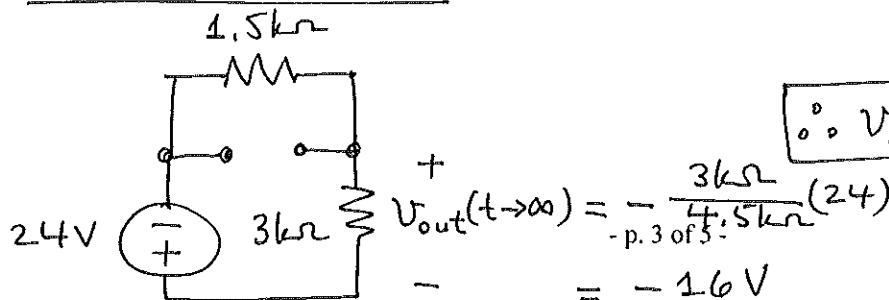

$$V_{\text{out}}(t \rightarrow \infty) = -\frac{3 \text{ k}\Omega}{4.5 \text{ k}\Omega} (24) = -16 \text{ V}$$

To find $\tau = R_{\text{eq}} C$:

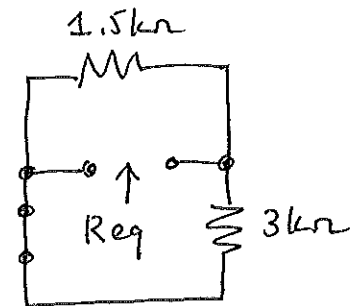


$$R_{\text{eq}} = 1.5 \text{ k}\Omega // 3 \text{ k}\Omega = 1 \text{ k}\Omega$$

$$\tau = R_{\text{eq}} C = (1 \text{ k}\Omega)(0.5 \text{ mF}) = 0.5 \text{ s}$$


$$\therefore V_{\text{out}}(t) = \begin{cases} 12 \text{ V}, & t < 0 \\ -30e^{-2t} - 16(1 - e^{-2t}) \text{ V}, & t > 0 \end{cases}$$

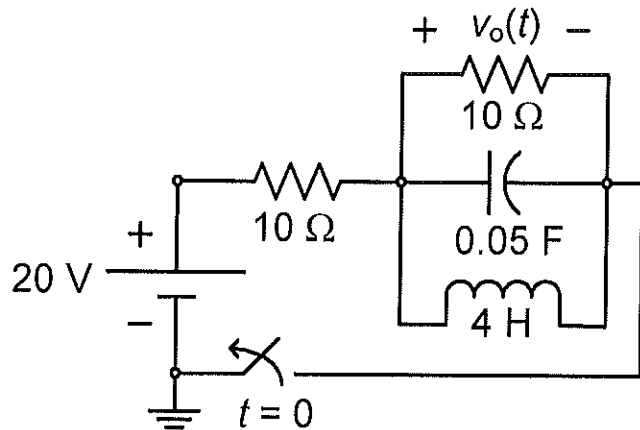3. (15 mins., Total: 40 points) For the circuit shown, the switch opens at $t = 0$, after being closed for a long time. Find the complete mathematical expression for the voltage $v_o(t)$ for $t \geq 0$.



- (a) (10 points) Determine the initial conditions.

At $t = 0^-$ (ss):

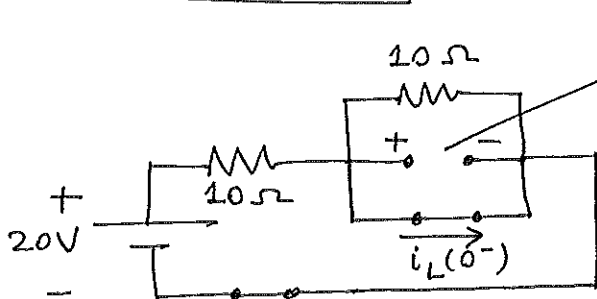


$$v_C(0^-) = 0 = v_o(0^-)$$

$$i_L(0^-) = \frac{20V}{10\Omega} = 2A$$

- (b) (10 points) Determine the characteristic roots and the type of the transient response.

For $t > 0$:

Parallel RLC circuit:

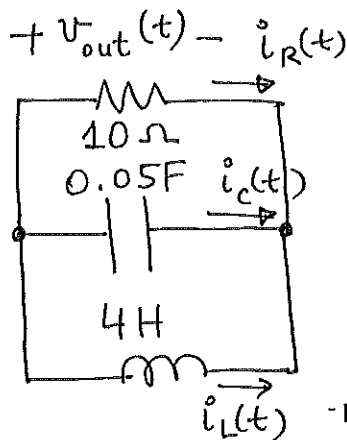

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

$$s^2 + 2s + 5 = 0$$

$$s_1, s_2 = \frac{-2 \pm \sqrt{4 - 20}}{2}$$

$$= -1 \pm j\sqrt{2}$$

- p. 4 of 5 -

Underdamped response!

(c) (20 points) Find the complete mathematical expression for the output voltage $v_o(t)$ for $t \geq 0$.

$$v_o(t) = A_1 e^{-t} \cos(2t) + A_2 e^{-t} \sin(2t) + A_3, t \geq 0.$$

First
initial
condition

$$\rightarrow v_o(0^+) = A_1 + A_3 = v_o(0^-) = 0$$

Final
condition

$$\rightarrow v_o(t \rightarrow \infty) = A_3 = 0 \rightarrow A_1 = 0$$

$$v_o(t) = A_2 e^{-t} \sin(2t)$$

$$\begin{aligned} \text{KCL} \rightarrow \dot{i}_L(t) &= -i_R(t) - \dot{i}_C(t) = -\frac{v_{\text{out}}(t)}{R} - C \frac{dv_{\text{out}}(t)}{dt} \\ &= -\frac{A_2 e^{-t} \sin(2t)}{10} - (0.05) \left[-A_2 e^{-t} \sin(2t) + 2A_2 e^{-t} \cos(2t) \right] \end{aligned}$$

Second
initial
condition

$$\rightarrow \dot{i}_L(0^+) = -0.1 A_2 = 2 \rightarrow A_2 = -20$$

$$\therefore v_o(t) = -20 e^{-t} \sin(2t) \text{ V, for } t \geq 0$$