

*University of Portland  
School of Engineering*

**EE 262- Signals & Systems-3 cr. hrs.**  
**Spring 2011**

**Midterm Exam # 2**

(Prepared by Professor A. S. Inan)



Bonjour!  
Obtenez l'ensemble!  
Pret? Allez!!

(Wednesday, March 30, 2011)

Name: \_\_\_\_\_ 😊

Signature: \_\_\_\_\_ 😊

*“Honesty is the best policy.”*

Aesop (~ 620B.C. -?)

*“An honest mind possesses a kingdom.”*


Lucius Annaeus Seneca (4B.C.–65A.D.)

*“Honest people are the true winners of the universe.”*


Anonymous

Select and do any 4 of the 5 problems assigned during class time. The fifth problem is a take-home problem due class time on Friday, April 1, 2011.

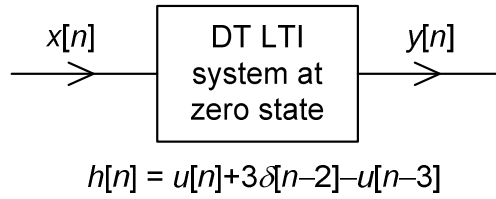(1) (20 points). **DT LTI system.** The unit impulse of a DT LTI system is given below. Find and sketch the zero-state response  $y_{zs}[n]$  of this system due to input signal  $x[n] = 2\delta[n] - 3\delta[n-2]$ .



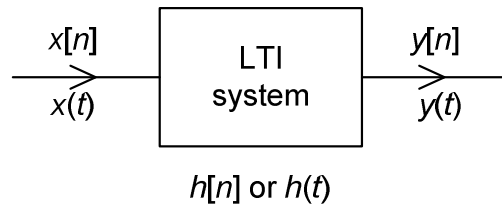
- (2) (Total: 15 points) **LTI system.** For each of the following unit impulse responses corresponding to an LTI system, determine whether the system is (a) Memoryless, (b) Causal, and (c) BIBO stable. Provide a clear justification for each answer.



(a) (7.5 points)  $h[n] = (1 - n)u[n - 1]$

(b) (7.5 points)  $h(t) = 2 \sin(\pi t)u(t - 1)$

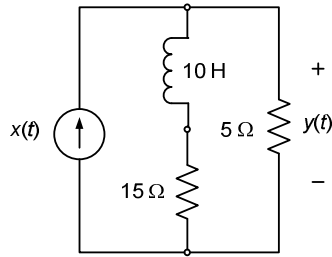(3) (Total: 25 points) **Electric circuits.** For the electric circuit shown:




(a) (10 points) Find its transfer function  $H(s)$ . Provide your work step by step.

(b) (10 points) Find the impulse response  $h(t)$ . Show your work.

(c) (5 points) Find the unit step response  $y_s(t)$ . Provide your work.

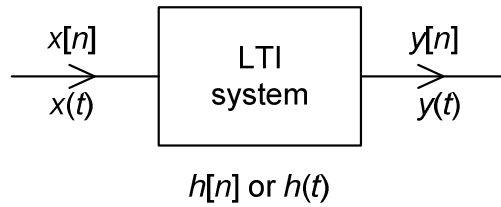(4) (Total: 20 points) **LTI system.** Consider an LTI system.



(a) (10 points) If the system is continuous time, given the unit-step response of the system to be

$$y_s(t) = (5te^{-t} + 11e^{-t} - 3)u(t)$$


Find the unit-impulse response  $h(t)$  of the system. What is  $h(2)$ ?

(b) (10 points) If the system is discrete time, given the impulse response of the system to be

$$h[n] = \left(\frac{1}{2}\right)^n u[n]$$

Find the unit-step response  $y_s[n]$  of the system. What is  $y_s[2]$ ?

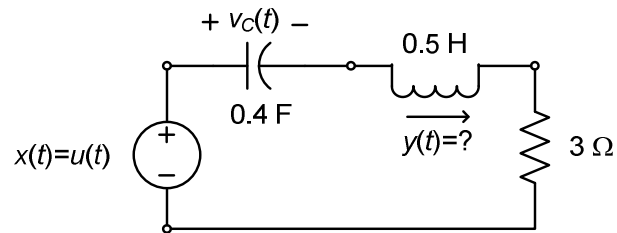- (5) (Total: 20 points) **Electric circuits.** In the circuit shown, assuming  $v_C(0^-) = -3 \text{ V}$  and  $y(0^-) = 0.5 \text{ A}$ , do the following:



- (a) (10) Draw the Laplace domain circuit with all the numerical values provided.

- (b) (10) Using part (a) circuit, obtain  $Y(s)$  and perform inverse Laplace on it to obtain  $y(t)$  for  $t > 0$ .