
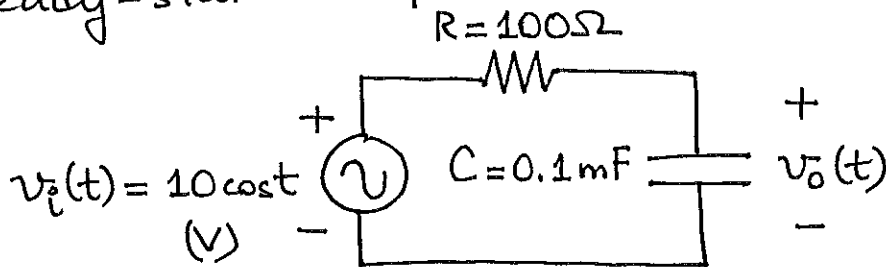


Review of Sinusoidal (AC) Steady-State Circuits

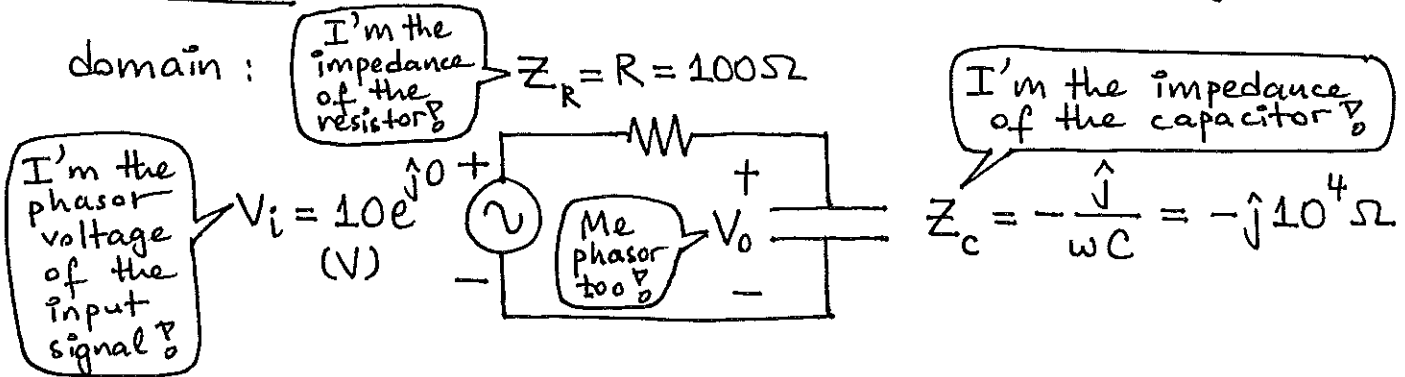Example #1 For the circuit shown, find the steady-state output voltage  $v_o(t)$ .



Solution: Beam the circuit into the imaginary phasor domain:



Using VDP, we can write:

$$V_o = \frac{Z_2}{Z_1 + Z_2} V_i = \left( \frac{-\frac{j}{\omega C}}{R - \frac{j}{\omega C}} \right) V_i = \frac{-j10^4}{100 - j10^4} \quad (10)$$

Note that  $H(j\omega) = H(s)|_{s=j\omega}$

Frequency response  $H(j\omega)$


$$= \frac{10^4 e^{-j\frac{\pi}{2}}}{\sqrt{10^4 + 10^8} e^{-j \tan^{-1}(100)}} \quad (10) = \frac{10^5}{\sqrt{10^4 + 10^8}} e^{j(\tan^{-1}(100) - \frac{\pi}{2})}$$

$$\approx 9.9995 e^{-j0.57294^\circ} \quad (V)$$


Converting phasor voltage  $V_o$  back into time domain:

$$v_o(t) \approx 9.9995 \cos(t - 0.57294^\circ) \quad (V)$$

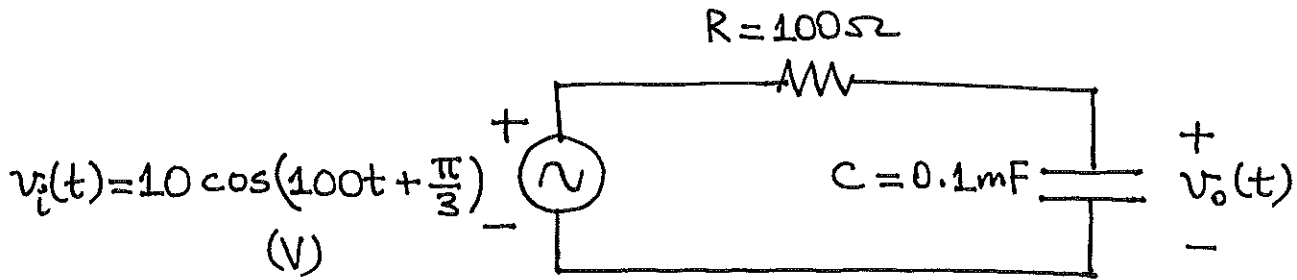Example # 2 For the circuit shown, find the steady-state voltage  $v_o(t)$ .



Solution: Following the same steps:

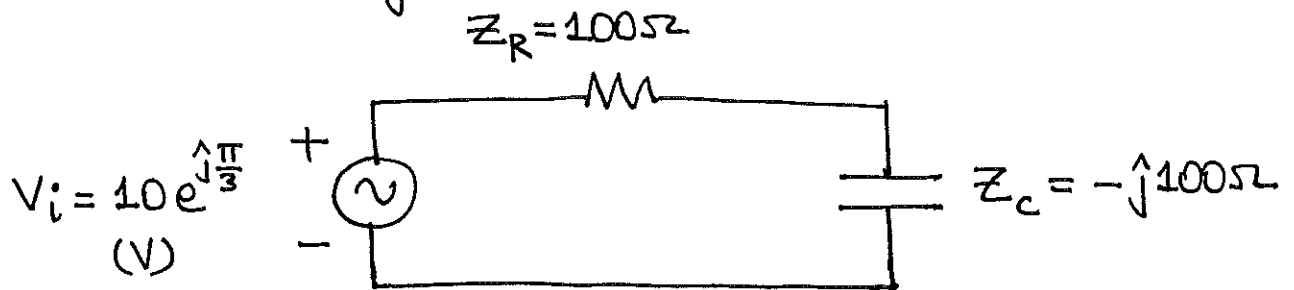


$$\begin{aligned} \text{VDP: } V_o &= H(j100) V_i = \frac{-j100}{100 - j100} (10 e^{j\frac{\pi}{3}}) \\ &= \frac{100 e^{-j\frac{\pi}{2}}}{100\sqrt{2} e^{-j\frac{\pi}{4}}} (10 e^{j\frac{\pi}{3}}) \\ &= \frac{10}{\sqrt{2}} e^{j(-\frac{\pi}{2} + \frac{\pi}{3} + \frac{\pi}{4})} = \frac{10}{\sqrt{2}} e^{j\frac{\pi}{12}} \approx 7.0711 e^{j15^\circ} \text{ (V)} \end{aligned}$$


or  $\pi/12$

$\therefore v_o(t) \approx 7.0711 \cos(100t + 15^\circ) \text{ (V)}$

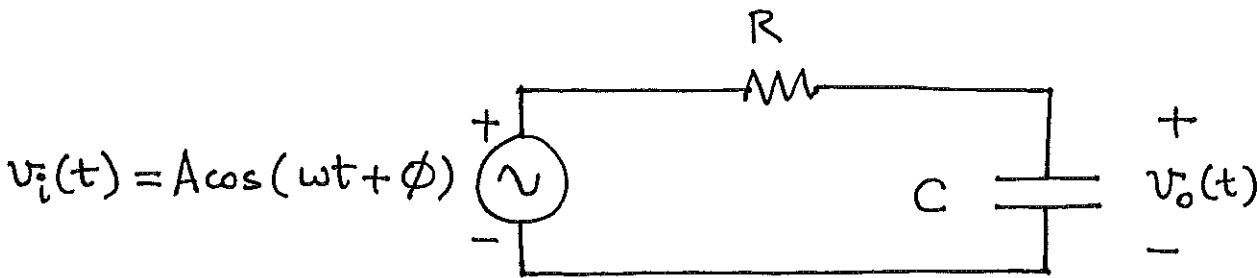Example #3 For the circuit shown, find the steady-state  $v_o(t)$ .



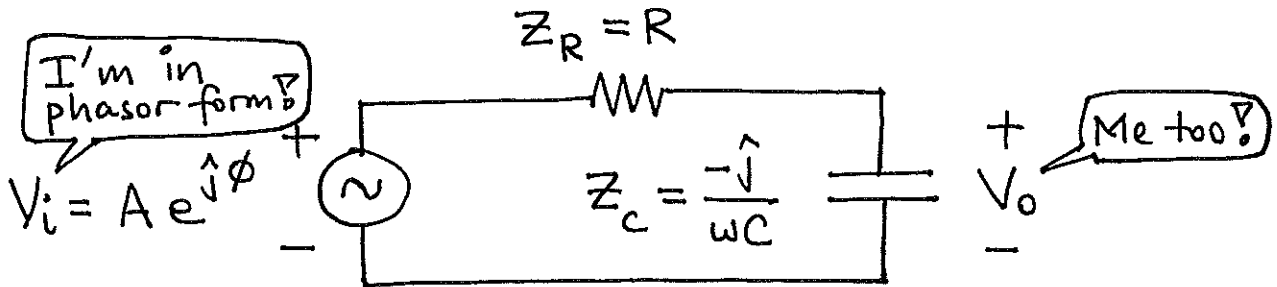Solution: Beam the circuit into phasor domain:



VDP:

$$V_o = \left( \frac{-\frac{j}{\omega C}}{R - \frac{j}{\omega C}} \right) (A e^{j\phi})$$

Note that this is  $H(j\omega)$

$$= \frac{\frac{1}{\omega C} e^{-j\pi/2}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} e^{j \tan^{-1}(1/\omega RC)}} (A e^{j\phi})$$

$$= \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{j \left( \tan^{-1}\left(\frac{1}{\omega RC}\right) - \frac{\pi}{2} \right)} A e^{j\phi}$$


I'm the magnitude of the frequency response

I'm the angle of the frequency response

$$= |H(j\omega)| A e^{j(\phi + \angle H(j\omega))}$$

$$\therefore v_o(t) = |H(j\omega)| A \cos(\omega t + \phi + \angle H(j\omega))$$

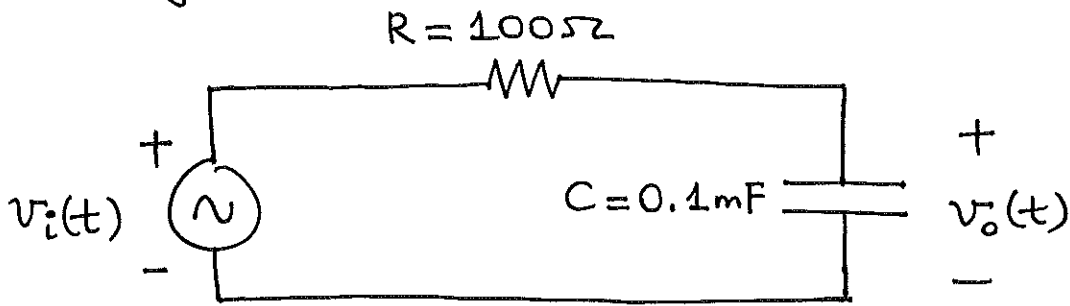Example #4 For the circuit shown, find page#4  
the steady-state output voltage  $v_o(t)$ .




$$v_i(t) = 10 + 10 \cos t + 10 \cos(100t) + 10 \cos(10^4 t) \text{ (V)}$$


I represent a periodic signal!

Indeed, I am its Fourier series!


Solution: Redraw the circuit as follows:

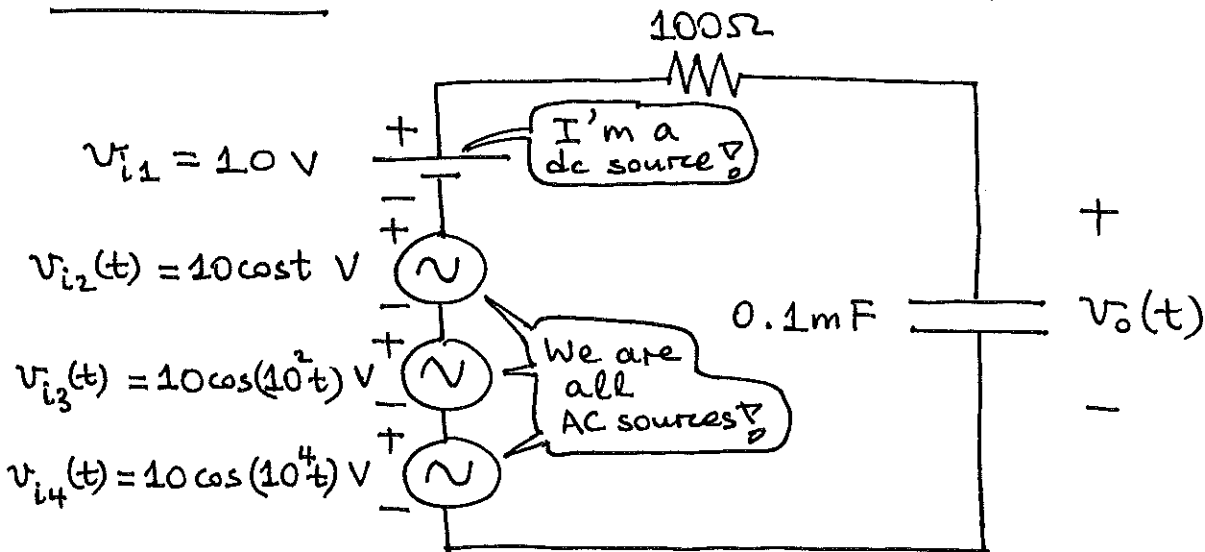

Using superposition principle:

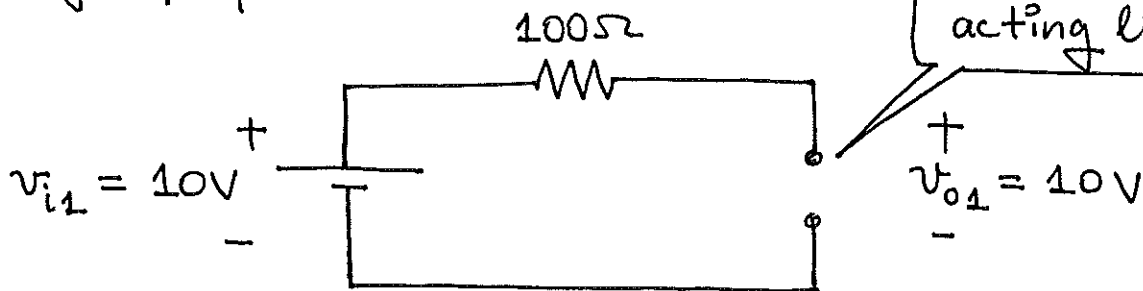

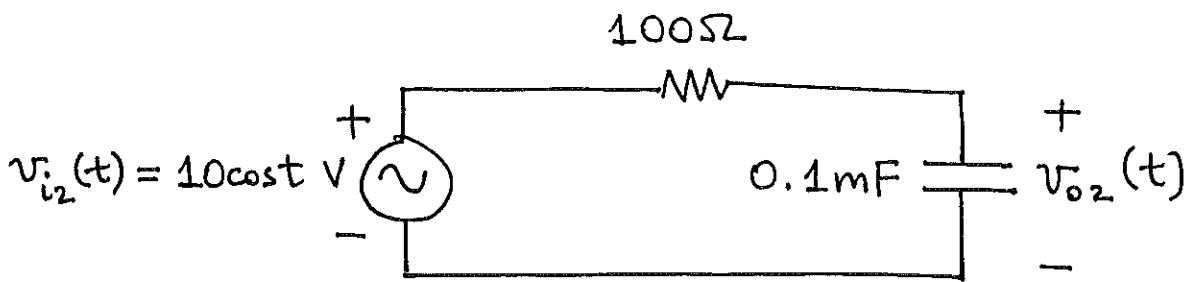(Note that from Example #1, at  $\omega = 0$ ,  $H(j\omega) = 1$ .)



Using the phasor-domain circuit, we find  $v_{o2}(t)$  to be


$$v_{o2}(t) = |H(j\omega)| (10) \cos(t + \angle H(j\omega))$$

From Example #3

$$= \frac{1}{\sqrt{1+10^{-4}}} (10) \cos(t + \underbrace{\tan^{-1}(100) - \pi/2}_{\angle H(j\omega)})$$

From Example #3
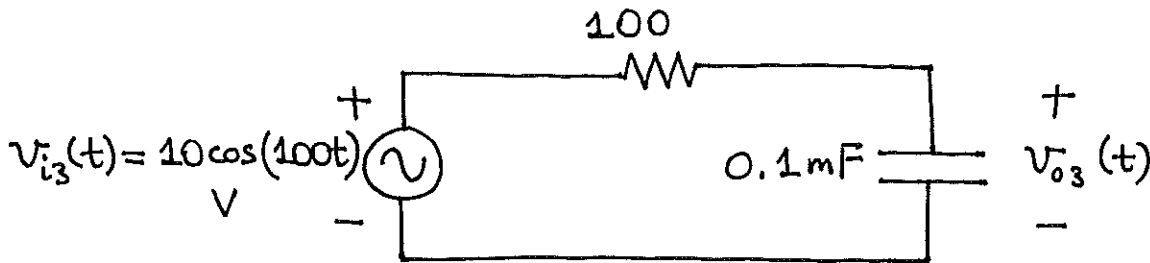
$$\approx 9.9995 \cos(t - 0.57294^\circ) \text{ (V)} \leftarrow \text{(Check Example #1)}$$



Following similar steps:


$$v_{o3}(t) = |H(j100)| (10) \cos(100t + \angle H(j100))$$

$$|H(j100)| = \frac{1}{\sqrt{1+(10^4)(10^{-4})}} = \frac{1}{\sqrt{2}} \approx 0.70711$$

Use the result of Example #3 to calculate us

$$\angle H(j100) = \tan^{-1}(1) - \frac{\pi}{2} = -\frac{\pi}{4}$$
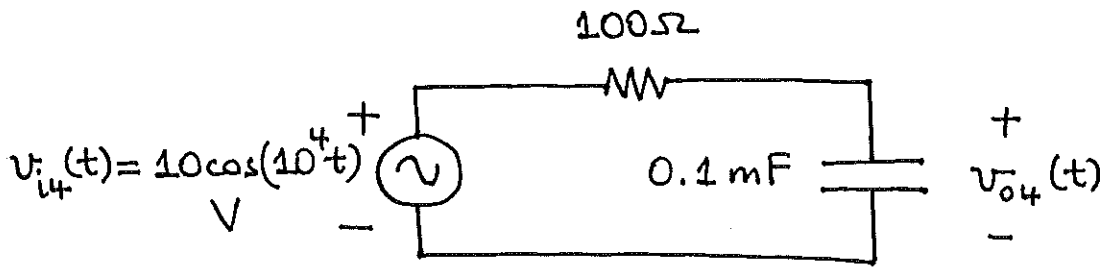
$$\therefore v_{o3}(t) \approx 7.0711 \cos(100t - \frac{\pi}{4}) \text{ (V)}$$



$$v_{o4}(t) = |H(j10^4)| (10) \cos(10^4 t + \angle H(j10^4))$$

Using the results of Example #3 :

$$|H(j10^4)| = \frac{1}{\sqrt{1+(10^8)(10^{-4})}} \approx 0.0099995$$

$$\angle H(j10^4) = \tan^{-1}(10^{-2}) - \frac{\pi}{2} \approx -89.427^\circ$$

$$\therefore v_{o4}(t) \approx \underbrace{0.099995}_{\sim 0.1} \cos(10^4 t - 89.427^\circ) \text{ (V)}$$

$$\therefore v_o(t) \approx 10 + 10 \cos(t - 0.573^\circ) + 7.07 \cos(100t - 45^\circ) + 0.1 \cos(10^4 t - 89.4^\circ) \text{ (V)}$$


I'm the Fourier series of the output signal?

Exercise # 1 For the circuit shown, given :

$$v_i(t) = 10 + 10 \sin t + 10 \sin(10t) + 10 \sin(100t)$$

Find the steady-state output voltage  $v_o(t)$ .

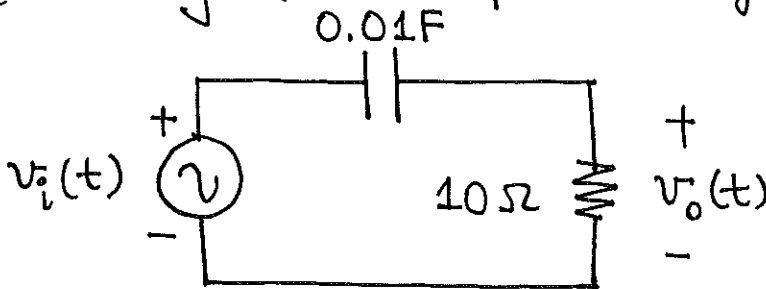I'm the Fourier series of a periodic signal?




Exercise # 2 For the circuit shown, given:

I'm also a Fourier series!

$$v_i(t) = 10 + 6 \cos(10t - \frac{\pi}{4}) - 8 \sin(100t + \frac{\pi}{3})$$

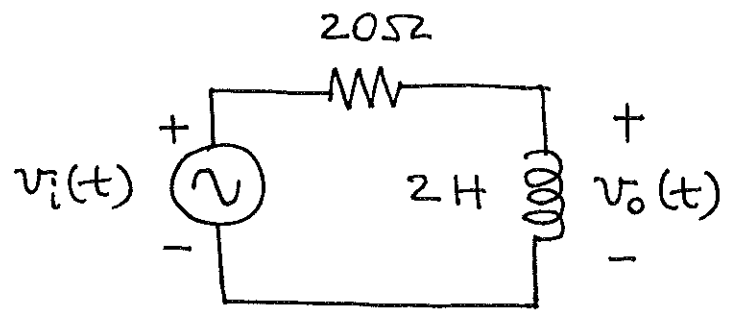Find the steady-state output voltage  $v_o(t)$ .



Exercise # 3 Repeat the previous exercise for the circuit shown below.

