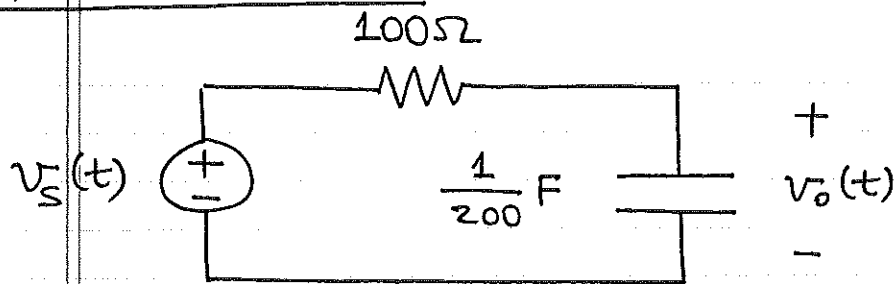


Practice Problem:




In the above circuit, $x(t) = v_s(t)$ and $y(t) = v_o(t)$.

Find the following:


- (a) $H(s)$ (transfer function)
- (b) $h(t)$ (impulse response)
- (c) $v_o(t)$ when $v_s(t) = 10u(t)$
- (d) $v_o(t)$ when $v_s(t) = 10u(-t)$
- (e) $v_o(t)$ when $v_s(t) = 10 + 10u(-t)$
- (f) $v_o(t)$ when $v_s(t) = 10e^{-t}u(t)$
- (g) $v_o(t)$ when $v_s(t) = 10te^{-t}u(t)$
- (h) $v_o(t)$ when $v_s(t) = 10\cos(3t)u(t)$
- (i) $v_o(t)$ when $v_s(t) = 10e^{-t}u(t) + 10u(-t)$
- (j) $v_o(t)$ when $v_s(t) = 10\cos(3t)u(t) - 10u(-t)$

Practice Problem:

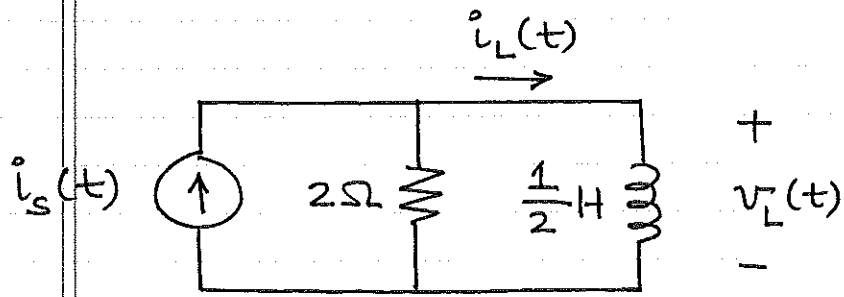


In the above circuit, $x(t) = i_s(t)$ and $y_1(t) = i_L(t)$ and $y_2(t) = v_L(t)$.

Practice Problem:

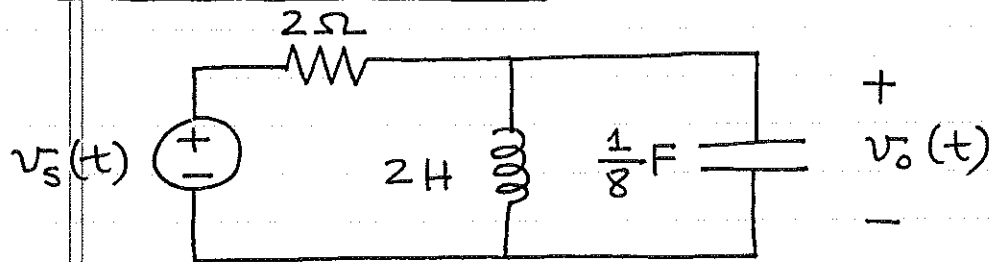


In the above circuit, $x(t) = v_s(t)$ and $y(t) = v_o(t)$.

Practice Problem:

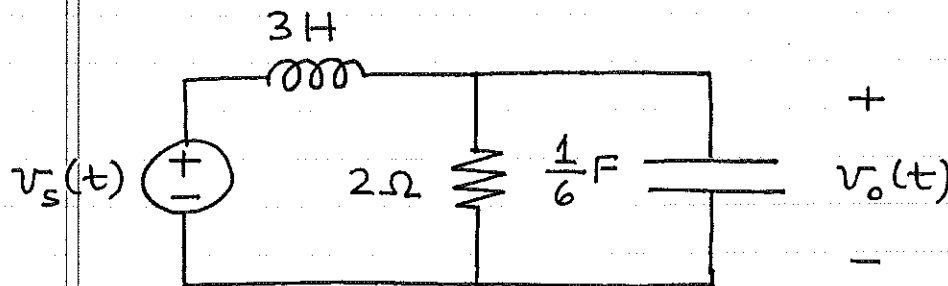


In the above circuit, $x(t) = v_s(t)$ and $y(t) = v_o(t)$.

Practice Problem:

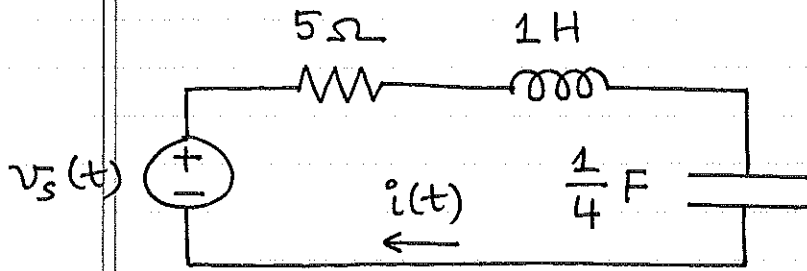

In the above circuit, $x(t) = v_s(t)$ and $y(t) = i(t)$.

Practice Problem:

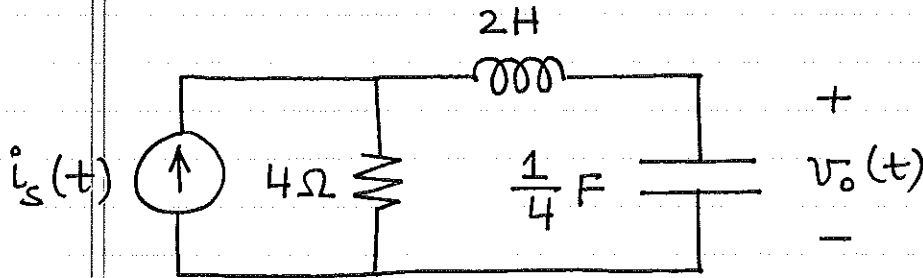

In the above circuit, $x(t) = i_s(t)$ and $y(t) = v_o(t)$.