
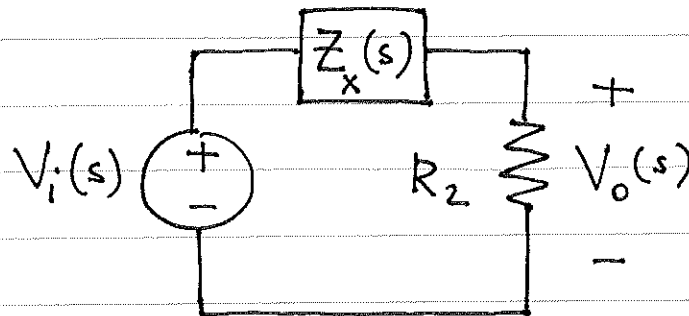


EE 262 SPRING 2014 FINAL EXAM :

SOLUTION TO PROBLEM (5) :

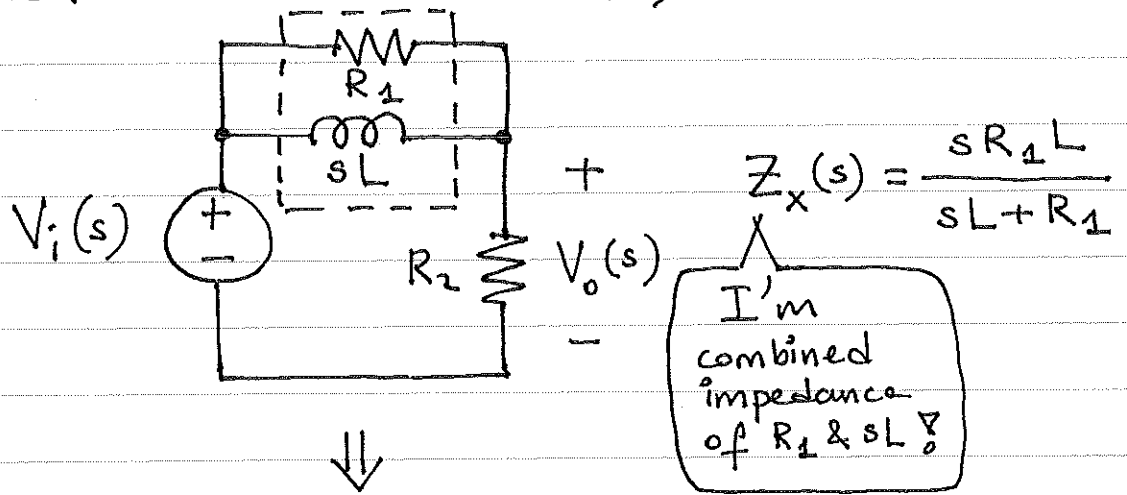

$$V_o(s) = \frac{R_2}{\frac{sR_1L}{sL + R_1} + R_2} V_i(s)$$

$$\rightarrow H(s) = \frac{V_o(s)}{V_i(s)} = \frac{R_2(sL + R_1)}{sL(R_1 + R_2) + R_1R_2}$$

I'm the transfer function!

$$= \frac{R_2L(s + R_1/L)}{L(R_1 + R_2) \left( s + \frac{R_1R_2}{(R_1 + R_2)L} \right)}$$

Substituting the values of the elements:

$$H(s) = \frac{3(s + 10^4\pi)}{4(s + 7500\pi)}$$

To find the frequency response, substitute  $s$  with  $j\omega$ :

$$H(j\omega) = \frac{3(j\omega + 10^4\pi)}{4(j\omega + 7500\pi)}$$

I'm the frequency response

$$= \frac{3}{4} \underbrace{\sqrt{\frac{\omega^2 + (10^4\pi)^2}{\omega^2 + (7500\pi)^2}}}_{|H(j\omega)|} e^{j \underbrace{\left[ \tan^{-1} \frac{\omega}{10^4\pi} - \tan^{-1} \frac{\omega}{7500\pi} \right]}_{\angle H(j\omega)}}$$

(harmonics)

The first three terms of the Fourier series of the input signal  $v_i(t)$  are given by:

$$v_i(t) = \frac{20}{\pi} \sin(\overbrace{3000\pi t}^{\omega_0}) - \frac{10}{\pi} \sin(\overbrace{6000\pi t}^{2\omega_0}) + \frac{20}{3\pi} \sin(\overbrace{9000\pi t}^{3\omega_0})$$

The first three terms (harmonics) of the Fourier series of the output signal  $v_o(t)$  can be found as follows:

$$v_o(t) = \frac{20}{\pi} |H(j\omega_0)| \sin(3000\pi t + \angle H(j\omega_0)) \\ - \frac{10}{\pi} |H(j2\omega_0)| \sin(6000\pi t + \angle H(j2\omega_0)) \\ + \frac{20}{3\pi} |H(j3\omega_0)| \sin(9000\pi t + \angle H(j3\omega_0))$$

3000 $\pi$

$$|H(j\omega_0)| = \frac{3}{4} \sqrt{\frac{(3000\pi)^2 + (10^4\pi)^2}{(3000\pi)^2 + (7500\pi)^2}} \approx 0.9694$$

$$|H(j2\omega_0)| = \frac{3}{4} \sqrt{\frac{(6000\pi)^2 + (10^4\pi)^2}{(6000\pi)^2 + (7500\pi)^2}} \approx 0.9106$$

$$|H(j3\omega_0)| = \frac{3}{4} \sqrt{\frac{(9000\pi)^2 + (10^4\pi)^2}{(9000\pi)^2 + (7500\pi)^2}} \approx 0.8613$$

$$\angle H(j\omega_0) = \underbrace{\tan^{-1}\left(\frac{3000\pi}{10^4\pi}\right)}_{\sim 16.7^\circ} - \underbrace{\tan^{-1}\left(\frac{3000\pi}{7500\pi}\right)}_{\sim 21.8^\circ} \approx -5.1^\circ$$


$$\angle H(j2\omega_0) = \underbrace{\tan^{-1}\left(\frac{6000\pi}{10^4\pi}\right)}_{\sim 30.96^\circ} - \underbrace{\tan^{-1}\left(\frac{6000\pi}{7500\pi}\right)}_{\sim 38.66^\circ} \cong -7.696^\circ$$

$$\angle H(j3\omega_0) = \underbrace{\tan^{-1}\left(\frac{9000\pi}{10^4\pi}\right)}_{\sim 41.99^\circ} - \underbrace{\tan^{-1}\left(\frac{9000\pi}{7500\pi}\right)}_{\sim 50.19^\circ} \cong -8.207^\circ$$

∴ The first three terms of the Fourier series of the output signal  $V_o(t)$  can be written as:

$$\begin{aligned} V_o(t) \cong & 6.171 \sin(3000\pi t - 5.1^\circ) \\ & - 2.899 \sin(6000\pi t - 7.696^\circ) \\ & + 1.828 \sin(9000\pi t - 8.207^\circ) \end{aligned}$$

I'm trying to impress Inan!

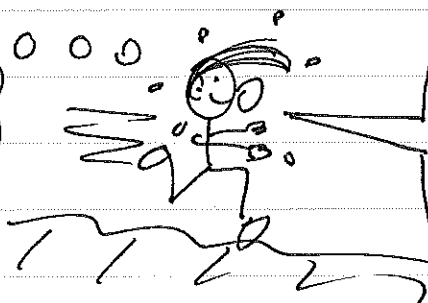

Inan's students never give up! Their perseverance is unbreakable!