

University of Portland School of Engineering

EE 262/Spring 2018

A. Inan


Homework # 5-Application of Laplace Transform in LTI Systems

(Assigned: Friday, March 9, 2018)

(Due: Monday, March 26, 2018, 9:15a.m.)


Inan problem # 11: Laplace transform in electric circuits.

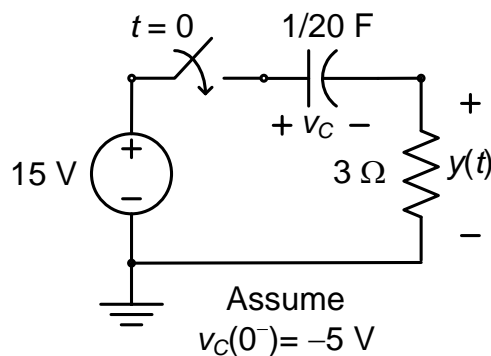For the electric circuit shown, given that $v_C(0^-) = -5\text{ V}$, find the mathematical expression for the signal $y(t)$ for $t > 0$ and sketch it.




Inan problem # 12: Laplace transform in electric circuits.

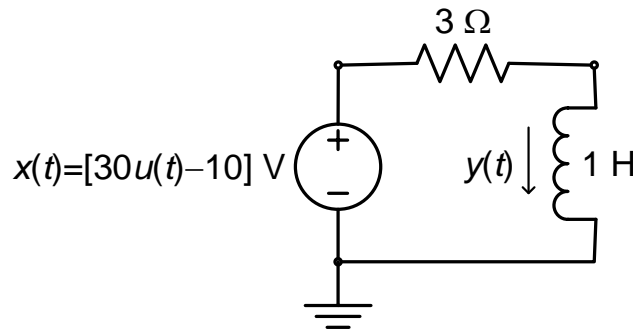For the electric circuit shown, find the signal $y(t)$ for $t \geq 0$.




Inan problem # 13: Laplace transform in electric circuits.

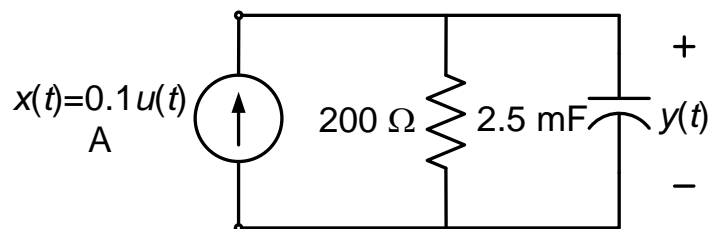For the electric circuit shown, find the signal $y(t)$ for $t \geq 0$.




Inan problem # 14: Laplace transform in electric circuits.

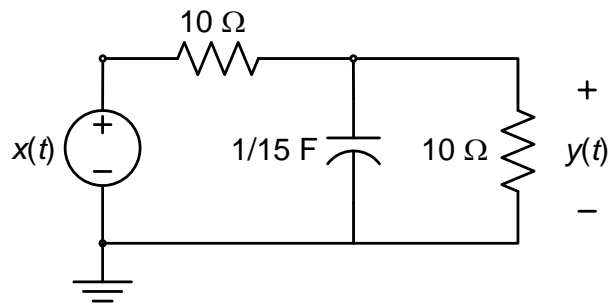Find (a) the transfer function; (b) the impulse response; and (c) the unit-step response of the electric circuit shown.




Inan problem # 15: Laplace transform in electric circuits.

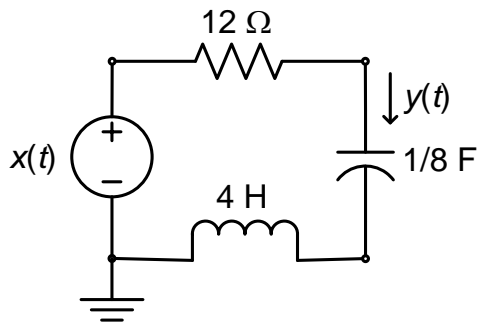Find (a) the transfer function; (b) the impulse response; and (c) the unit-step response of the electric circuit shown.



Inan problem # 16: Laplace transform in electric circuits.

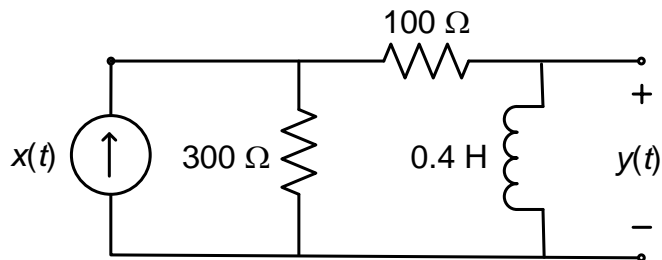Find (a) the transfer function; (b) the impulse response; and (c) the unit-step response of the electric circuit shown.



Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #5-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 262/Spring 2018 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.