
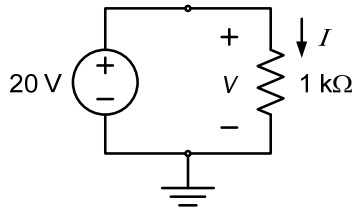


In this quiz, you are welcome to use your lab notebook as well as the lab manual.

- (10 points) What is the minimum value of electric current that could result in electrocution?
- (10 points) While working with electricity, you should not (a) work with wet hands; (b) cut wires carrying electric current; (c) install or remove any electrical components while the circuit is connected to a power source. Which part is false?
- (20 points) What color bands would be used to label a $27\text{ k}\Omega$ resistor with 10% tolerance?
- (20 points) Is it safe to use a resistor that can handle 0.5 W in the circuit below?

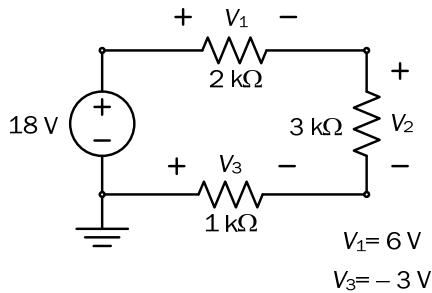

- (20 points) Voltages V_1 and V_3 in the circuit shown below are measured to be 6 V and -3 V respectively. Determine the value of voltage V_2 .



- (20 points) Suppose in the circuit below that the two currents I_2 and I_3 are measured to be $I_2 = -4\text{ mA}$ and $I_3 = 2\text{ mA}$. Determine the value of current I_1 .

