

**EE 271-Experiment # 5:**  
**Digital-to-Analog Converter (DAC)  $R-2R$  Ladder Network**

Table 1. Predicted and measured output voltage values.

<b>S<sub>3</sub></b>	<b>S<sub>2</sub></b>	<b>S<sub>1</sub></b>	<b>V<sub>out</sub> (predicted) (V)</b>	<b>V<sub>out</sub> (measured) (V)</b>	<b>Error (%)</b>
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			