

You are allowed to use your lab manual and lab notebook during the quiz.

- (1) (100 points) For each circuit shown, find the time constant and the approximate time it takes for the capacitor(s) to fully charge (i.e., to reach approximately 99% of its final steady-state voltage value). Show your work. Note that you will have two answers for each circuit. Please box your answers.

