

*University of Portland*  
*School of Engineering*

**EE 271–Electrical Circuits Laboratory**  
**Spring 2016**

**Lab Experiment #2: Simple Resistive**  
**Circuits**

# Simple Resistive Circuits

## I. Objective

In this experiment, the students will design, build and/or experiment simple resistive electrical circuits to gain some experience in using Ohm's law, Kirchhoff's laws, and their extensions such as voltage and current divider principles to analyze circuits consisting of series- and parallel-connected resistors.

## II. Procedure

### PART A: Voltage and Current Divider Principles

#### Part A.1: Verification of the Voltage Divider Circuit

**Pre-lab Assignment A.1:** For the circuit shown in Fig. 1, using the voltage divider principle, provide a general equation for  $V_{out}$  and calculate its numerical value. Box your answer.

**Lab Experiment A.1:** Construct the circuit shown in Fig. 1. Using the handheld DMM in DC mode set to read resistance, measure and record the actual values of the resistors  $R_1$  and  $R_2$  used in your circuit in Table 1. Calculate the % error in each resistor value as follows:

$$\% \text{ error in } R \text{ value} = \frac{R_{\text{theoretical}} - R_{\text{measured}}}{R_{\text{theoretical}}} \times 100$$

Table 1. Resistor values and percentage errors. (Circuit in Figure 1.)

$R_1$ (k $\Omega$ ) (theoretical)	$R_1$ (k $\Omega$ ) (measured)	% error in $R_1$	$R_2$ (k $\Omega$ ) (theoretical)	$R_2$ (k $\Omega$ ) (measured)	% error in $R_2$

Provide the calculated percentage errors in the resistor values in Table 1. Measure and record the output voltage  $V_{out}$ . Also calculate the % error of the  $V_{out}$  value as follows:

$$\% \text{ error in } V_{out} \text{ value} = \frac{V_{out, \text{prelab}} - V_{out, \text{measured}}}{V_{out, \text{prelab}}} \times 100$$

Box your results. Comment on the differences between the theoretical and measured values.

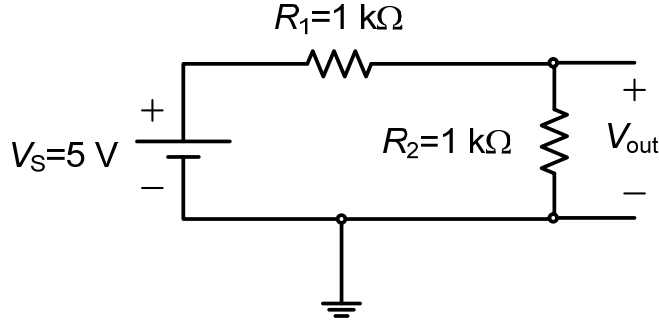


Figure 1. The voltage divider circuit.

**Part A.2: Verification of the Current Divider Principle**

**Pre-lab Assignment A.2:** Connect a shunt resistor  $R_{shunt}$  across the  $R_2=1\text{ k}\Omega$  resistance of Fig. 1, as shown in Fig. 2. (Note that “shunt resistor” means “parallel resistor”.) Provide simplified general equations for currents  $I_2$  and  $I_{shunt}$  flowing through the resistors  $R_2$  and  $R_{shunt}$  and voltage  $V_{out}$  across  $R_2$  and  $R_{shunt}$  in terms of  $V_S$ ,  $R_1$ ,  $R_2$ , and  $R_{shunt}$ . Box these three equations. Using these equations, calculate the values of  $I_2$  and  $I_{shunt}$  flowing through the resistors  $R_2$  and  $R_{shunt}$  and the voltage  $V_{out}$  for three different values of  $R_{shunt}$  resistance which are  $100\Omega$ ,  $1\text{ k}\Omega$ , and  $10\text{ k}\Omega$  respectively. Present your calculated current and voltage values in a table as shown in Table 2.

Provide Table 2 in your lab notebook including the measurements and calculated values related to the circuit shown in Figure 2.

Table 2. Prelab values of  $R_{shunt}$ ,  $I_2$ ,  $I_{shunt}$ , and  $V_{out}$ . (Figure 2 circuit).

$R_{shunt}$ (kΩ)	$I_2$ (mA)	$I_{shunt}$ (mA)	$V_{out}$ (V)
0.1			
1.0			
10.0			

**Lab Experiment A.2:** Construct the circuit shown in Fig. 2. Measure and record the actual values of the resistors  $R_1$ ,  $R_2$  and  $R_{shunt}$  used in your circuit in Table 2. Recalculate the values of currents  $I_2$  and  $I_{shunt}$  and voltage  $V_{out}$  for three different cases (for three different  $R_{shunt}$  values) using the measured values of the resistors  $R_1$ ,  $R_2$  and  $R_{shunt}$  and provide your recalculated values in Table 3.

Table 3. Recalculated values of  $I_2$ ,  $I_{shunt}$ , and  $V_{out}$  using actual  $R$  values.

$R_1$ (kΩ)	$R_2$ (kΩ)	$R_{shunt}$ (kΩ)	$I_2$ (mA)	$I_{shunt}$ (mA)	$V_{out}$ (V)

Measure and record the value of the output voltage  $V_{out}$  for each  $R_{shunt}$  resistor connected across the  $R_2$  resistance. Use the measured values of  $V_{out}$ ,  $R_2$ , and  $R_{shunt}$  along with Ohm's law to obtain the measured values of currents  $I_2$  and  $I_{shunt}$ . Present your measured current and voltage values in Table 4.

Table 4. Measured values of  $R_{shunt}$ ,  $I_2$ ,  $I_{shunt}$ , and  $V_{out}$ . (Figure 2 circuit).

$R_{shunt}$ (k $\Omega$ )	$I_2$ (mA)	$I_{shunt}$ (mA)	$V_{out}$ (V)

Using the recalculated and measured values (given in Tables 3 and 4), calculate and present in Table 5 the percentage errors in the current and voltage values in each case and comment. Also, comment on what happens to the values of the two currents  $I_2$  and  $I_{shunt}$  with respect to one another as  $R_{shunt}$  resistor increases. Why?

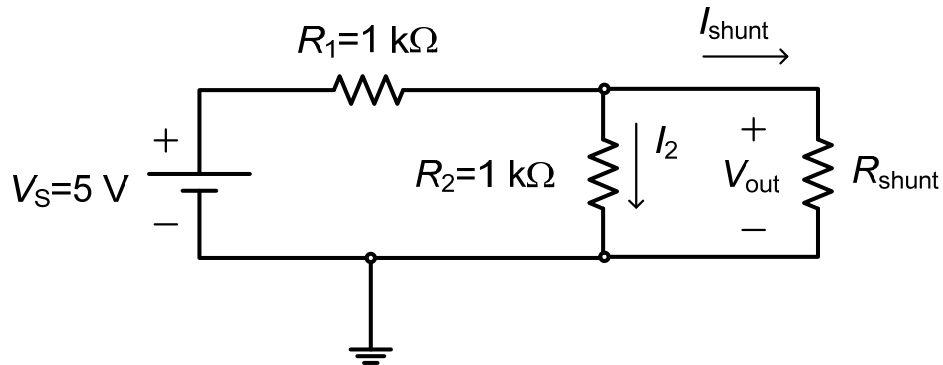


Figure 2. The current divider circuit.

Table 5. Percentage errors in measured values of  $I_2$ ,  $I_{shunt}$ , and  $V_{out}$ .

$R_{shunt}$ (k $\Omega$ )	% error in $I_2$	% error in $I_{shunt}$	% error in $V_{out}$

### **PART B: Design of a Voltage Divider Circuit**

**Pre-lab Assignment B:** Design a voltage divider circuit similar to the one shown in Fig. 3 to convert a fixed power supply voltage of 5 V to a voltage equal to 2 V. For the circuit, all you have available are four 1 k $\Omega$  resistors. Draw the circuit you designed on paper and clearly provide the terminals where the 2 V appears. (Note that more than one circuit design is possible.)

**Lab Experiment B.1:** Test your designed voltage-divider circuit in the lab. Measure and record the value of the output voltage  $V_{out}$  in the circuit and verify that your design works.

**Lab Experiment B.2:** Next, to investigate *loading effect*, use the voltage divider circuit designed in Fig. 3 to supply 2 V to an unknown resistive load (which will be provided during the lab). Connect the unknown resistive load across the output terminals of the voltage-divider circuit you designed and measure the voltage supplied to the unknown load in each circuit. Does your voltage-divider circuit indeed supply a 2 V voltage to the unknown load? If no, explain why.

**Lab Experiment B.3:** Measure the resistance of the unknown resistive load and redesign your voltage divider circuit accordingly so that your circuit takes the fixed 5 V voltage and supplies 2 V to the load. Again, as before, all you have are four 1 k $\Omega$  resistors. (Hint: If you design your voltage-divider circuit correctly, it only dissipates power when the load resistance is connected across it.)

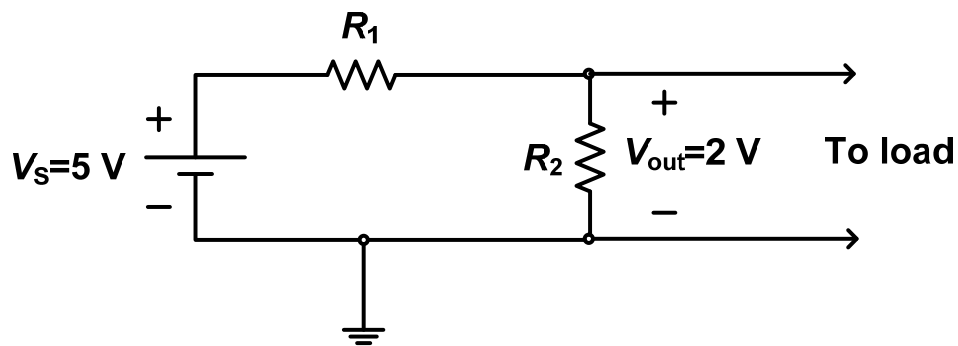


Figure 3. Voltage divider circuit.

### **III. Discussions & Conclusion**

In this section, discuss the various aspects of Experiment #2 and make some conclusions. In your write-up, you should at least address the following questions:

1. What was the objective of this experiment and was the objective achieved?
2. Explain briefly what is meant by loading effect.
3. Did any of your measurements have more than 5% error? What was your maximum % error?
4. What sources of error may have contributed to the differences between the theoretical values and the measured values?
5. Other comments relevant to this experiment.