

Sample Problem for EE 301-Midterm # 2-Three Cascaded Transmission Lines

Three cascaded transmission lines. In the following transmission line circuit shown, find the following using equations as well as the Smith chart:

- Find the two input impedances at frequency f_1 (which corresponds to wavelength λ_1)
- Find the standing wave ratio on each line (i.e., S_3 , S_2 , and S_1) at frequency f_1
- Repeat the first two parts at frequency $f_2=2f_1$

Answers: 180Ω , 80Ω , 3, 1.5, 1, $30-j40 \Omega$, $30-j40 \Omega$, 3, $\sim 4.47(?)$, $\sim 3.42(?)$. (I hope my answers are correct, I did my calculations pretty fast! 😊)

