

UNIVERSITY ☺ F P☺ RTLAND
Sch☺ ol ☺ f Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2003

Midterm Exam # 1

(Prepared by Professor A. S. Inan)

(Friday, February 28, 2003)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

Name: _____ ☺

Signature: _____ ☺

“Honesty is the best policy.”

Aesop (~ 620B.C. - ?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.- 65A.D.)

“Honest people are the true winners of the universe.”

Anonymous

(1) (15 mins., 30 points) **Step excitation of a lossless transmission line terminated with $R_L \gg Z_0$.** Consider a 3-inches long lossless transmission line, characterized with per-unit-length parameters $L = 45 \text{ nH-(inch)}^{-1}$ and $C = 8 \text{ pF-(inch)}^{-1}$, excited at $t = 0$ by a step-voltage source of amplitude $V_0 = 4 \text{ V}$ (i.e., $4u(t)$) and source resistance of $R_s = 25 \text{ } \Omega$ at one end and terminated with a resistive load of value $R_L \gg Z_0$ at the other end. Find the exact time (with the appropriate unit!) at which the load-end voltage V_L across R_L not only exceeds 3.7 V but also never falls below this voltage level beyond this time. (Show your work with a bounce diagram.)

(2) (15 mins., 30 points) **Step excitation of a loss-less transmission line terminated with an inductor.** Connect an extra lumped inductor of value 15 nH in parallel with the load resistor R_L at the load end of the transmission-line circuit of Problem (1) and reconsider the transient response of this circuit due to the same step voltage source with voltage $4u(t)$. Sketch the total voltage distribution along the transmission line at time $t = 2.7$ ns. Provide all the pertinent values on your sketch.

(3) (10 mins., 20 points) **The input impedance of a transmission line.** Consider a 20-cm long $100\text{-}\Omega$ air transmission line excited by a 1.5 GHz sinusoidal voltage source at one end and terminated by an inductive load with impedance $Z_L = (75 + j25)\ \Omega$ at the other end. Find the input impedance Z_{in} of this line seen from the source end at steady state. Provide your answer in its simplest form.

(4) (10 mins., 20 points) **Transmission-line inductor design.** A short-circuit or open-circuit terminated $50\text{-}\Omega$ air transmission line is to be designed to provide an inductance of value 50 nH at 3 GHz .

(a) (10 points) Design the above transmission-line inductor with the shortest possible length. Sketch your design with all the pertinent values provided on your sketch.

(b)(10 points) Find the new lumped element value of the transmission-line element designed in part (a) at 4 GHz. (Use the exact same circuit you designed in part (a). Provide the appropriate unit for your answer.)