

UNIVERSITY ☺ F P ☺ RTLAND
Sch ☺ ol ☺ of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2003

Midterm Exam # 2

(Prepared by Professor A. S. Inan)

(Monday, April 14, 2003)

(Closed Book Exam; Formula Sheets Allowed)

(Total Time: 55 mins.)

Name: _____ ☺

Signature: _____ ☺

“Honesty is the best policy.”

Aesop (~ 620B.C. - ?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.- 65A.D.)


“Honest people are the true winners of the universe.”

Anonymous

Points lost on each problem:


- #1
- #2
- #3
- #4

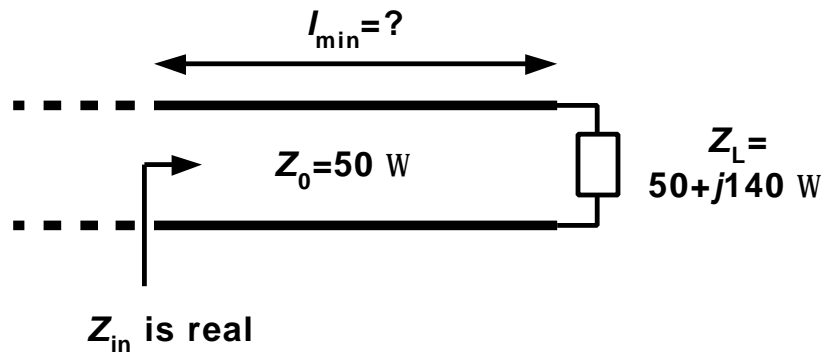(1) (Total time: 10 mins.) **Real Z_{in} position.** Consider the transmission-line circuit shown. Assume sinusoidal steady-state conditions to apply. Find the following:




- (a) (5 points) The electrical position nearest to the load where the input impedance of the transmission line is purely resistive. (You are welcome to use the Smith chart on the next page.)
- (b) (5 points) The approximate value of Z_{in} at that position.
- (c) (5 points) The approximate value of the standing-wave-ratio S on the line.

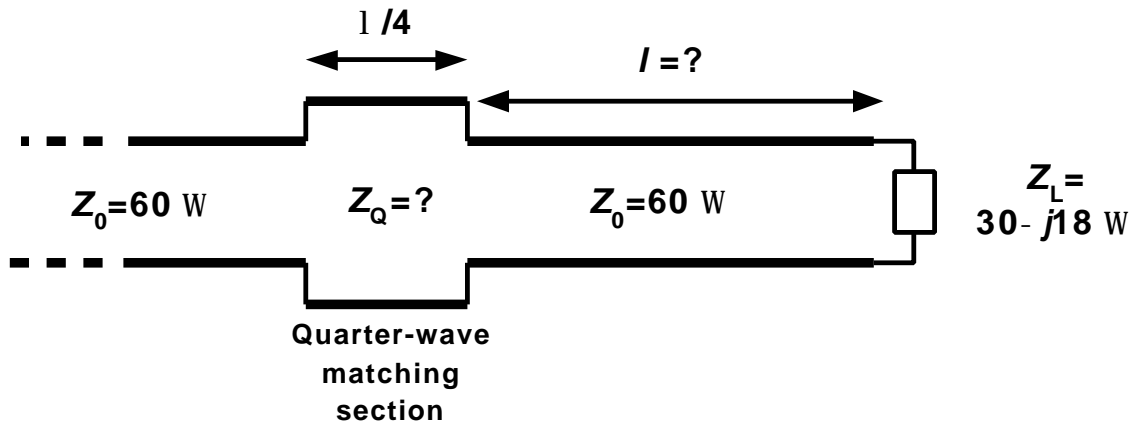(2) (10 mins., 25 points) **Quarter-wave transformer design.** Consider the transmission-line circuit as shown. Design the quarter-wave transformer matching network shown (i.e., determine its electrical position l away from the load and its characteristic impedance Z_Q) to match Z_L to Z_0 such that $Z_Q > Z_0$. (Assume sinusoidal steady-state condition to apply.)



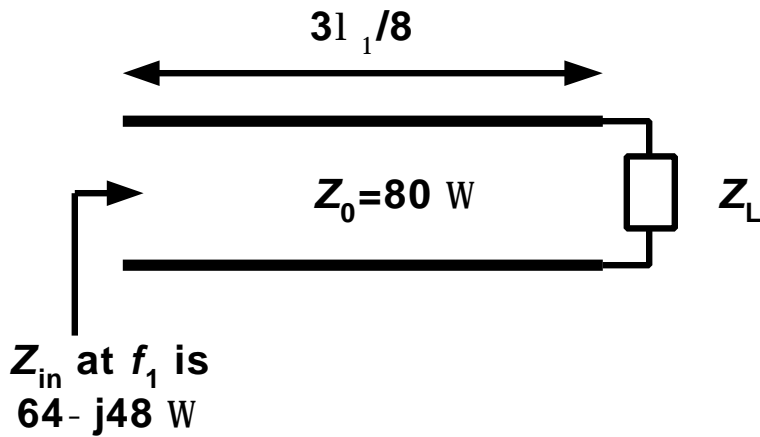(3) (10 mins., 30 points) **The input impedance of a transmission line.** In the transmission-line circuit shown, the load impedance is unknown. The input impedance of the line is measured to be $Z_{in} = 64 - j48 \Omega$ at source frequency f_1 . Assuming both Z_L and Z_0 values to be independent of the source frequency, find the input impedance Z_{in} of the line at source frequency $f_2 = 2f_1$. (Assume sinusoidal steady-state condition to apply.)



(4) (15 mins., 30 points) **Distributed matching network design.** Consider the transmission-line circuit as shown. As a design engineer, your task is to determine the electrical lengths of the two short-circuited stubs (each 50Ω) connected at the load position as shown so that not only you match Z_L to Z_0 but you also keep the total stub length $l_s + l_p$ minimum. Assume sinusoidal steady state. (Note the order in which the stubs are connected. **DO NOT CHANGE THAT ORDER!!**)

