

UNIVERSITY ☺ OF ☺ PORTLAND
Sch☺☺l ☺ of Engineering

EE 301
 Spring 2004
 A.Inan

EE 301/Handout # 10
 (Wednesday, March 3, 2004)

Transmission Lines: The Real and Imaginary Parts of Z_{in}

The following steps lead to the real and imaginary parts of the input impedance Z_{in} of a lossless transmission line with characteristic impedance Z_0 , length l and terminated with a load impedance $Z_L = R_L + jX_L$:

$$\begin{aligned}
 Z_{in} = R_{in} + jX_{in} &= Z_0 \frac{Z_L + jZ_0 \overbrace{\tan(\beta l)}^T}{Z_0 + jZ_L \underbrace{\tan(\beta l)}_T} = Z_0 \frac{R_L + jX_L + jZ_0 T}{Z_0 + j(R_L + jX_L)T} \\
 &= Z_0 \frac{R_L + j(X_L + Z_0 T)}{(Z_0 - X_L T) + jR_L T} \times \frac{(Z_0 - X_L T) - jR_L T}{(Z_0 - X_L T) - jR_L T} \\
 &= Z_0 \frac{[R_L(Z_0 - X_L T) + R_L T(X_L + Z_0 T)] + j[(X_L + Z_0 T)(Z_0 - X_L T) - R_L^2 T]}{(Z_0 - X_L T)^2 + (R_L T)^2} \\
 &= Z_0 \underbrace{\frac{R_L Z_0 (1 + T^2)}{(Z_0 - X_L T)^2 + (R_L T)^2}}_{\text{Re}\{Z_{in}\}=R_{in}} + jZ_0 \underbrace{\frac{X_L Z_0 + (Z_0^2 - R_L^2 - X_L^2)T - Z_0 X_L T^2}{(Z_0 - X_L T)^2 + (R_L T)^2}}_{\text{Im}\{Z_{in}\}=X_{in}}
 \end{aligned}$$

Please check my steps one more time to make sure I did it correctly.