

University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2005

Midterm Exam # 1

(Prepared by Professor A. S. Inan)

(Wednesday, March 2, 2005)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

Name: _____ 😊

Signature: _____ 😊

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)


“Honest people are the true winners of the universe.”

Anonymous


“Honesty is not for sale.”

A. Inan

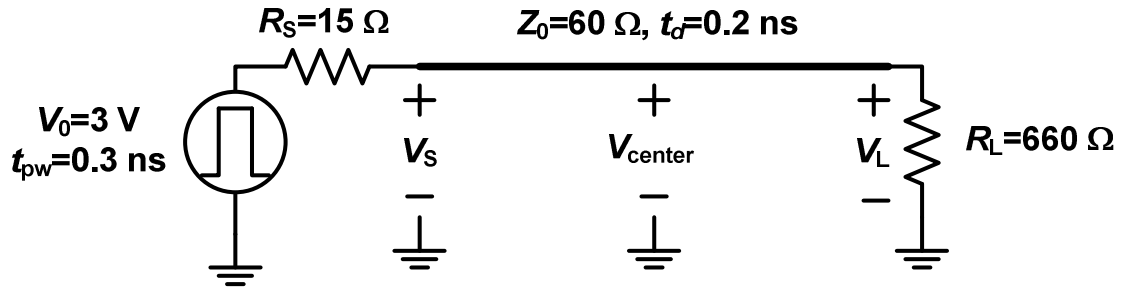- (1) (15 mins., 30 points) **Pulse excitation of a lossless transmission line.**
 For the transmission line circuit shown, sketch the voltages V_S , V_{center} , and V_L as a function of time between $t = 0$ and $t = 1^+$ ns. Provide all the relevant values on your sketches. Also provide a bounce diagram for your solution.



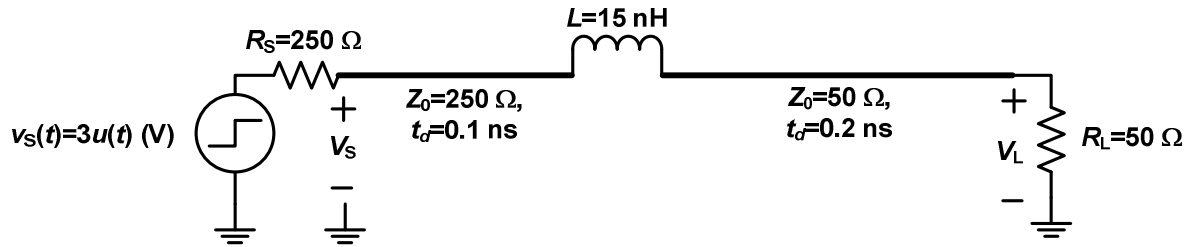- (2) (20 mins., 40 points) **Lumped inductive element between two lossless transmission lines.** For the transmission line circuit shown, find and sketch the source-end and load-end voltages as a function of time. Show your work and provide all the appropriate values on your sketches.



- (3) (15 mins., 30 points) **Load reflection coefficient, standing wave ratio and input impedance.** Consider the transmission line circuit shown. Assuming sinusoidal steady-state condition, find (a) the load reflection coefficient; (b) the standing wave ratio on the line; and (c) the input impedance of the line. Show your work and provide all your results in their simplest form.

