

*University of Portland*  
*School of Engineering*

**EE 301-Electromagnetic Fields-3 cr. hrs.**  
**Spring 2005**

**Midterm Exam # 2**  
**Sinusoidal Steady-State Waves on Transmission Lines**

(Prepared by Professor A. S. Inan)

(Monday, April 11, 2005)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

**Name:** \_\_\_\_\_ ☺

**Signature:** \_\_\_\_\_ ☺

*“Honesty is the best policy.”*

Aesop (~ 620B.C. -?)

*“An honest mind possesses a kingdom.”*

Lucius Annaeus Seneca (4B.C.-65A.D.)

*“Honest people are the true winners of the universe.”*

Anonymous


*“Honesty is not for sale.”*

A. Inan

*This table will be used by Inan for grading!*

Problem #	Points gained
#1	
#2	
#3	
<b>Total</b>	

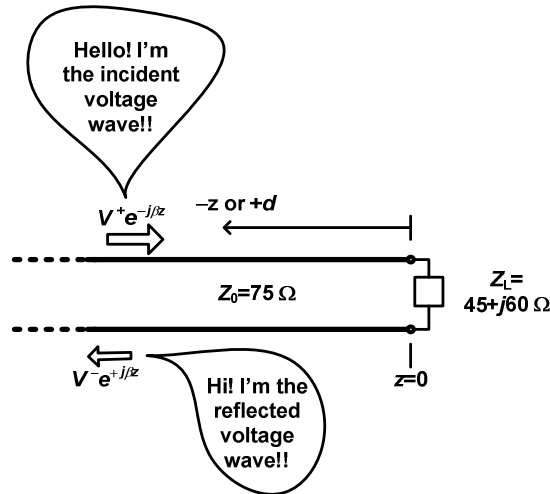(1) (15 mins., Total: 40 points) **A lossless transmission line terminated with a complex impedance.** A  $75\ \Omega$  transmission line is terminated with an inductive load impedance given by  $Z_L = 45 + j60\ \Omega$ , as shown.




(a) (10 points) Calculate the load reflection coefficient,  $\Gamma_L$ . (Provide your answer in polar form.) Show your work!

(b) (10 points) What is the value of the standing wave ratio,  $S$ , on the line?

(c) (10 points) Find the percentage time-average incident power that is absorbed by the load.

(d) (10 points) Find the  $V_{\max}$  and  $V_{\min}$  positions nearest to the load. Provide your answers as electrical lengths.

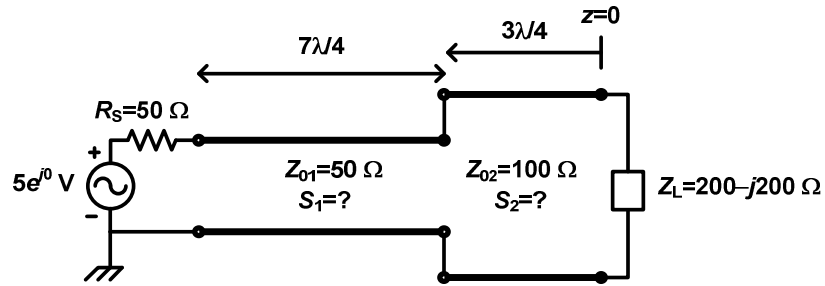(2) (15 mins., Total: 30 points) **Two cascaded transmission lines.** Consider the transmission line circuit as shown.



(a) (15 points) Find the standing wave ratio on each line. Show your work!

(b) (15 points) Find the time-average power delivered to the load impedance.

(3) (15 mins., 30 points) **Input impedance.** Consider the transmission line circuit as shown where  $Z_p$  impedance represents a parallel lumped element. Find the input impedance  $Z_{in}$ . Show your work step by step.

