

University of Portland
School of Engineering

EE 301
Spring 2006
A.Inan


Homework # 6

(Assigned: March 24, 2006)


Sinusoidal Steady-State (SSS) Waves on Transmission Lines-II

(Due: Friday, March 31, 2006, 11:25a.m.)

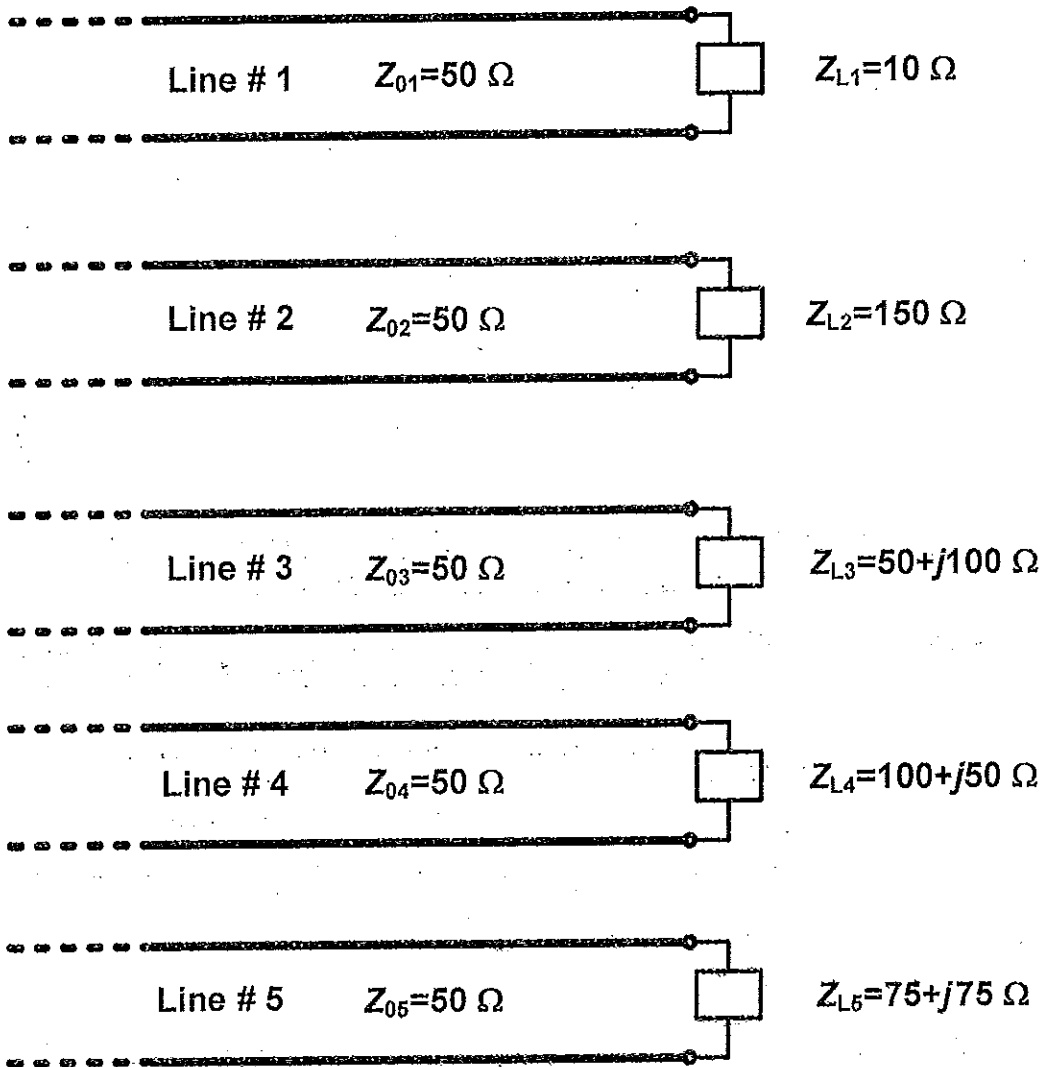
- (1) Standing wave ratio. Calculate the standing wave ratio S on each line shown below and find out which line has the largest S value.



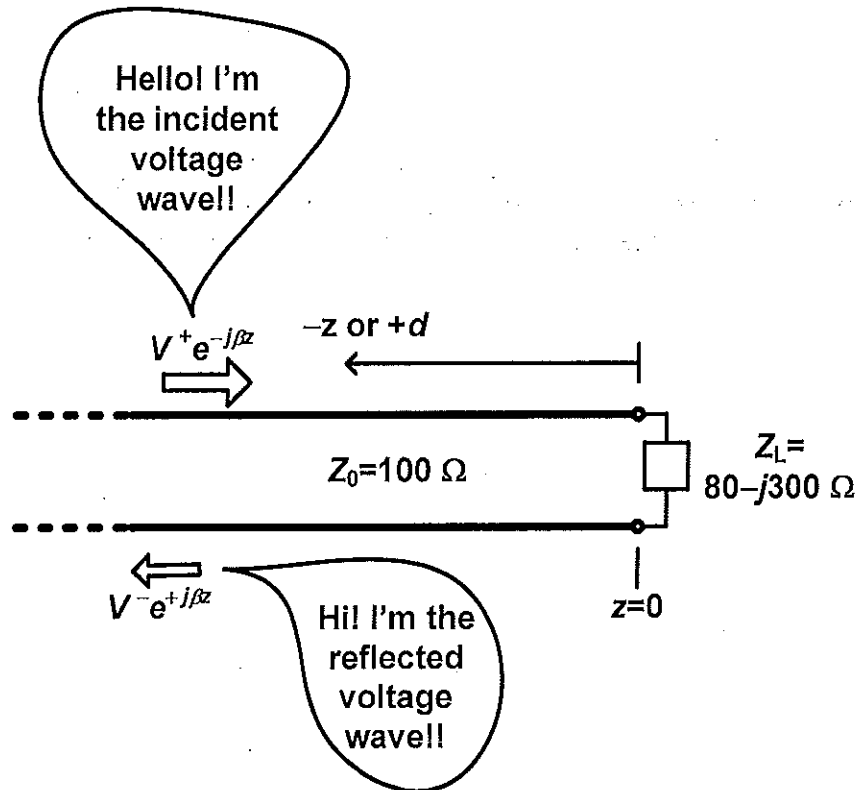
- (2) A lossless transmission line terminated with a complex impedance. A 100Ω transmission line is terminated with a capacitive load having a load impedance given by $Z_L = 80 - j300 \Omega$, as shown. (a) Find the load reflection coefficient Γ_L . (b) Find the standing wave ratio S on the line. (c) Find the nearest V_{\max} position with respect to the load. (d) Find the nearest V_{\min} position with respect to the load. (e) Find the nearest position with respect to the load where the line impedance is given by $Z_{\text{line}} = 100 + jX$. (Note that your answers for parts (c), (d) and (e) will be electrical lengths or positions.)



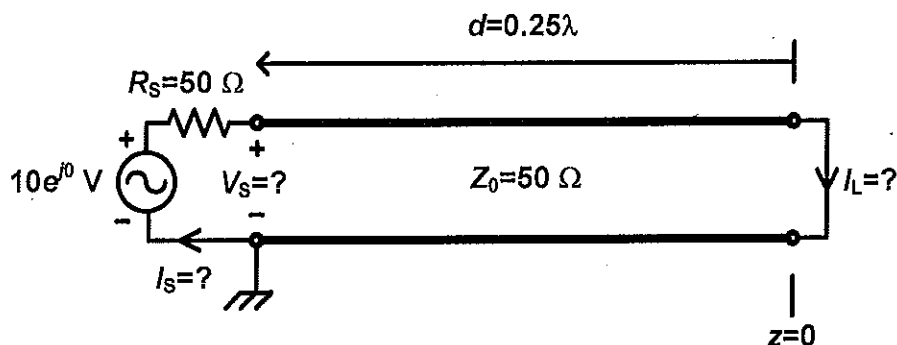
- (3) A lossless transmission line terminated with a short circuit. Consider a short-circuit terminated 50Ω quarter-wavelength transmission line excited by a sinusoidal voltage source as shown. Calculate the source-end phasor voltage V_S , source-end phasor current I_S , and load-end phasor current I_L .



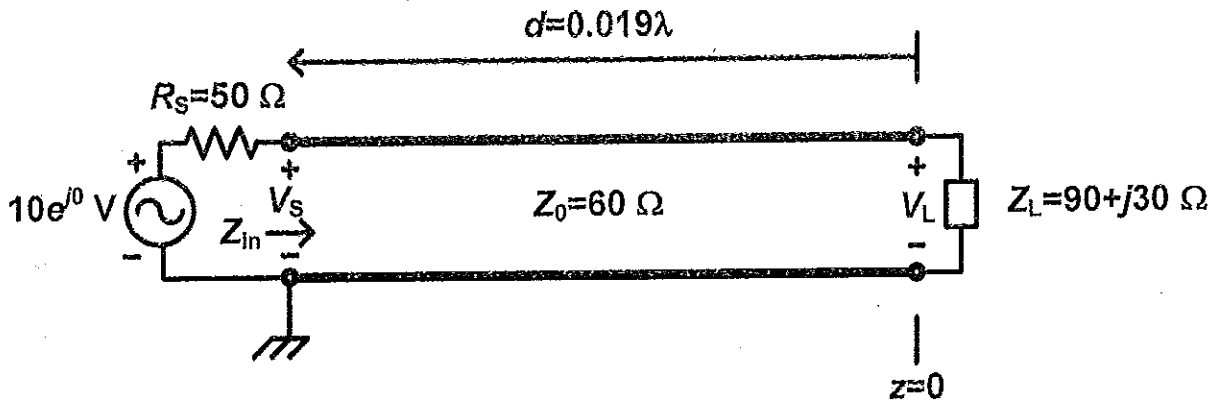
- (4) A lossless transmission line terminated with an inductive load. A 60Ω transmission line is terminated with an inductive load having a load impedance given by $Z_L = 90 + j30 \Omega$, as shown. (a) Find the load reflection coefficient Γ_L . (b) Find the standing wave ratio S on the line. (c) Find the input impedance Z_{in} . (d) Find the phasor voltages V_S and V_L . (e) Find the time-average power delivered to the load.



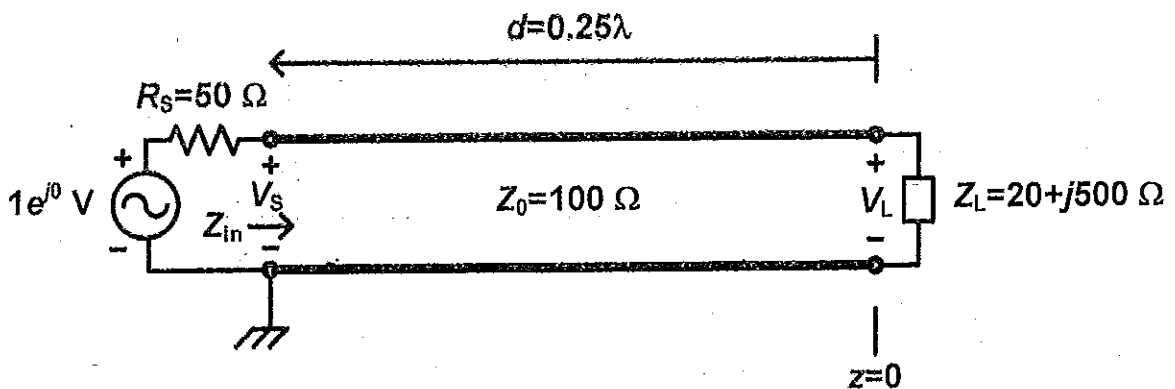
- (5) A lossless transmission line terminated with a complex impedance. A 100Ω transmission line is terminated with an inductive load having a load impedance given by $Z_L = 20 + j500 \Omega$, as shown. (a) Find the load reflection coefficient Γ_L . (b) Find the standing wave ratio S on the line. (c) Find the total time-average power supplied by the sinusoidal voltage source and how this power splits between the source resistance and the load impedance. (d) Repeat part (c) for $d = 0.5\lambda$.



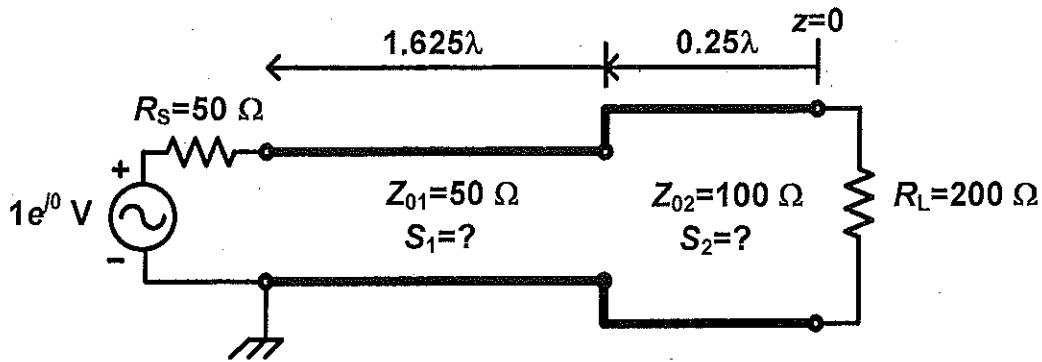
- (6) Cascaded transmission lines. For the two cascaded transmission lines shown, (a) find the standing wave ratio on each line; and (b) the time-average power delivered to the load resistance.



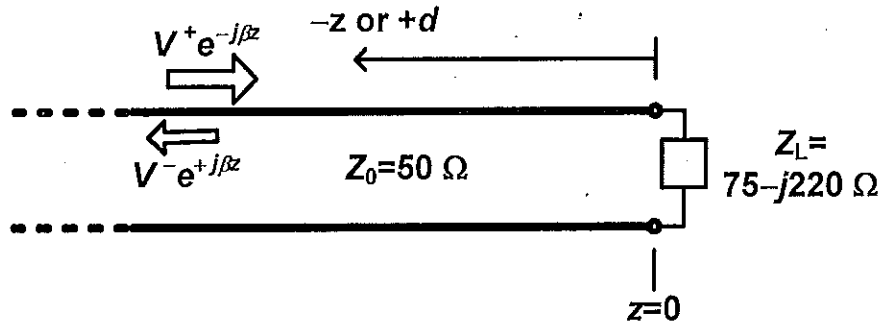
- (7) **Resistive line impedance.** A 50Ω transmission line is terminated with a capacitive load $Z_L = 75 - j220 \Omega$, as shown. (a) Find the load reflection coefficient Γ_L and the standing wave ratio S on the line. (b) What percentage of the incident power reflects back from the load? (c) Find the two nearest positions on the line with respect to the load where the line impedance is purely real. (d) Calculate the line impedances at the positions found in part (c).



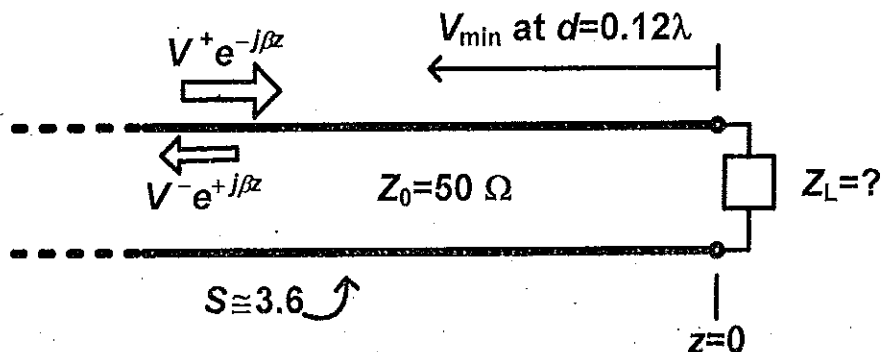- (8) **Unknown load impedance.** If the standing wave ratio and the voltage minimum position on a 50Ω transmission line terminated with an unknown load impedance are measured to be $S \approx 3.6$ and $d = 0.12\lambda$, determine the value of the unknown load impedance.



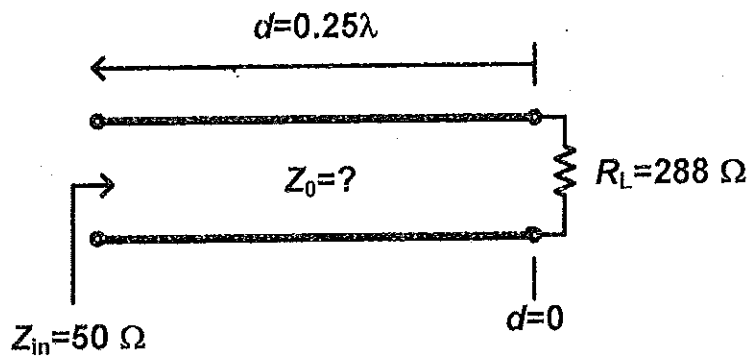(9) **Unknown characteristic impedance.** If the input impedance of a quarter-wavelength long lossless transmission line terminated with a resistive load $R_L = 288 \Omega$ is measured to be $Z_{in} = 50 \Omega$, find the characteristic impedance, Z_0 , of the line.



Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top, indicate that this is EE 301/Spring 2006/HW #6 Solutions and provide your name somewhere on that sheet where the grader can easily see it.
- 2) Solve each problem on a separate sheet unless the solution is very short.
- 3) Do not use the back of the sheets unless you have to.
- 4) Staple your solutions in the above order before you turn them in.

Please turn in your homework solutions on time. The solutions (or answers) for each homework assignment will be provided as a separate handout on the due date. **Late homework solutions will not be accepted!**

An important reminder note:

EE 301-Midterm # 2 is scheduled to be given on Friday, April 7, 2006
(It will be in-class closed-book exam. One formula sheet will be allowed.)

SOLUTIONS TO HOMEWORK # 6

Lets gooooo!

#1

$$\Gamma_{L_1} = \frac{Z_{L_1} - Z_{01}}{Z_{L_1} + Z_{01}} = \frac{10 - 50}{10 + 50} = -\frac{2}{3} = \frac{2}{3} e^{j\pi}$$

$$S_1 = \frac{1 + |\Gamma_{L_1}|}{1 - |\Gamma_{L_1}|} = \frac{1 + 2/3}{1 - 2/3} = \boxed{5}$$

$$\Gamma_{L_2} = \frac{150 - 50}{150 + 50} = \frac{1}{2}$$

$$S_2 = \frac{1 + |\Gamma_{L_2}|}{1 - |\Gamma_{L_2}|} = \frac{1 + 1/2}{1 - 1/2} = \boxed{3}$$

$$\begin{aligned} \Gamma_{L_3} &= \frac{50 + j100 - 50}{50 + j100 + 50} = \frac{j100}{100 + j100} = \frac{j}{1+j} \cdot \frac{(1-j)}{(1-j)} \\ &= \frac{1+j}{2} = \frac{1}{\sqrt{2}} e^{j\pi/4} \end{aligned}$$

$$S_3 = \frac{1 + |\Gamma_{L_3}|}{1 - |\Gamma_{L_3}|} = \frac{1 + 1/\sqrt{2}}{1 - 1/\sqrt{2}} = \frac{\sqrt{2} + 1}{\sqrt{2} - 1} \approx \boxed{5.83}$$

$$\begin{aligned} \Gamma_{L_4} &= \frac{100 + j50 - 50}{100 + j50 + 50} = \frac{50(1+j)}{50(3+j)} \cdot \frac{(3-j)}{(3-j)} \\ &= \frac{4 + j2}{10} = \frac{2 + j}{5} = \frac{1}{\sqrt{5}} e^{j \tan^{-1}(1/2)} \approx 0.447 e^{j26.6^\circ} \end{aligned}$$

$$S_4 = \frac{1 + |\Gamma_{L4}|}{1 - |\Gamma_{L4}|} = \frac{1 + 1/\sqrt{5}}{1 - 1/\sqrt{5}}$$

$$= \frac{\sqrt{5} + 1}{\sqrt{5} - 1} \approx \boxed{2.62}$$

$$\Gamma_{L5} = \frac{75 + j75 - 50}{75 + j75 + 50} = \frac{25 + j75}{125 + j75} = \frac{1 + j3}{5 + j3}$$

$$= \frac{(1 + j3)(5 - j3)}{5^2 + 3^2} = \frac{14 + j12}{34} = \frac{7 + j6}{17}$$

$$= \sqrt{\frac{5}{17}} e^{j \tan^{-1}(6/7)} \approx 0.542 e^{j 40.6^\circ}$$


$$S_5 = \frac{1 + |\Gamma_{L5}|}{1 - |\Gamma_{L5}|} = \frac{1 + \sqrt{5/17}}{1 - \sqrt{5/17}}$$

$$= \frac{\sqrt{17} + \sqrt{5}}{\sqrt{17} - \sqrt{5}} \approx \boxed{3.37}$$

∴ Line # 3 has the largest S value which

is $S \approx 5.83$.

#2

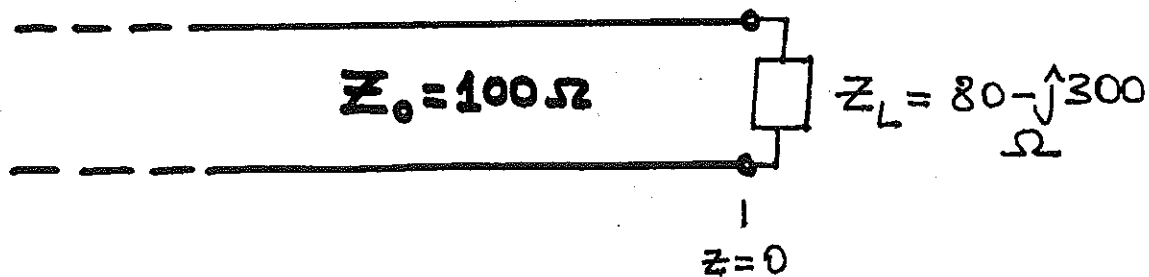

$$\begin{aligned} (a) \quad \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(80 - j300) - 100}{(80 - j300) + 100} \\ &= \frac{-20 - j300}{180 - j300} = \frac{-1 - j15}{9 - j15} \\ &= \frac{\sqrt{226} e^{j \tan^{-1}(-15/-1) + j\pi}}{\sqrt{306} e^{j \tan^{-1}(-15/9)}} \\ &= \sqrt{\frac{113}{153}} e^{j \tan^{-1}(15) + j\pi - j \tan^{-1}(-15/9)} \\ &\approx \boxed{0.859 e^{-j34.8^\circ}} \end{aligned}$$

$$(b) \quad S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \approx \frac{1 + 0.859}{1 - 0.859} \approx \boxed{13.2}$$

$$\begin{aligned} (c) \quad -34.8^\circ \times \frac{\pi}{180^\circ} + 4\pi \left(\frac{z_{\max}}{\lambda} \right) &= -2\pi \\ \rightarrow z_{\max} &\approx \boxed{-0.4517 \lambda} \end{aligned}$$

$$(d) \quad z_{\min} = z_{\max} + 0.25\lambda \cong \boxed{-0.2017\lambda}$$

$$(e) \quad \operatorname{Re}\{z_{\text{in}}\} = R_{\text{in}} = 100 \Omega$$

From Inan's z_{in} handout!

$$\frac{R_L z_0^2 (1+T^2)}{(z_0 - X_{LT})^2 + R_L^2 T^2} = \frac{80(100)^2 (1+T^2)}{(100 - (-300)T)^2 + (80)^2 T^2} = 100$$

$$8,000(1+T^2) = (100 + 300T)^2 + 6,400T^2$$

$$80 + 80T^2 = 100 + 600T + 900T^2 + 64T^2$$

$$884T^2 + 600T + 20 = 0$$

$$221T^2 + 150T + 5 = 0$$

$$T_1, T_2 = \frac{-75 \pm \sqrt{(75)^2 - 5(221)}}{221} \cong \begin{matrix} -3.515 \times 10^{-2} \\ -6.436 \times 10^{-4} \end{matrix}$$



Since $T = \tan(\beta l) = \tan\left(2\pi \frac{l}{\lambda}\right)$, we have

$$l_1, l_2 \cong 0.4944, 0.4090$$

∴ The nearest position with respect to the

load where $z_{\text{line}} = 100 + jX$ is $\boxed{l_{\text{nearest}} \cong 0.409\lambda}$.

#3

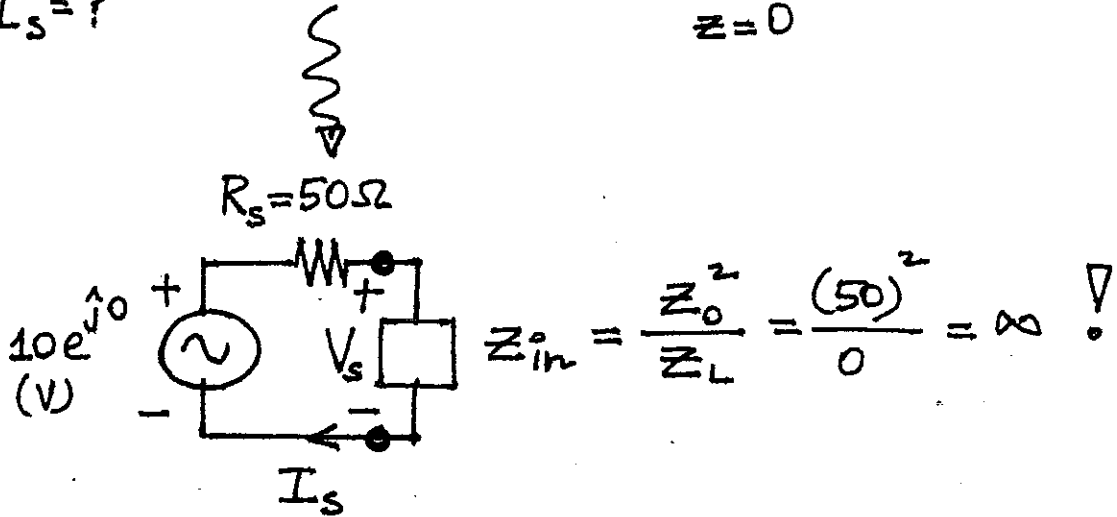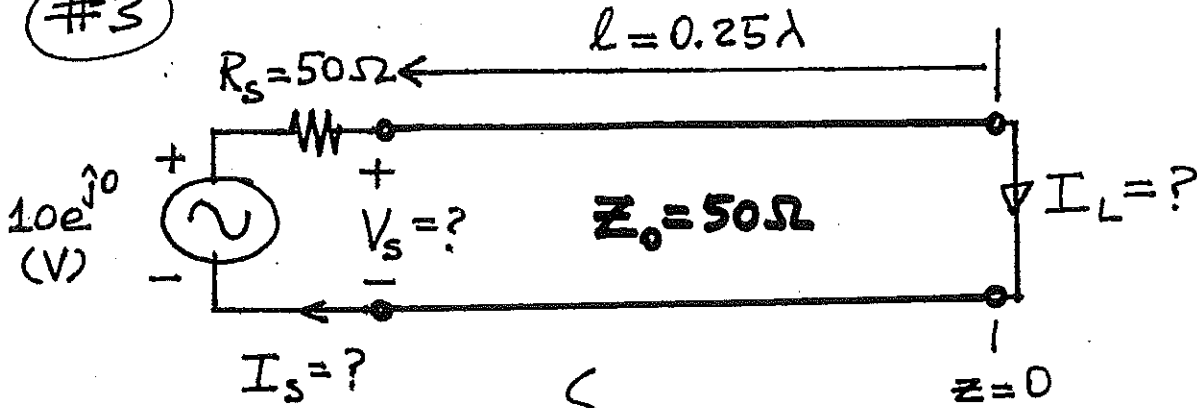

$\therefore I_s = 0$ & $V_s = 10e^{j0}$ (V)

Since $V(l) = V^+ e^{j\beta l} + V^- e^{-j\beta l}$
 $= V^+ e^{j2\pi l/\lambda} + V^- e^{-j2\pi l/\lambda}$
 At $l = 0.25\lambda \rightarrow V(l=0.25\lambda) = V^+ e^{j\pi/2} + V^- e^{-j\pi/2}$
 $= V^+ j + V^- (-j) = V_s$

Since $\Gamma_L = -1 \rightarrow V^- = -V^+$, therefore

$V(l=0.25\lambda) = 2jV^+ = V_s = 10e^{j0} \rightarrow V^+ = \frac{10e^{j0}}{2j} = 5e^{-j\pi/2}$ (V)


The total current $I(l)$ is given by

$$\begin{aligned} I(l) &= I^+ e^{j\beta l} + I^- e^{-j\beta l} = \frac{V^+}{Z_0} e^{j\beta l} - \frac{V^-}{Z_0} e^{-j\beta l} \\ &= \frac{V^+}{Z_0} (e^{j\beta l} + e^{-j\beta l}) = \frac{2V^+}{Z_0} \cos(\beta l) \end{aligned}$$

$$\begin{aligned} \therefore I(l) &= \frac{2 \times 5 e^{-j\pi/2}}{50} \cos(\beta l) \\ &= 0.2 e^{-j\pi/2} \cos(\beta l) \end{aligned}$$

$$\therefore I(l=0) = I_L = 0.2 e^{-j\pi/2} = \boxed{-j0.2 \text{ A}}$$

#4

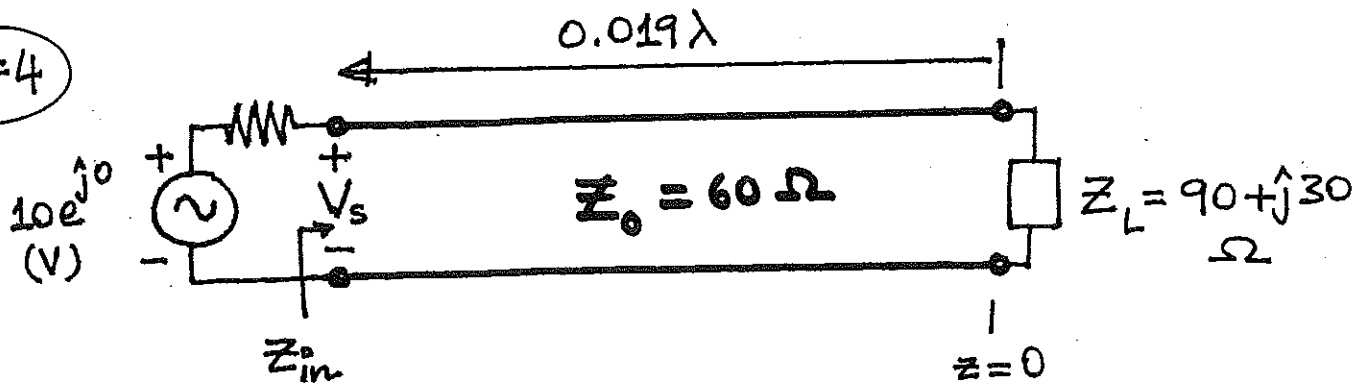

$$(a) \quad \Gamma_L = \frac{90 + j30 - 60}{90 + j30 + 60} = \frac{30 + j30}{150 + j30} = \frac{1 + j}{5 + j}$$

$$= \frac{\sqrt{2} e^{j45^\circ}}{\sqrt{26} e^{j \tan^{-1}(0.2)}} \approx \boxed{0.277 e^{j33.7^\circ}}$$

$$(b) \quad S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \approx \frac{1 + 0.277}{1 - 0.277} \approx \boxed{1.77}$$


$$(c) \quad Z_{in} = 60 \frac{(90 + j30) + j60 \tan\left(\frac{2\pi}{\lambda}(0.019\lambda)\right)}{60 + j(90 + j30) \tan\left(\frac{2\pi}{\lambda}(0.019\lambda)\right)}$$

$$\approx 60 \frac{(90 + j30) + j60(0.120)}{60 + j90(0.120) - 30(0.120)}$$

$$\approx 60 \frac{90 + j37.2}{56.4 + j10.8}$$

$$\approx 102 e^{j11.6^\circ} \approx \boxed{(99.7 + j20.5) \Omega}$$

(d)

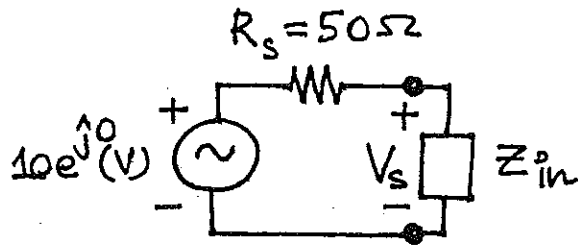

Using the voltage divider principle, we have

$$V_s = \frac{Z_{in}}{R_s + Z_{in}} (10e^{j0}) \cong \frac{99.7 + j20.5}{149.7 + j20.5} (10e^{j0})$$

$$\cong 6.736 e^{j3.82^\circ} \text{ (V)}$$

$$\text{Since } V(l) = V^+ e^{j\beta l} + V^- e^{-j\beta l}$$

$$= V^+ e^{j\frac{2\pi}{\lambda} \cdot l} (1 + \Gamma_L e^{-j2\frac{2\pi}{\lambda} l})$$

$$V(l=0.019\lambda) \cong V^+ e^{j6.84^\circ} (1 + 0.277 e^{j33.7^\circ} e^{-j13.7^\circ})$$

$$= V_s \cong 6.736 e^{j3.82^\circ}$$

$$\rightarrow V^+ \cong \frac{6.736 e^{j3.82^\circ}}{e^{j6.84^\circ} (1 + 0.277 e^{j20.0^\circ})}$$

$$\sim 1.26 + j0.0949$$

$$\cong 5.33 e^{-j7.32^\circ}$$

$$\therefore V(l) \cong 5.33 e^{-j7.32^\circ} e^{j\frac{2\pi}{\lambda} l} (1 + 0.277 e^{j33.7^\circ} e^{-j2\frac{2\pi}{\lambda} l})$$

The load-end voltage can be calculated as


$$V_L = V(l=0) \approx 5.33 e^{-j\hat{7.32}^\circ} \left(\underbrace{1 + 0.277 e^{j\hat{33.7}^\circ}}_{\sim 1.23 + j\hat{0.154}} \right)$$

$$\approx 5.33 e^{-j\hat{7.32}^\circ} \left(1.24 e^{j\hat{7.125}^\circ} \right) \approx \boxed{6.61 e^{-j\hat{0.198}^\circ} \text{ (V)}}$$

$$(e) \quad P_{Z_{in}} = P_{Z_L} = \frac{1}{2} \frac{|V_s|^2}{|Z_{in}|} \cos(\angle Z_{in})$$

$$\approx \frac{1}{2} \frac{(6.736)^2}{(102)} \cos(11.62^\circ) \approx \boxed{0.218 \text{ W}}$$

#5

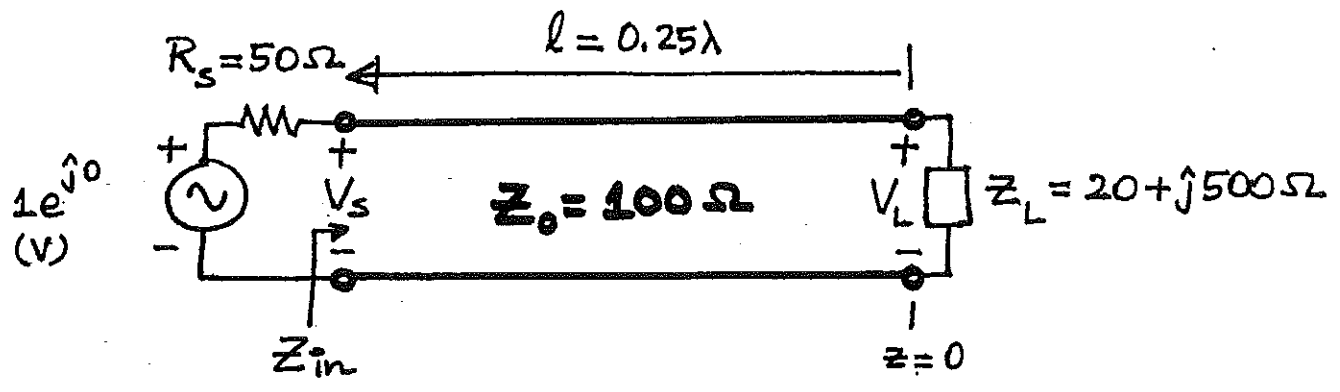

$$(a) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{20 + j500 - 100}{20 + j500 + 100}$$


$$= \frac{-80 + j500}{120 + j500} = \frac{-4 + j25}{6 + j25}$$

$$= \frac{\sqrt{641} e^{j \tan^{-1}(-25/4) + j\pi}}{\sqrt{661} e^{j \tan^{-1}(25/6)}} \approx \boxed{0.985 e^{j22.6^\circ}}$$

$$(b) S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \approx \frac{1 + 0.985}{1 - 0.985} \approx \boxed{130.2}$$

$$(c) Z_{in} = \frac{Z_0^2}{Z_L} = \frac{(100)^2}{20 + j500} = \frac{500}{1 + j25} \cdot \frac{1 - j25}{1 - j25}$$
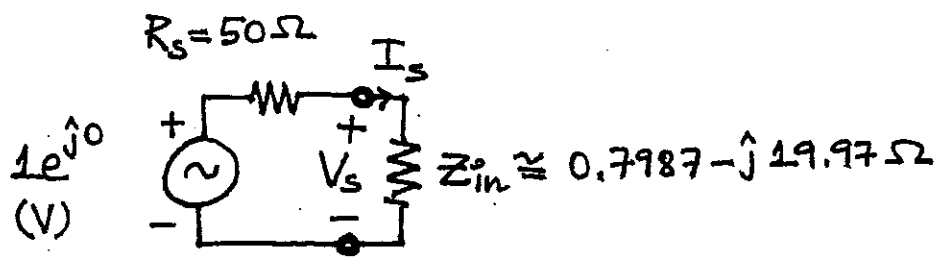
$$= \frac{500(1 - j25)}{1^2 + (25)^2} \approx 0.7987 - j19.97 \Omega$$



Using Ohm's law & KVL $\Rightarrow I_s = \frac{1e^{j0} \text{ (V)}}{(50 + 0.7987 - j19.97) \Omega}$

$$\approx 18.32 e^{j21.46^\circ} \text{ (mA)}$$


$$\therefore P_{R_s} = \frac{1}{2} R_s |I_s|^2 \approx \frac{1}{2} (50) (18.32 \text{ m})^2 \approx \boxed{8.39 \text{ mW}}$$

$$\& P_{R_L} = P_{z_{in}} = \frac{1}{2} R_{in} |I_s|^2 \approx \frac{1}{2} (0.7987) (18.32 \text{ m})^2$$

$$\approx \boxed{134 \mu\text{W}}$$

$$\therefore P_{\text{TOTAL}} = P_{R_s} + P_{R_L} \approx \boxed{8.52 \text{ mW}}$$

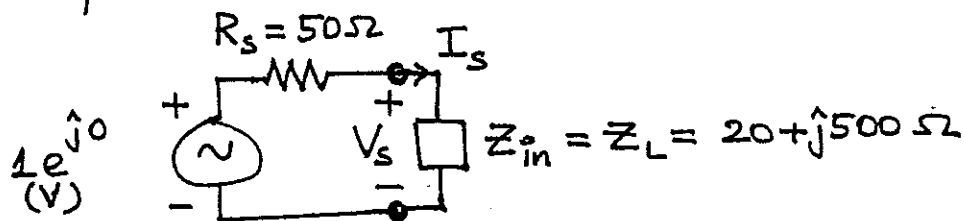(d) For $l = 0.5\lambda$, the Thevenin equivalent circuit seen from the source end will be




$$I_s = \frac{1e^{j0} \text{ (V)}}{(50 + 20 + j500) \Omega} \approx 1.98 e^{-j82.03^\circ} \text{ (mA)}$$

$$\therefore P_{R_s} \approx \frac{1}{2} (50) (1.98 \text{ m})^2 \approx \boxed{98 \mu\text{W}}$$

$$\& P_{R_L} \approx \frac{1}{2} (20) (1.98 \text{ m})^2 \approx \boxed{39.2 \mu\text{W}}$$

$$\therefore P_{\text{TOTAL}} \approx \boxed{137 \mu\text{W}}$$


#6

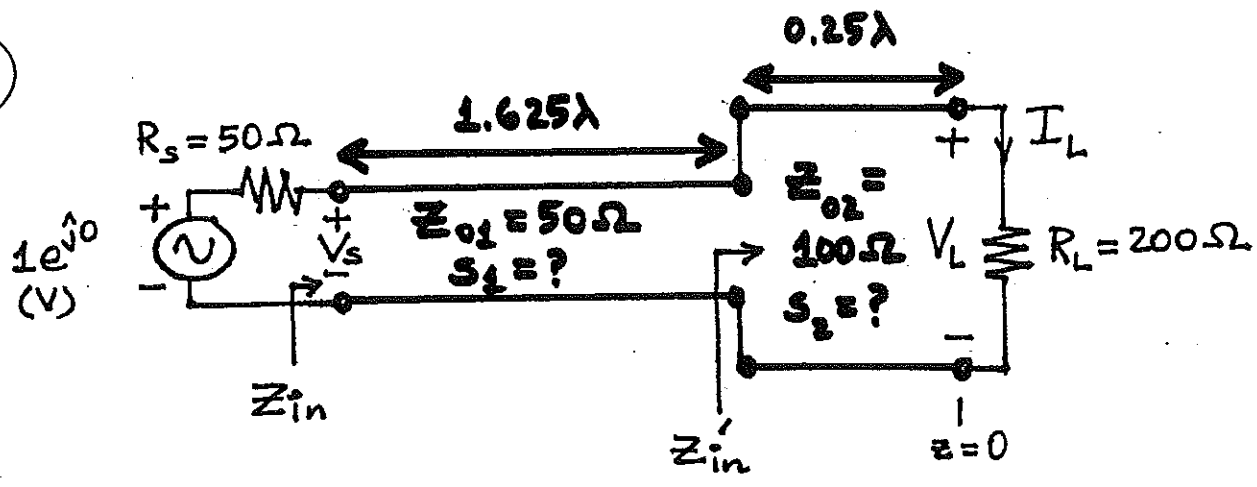


$$(a) \Gamma_L = \frac{R_L - Z_{02}}{R_L + Z_{02}} = \frac{200 - 100}{200 + 100} = \frac{1}{3}$$

$$\therefore S_2 = \frac{1 + |\Gamma_L(z)|}{1 - |\Gamma_L(z)|} = \frac{1 + 1/3}{1 - 1/3} = \frac{4/3}{2/3} = \boxed{2}$$
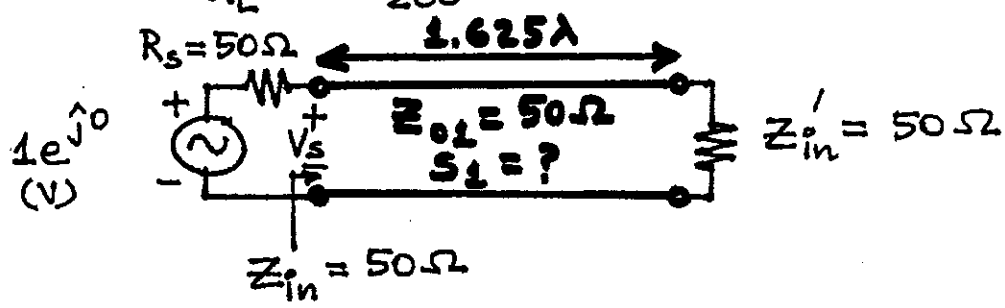
$$Z'_{in} = \frac{Z_{02}^2}{R_L} = \frac{(100)^2}{200} = 50 \Omega$$




$$\therefore \Gamma_1(z) = 0 \rightarrow S_1 = \frac{1 + |\Gamma_1(z)|}{1 - |\Gamma_1(z)|} = \boxed{1}$$

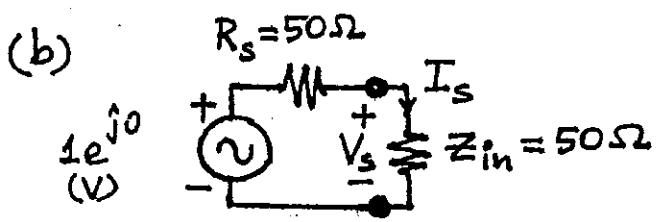

$$V_s = \frac{Z_{in}}{R_s + Z_{in}} (1e^{j0}) = 0.5V, I_s = V_s / Z_{in} = 10mA$$

$$P_{Z_{in}} = P_{R_L} = \frac{1}{2} |V_s| |I_s| \cos(\underbrace{\angle V_s - \angle I_s}_0) = \frac{1}{2} (0.5) (10m) = \boxed{2.5mW}$$

#7

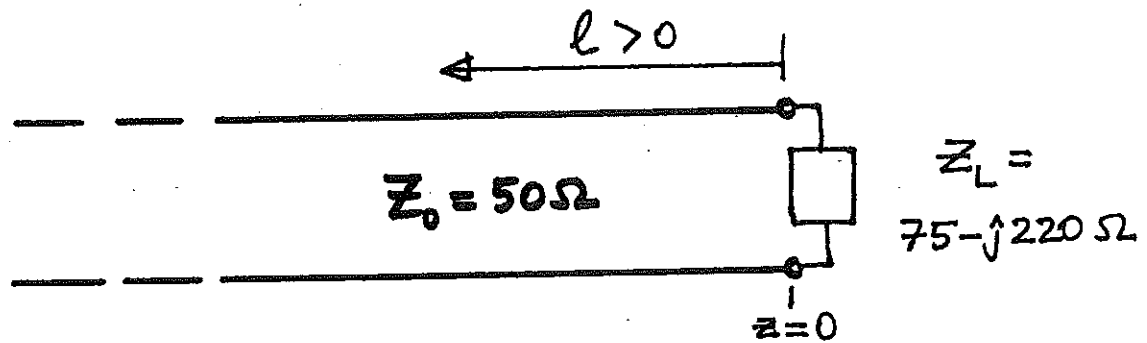

(a)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{75 - j220 - 50}{75 - j220 + 50}$$

$$= \frac{25 - j220}{125 - j220} = \frac{5 - j44}{25 - j44} \approx \boxed{0.875 e^{-j23.1^\circ}}$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \approx \frac{1 + 0.875}{1 - 0.875} \approx \boxed{15.0}$$

$$(b) \quad \% \text{ reflected power} = |\Gamma_L|^2 \times 100 \approx (0.875)^2 \times 100 \approx \boxed{76.6\%}$$

$$(c) \quad \text{Im} \{ Z_{in} \} = X_{in} = 0$$

$$X_L Z_0 + T(Z_0^2 - R_L^2 - X_L^2) - Z_0 X_L T^2 = 0$$

$$(-220)(50) + T(50^2 - 75^2 - (-220)^2) - (50)(-220)T^2 = 0$$

$$11,000T^2 - 51,525T - 11,000 = 0$$

From Inan's Z_{in} handout!

$$440T^2 - 2,061T - 440 = 0$$

$$T_{1,2} = \frac{2,061 \pm \sqrt{(2,061)^2 + 4(440)^2}}{2 \times 440}$$

$$\approx 4.89, -2.05 \times 10^{-1}$$

Since $T = \tan(\beta l) = \tan\left(2\pi \frac{l}{\lambda}\right)$, then

$$l_1, l_2 \approx 0.218\lambda, 0.468\lambda$$

From Inan's
Z_{in} handout!

$$\text{Using } \operatorname{Re}\{Z_{in}\} = R_{in} = \frac{R_L Z_0^2 (1+T^2)}{(Z_0 - X_L T)^2 + R_L^2 T^2}$$

we can find Z_{in} at the above two positions as follows:


At $l_1 \approx 0.218\lambda$, we have

$$Z_{in_1} \approx \frac{75(50)^2(1+(4.89)^2)}{(50 - (-220)(4.89))^2 + (75)^2(4.89)^2} \approx \boxed{3.33 \Omega}$$

At $l_2 \approx 0.468\lambda$, we have

$$Z_{in_2} \approx \frac{75(50)^2(1+(-0.205)^2)}{(50 - (-220)(-0.205))^2 + (75)^2(-0.205)^2} \approx \boxed{750.3 \Omega}$$


#8

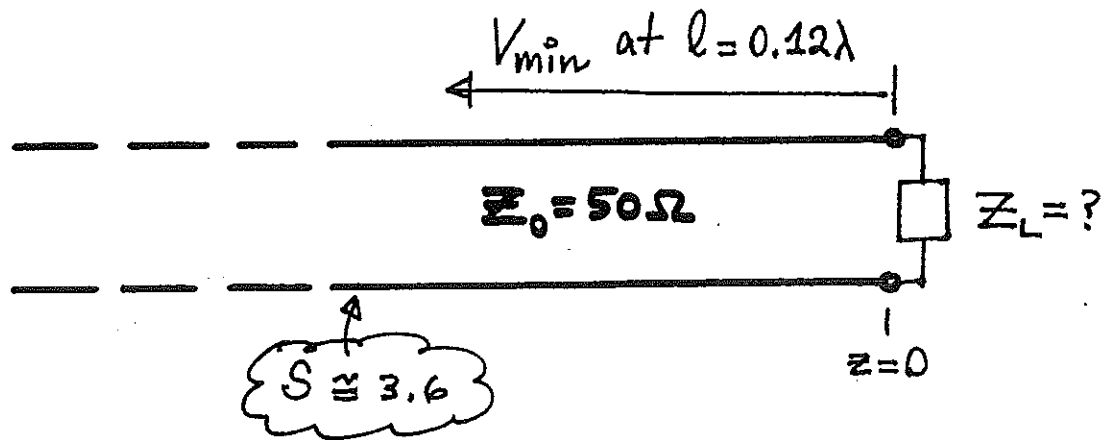

From Inan² text, p. 139, we have

$$\begin{aligned}
 Z_L &= Z_0 \frac{1 - \hat{j} S \tan(\beta l_{min})}{S - \hat{j} \tan(\beta l_{min})} \\
 &\cong 50 \frac{1 - \hat{j} 3.6 \tan(2\pi(0.12))}{3.6 - \hat{j} \tan(2\pi(0.12))} \\
 &\cong 50 \frac{1 - \hat{j} 3.38}{3.6 - \hat{j} 0.939} \cdot \frac{3.6 + \hat{j} 0.939}{3.6 + \hat{j} 0.939} \\
 &\cong 50 \cdot \frac{3.6 + 3.38(0.939) - \hat{j} [(3.38)(3.6) - 0.939]}{(3.6)^2 + (0.939)^2} \\
 &\cong \boxed{24.5 - \hat{j} 40.6 \Omega}
 \end{aligned}$$

#9

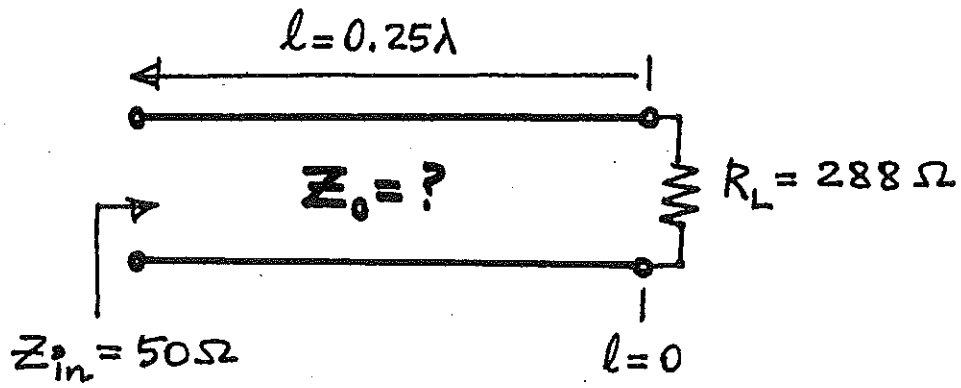

$$Z_{in} = \frac{Z_0^2}{R_L} \rightarrow Z_0 = \sqrt{(50)(288)}$$
$$= \boxed{120\Omega}$$