

University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2006

Midterm Exam # 2
Sinusoidal Steady-State Waves on Transmission Lines

(Prepared by Professor A. S. Inan)

(Friday, April 21, 2006)

(Closed Book Exam; 2 Formula Sheets Allowed)

(Total Time: 55 mins.)

Name: _____ ☺

Signature: _____ ☺

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”

Anonymous


“Honesty is not for sale.”

A. Inan

This table will be used by Inan for grading!

Problem #	Points gained
#1	
#2	
#3	
Total	

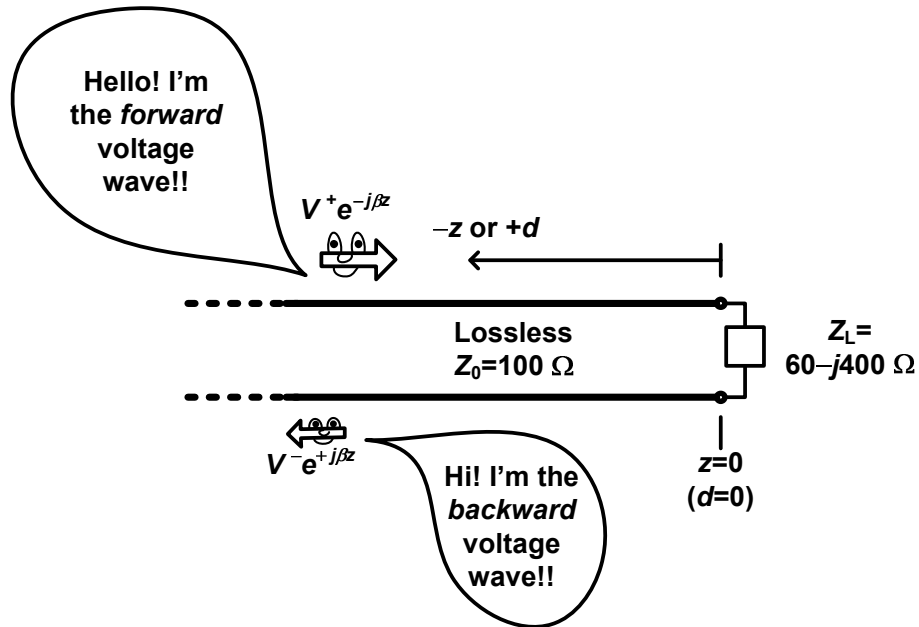
(1) (15 mins., Total: 40 points) **A lossless transmission line terminated with a complex impedance.** A $100\ \Omega$ transmission line is terminated with an inductive load impedance given by $Z_L = 60 - j400\ \Omega$, as shown.



(a) (10 points) Find the load reflection coefficient, Γ_L . (Provide your answer in polar form.) Show your work!

- (b) (10 points) What is the value of the standing wave ratio, S , on the line? (Show your work!)
- (c) (10 points) Calculate the percentage time-average incident power that reflects back from the load.
- (d) (10 points) Find the V_{\max} and V_{\min} positions nearest to the load. Provide your answers as electrical lengths.

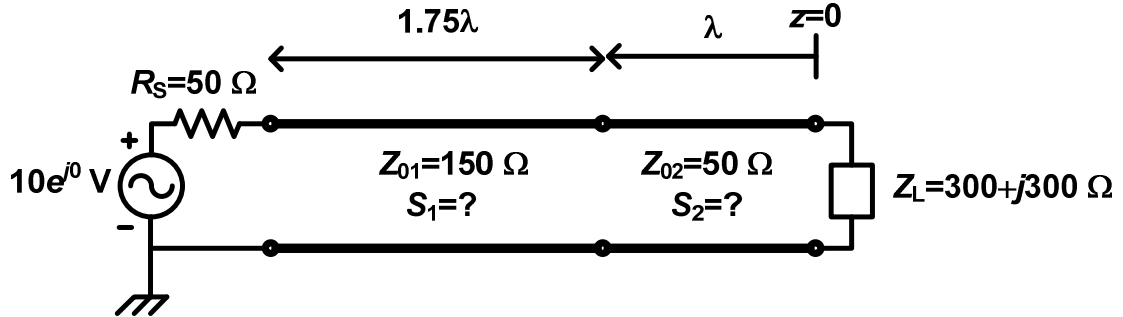(2) (15 mins., Total: 30 points) **Two cascaded transmission lines.** Consider the transmission line circuit as shown. Assume lossless lines.




(a) (15 points) Find the standing wave ratio on each line. Show your work!

(b) (15 points) Find the time-average power delivered to the load impedance.

(3) (15 mins., Total: 30 points) **Input impedance.** Consider the transmission line circuit as shown where Z_P impedance represents a parallel lumped element.

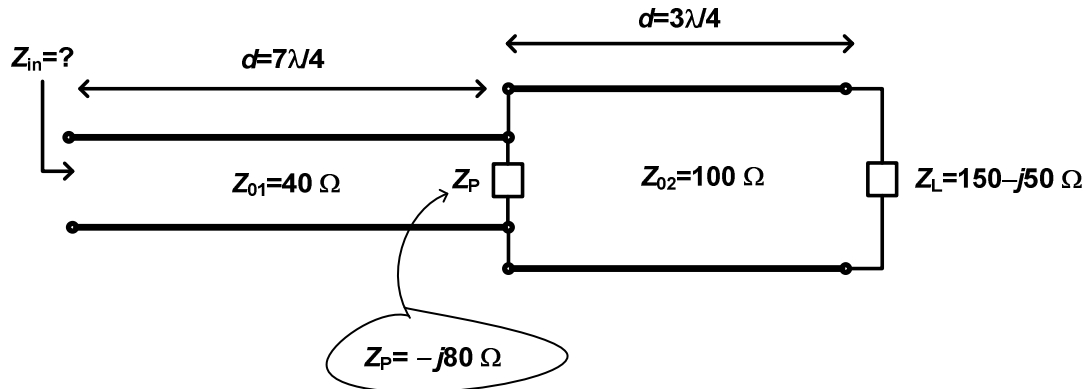(a) (20 points) Find the input impedance Z_{in} . Show your work step by step.



(b) (10 points) Assume that the physical length of each transmission line stays the same, however, the wavelength reduces by a factor of 2. What will be the new value of the input impedance Z_{in} ? Why? (Assume the values of Z_L , Z_P , Z_{01} and Z_{02} to stay the same.)