

University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2007

Midterm Exam # 2
Sinusoidal Steady-State Waves on Transmission Lines

(Prepared by Professor A. S. Inan)

(Monday, April 16, 2007)

(Closed Book Exam; 2 Formula Sheets Allowed)

(Total Time: 55 mins.)

Name: _____ ☺

Signature: _____ ☺

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”

Anonymous


“Honesty is not for sale.”

A. Inan

This table will be used by Inan for grading!

Problem #	Points gained
#1	
#2	
#3	
Total	

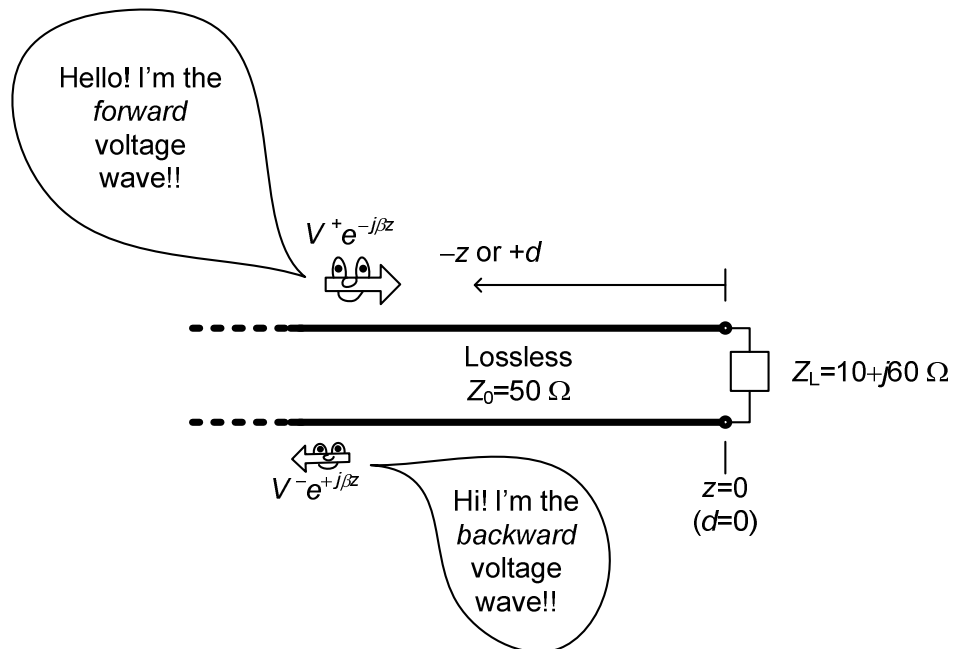(1) (15 mins., Total: 40 points) **A lossless transmission line terminated with a complex impedance.** A $50\ \Omega$ transmission line is terminated with an inductive load impedance given by $Z_L = 10 + j60\ \Omega$, as shown.




(a) (10 points) Find the load reflection coefficient, Γ_L . (Provide your answer in polar form.) Show your work!

(b) (10 points) What is the value of the standing wave ratio, S , on the line? (Show your work!)

(c) (10 points) Calculate the percentage time-average incident power that reflects back from the load.

(d) (10 points) Find the V_{\max} and V_{\min} positions nearest to the load. Provide your answers as electrical lengths.

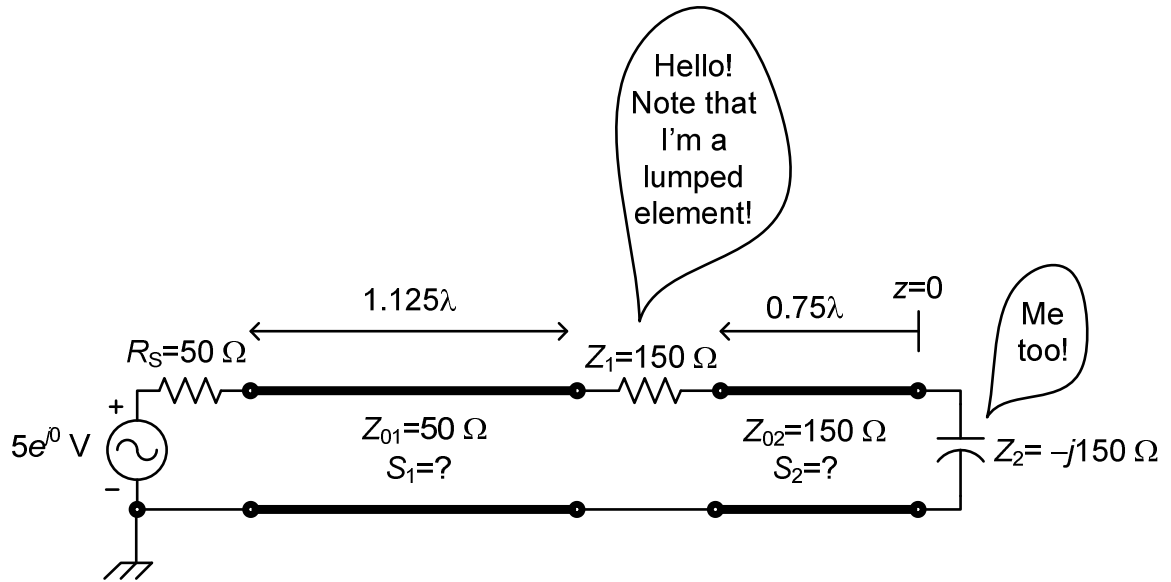(2) (15 mins., Total: 30 points) **Two cascaded transmission lines.** Consider the transmission line circuit as shown. Assume lossless lines.




(a) (15 points) Find the standing wave ratio on each line. Show your work!

(b) (15 points) Find the time-average power delivered to each impedance $Z_1=150 \Omega$ and $Z_2= -j150 \Omega$.

(3) (15 mins., Total: 30 points) **Unknown load impedance.** Consider a $50\ \Omega$ transmission line terminated with an unknown load Z_L . If the standing-wave ratio on the line is measured to be $S \cong 4.2$ and the nearest voltage minimum point with respect to the load is located at 0.21λ , find the following:

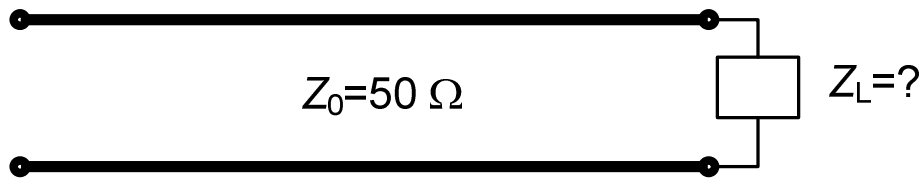(a) (10 points) The load impedance Z_L . Show your work step by step.



(b) (10 points) The nearest voltage maximum position to the load.

(c) (10 points) The input impedance Z_{in} at the nearest voltage minimum and maximum positions found in parts (a) and (b).