

4/23/2007

*University of Portland
School of Engineering*

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2007

Midterm Exam # 2
Sinusoidal Steady-State Waves on Transmission Lines
(Prepared by Professor A. S. Inan)

(Monday, April 16, 2007)
(Closed Book Exam; 2 Formula Sheets Allowed)
(Total Time: 55 mins.)

Name: SOLUTIONS  

Signature: Solutions 

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”

Anonymous

“Honesty is not for sale.”

A. Inan



4/23/2007


This table will be used by Inan for grading!

Problem #	Points gained
#1	
#2	
#3	
Total	

Put maximum points for each entry!



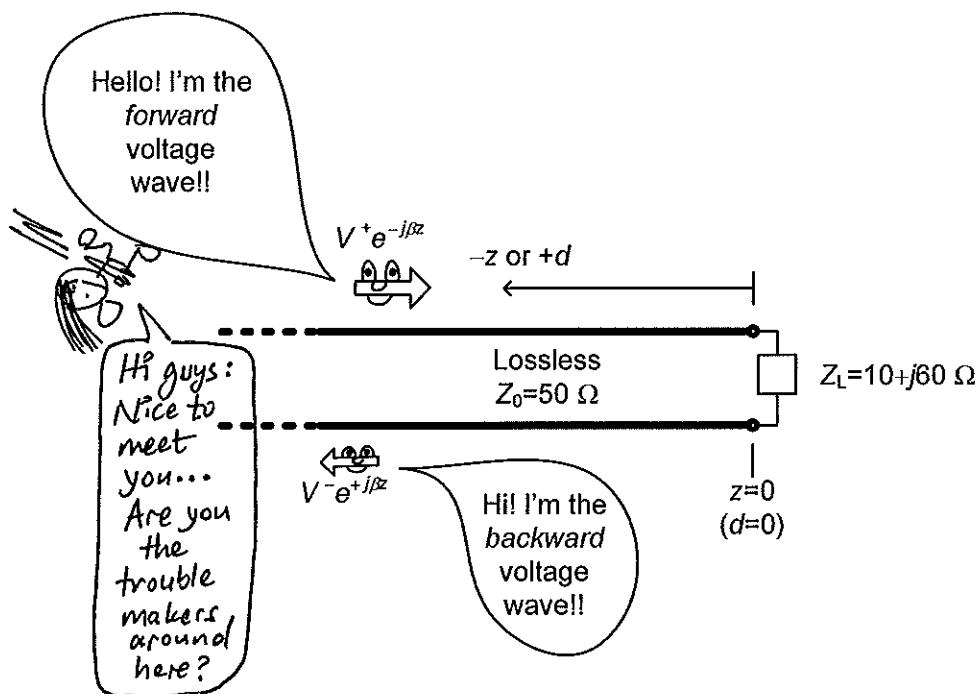- (1) (15 mins., Total: 40 points) A lossless transmission line terminated with a complex impedance. A 50Ω transmission line is terminated with an inductive load impedance given by $Z_L = 10 + j60\Omega$, as shown.



- (a) (10 points) Find the load reflection coefficient, Γ_L . (Provide your answer in polar form.) Show your work!

$$\begin{aligned}
 \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{10 + j60 - 50}{10 + j60 + 50} = \frac{-40 + j60}{60 + j60} \\
 &= \frac{-2 + j3}{3 + j3} \times \frac{3 - j3}{3 - j3} = \frac{(-6 + 9) + j(6 + 9)}{9 + 9} \\
 &= \frac{1 + j5}{6} \approx \boxed{0.85 e^{j78.7^\circ}}
 \end{aligned}$$



4/23/2007

- (b) (10 points) What is the value of the standing wave ratio, S , on the line? (Show your work!)

$$S = \frac{1 + |P_L|}{1 - |P_L|} \approx \frac{1 + 0.85}{1 - 0.85} \approx 12.3$$

This is
baby
stuff.
I had
more
difficult
stuff in high school!

- (c) (10 points) Calculate the percentage time-average incident power that reflects back from the load.

$$\frac{\text{I'm the time-average reflected power!}}{\frac{P^-}{P^+}} \times 100 = \frac{\frac{1}{2} \frac{|V^-|^2}{Z_0}}{\frac{1}{2} \frac{|V^+|^2}{Z_0}} \times 100 = |P_L|^2 \times 100$$

$$\approx (0.85)^2 \times 100 \approx 72.2\%$$

I'm the
time-average
incident power!



So only
27.8%
of the
incident
power
is
delivered
to the
load!

- (d) (10 points) Find the V_{\max} and V_{\min} positions nearest to the load. Provide your answers as electrical lengths.

I'm the
angle of P_L
and I'm
in radians!

$$\phi_L + 2Bz_{\max} = 0$$

$$\rightarrow 78.7^\circ \left(\frac{\pi}{180^\circ} \right) + 2 \left(\frac{2\pi}{\lambda} \right) z_{\max} = 0$$

$$\rightarrow \therefore z_{\max} \approx -0.109\lambda \quad \text{or} \quad \bar{z}_{\max} = \frac{z_{\max}}{\lambda} \approx -0.109$$

$$\therefore \bar{z}_{\min} = \frac{z_{\min}}{\lambda} \approx -0.109 - 0.25 = -0.359$$




Max-min points
are always apart
by quarter wavelength
if they are neighbors!

Come
out
you
coward
Indian
problem!

4/23/2007

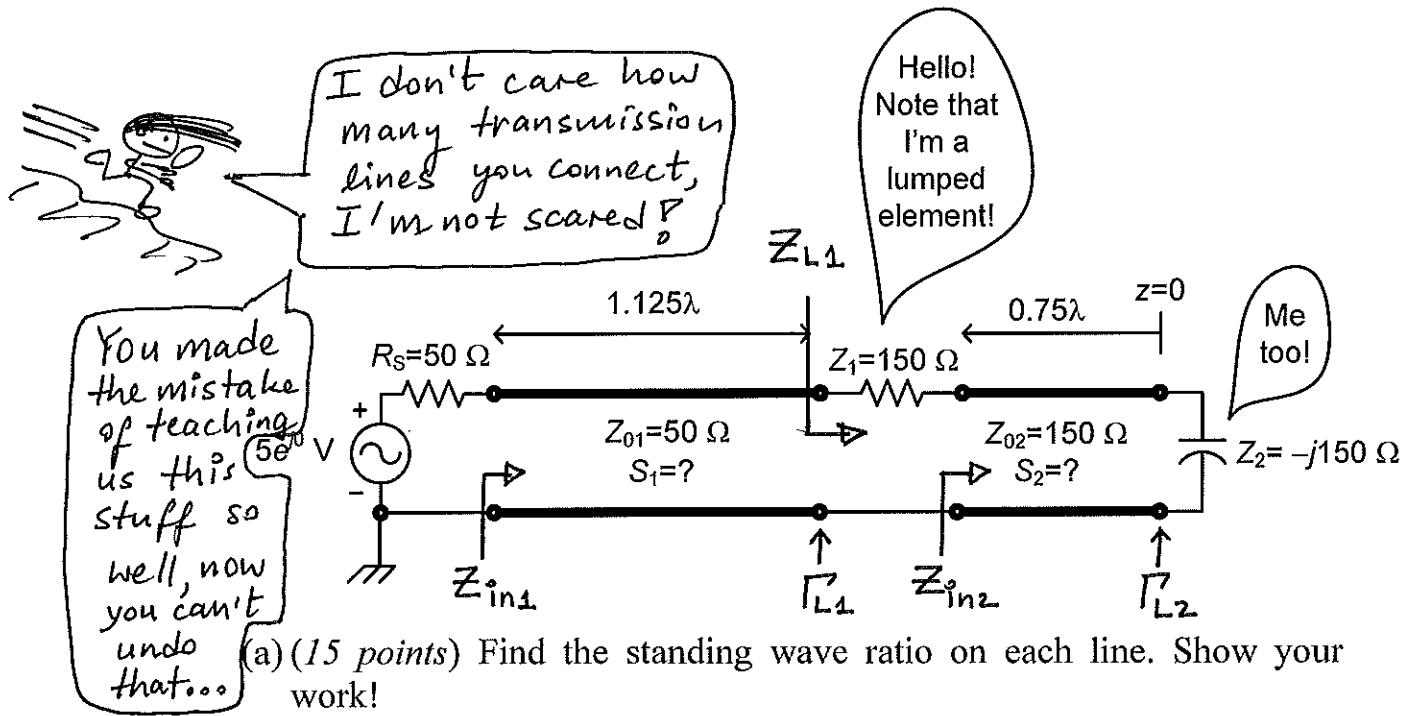(2) (15 mins., Total: 30 points) Two cascaded transmission lines. Consider the transmission line circuit as shown. Assume lossless lines.



(a) (15 points) Find the standing wave ratio on each line. Show your work!


$$\begin{aligned} \Gamma_{L_2} &= \frac{Z_2 - Z_{02}}{Z_2 + Z_{02}} = \frac{-j150 - 150}{-j150 + 150} \\ &= \frac{-j-1}{-j+1} = \frac{\sqrt{2} e^{j\pi/4}}{\sqrt{2} e^{-j\pi/4}} = 1 e^{j3\pi/2} = 1 e^{-j\pi/2} \end{aligned}$$

$$\therefore S_2 = \frac{1 + |\Gamma_{L_2}|}{1 - |\Gamma_{L_2}|} = \frac{1 + 1}{1 - 1} = \boxed{\infty}$$

$$Z_{i_{n2}} = \frac{Z_{02}^2}{Z_2} = \frac{(150)^2}{-j150} = j150 \Omega$$

$$Z_{L_1} = Z_1 + Z_{i_{n2}} = 150 + j150 \Omega$$

$$\begin{aligned} \Gamma_{L_1} &= \frac{Z_{L_1} - Z_{01}}{Z_{L_1} + Z_{01}} = \frac{150 + j150 - 50}{150 + j150 + 50} = \frac{2 + j3}{4 + j3} \times \frac{4 - j3}{4 - j3} \\ &= \frac{17 + j6}{25} \cong 0.721 e^{j19.4^\circ} \quad \therefore S_1 = \frac{1 + |\Gamma_{L_1}|}{1 - |\Gamma_{L_1}|} \cong \boxed{6.17} \end{aligned}$$

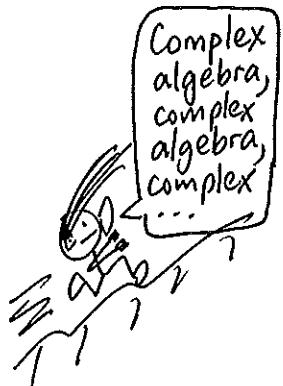

4/23/2007




I will deliver power
to Z_1 and Z_2 with
my own hands!

(b) (15 points) Find the time-average power delivered to each impedance
 $Z_1 = 150 \Omega$ and $Z_2 = -j150 \Omega$.

$$Z_{in1} = 50 \frac{150 + j150 + j50 \tan(\pi/4)}{50 + j(150 + j150) \tan(\pi/4)}$$

$$= 50 \frac{150 + j200}{-100 + j150} = 50 \frac{3 + j4}{-2 + j3} \times \frac{-2 - j3}{-2 - j3}$$
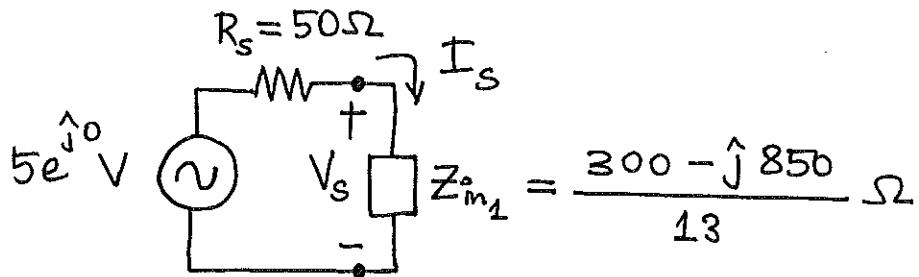
$$= 50 \frac{(-6 + j12) + j(-8 - 9)}{(-2)^2 + 3^2} = \frac{50}{13} (6 - j17) \Omega$$



$$I_s = \frac{5e^{j0}}{R_s + Z_{in1}} \cong \frac{5e^{j0}}{\underbrace{50 + 23.1 - j65.4}_{73.1}} \cong 51 e^{j41.8^\circ} (\text{mA})$$

$$\therefore P_{Z_{in1}} = \frac{1}{2} R_{in1} |I_s|^2 \cong 30 \text{ mW}$$

$$\therefore P_{Z_1} \cong \boxed{30 \text{ mW}} \text{ and } P_{Z_2} = \boxed{0} \text{ since both}$$

lines are lossless and Z_2 is purely reactive impedance.




Sorry Z_2 , you
need to hook up
with a resistance
otherwise you will
be powerless for the
rest of your life!

4/23/2007

(3) (15 mins., Total: 30 points) Unknown load impedance. Consider a 50Ω transmission line terminated with an unknown load Z_L . If the standing-wave ratio on the line is measured to be $S \cong 4.2$ and the nearest voltage minimum point with respect to the load is located at 0.21λ , find the following:

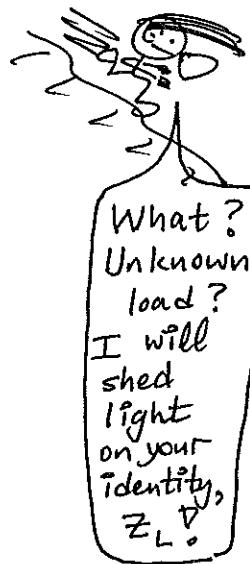(a) (10 points) The load impedance Z_L . Show your work step by step.



$$|\Gamma_L| = \frac{S-1}{S+1} = \frac{4.2-1}{4.2+1} \cong 0.615$$


$$\phi_L + 2Bz_{min} = \phi_L + 2\left(\frac{2\pi}{\lambda}\right)(-0.21\lambda) = -\pi$$

$$\rightarrow \phi_L = 0.84\pi - \pi = -0.16\pi \cong -28.8^\circ$$

$$\therefore \Gamma_L \cong 0.615 e^{-j0.16\pi} \cong 0.539 - j0.296$$

$$\rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{R_L + jX_L - 50}{R_L + jX_L + 50} \cong 0.539 - j0.296$$
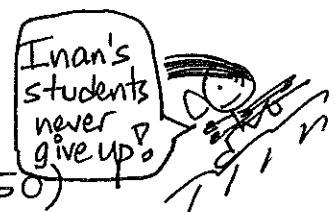
$$\rightarrow R_L + jX_L - 50 \cong 0.539(R_L + 50) + 0.296X_L + j0.539X_L - j0.296(R_L + 50)$$



$$\begin{cases} R_L - 50 = 0.539(R_L + 50) + 0.296X_L & \leftarrow \text{Real parts are equal...} \\ X_L = 0.539X_L - 0.296(R_L + 50) & \leftarrow \text{Imaginary parts are equal...} \end{cases}$$

$$\begin{cases} 0.461R_L - 0.296X_L = 76.96 \\ 0.296R_L + 0.461X_L = -14.8 \end{cases} \quad \begin{array}{l} \text{Solving simultaneously} \\ \text{yields} \end{array}$$



$R_L \cong 103.5 \Omega$
$X_L \cong -98.77 \Omega$



4/23/2007

(b) (10 points) The nearest voltage maximum position to the load.

$$\bar{z}_{\max} = \frac{z_{\max}}{\lambda} = \bar{z}_{\min} - 0.25 \\ = -0.21 - 0.25 = -0.46$$

Inan must
be shocked
with my
perseverance
and
confidence...

or $z_{\max} = \boxed{-0.46\lambda}$



I'm fired up!
I'm unstoppable!

(c) (10 points) The input impedance Z_{in} at the nearest voltage minimum and maximum positions found in parts (a) and (b).

Z_{in} at the voltage minimum position
is given by

$$Z_{in\min} = \frac{Z_0}{S} = \frac{50}{4.2} \approx \boxed{11.9\Omega}$$

Z_{in} at the voltage maximum position

is given by

$$Z_{in\max} = S Z_0 = (4.2)(50\Omega) = \boxed{210\Omega}$$



Note that both Z_{in}
are purely resistive...
One can also calculate
these values using the
 R_{in} expression...

That's it
for this time
folks...
Hope to talk
to you at
another episode
of Inan's
tests...

Inan: Your students are
more competent than what
you think and your tests are
a piece of cake!