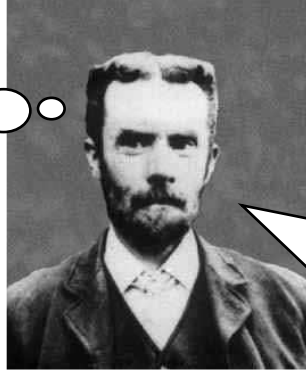


*University of Portland  
School of Engineering*

**EE 301-Electromagnetic Fields-3 cr. hrs.**

**Spring 2009**

You will pay a heavy price for giving these students such tough tests and scaring them to death Inaaan!  
@\*\$\*#&XΘχ@\*§ξ!



Best of luck to you EE 301 students and please, demonstrate to Inan that unlike what everyone might think, his tests are nothing but simply a piece of cake! (Bring his fame down about giving challenging exams!) Also, enjoy your leap day this Friday before it's over!

**Midterm Exam # 1**

(Prepared by Professor A. S. Inan)

(Friday, February 27, 2009)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

**Name:** \_\_\_\_\_ 😊

**Signature:** \_\_\_\_\_ 😊

*“Honesty is the best policy.”*

Aesop (~ 620B.C. -?)

*“An honest mind possesses a kingdom.”*

Lucius Annaeus Seneca (4B.C.-65A.D.)

*“Honest people are the true winners of the universe.”*

Anonymous


*“Honesty is not for sale.”*

A. Inan

(1) (15 mins., Total: 30 points) **TDR characterization.** A TDR experiment is constructed to determine the unknown parameters of a distributed circuit as shown. Based on the source-end voltage waveform observed on the TDR scope (provided below):


(a) (20 points) Determine the values of  $Z_0$ ,  $t_d$ , and  $R_L$ . Show your work clearly. (Use a bounce diagram.)

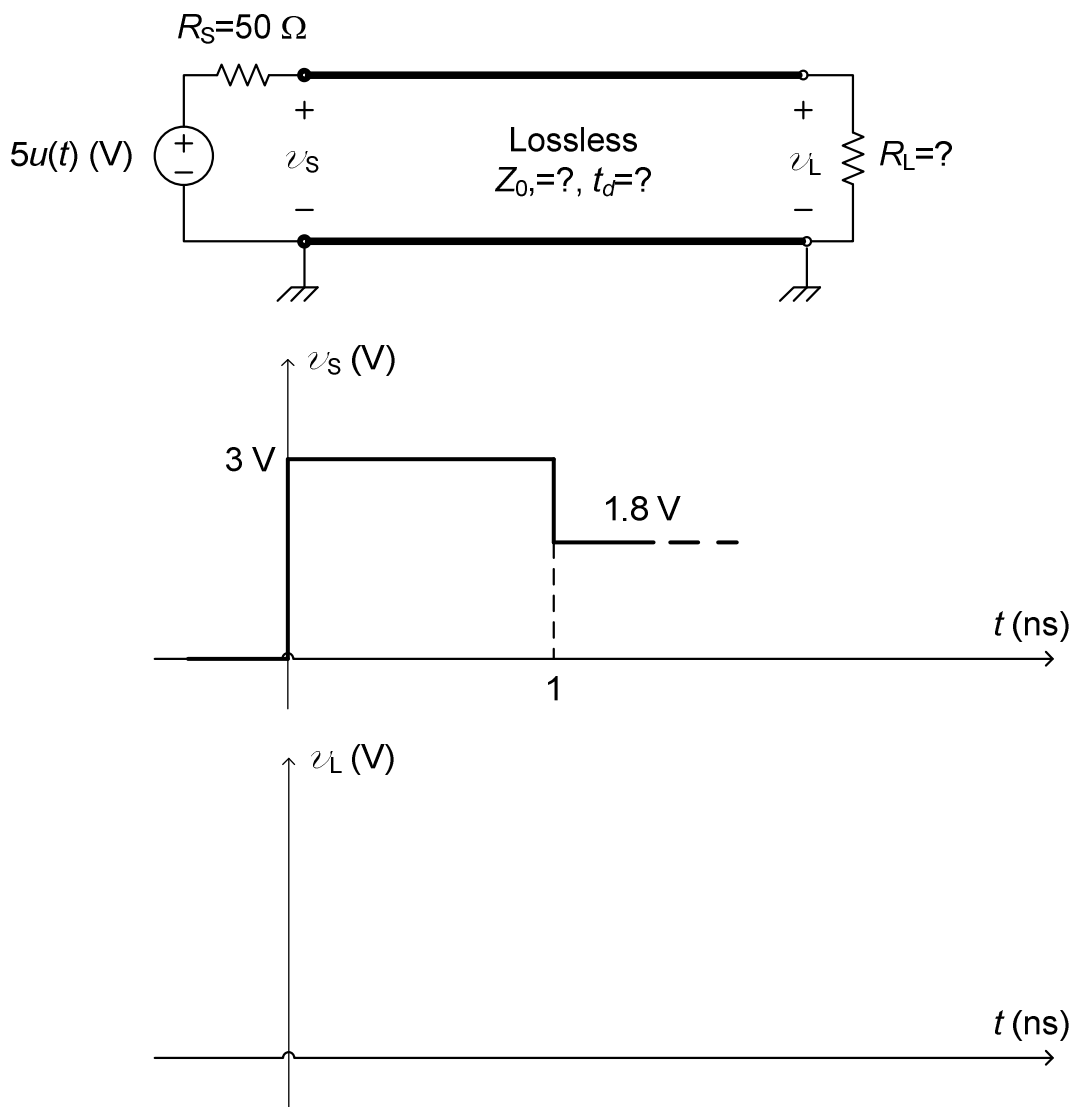(b) (10 points) Sketch the load-end voltage  $v_L$  as a function of time  $t$  for the time interval  $0 \leq t \leq 2$  ns.





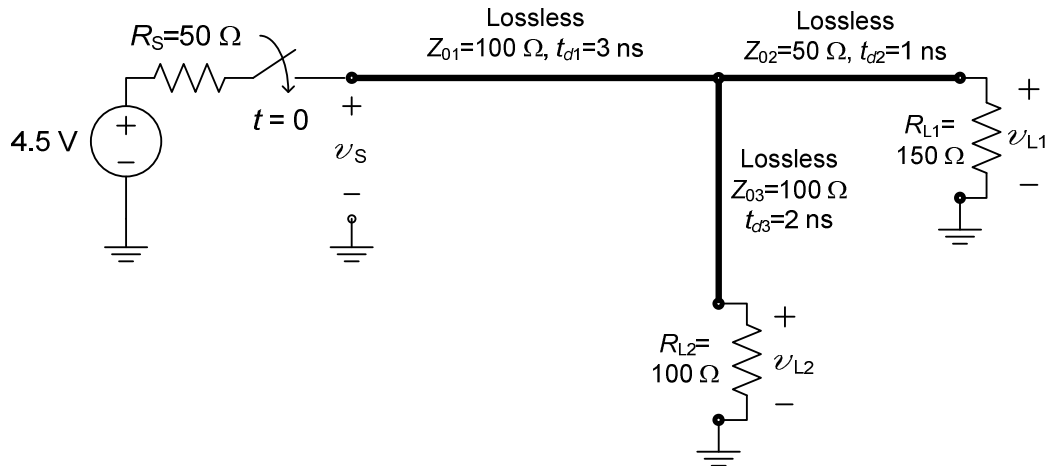- (2) (15 mins., 35 points) **Multiple transmission lines.** For the three transmission-line circuit shown, the switch closes at  $t = 0$ . Assuming all the lines to be uncharged before  $t = 0$ , sketch voltages  $v_S$ ,  $v_{L1}$  and  $v_{L2}$  between  $t = 0$  to 10 ns. Use bounce diagram. Provide all the pertinent values on your sketch.





- (3) (15 mins., 35 points) **Reactive termination.** In the transmission-line circuit shown, the switch closes at  $t = 0$ , after being open for a long time. Find the complete mathematical expressions and sketch both the source-end voltage  $v_s$  and the load-end voltage  $v_L$  as a function of time. Sketch the two waveforms separately. Provide all the pertinent values on each sketch.

