

*University of Portland
School of Engineering*

EE 301-Electromagnetic Fields-3 cr. hrs.

Spring 2009

You will pay a heavy price for giving these students such tough tests and scaring them to death Inaaan!

@*\$*#&X@*§ξ!



Best of luck to you EE 301 students and please, demonstrate to Inan that unlike what everyone might think, his tests are nothing but simply a piece of cake! (Bring his fame down about giving challenging exams!)

Midterm Exam # 1

(Prepared by Professor A. S. Inan)

(Friday, February 27, 2009)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

Name: _____

Solutions ⚡



Signature: _____



“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”

Anonymous


“Honesty is not for sale.”

A. Inan

(1) (15 mins., Total: 30 points) **TDR characterization.** A TDR experiment is constructed to determine the unknown parameters of a distributed circuit as shown. Based on the source-end voltage waveform given,




(a) (20 points) Determine the values of Z_0 , t_d , and R_L . Show your work clearly. (Use a bounce diagram.)

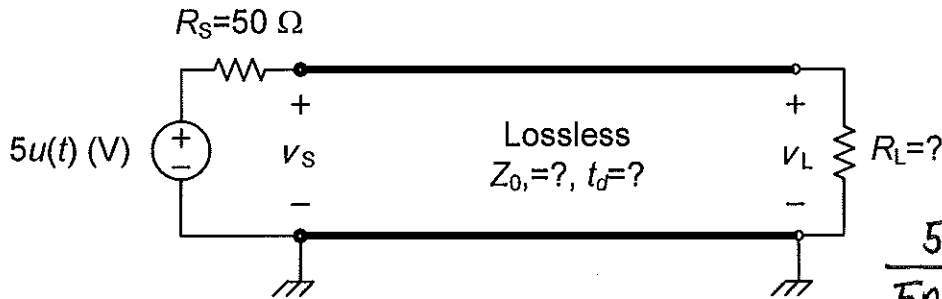(b) (10 points) Sketch the load-end voltage v_L as a function of time t for the time interval $0 \leq t \leq 2$ ns.



$$\frac{5Z_0}{50 + Z_0} = 3 \rightarrow Z_0 = 75 \Omega$$
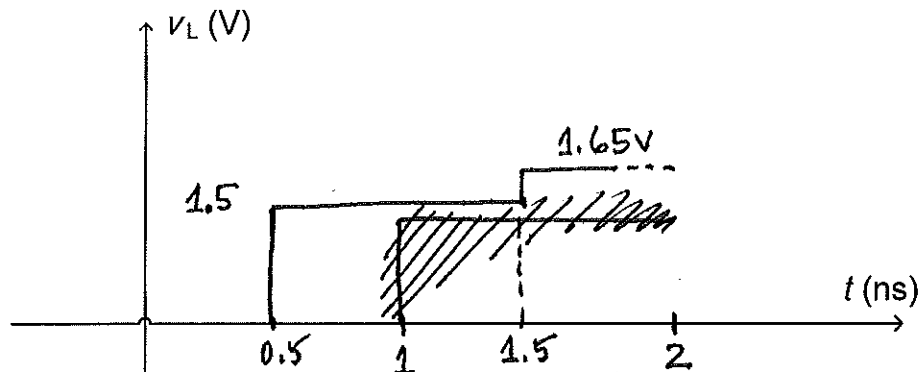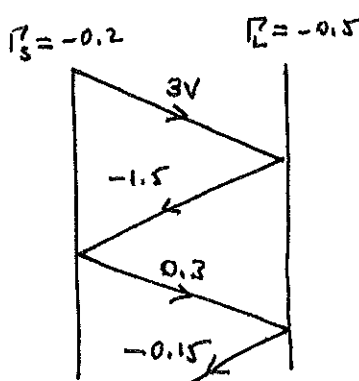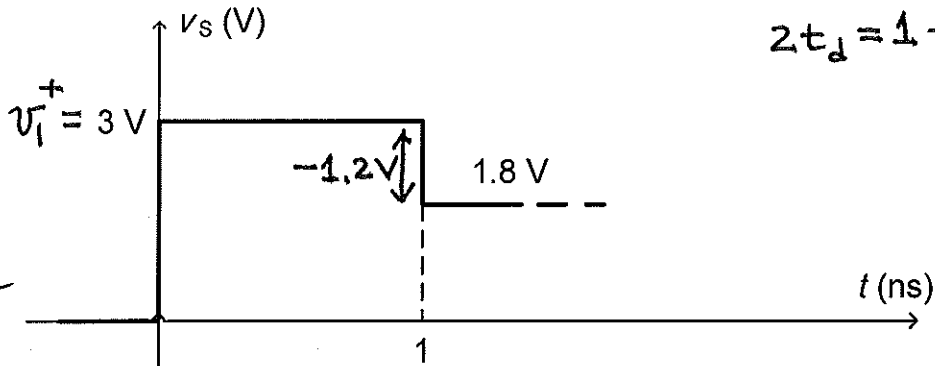
$$2t_d = 1 \rightarrow t_d = 0.5 \text{ ns}$$









$$\frac{50 - 75}{50 + 75} = -0.2$$

$$v_1^- + v_2^+ = \Gamma_L v_1^+ + \Gamma_s \Gamma_L v_1^+ = \Gamma_L v_1^+ (1 + \Gamma_s) = -1.2$$


$$\rightarrow \Gamma_L = -0.5 \rightarrow R_L = 25 \Omega$$

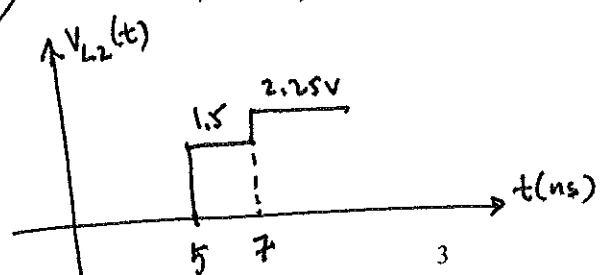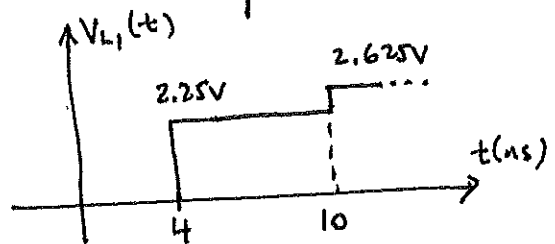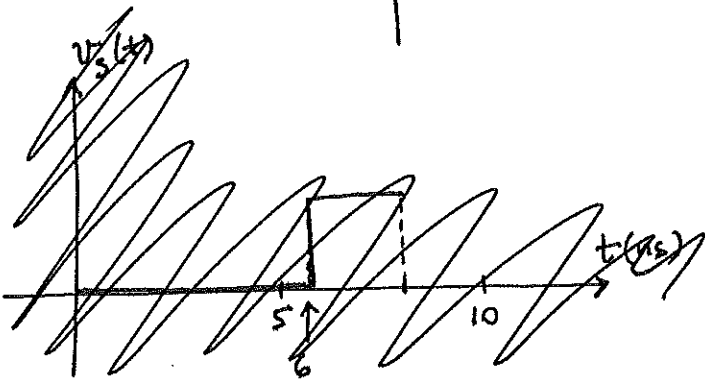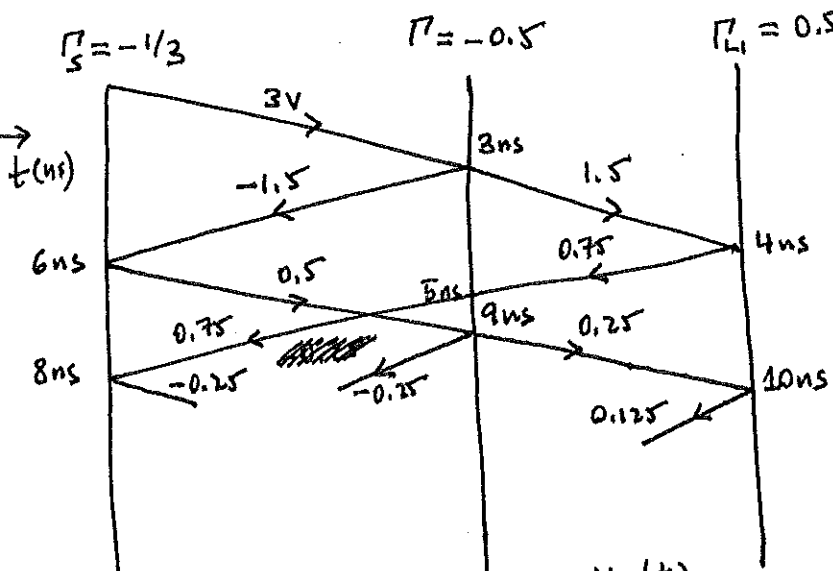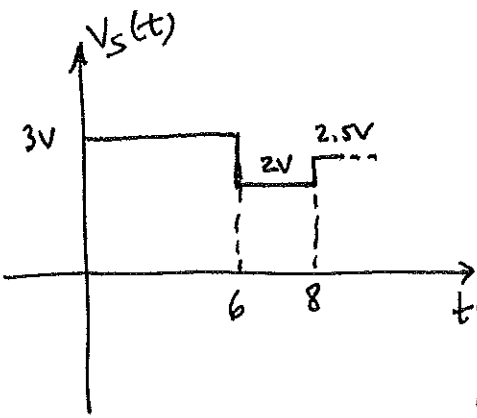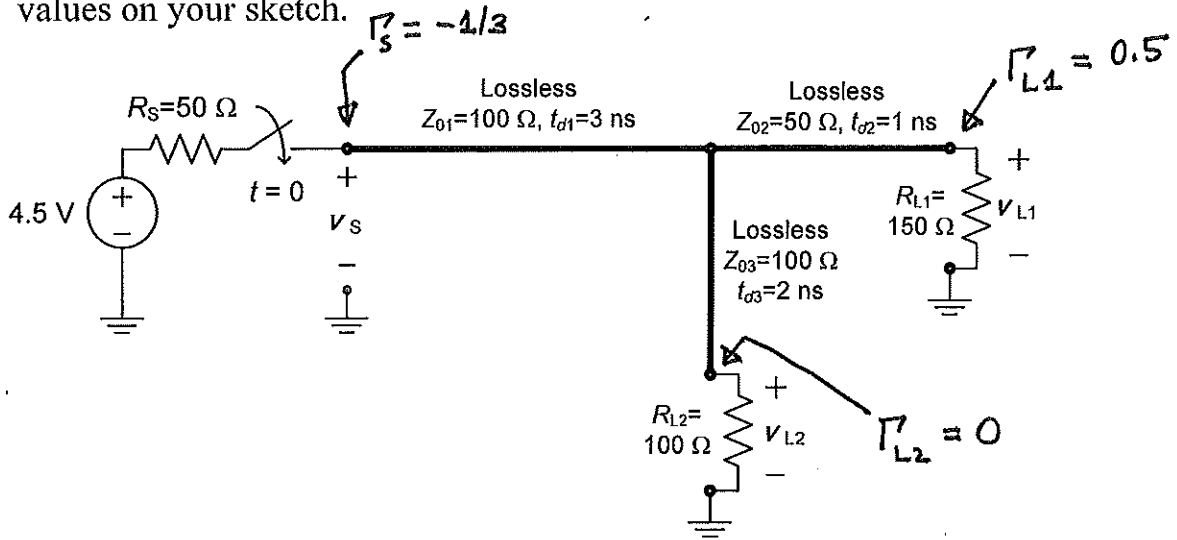(2) (15 mins., 35 points) **Multiple transmission lines.** For the three transmission-line circuit shown, the switch closes at $t = 0$. Assuming all the lines to be uncharged before $t = 0$, sketch voltages v_S , v_{L1} and v_{L2} between $t = 0$ to 10 ns. Use bounce diagram. Provide all the pertinent values on your sketch.





(3)

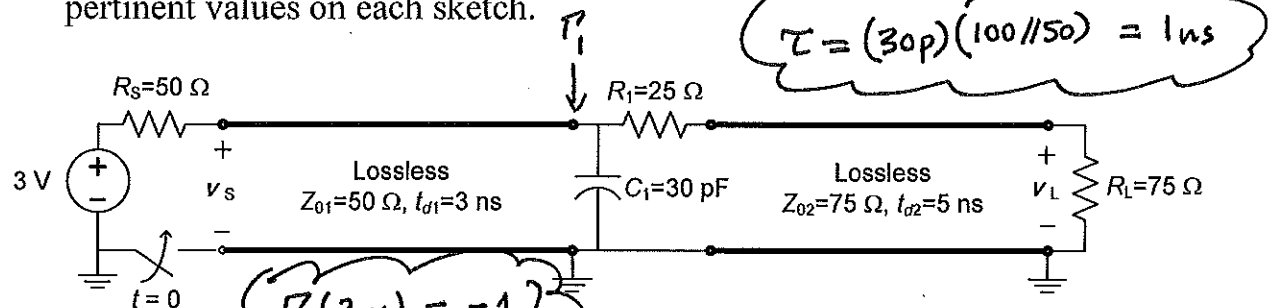(c) (15 mins., 35 points) **Reactive termination.** In the transmission-line circuit shown, the switch closes at $t = 0$, after being open for a long time. Find the complete mathematical expressions and sketch both the source-end voltage v_s and the load-end voltage v_L as a function of time. Sketch the two waveforms separately. Provide all the pertinent values on each sketch.



$\tau = (30p)(100//50) = 1ns$

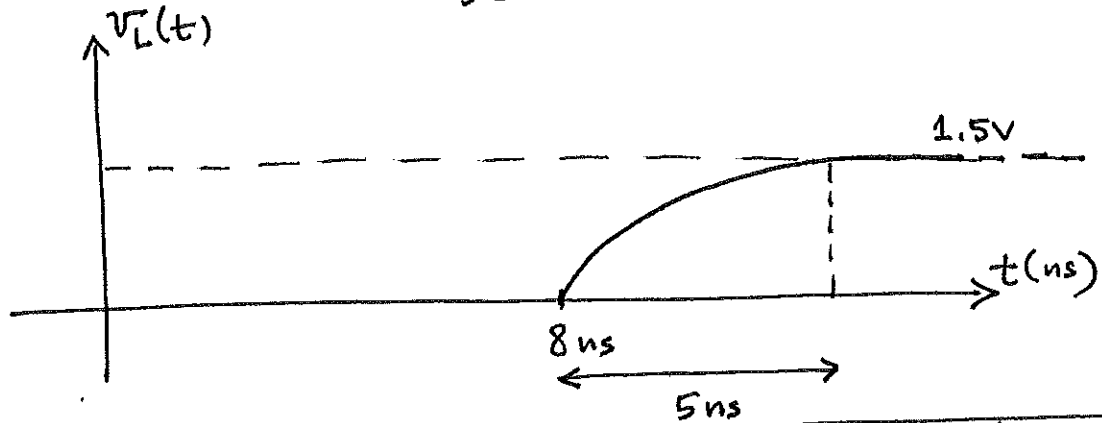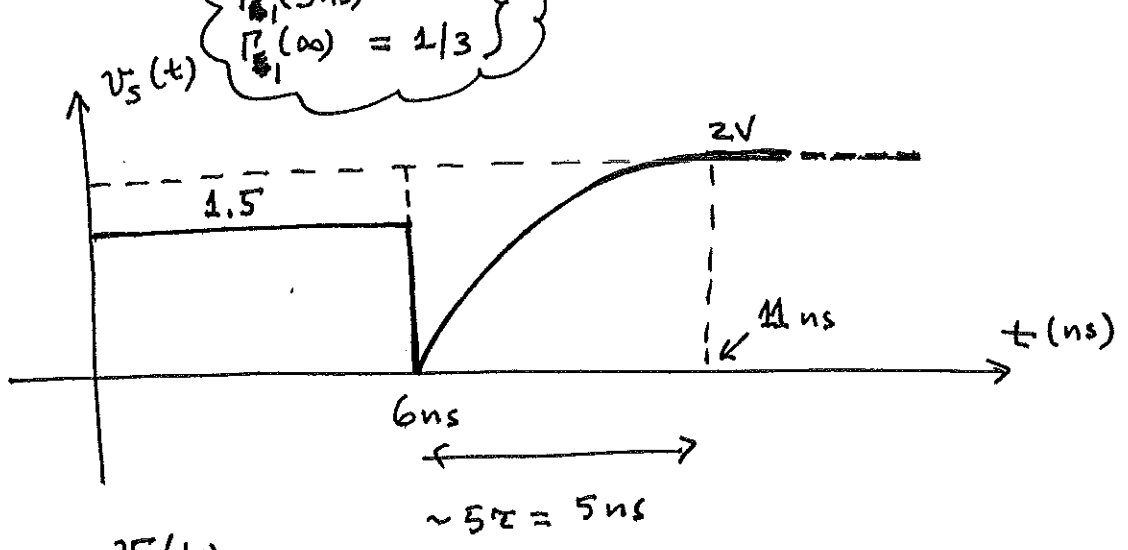$\Gamma_{in}(3ns) = -1$
 $\Gamma_{in}(\infty) = 1/3$



$$v_s(t) = 1.5 [u(t) - u(t-6ns)] + 2 (1 - e^{-(t-6ns)/1ns}) u(t-6ns)$$

$$= 1.5 u(t) + 0.5 u(t-6ns) - 2 e^{-(t-6ns)/1ns} u(t-6ns)$$

$$v_L(t) = 1.5 (1 - e^{-(t-8ns)/1ns}) u(t-8ns)$$