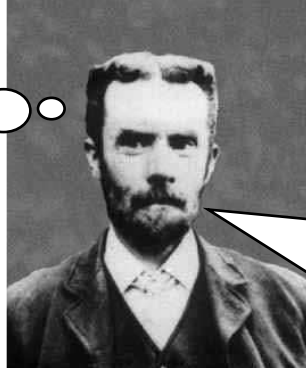


University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.

Spring 2011

You will pay a heavy price for giving these students such tough tests and scaring them to death Inaaan!
@*\$*#&XΘχ@*§ξ!



Best of luck to you EE 301 students and please, demonstrate to Inan that unlike what everyone might think, his tests are nothing but simply a piece of cake! (Bring his fame down about giving challenging exams!)

Midterm Exam # 1

(Prepared by Professor A. S. Inan)

(Friday, March 4, 2011)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

Name: _____ 😊

Signature: _____ 😊

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”

Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”


Anonymous

“Honesty is not for sale.”


A. Inan

(1) (15 mins., Total: 32.5 points) **Step excitation of a lossless line.** A uniform, lossless transmission line is excited with a step source as shown.

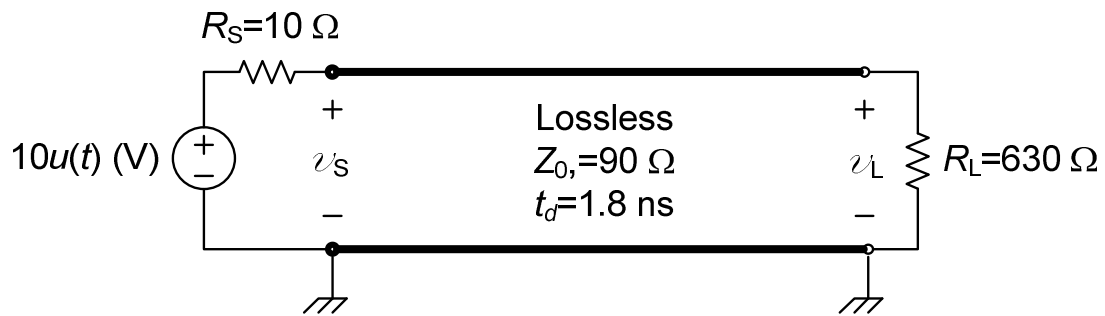
(a) (20 points) Provide an appropriate bounce diagram and use it to sketch both the source-end voltage v_s and the load-end voltage v_L as a function of time between 0 and 10 ns. Provide all the pertinent values on your sketches.



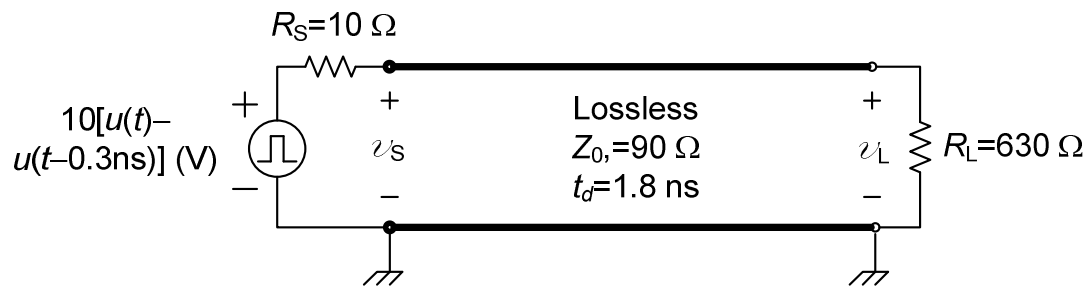(b) (12.5 points) Redo part (a) if the step source was a pulse source with 0.3 ns pulse width as shown.



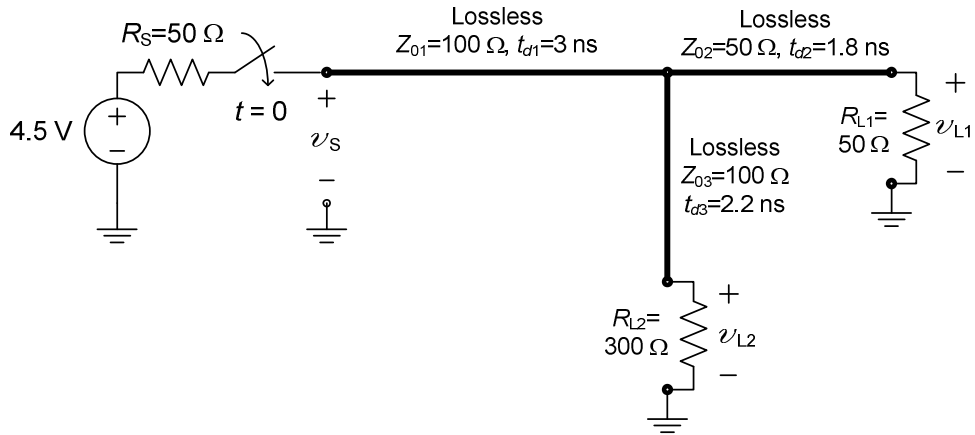- (2) (15 mins., 32.5 points) **Multiple transmission lines.** For the three transmission-line circuit shown, the switch closes at $t = 0$. Assuming all the lines to be uncharged before $t = 0$, sketch voltages v_S , v_{L1} and v_{L2} between $t = 0$ to 10 ns. Use bounce diagram. Provide all the pertinent values on your sketch.



- (3) (15 mins., 35 points) **Reactive element at the junction.** In the transmission-line circuit shown, find the complete mathematical expressions and sketch both the source-end voltage v_s and the load-end voltage v_L as a function of time. Sketch the two waveforms separately. Provide all the pertinent values on each sketch.

