

University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2011

Midterm Exam # 2
Sinusoidal Steady-State Waves on Transmission Lines

(Prepared by Professor A. S. Inan)

(Monday, April 18, 2011)

(Closed Book Exam; Formula Sheets Allowed)

(Total Time: 55 mins.)

Did you know that yesterday in the 21st century was the 221st anniversary of Benjamin Franklin's death? ☺ (He died on April 17, 1790, at age 84.)

Name: _____ ☺

Signature: _____ ☺

“Honesty is the best policy.”
Aesop (~ 620B.C. -?)


“An honest mind possesses a kingdom.”
Lucius Annaeus Seneca (4B.C.-65A.D.)

“Honest people are the true winners of the universe.”
Anonymous

This table will be used by Inan for grading!

Problem #	Points gained
#1	
#2	
#3	
Total	

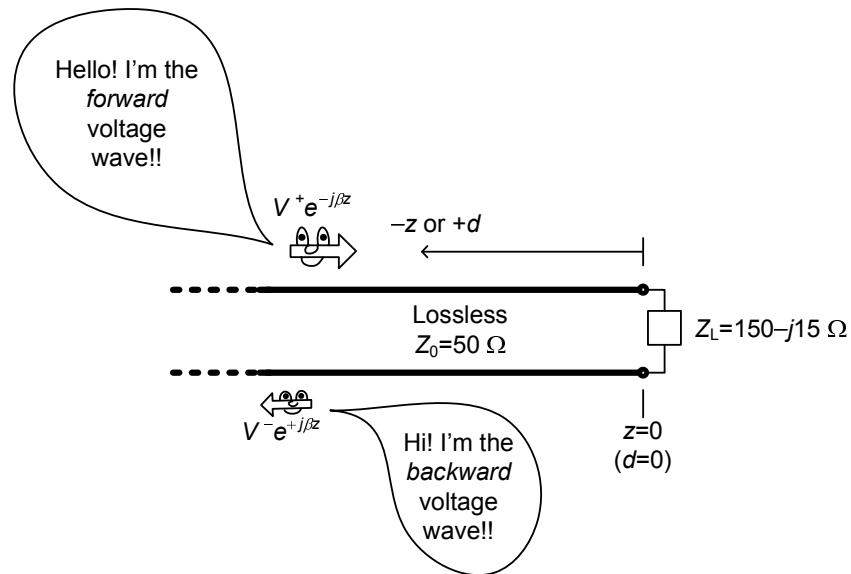(1) (15 mins., Total: 40 points) **A lossless transmission line terminated with a complex impedance.** A $50\ \Omega$ transmission line is terminated with an capacitive load impedance given by $Z_L = 150 - j15\ \Omega$, as shown.




(a) (10 points) Calculate the load reflection coefficient, Γ_L . (Provide your answer in polar form.) Show your work!

(b) (10 points) What is the value of the standing wave ratio, S , on the line?

(c) (10 points) Find the percentage time-average incident power that is absorbed by the load.

(d) (10 points) Find the V_{\max} and V_{\min} positions nearest to the load. Provide your answers as electrical lengths.

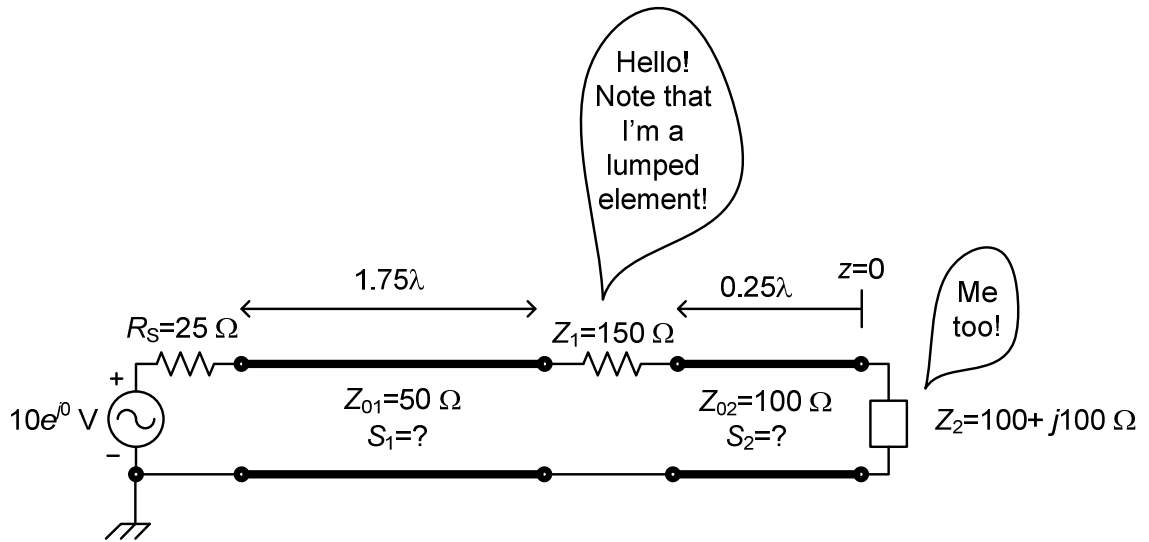(2) (15 mins., Total: 30 points) **Two cascaded transmission lines.** Consider the transmission line circuit as shown.



(a) (15 points) Find the standing wave ratio on each line. Show your work!

(b) (15 points) Find the time-average power delivered to the load impedance Z_2 .

(3) (15 mins., 30 points) **Input impedance.** Consider the transmission line circuit as shown where Z_p impedance represents a parallel lumped element. Find the input impedance Z_{in} . Show your work step by step.

