
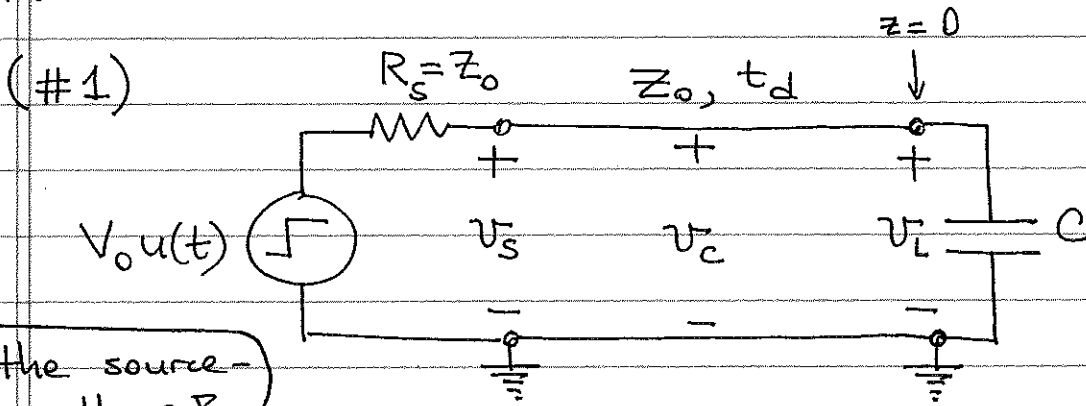


SOLUTIONS TO HOMEWORK #3

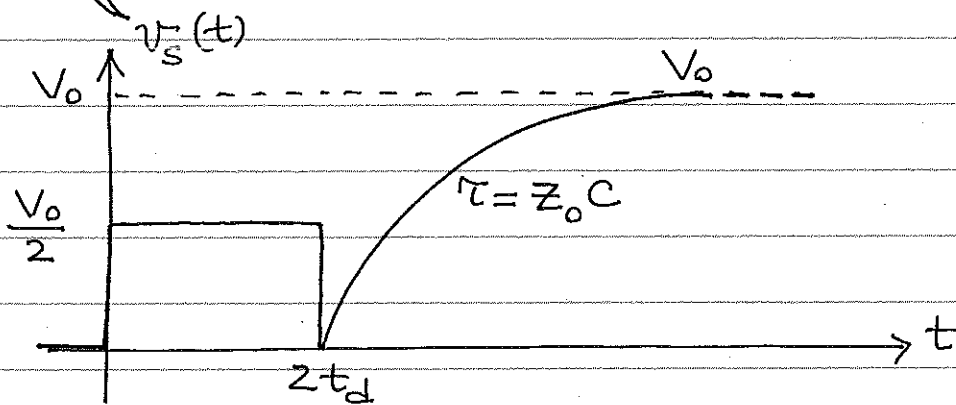


I'm the source-end voltage?



$$v_s(t) = \frac{V_0}{2} [u(t) - u(t-2t_d)] + V_0 (1 - e^{-(t-2t_d)/(Z_0 C)}) u(t-2t_d)$$


$$\text{or } \frac{V_0}{2} u(t) + \frac{V_0}{2} u(t-2t_d) - V_0 e^{-(t-2t_d)/(Z_0 C)} u(t-2t_d)$$

I'm the load-end voltage?

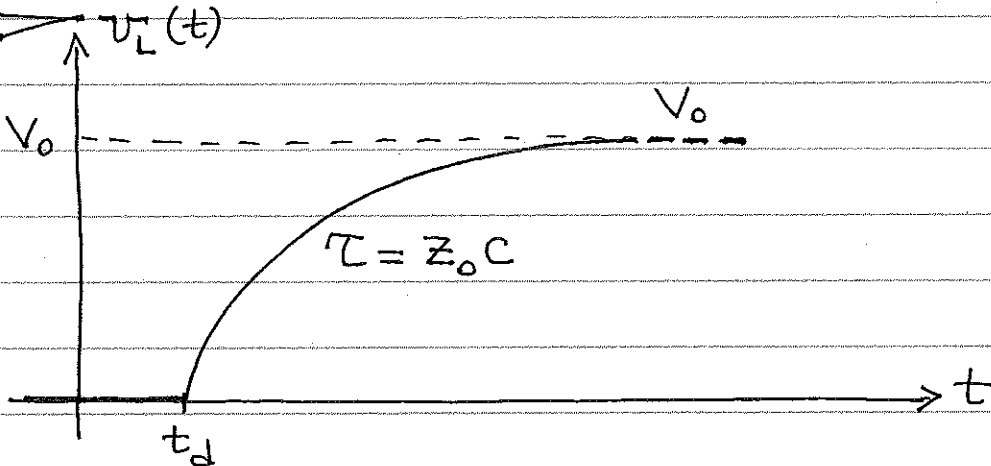

$$v_L(t) = V_0 \left(1 - e^{-(t-t_d)/(z_0 C)} \right) u(t-t_d)$$

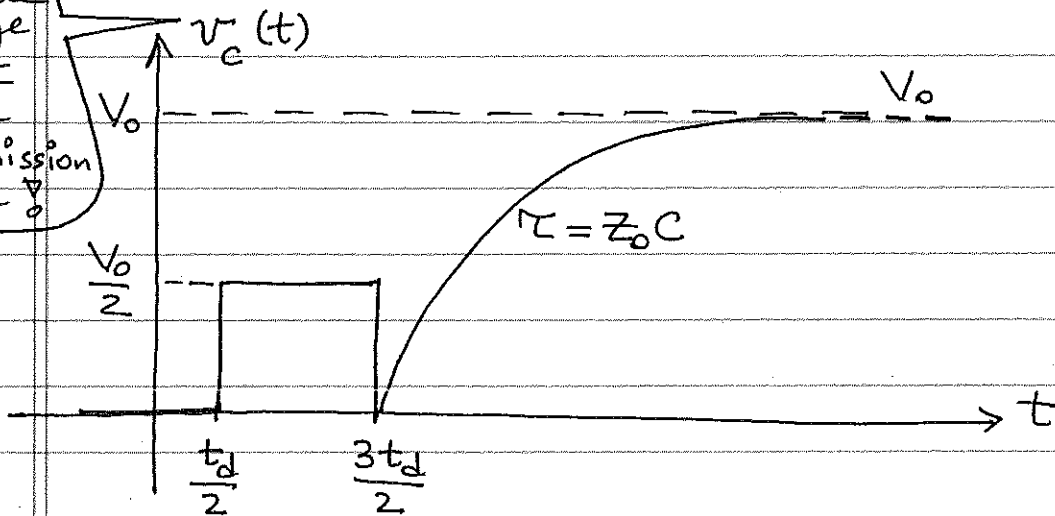
I'm the voltage at the center of the transmission line?




$$v_c(t) = \frac{V_0}{2} \left[u\left(t - \frac{t_d}{2}\right) - u\left(t - \frac{3t_d}{2}\right) \right] + V_0 \left(1 - e^{-(t-3t_d/2)/(z_0 C)} \right) u\left(t - \frac{3t_d}{2}\right)$$


$$\text{or } \frac{V_0}{2} u\left(t - \frac{t_d}{2}\right) + \frac{V_0}{2} u\left(t - \frac{3t_d}{2}\right) - V_0 e^{-(t-3t_d/2)/(z_0 C)} u\left(t - \frac{3t_d}{2}\right)$$

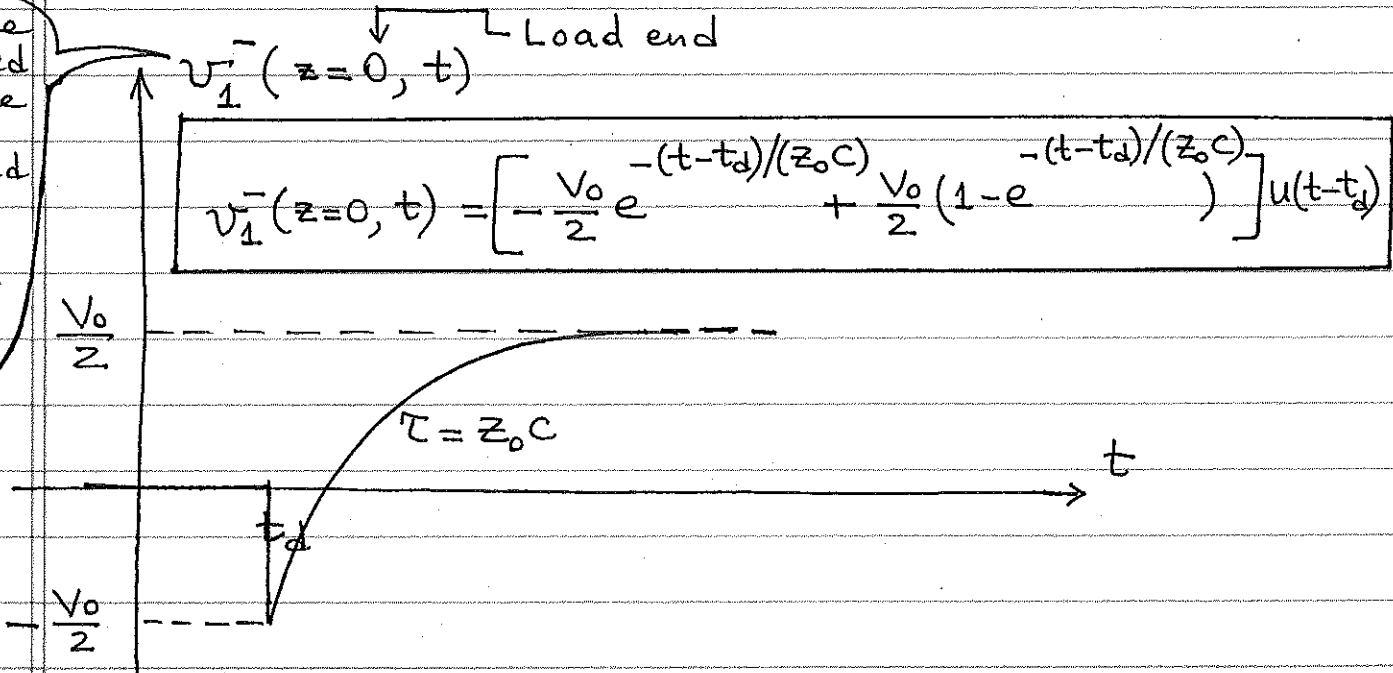I'm the reflected voltage wave observed at the load end of the line?




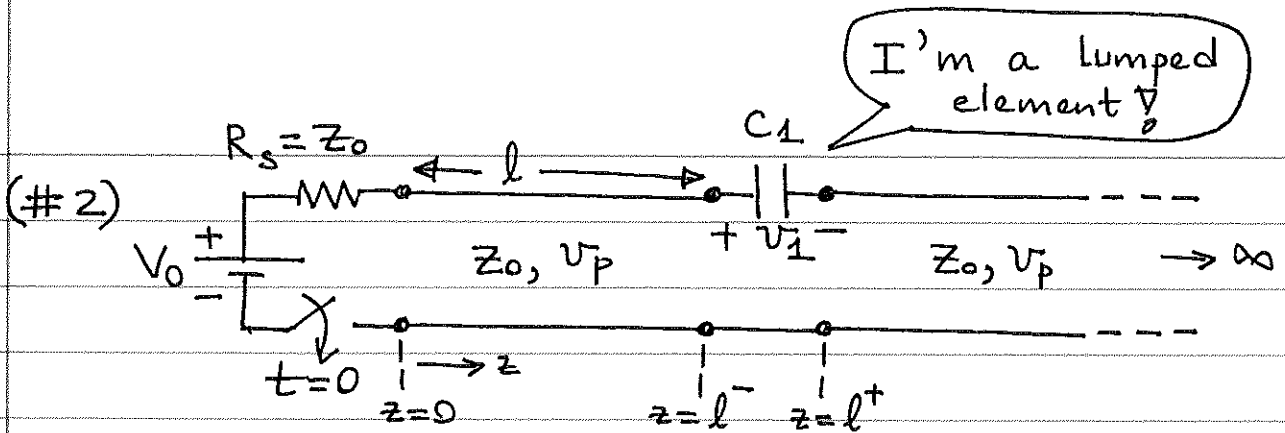

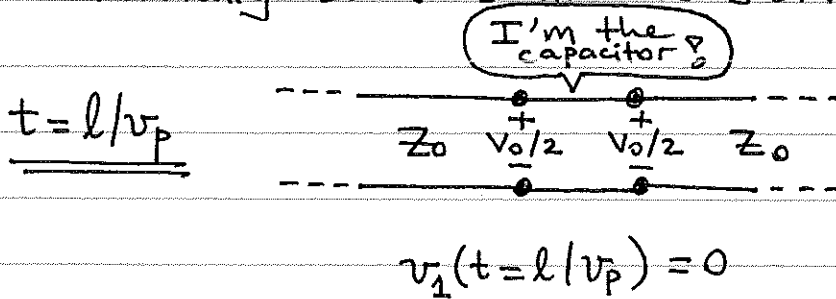
(a) At $t = l/v_p$, $\Gamma_L(t = l/v_p) = 0$ since the capacitor initially behaves like a short circuit.



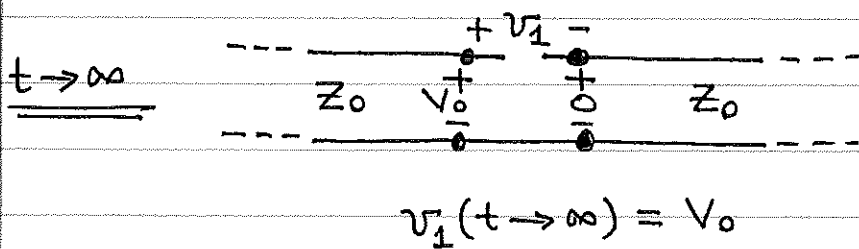
At $t \rightarrow \infty$, $\Gamma_L(t \rightarrow \infty) = +1$ since the capacitor behaves like an open circuit at steady state.



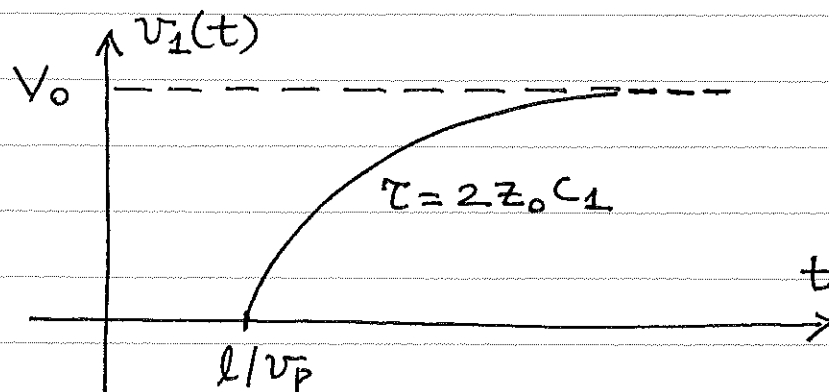
$$\therefore v_1(t) = V_0 \left(1 - e^{-\frac{(t - l/v_p)}{2Z_0 C_1}} \right) u(t - l/v_p)$$




(b) $t_1 = l/(2v_p)$

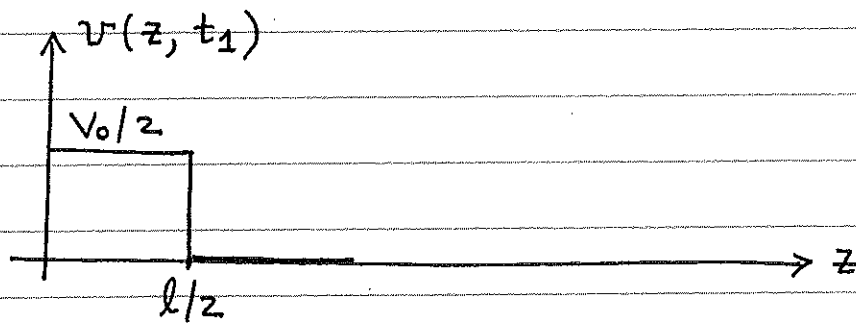

$t_2 = 3l/(2v_p)$

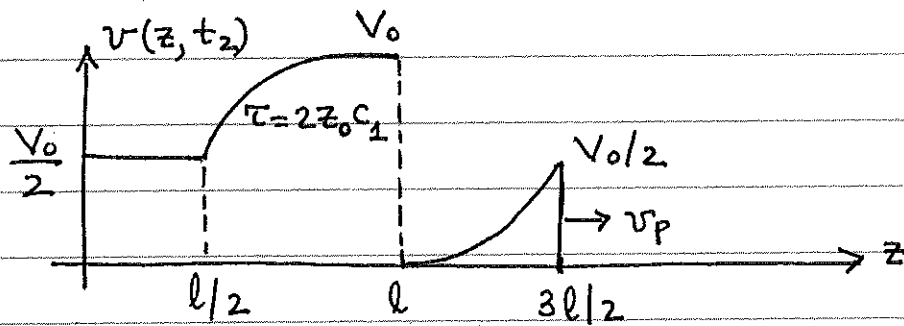


$t_3 = 2l/v_p$

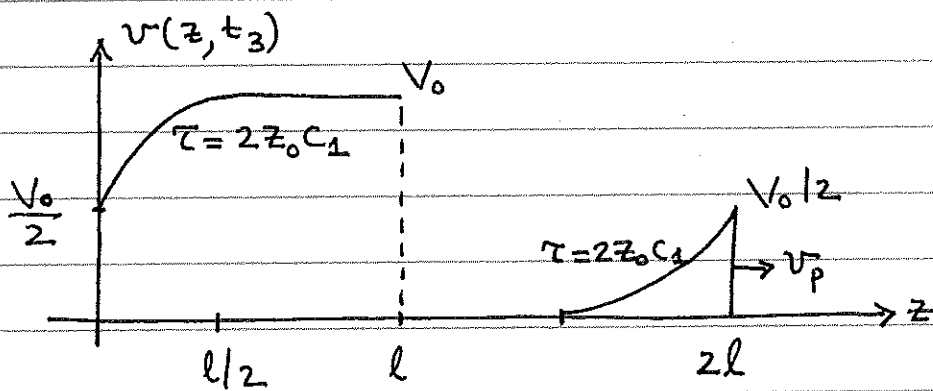


(c)

$$v(z = l/2, t) = v_c(t)$$

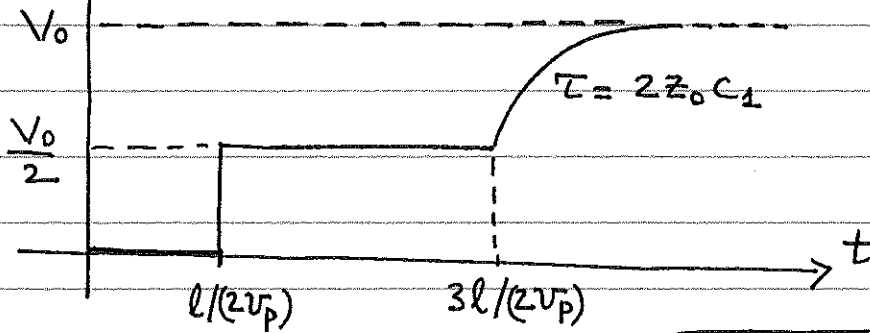


I'm the center voltage for the transmission line on the left side?

$$v(z = l, t) = v_L(t)$$

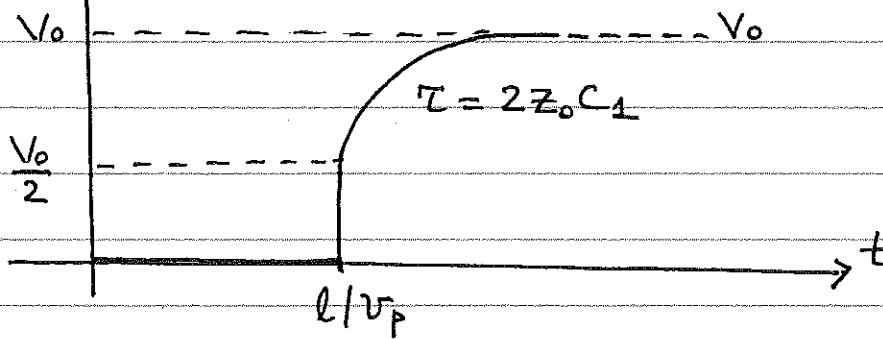

I'm the load-end voltage for the line on the left side?

$$v(z = 3l/2, t)$$

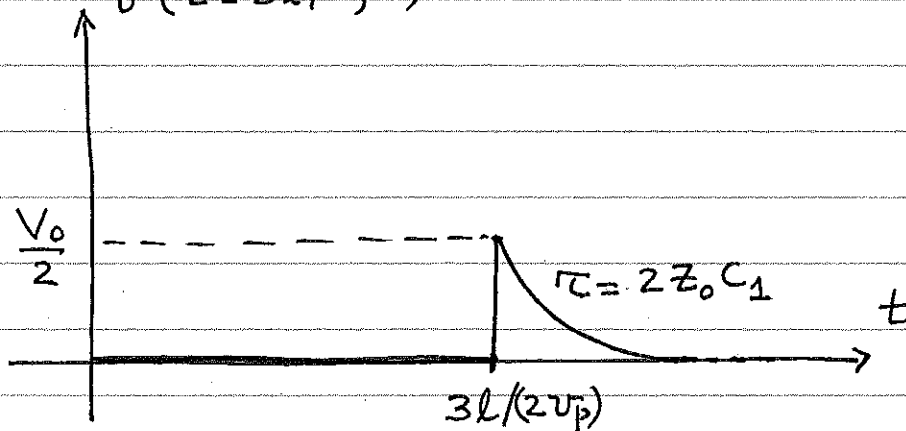

(#3) The complete mathematical expressions for the TDR waveforms shown in Figure 2.34 (Inan & Inan, page 80) are as follows:

$$v_{s1}^-(t) = u(t) + \frac{R}{R+2Z_0} u(t-2t_d)$$

$$v_{s2}^-(t) = u(t) - \frac{Z_0}{2R+Z_0} u(t-2t_d)$$

$$v_{s3}^-(t) = u(t) + e^{-(t-2t_d)2Z_0/L} u(t-2t_d)$$

$$v_{s4}^-(t) = u(t) - \left(1 - e^{-(t-2t_d)Z_0/(2L)}\right) u(t-2t_d)$$

$$v_{s5}^-(t) = u(t) + \left(1 - e^{-(t-2t_d)/(2Z_0c)}\right) u(t-2t_d)$$

$$\begin{aligned} v_{s6}^-(t) &= u(t) - u(t-2t_d) + \left(1 - e^{-2(t-2t_d)/(Z_0c)}\right) u(t-2t_d) \\ &= u(t) - e^{-2(t-2t_d)/(Z_0c)} u(t-2t_d) \end{aligned}$$

(Note that for all of these waveforms, v_1^+ approaching from the left-hand-side is assumed to be 1V.)