

SOLUTIONS TO HOMEWORK #5

$$\begin{aligned}
 (1) \quad (a) \quad \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{70 + j10 - 50}{70 + j10 + 50} = \frac{20 + j10}{120 + j10} \\
 &= \frac{2 + j}{12 + j} \times \frac{12 - j}{12 - j} = \frac{25 + j10}{(12)^2 + 1^2} = \frac{5 + j2}{29} \\
 &= \frac{\sqrt{5^2 + 2^2}}{29} e^{j \tan^{-1}(2/5)} = \frac{1}{\sqrt{29}} e^{j \tan^{-1}(0.4)} \\
 &\approx \boxed{0.1857 e^{j 21.8^\circ}}
 \end{aligned}$$

$$\begin{aligned}
 (b) \quad S &= \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 1/\sqrt{29}}{1 - 1/\sqrt{29}} = \frac{\sqrt{29} + 1}{\sqrt{29} - 1} \\
 &\approx \boxed{1.456}
 \end{aligned}$$

$$(c) \quad \phi_L + 2\beta z_{\max_1} = 0$$

$$\lambda_{\text{air}} = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{50 \times 10^6 \text{ Hz}} = 6 \text{ m}$$

$$(21.8^\circ) \frac{\pi}{180^\circ} + \frac{4\pi}{6} z_{\max_1} = 0 \rightarrow z_{\max_1} \approx \boxed{-0.5708 \text{ (m)}}$$

$$z_{\min_1} = z_{\max_1} - \frac{\lambda_{\text{air}}}{4} = -0.5708 - 1.5 = \boxed{-2.0708 \text{ (m)}}$$

$$z_{\max_2} = z_{\max_1} - \frac{\lambda_{\text{air}}}{2} = \boxed{-3.5708 \text{ (m)}}$$

$$z_{\min_2} = z_{\min_1} - \frac{\lambda_{\text{air}}}{2} = \boxed{-5.0708 \text{ (m)}}$$

$$z_{\max_3} = z_{\max_2} - \frac{\lambda_{\text{air}}}{2} = \boxed{-6.5708 \text{ (m)}}$$

$$z_{\min_3} = z_{\min_2} - \frac{\lambda_{\text{air}}}{2} = \boxed{-8.0708 \text{ (m)}}$$

$$z_{\max_4} = z_{\max_3} - \frac{\lambda_{\text{air}}}{2} = \boxed{-9.5708 \text{ (m)}}$$

$z_{\max} \text{ (m)}$	$z_{\min} \text{ (m)}$
-0.5708	-2.0708
-3.5708	-5.0708
-6.5708	-8.0708
-9.5708	

So all together, there are four V_{\max} and three V_{\min} positions on the transmission line.

(d) The input impedances at both V_{\max} and V_{\min} positions are real (purely resistive). The input impedance at each V_{\max} position is given by

$$z_{\text{in}} \Big|_{V_{\max}} = S z_0 \approx (1.456)(50) \approx \boxed{72.804 \text{ } (\Omega)}$$

The input impedance at each V_{\min} position is given by


$$z_{\text{in}} \Big|_{V_{\min}} = \frac{z_0}{S} \approx \frac{50}{1.456} \approx \boxed{34.34 \text{ } (\Omega)}$$

(e) Since the electrical length of the transmission line is given by

$$\frac{l}{\lambda_{air}} = \frac{10.5m}{6m} = 1.75$$

The input impedance of this line can be calculated as
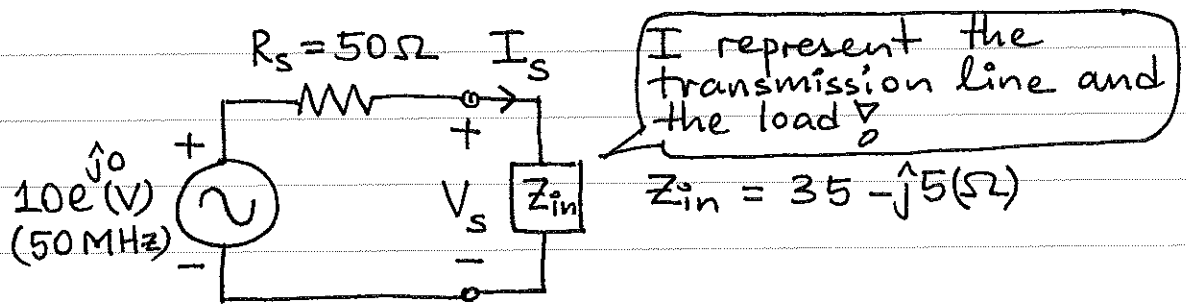
$$\begin{aligned} Z_{in} &= \frac{Z_0^2}{Z_L} = \frac{50^2}{70 + j10} \times \frac{70 - j10}{70 - j10} \\ &= \frac{(50)^2 (70 - j10)}{(70)^2 + (10)^2} = \boxed{35 - j5(\Omega)} \end{aligned}$$



(f) Using VDP:

$$\begin{aligned} V_s &= \frac{Z_{in}}{R_s + Z_{in}} (10e^{j0}) = \frac{35 - j5}{85 - j5} (10) \\ &= \frac{70 - j10}{17 - j} \times \frac{17 + j}{17 + j} = \frac{1200 - j100}{(17)^2 + 1^2} \\ &= \frac{10}{29} (12 - j) \cong \boxed{4.152 e^{-j4.764^\circ} (V)} \end{aligned}$$

Using $V^+ = \frac{V_s}{e^{j\beta l} (1 + \Gamma_L e^{-j2\beta l})}$

we have

$$\begin{aligned}
 V^+ &= \frac{4.152 e^{-j4.764^\circ}}{e^{j\frac{7\pi}{2}} (1 + 0.1857 e^{j21.8^\circ} \underbrace{e^{-j7\pi}}_{-1})} \\
 &\approx \frac{4.152 e^{-j4.764^\circ}}{j(1 - 0.1724 - j0.06897)} \\
 &= \frac{4.152 e^{-j4.764^\circ}}{0.06897 + j0.8276} \\
 &\approx \frac{4.152 e^{-j4.764^\circ}}{0.83045 e^{j85.24^\circ}} \\
 &\approx \boxed{5.00 e^{-j90^\circ} \text{ (V)}}
 \end{aligned}$$

$$\begin{aligned}
 V^- &= \Gamma_L V^+ \approx (0.1857 e^{j21.8^\circ}) (5 e^{-j90^\circ}) \\
 &\approx \boxed{0.9285 e^{-j68.2^\circ} \text{ (V)}}
 \end{aligned}$$

$$\begin{aligned}
 V_L &= V^+ + V^- \cong 5e^{-j90^\circ} + 0.9285e^{-j68.2^\circ} \\
 &\cong -j5 + 0.3448 - j0.8621 \\
 &\cong \boxed{5.872e^{-j86.63^\circ} \text{ (V)}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(g)} \quad V_{\max} &= |V^+| (1 + |\Gamma|) \cong 5(1 + 0.1857) \\
 &\cong \boxed{5.9285 \text{ (V)}}
 \end{aligned}$$

$$\begin{aligned}
 V_{\min} &= |V^+| (1 - |\Gamma|) \cong 5(1 - 0.1857) \\
 &\cong \boxed{4.0715 \text{ (V)}}
 \end{aligned}$$

$$\text{(h)} \quad P^+ = \frac{|V^+|^2}{2Z_0} \cong \frac{5^2}{2 \times 50} = \boxed{0.25 \text{ (W)}}$$

$$\begin{aligned}
 P^- &= \frac{|V^-|^2}{2Z_0} = |\Gamma|^2 P^+ \cong (0.1857)^2 (0.25) \\
 &\cong \boxed{8.621 \text{ (mW)}}
 \end{aligned}$$

From the equivalent circuit, we have

$$\begin{aligned}
 I_s &= \frac{10e^{j0}}{R_s + Z_{in}} = \frac{10}{\underbrace{50 + 35 - j5}_{85 - j5}} = \frac{2}{17 - j} \\
 &= \frac{2(17 + j)}{(17)^2 + 1^2} = \frac{17 + j}{145} \cong 0.1174e^{j3.3665^\circ} \text{ (A)}
 \end{aligned}$$

$$P_{R_s} = \frac{1}{2} |I_s|^2 R_s \cong \frac{1}{2} (0.1174)^2 (50) \\ \cong \boxed{0.3448 \text{ (W)}}$$

$$P_L = P_{z_{in}} = \frac{1}{2} |I_s|^2 R_{in} \cong \frac{1}{2} (0.1174)^2 (35) \\ \cong \boxed{0.2414 \text{ (W)}}$$

$$P_{\text{source}} = P_{R_s} + P_{z_{in}} \cong 0.3448 + 0.2414 \\ = \boxed{0.5862 \text{ (W)}}$$

% of incident ^{wave} power that reflects back to the source can be found as

$$|\Gamma_L|^2 \times 100 \cong (0.1857)^2 \times 100 \\ \cong \boxed{3.448 \%}$$