

University of Portland School of Engineering


EE 301
Spring 2013
A.Inan

Homework # 2 Distributed-Circuit Parameters of Simple Transmission-Line (TL) Structures & Digital Signal Propagation on Lossless TLs

(Copyright by A. S. Inan)
(Assigned: Monday, January 28, 2013)
(Due: Wednesday, February 6, 2013, 11:25a.m.)

(1) A resistively terminated transmission line. Consider the transmission-line circuit excited by an ideal step voltage source as shown. Assuming lossless transmission line and using a bounce diagram, determine the values of the source-end and load-end voltages v_s and v_L and the source-end and the load-end currents i_s and i_L at the following times:

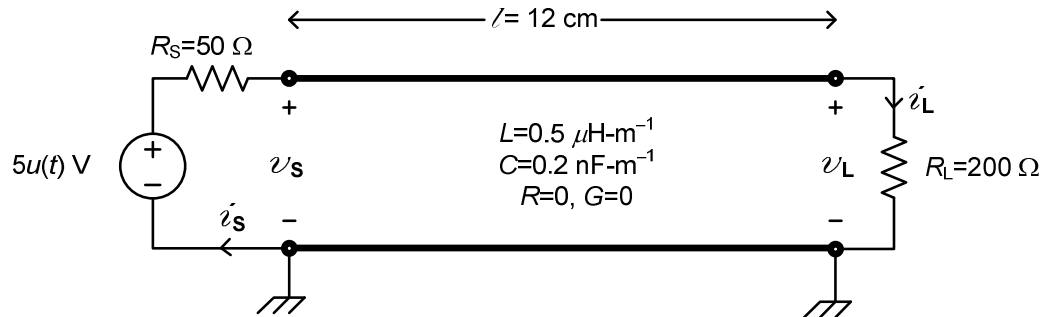- (a) $t_1 = 1$ ns.
- (b) $t_1 = 2$ ns.
- (c) $t_1 = 3$ ns.




Provide all of your answers in a table form. A sample table could be of the form given by

t (ns)	v_s (V)	v_L (V)	i_s (mA)	i_L (mA)
1				
2				
3				


(2) Transient response of a cascaded transmission-line circuit. Consider the circuit consisting of two cascaded lossless transmission lines each with characteristic impedance and one-way time delay provided as shown. Assuming both lines to be uncharged before $t = 0$, sketch the source-end, junction and load-end voltages v_s , v_J , and v_L as a function of time for the following three cases:

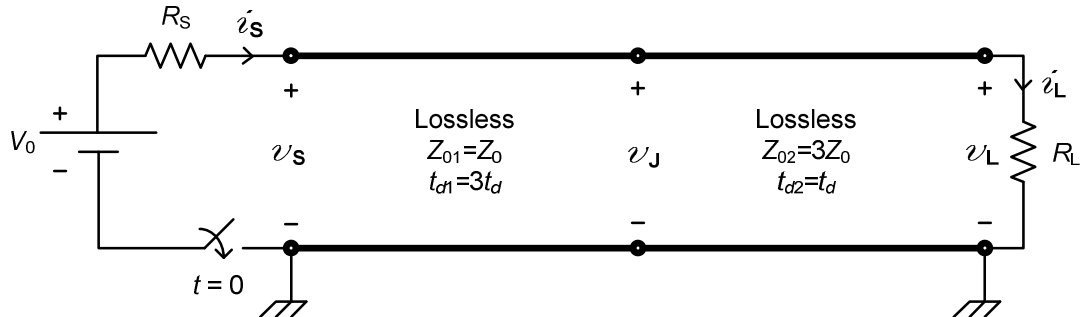- (a) $R_S = Z_0$ and $R_L = 3Z_0$.
 (b) $R_S = Z_0$ and $R_L = Z_0$.
 (c) $R_S = Z_0/3$ and $R_L = 3Z_0$.




For each case, provide a complete bounce diagram. Sketch each voltage waveform only over the time interval $0 < t < 9t_d$. Note that in your sketches, your voltage values will be in terms of V_0 and your time axis will be in terms of t_d .

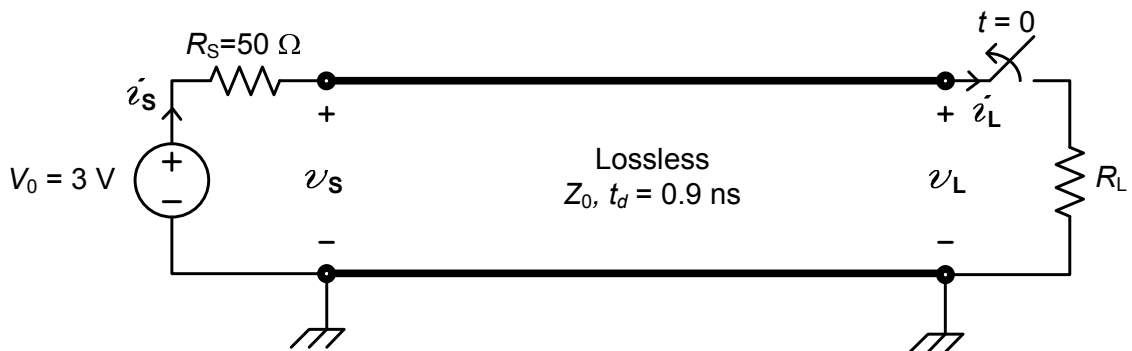(3) A resistively terminated transmission line. Consider the transmission line circuit terminated with a resistive load as shown. If the switch at the load end opens at $t = 0$ after being closed for a long time, calculate and fill out the source-end and load-end voltage values in the table provided below. Provide a bounce diagram in each case to justify your voltage values.




Z_0 (Ω)	R_L (Ω)	t (ns)	v_s (V)	v_L (V)
50	50	0^+		
50	50	1		
50	50	2		
50	0	0^+		
50	0	1		
150	0	1		
150	0	2		

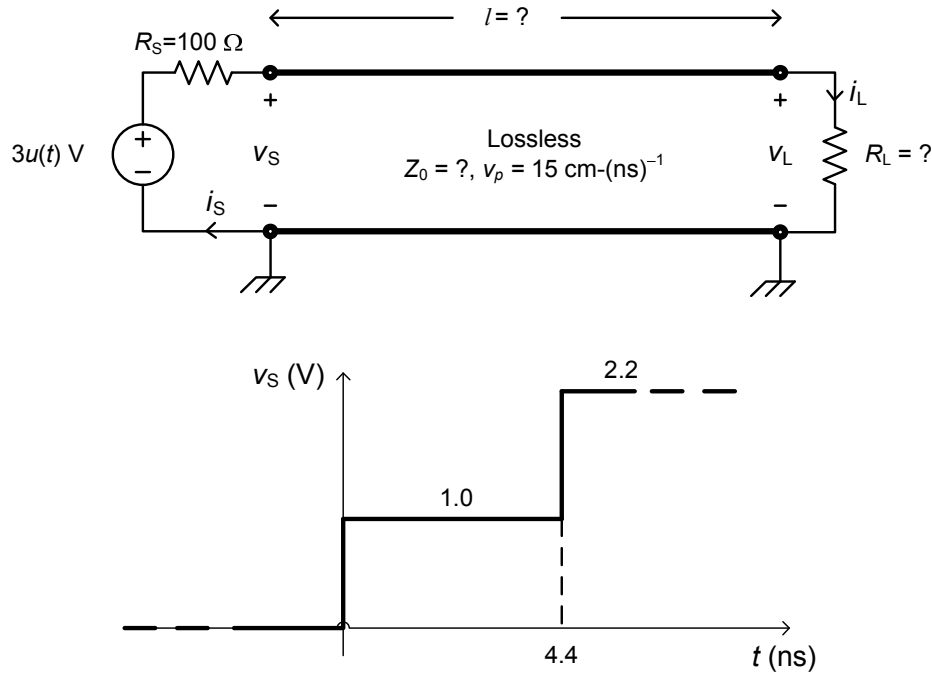
- (4) **Characterizing a transmission-line circuit using a TDR waveform.** Consider the transmission-line circuit below. At $t = 0$, the circuit is excited by an ideal step voltage source of 3 V peak value. Using the source-end voltage waveform v_s observed on a TDR display as shown, determine the characteristic impedance and the length of the line, Z_0 and l , and the unknown load resistor, R_L . Show your work step-by-step.



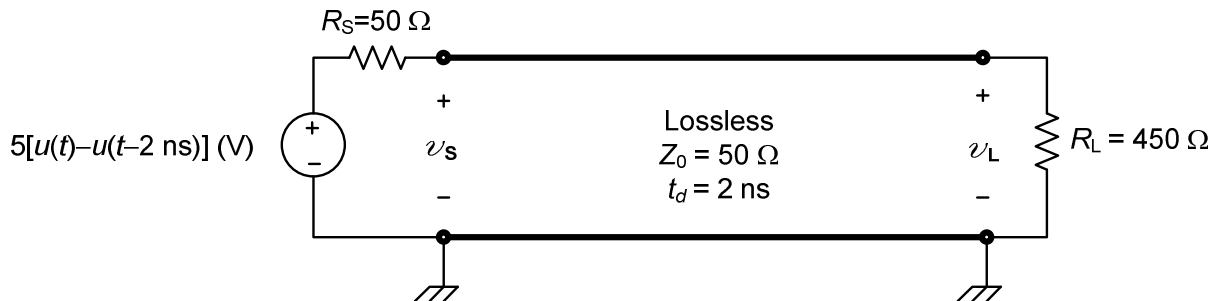- (5) **A pulse excited transmission line.** Consider the transmission-line circuit excited by a voltage pulse with 5 V peak value and 2 ns duration, as shown. Using a bounce diagram, find and sketch the source-end and load-end voltages v_s and v_L as a function of time up to $t = 9$ ns.



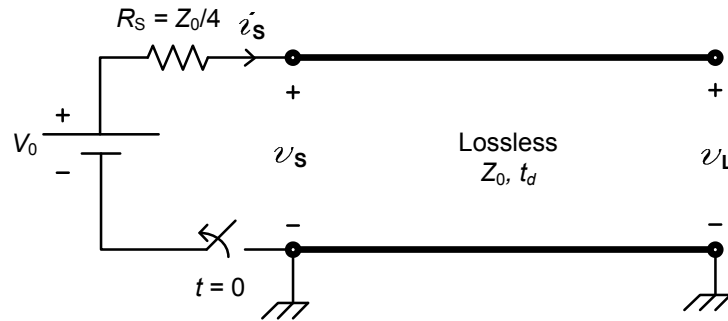- (6) **An open-circuit terminated transmission line excited by a dc voltage source.** Consider a lossless open-circuit terminated transmission line excited by a dc voltage source with voltage V_0 as shown. At $t = 0$, the switch opens. Assuming steady-state condition to apply at $t = 0^-$, complete the values of the source-end and load-end voltages v_s and v_L in terms of the dc voltage V_0 in the table provided below. Provide a bounce diagram to justify your values.



t/t_d	v_s/V_0	v_L/V_0
0.5		
1.5		
2.5		

Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #2-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 301/Spring 2013 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.