

# University of Portland School of Engineering

EE 301  
Spring 2013  
A.Inan

## Homework # 4

(Monday, February 25, 2013)


### Sinusoidal Steady-State (SSS) Waves on Transmission Lines

(Due Monday, March 4, 2013, 11:25a.m.)


(1) **Electrical length of transmission lines.** Find the electrical lengths of the following transmission lines:

- (a) 100-kilometer long air transmission line at 60 Hz;
- (b) 100-meter long coaxial line with a velocity factor of 0.67 at 300 MHz.

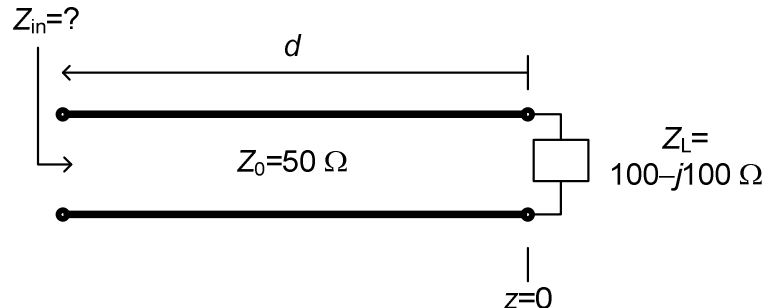
(2) **Load reflection coefficient, standing wave ratio, and input impedance.** A  $50\ \Omega$  transmission line is terminated with a capacitive load having a load impedance of  $Z_L = 100 - j100\ \Omega$ , as shown. (a) Find the load reflection coefficient, i.e.,  $\Gamma_L$ . (b) Find the standing wave ratio  $S$  on the line. (c) Find the input impedance of the line,  $Z_{in}$ , for four different line lengths:  $d_1 = 0.125\lambda$ ,  $d_2 = 0.25\lambda$ ,  $d_3 = 0.375\lambda$ , and  $d_4 = 0.5\lambda$ , respectively.



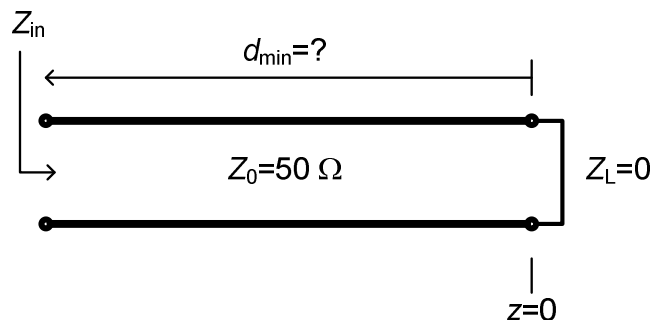
(3) **Input impedance of a transmission line.** Consider a short-circuited  $50\ \Omega$  transmission line (a short-circuited stub) as shown. Find the shortest electrical length of the line such that (a)  $Z_{in} = j50\ \Omega$ ; (b)  $Z_{in} = -j150\ \Omega$ ; (c)  $Z_{in} = \infty$ , and (d)  $Z_{in} = 0$ .



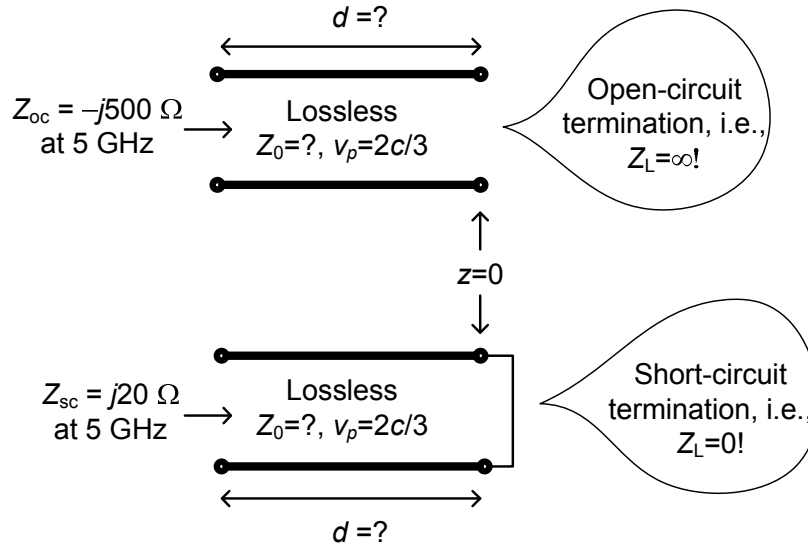
- (4) **Open- and short-circuit impedance measurements.** If the open- and short-circuit terminated input impedances of a lossless transmission line with characteristic impedance  $Z_0$ , length  $d$  and phase velocity  $v_p = 2c/3$  are measured at 5 GHz to be  $Z_{oc} = -j500 \Omega$  and  $Z_{sc} = j20 \Omega$  respectively, calculate  $Z_0$  and the length  $d$  of this line. (Note that  $c = 3 \times 10^8$  m/s.)




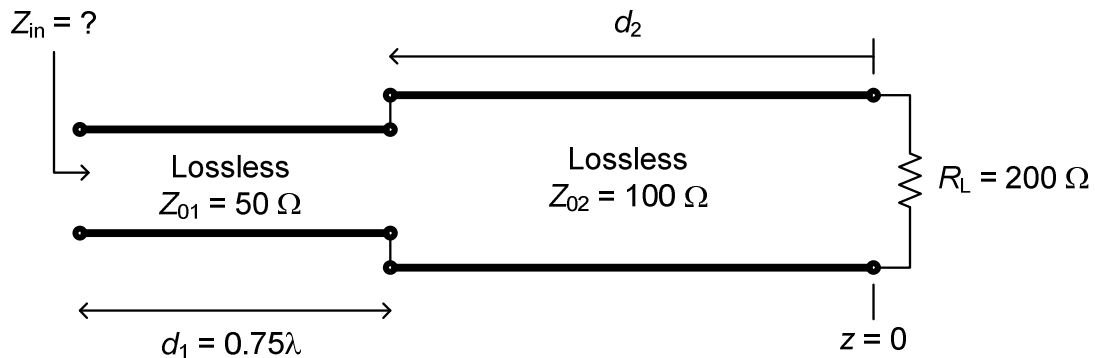
- (5) **Input impedance.** Find the input impedance  $Z_{in}$  of the transmission line system shown for (a)  $d_2 = 0.25\lambda$ ; (b)  $d_2 = 0.5\lambda$ ; and (c)  $d_2 = 0.125\lambda$ .



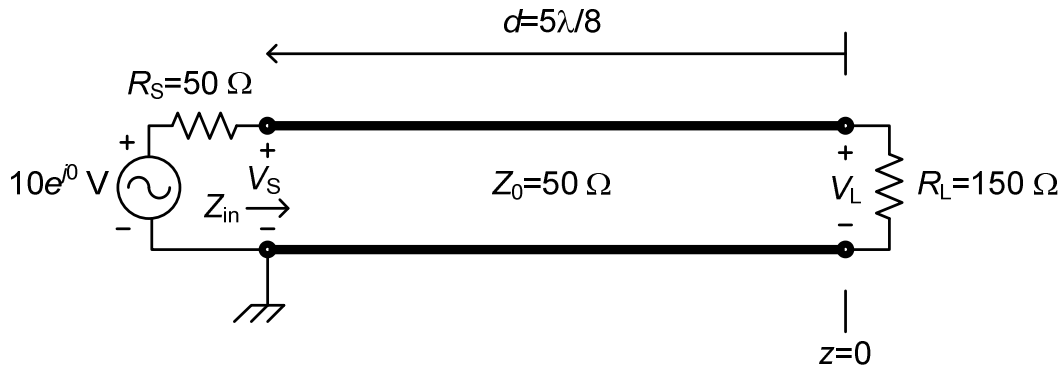- (6) **Source- and load-end voltages.** For the transmission line shown, assuming sinusoidal steady state, calculate the source-end and load-end voltages  $V_S$  and  $V_L$  in phasor form.



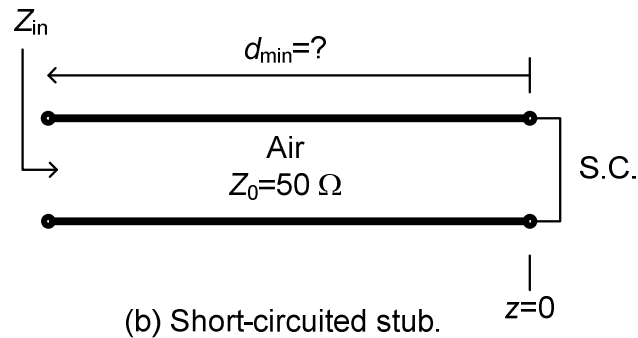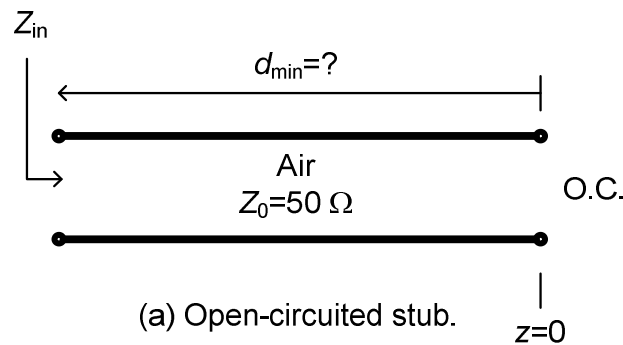- (7) **Designing a capacitor using a stub.** Capacitive and inductive circuit elements can be designed using short-circuit or open-circuited stubs. The lengths of these stubs are typically short with respect to the associated wavelength. (a) Design an open-circuited  $50 \Omega$  air stub that will provide the impedance of a  $4 \text{ nF}$  capacitor at  $10 \text{ GHz}$ . Find the shortest length of the stub. (b) Redesign the capacitor in part (a) using a short-circuited  $50 \Omega$  air stub. (c) Which design yields the shortest length and why?



- (8) **Designing an inductor using a stub.** (a) Design an open-circuited  $50 \Omega$  microstrip transmission-line stub having an effective relative dielectric constant of  $\epsilon_r \cong 6$  that will provide the impedance of a  $5 \text{ nH}$  inductor at  $5 \text{ GHz}$ . Find the shortest length of the stub. (b) Repeat the same design using a short-circuited  $50 \Omega$  microstrip line stub having an effective relative dielectric constant of  $\epsilon_r \cong 6$ . (c) Which design resulted in a shorter stub and why?

Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #4-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 301/Spring 2013 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.

***An Important Reminder Note:***

**EE 301-Midterm # 2 is scheduled to be given on Friday, April 5, 2013**

(It will be in-class closed-book exam. Two formula sheets will be allowed.)