

**University of Portland**  
**School of Engineering**


EE 301  
Spring 2014  
A.Inan

**Introduction to Smith Chart—Practice Problems**  
(Monday, March 24, 2014)

1. **Impedance points on the Smith chart.** Given the impedance values  $Z_A = 500 \Omega$ ,  $Z_B = 20 - j75 \Omega$ ,  $Z_C = 80 + j50 \Omega$ ,  $Z_D = -j13 \Omega$ , and  $Z_E = 10 + j100 \Omega$ , enter each one of them on the Smith chart. (Use the Smith chart as an impedance chart and assume  $Z_0 = 50 \Omega$ .)
2. **Open- and short-circuit points on the Smith chart.** Show the open- and short-circuit points on the Smith chart if the Smith chart is used as an (a) impedance chart, and (b) admittance chart.
3. **Standing-wave-ratio circles on the Smith chart.** Draw the three constant standing-wave ratio circles with values  $S = 2, 4$  and  $10$  on the Smith chart. Then, use the reflection coefficient scale provided at the left bottom of the Smith chart to read the approximate value of each reflection coefficient magnitude corresponding to each one of these constant  $S$ -circles.
4. **Input impedance of a quarter-wavelength long (quarter-wave) transmission line.** Consider a quarter-wavelength long  $100\text{-}\Omega$  transmission line terminated with a load impedance of  $Z_L = 60 \Omega$ .
  - (a) Use the Smith chart to find the approximate value of the input impedance of this line.
  - (b) Assume the source wavelength is changed by a factor of  $2/3$ , i.e.,  $\lambda_{new} = 2\lambda_{old}/3$ . Again, use the Smith chart to find the approximate value of the input impedance of the same line. (Assume the  $Z_0$  and  $Z_L$  values to stay the same.)
5. **Converting impedance to admittance on the Smith chart.** Use the Smith chart to find the approximate value of the admittance corresponding to the impedance given by  $Z = 120 + j40 \Omega$ . (Use  $Z_0 = 100 \Omega$ .)

6. **Input admittance of a transmission line.** Consider a 6.5-m long, 50- $\Omega$  coaxial line terminated with a load impedance of 150  $\Omega$ .
- What is the standing-wave-ratio on this line? (Use the Smith chart to read this value.)
  - Using the Smith chart, find the approximate value of the input admittance  $Y_{in}$  of this line at a frequency of  $f = 250$  MHz. Assume the velocity factor of the coax to be  $v_p/c = 2/3$ .
7. **What nearest positions  $Z_{in}$  is purely resistive?** Consider a 50- $\Omega$  transmission line terminated with a load impedance of  $Z_L = 50 - j50 \Omega$ .
- Use the Smith chart to find the electrical position (i.e.,  $l/\lambda$ ) on the line which is nearest to the load where the input impedance is purely resistive.
  - What is the approximate value of  $Z_{in}$  at this position?
  - Find the second nearest position on the line where again  $Z_{in}$  is purely real and its value at that position.
8. **What nearest positions  $Z_{in} = Z_0 + j X_{in}$  ?** Consider a 50- $\Omega$  transmission line terminated with a load impedance of  $Z_L = 10 - j25 \Omega$ . Using the Smith chart, find the two nearest electrical positions away from the load where the real part of the input impedance is equal to  $Z_0$ . Provide the approximate value of  $Z_{in}$  at each one of these positions.
9. **Standing-wave-ratio.** Consider a 75- $\Omega$  transmission line terminated by a load impedance given by  $Z_L = j270 \Omega$ . Use the Smith chart to find the standing-wave ratio  $S$  on this line. Provide some explanation for your  $S$  value.
10. **Unknown load impedance.** The input impedance of a  $0.375\lambda$  long 50- $\Omega$  transmission line terminated with an unknown load is approximately measured to be  $Z_{in} \approx 20 \Omega$ . Use the Smith chart to find the approximate value of the unknown load impedance  $Z_L$ .
11. **A transmission line terminated with a complex load.** Consider a  $1.625\lambda$  long 90- $\Omega$  transmission line terminated with a load having an impedance of value  $Z_L = 72 - j270 \Omega$ . Use the Smith chart to find the approximate values of the following:
- The standing-wave-ratio value on the line.
  - The input impedance and the input admittance of the line.
12. **Region on the Smith chart.** Shade the region of the Smith chart where the real and imaginary parts of the impedance  $Z = R + jX$  satisfy  $Z_0/2 < R < 2Z_0$  and  $Z_0/2 < |X| < 2Z_0$  simultaneously.


Problem # 1

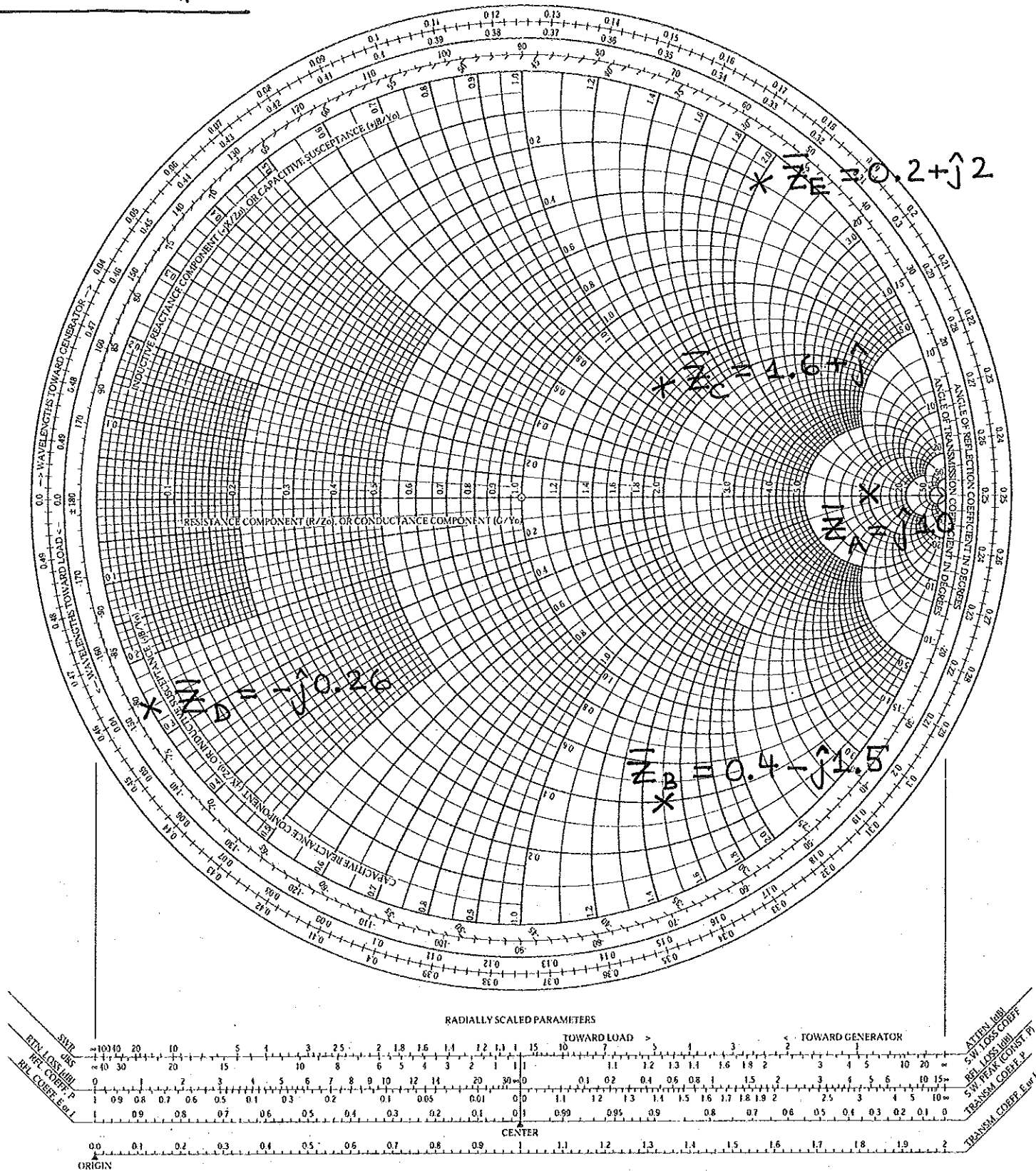


# The Complete Smith Chart

Black Magic Design

## Problem #2

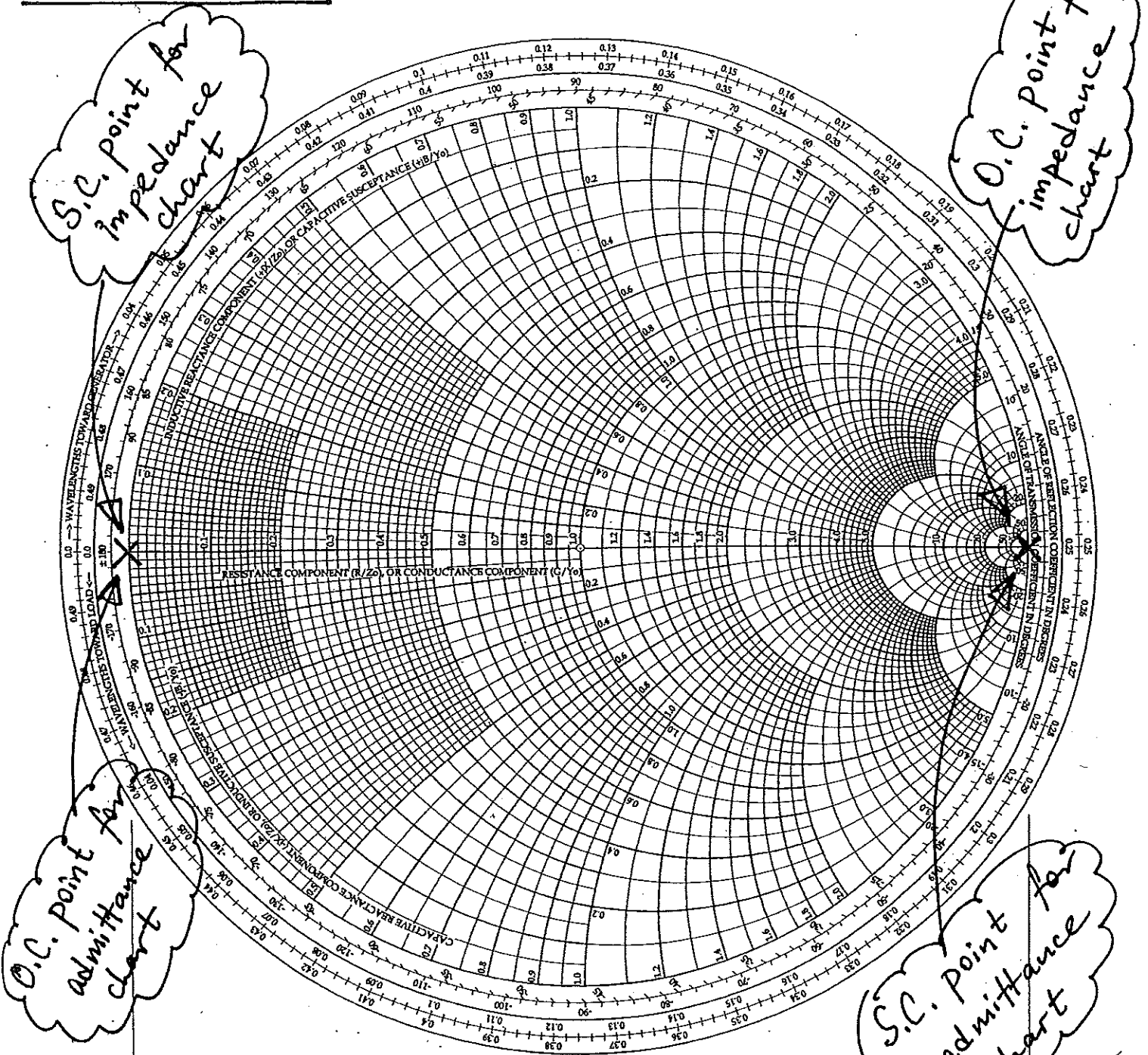

### RADIALLY SCALED PARAMETERS

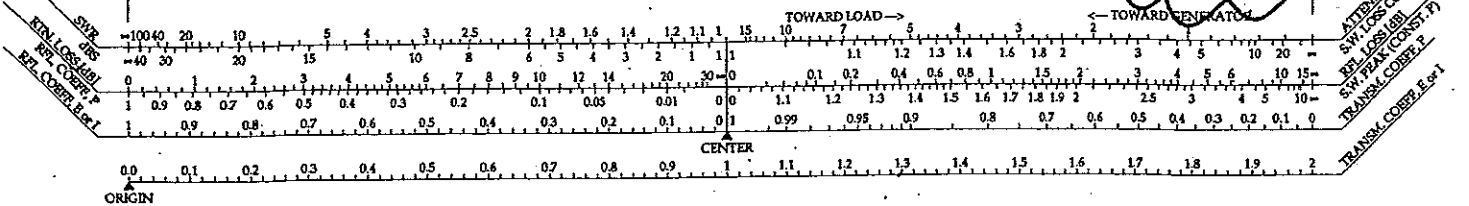


ATTEL LOSS  
SWR LOSS COEFF  
RETN LOSS (dB)  
RETN COEFF (P)  
TRANSM COEFF (P)

# The Complete Smith Chart

Black Magic Design

## Problem #3

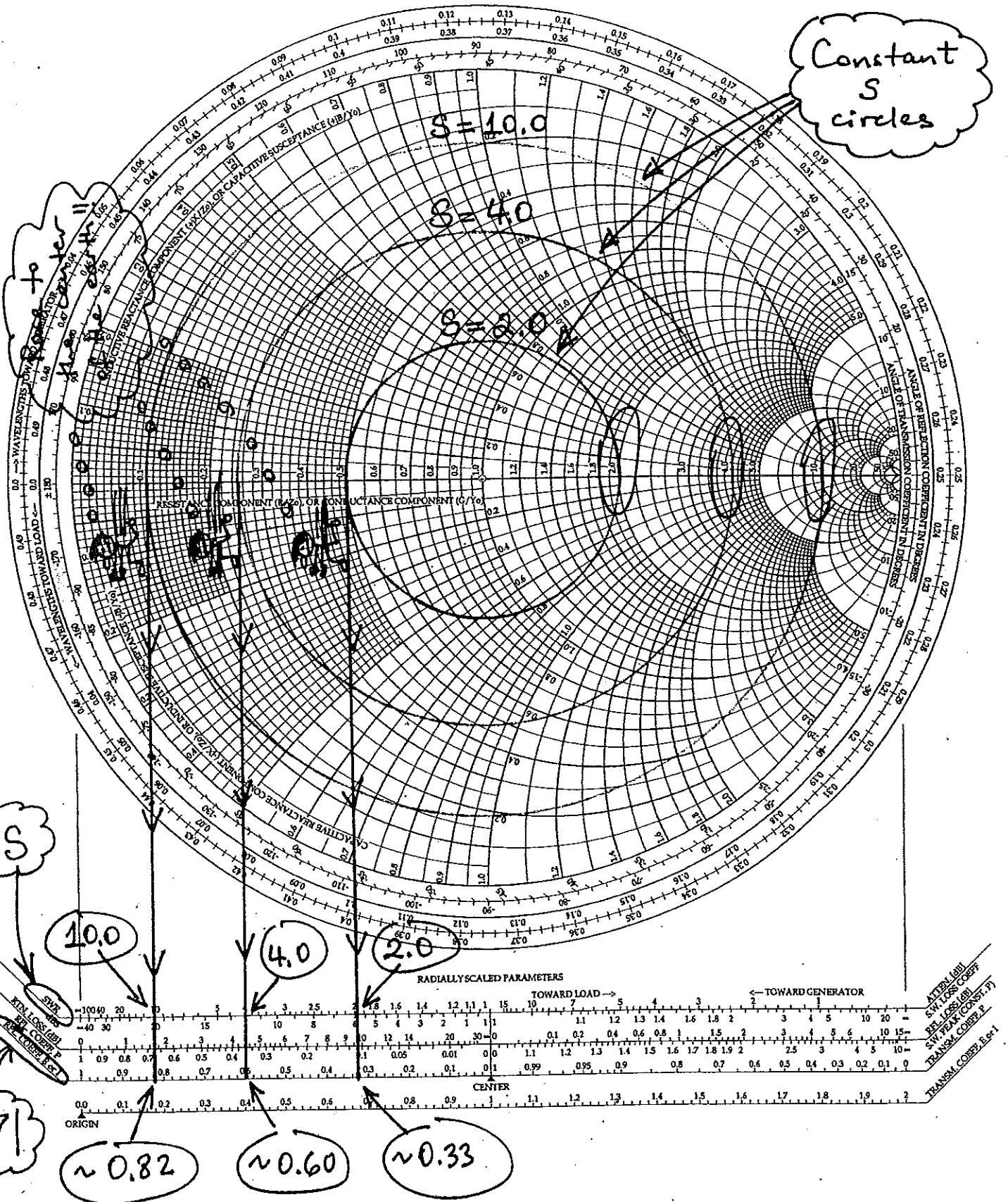


# The Complete Smith Chart

Black Magic Design

Problem #4

Part (a)

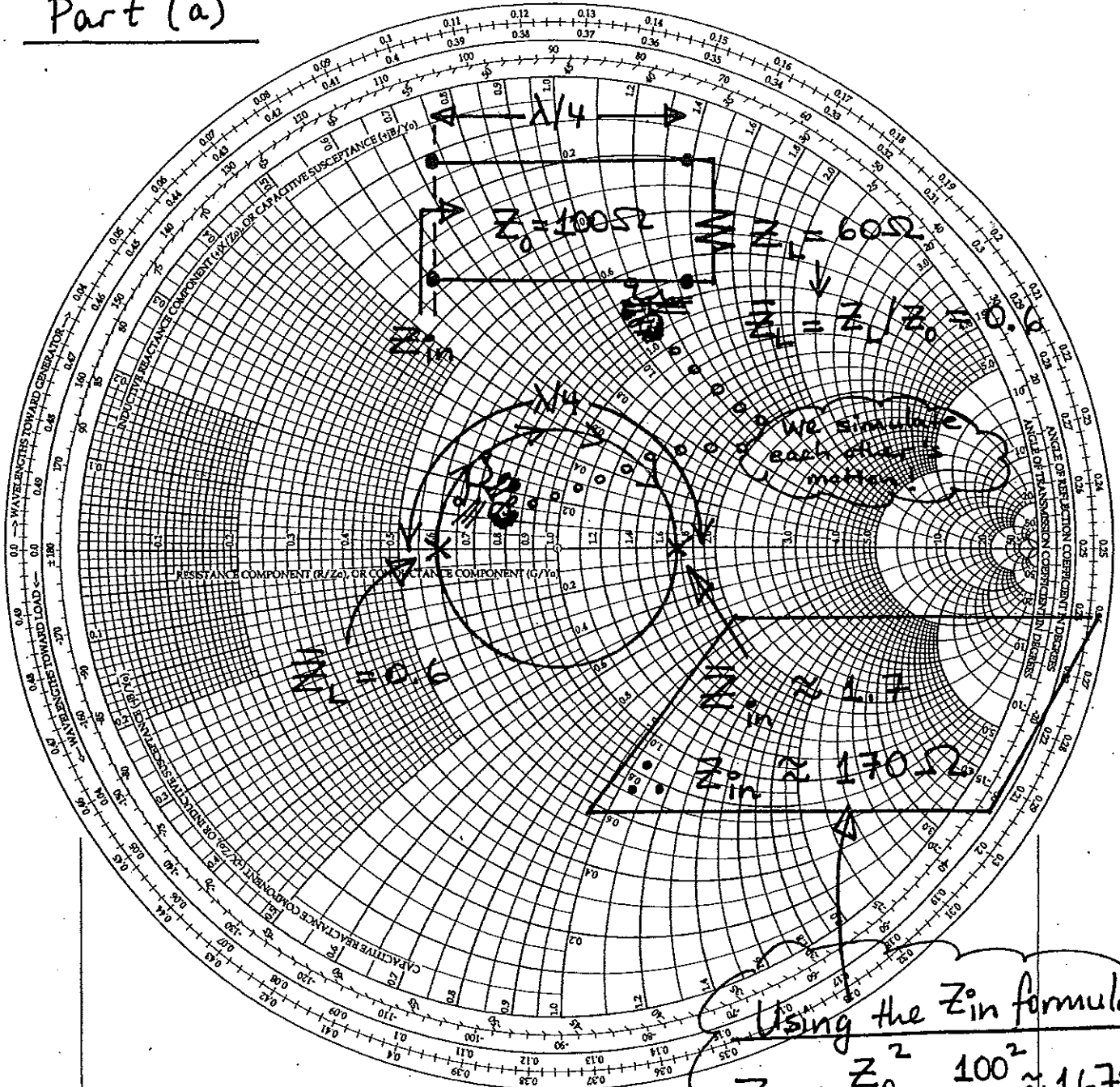

RADIALLY SCALED PARAMETERS

TOWARD LOAD →

← TOWARD GENERATOR

CENTER

ORIGIN

SWR  
VOLTAGE LOSS COEFF. P  
REFL. COEFF. V  
SWR LOSS COEFF. P  
SWR LOSS COEFF. P  
TRANSM. COEFF. P


# Problem #4

## The Complete Smith Chart

Black Magic Design
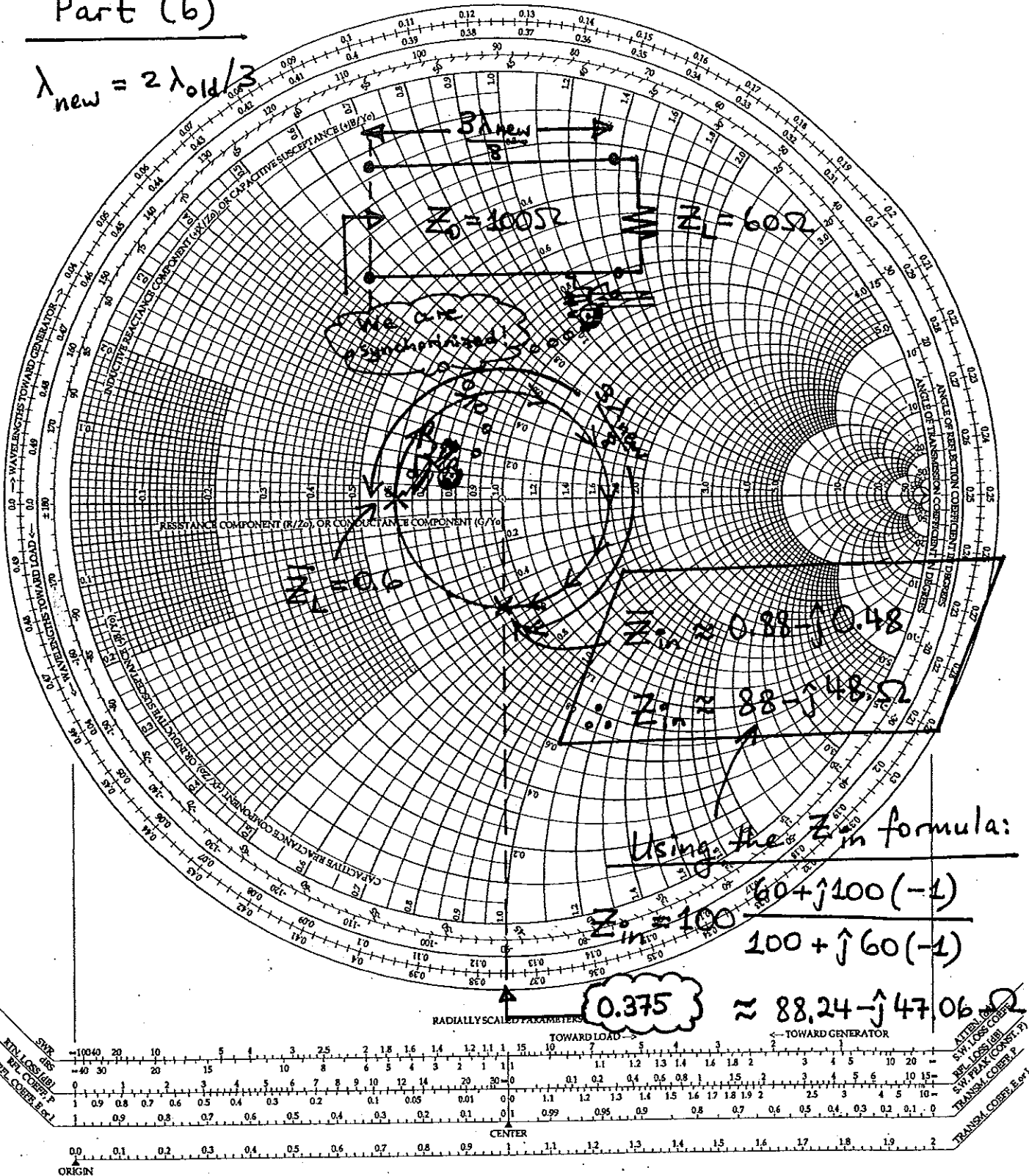
### Part (b)

$$\lambda_{\text{new}} = 2\lambda_{\text{old}}/3$$






# The Complete Smith Chart

## Black Magic Design

### Problem #5

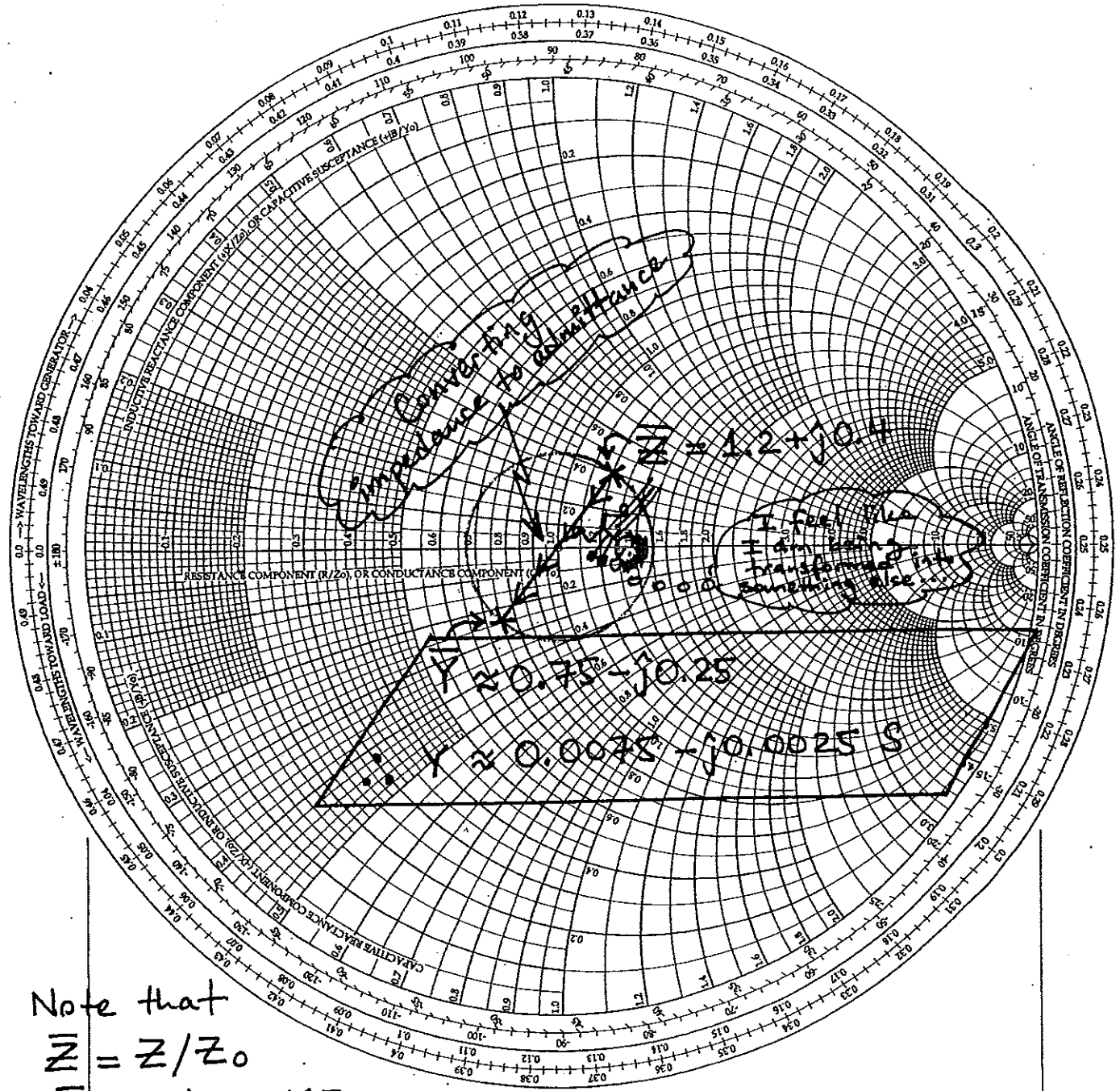

Note that


$$\bar{Z} = Z/Z_0$$

$$\bar{Y} = Y/Y_0 = Y Z_0$$

RADIALLY SCALED PARAMETERS

TOWARD LOAD →

← TOWARD GENERATOR

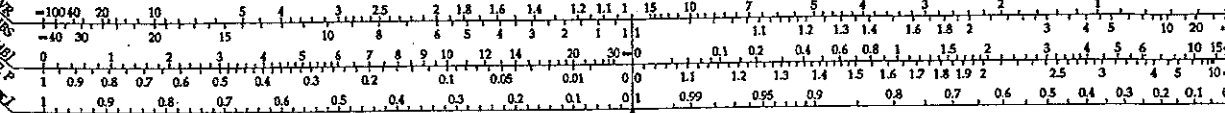

ATTEN (dB)  
SW LOSS COEFF  
REF LOSS COEFF  
SW PWR LOSS COEFF (1-Γ²)



# The Complete Smith Chart

Black Magic Design

## Problem #6

$$\lambda = \frac{v_p}{f} = \frac{(2c/3)}{f} \approx 0.8m$$

250 MHz

6.5m

$8.125\lambda$

$Z_0 = 50\Omega$

$R_L = 150\Omega$

$8.125\lambda = 0.125\lambda$

means 90° turn

$Z_{in} = 0.6 - j0.8$

$Z_{in} = 30 - j40\Omega$

0.25

0.375

RADIALLY SCALED PARAMETERS


TOWARD LOAD

TOWARD GENERATOR

CENTER

ORIGIN

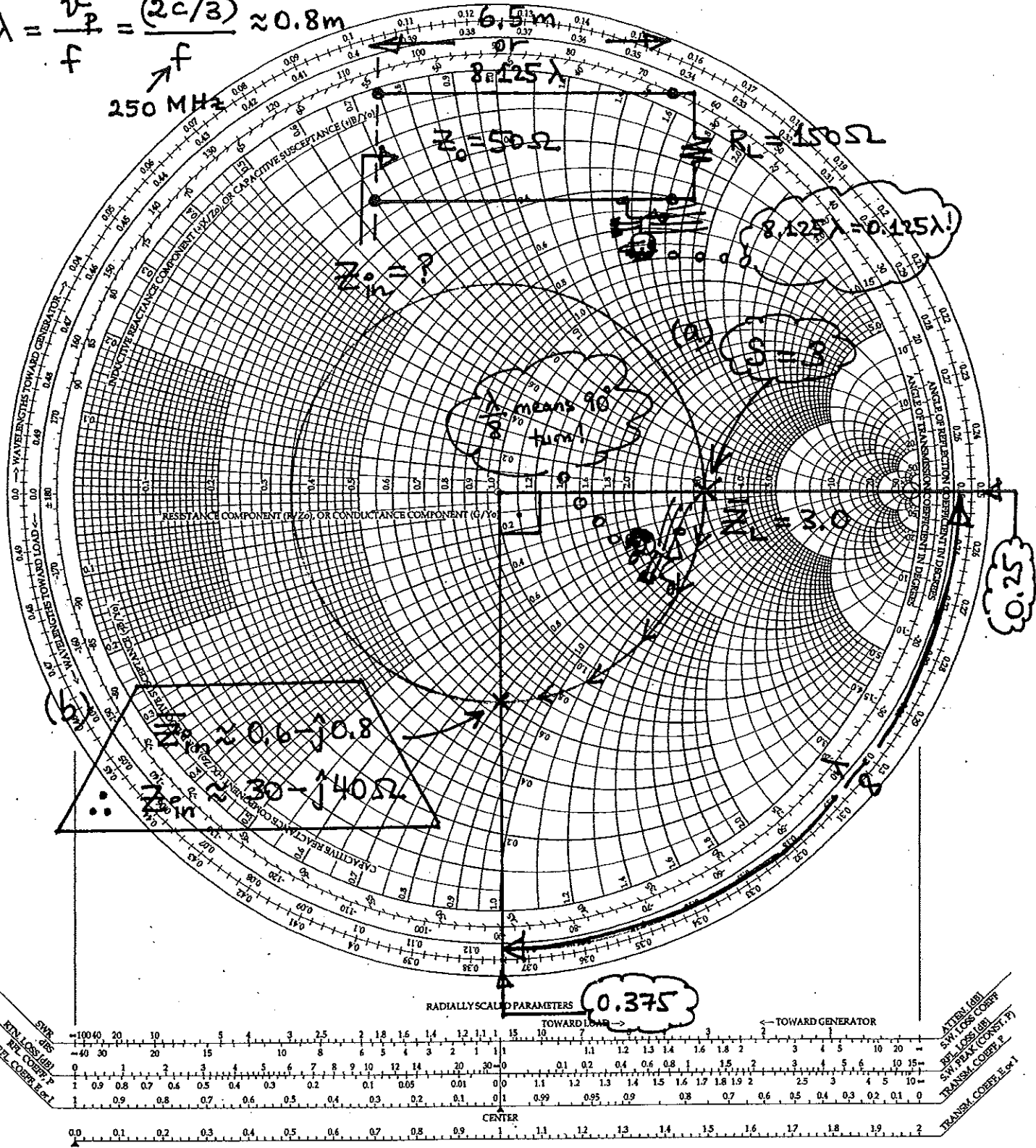ATTEN [dB]  
SWR LOSS COEFF  
REFL LOSS [dB]  
SWR PEAK COEFF P  
TRANSM COEFF P  
TRANSM COEFF P



# The Complete Smith Chart

Problem #7

Black Magic Design

$\sim 0.162\lambda$

$l=0$

Get set!  
Ready?  
Gooo!!

$\sim 0.412\lambda$




Where is the second nearest nearest position?

$Z_0 = 50\Omega$

$Z_L = 50 - j50\Omega$

$Z_{in} \approx 130\Omega$

$Z_{in} \approx 19.5\Omega$

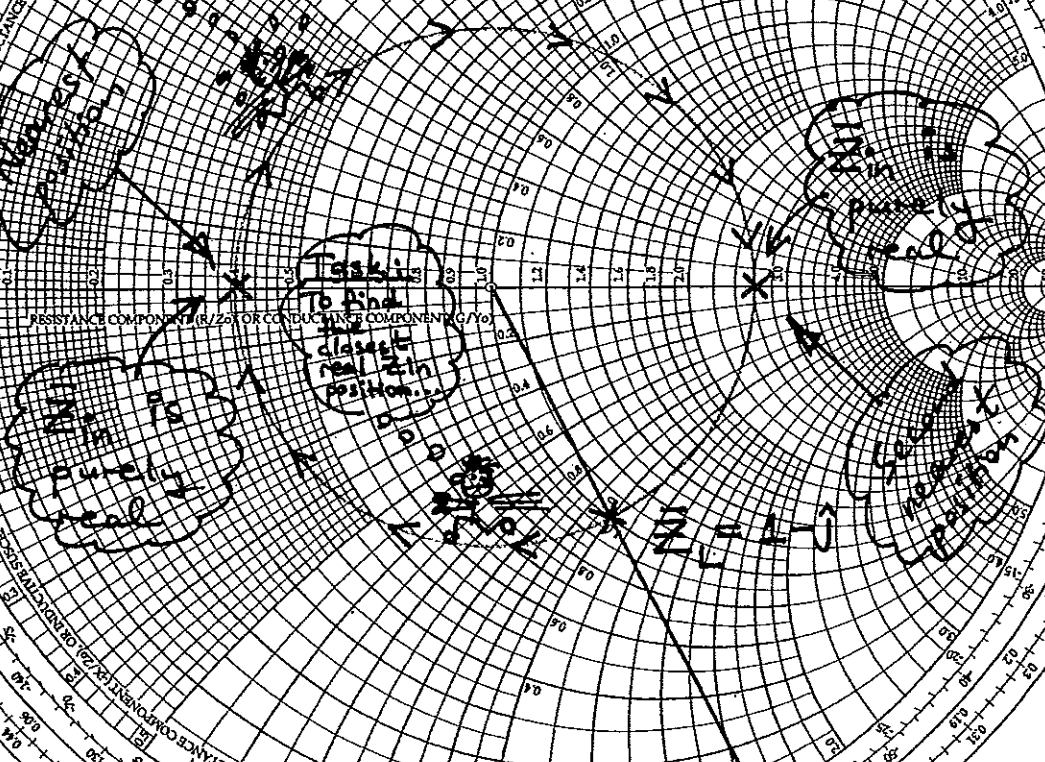


(a)  $l_{\text{nearest}} \approx (0.5 - 0.338)\lambda$

$\therefore l_{\text{nearest}} / \lambda \approx 0.162$

$0.338$

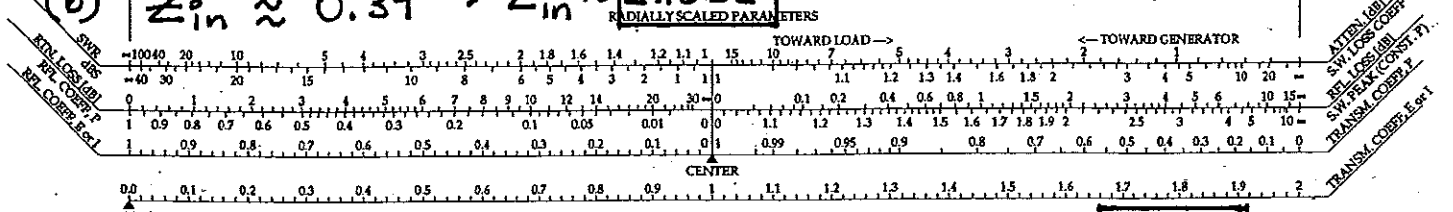(b)  $Z_{in} \approx 0.39 \rightarrow Z_0 \approx 19.5\Omega$




(c)  $l_{\text{second nearest}} \approx (0.162 + 0.25)\lambda \rightarrow \therefore l_{\text{second nearest}} / \lambda \approx 0.412$

$Z_{in} \approx 2.6 \rightarrow Z_{in} \approx 130\Omega$

# The Complete Smith Chart

## Problem #8

Black Magic Design

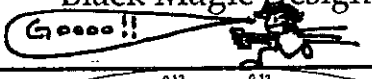

$$Z_L = 10 - j25 \Omega$$

$$Z_0 = 50 \Omega$$

~0.19



Perseverance  
determination  
persistence  
firmness

Nearest

Minor and  
major axis  
position  
resistance  
reactance


Approach  
Success  
Determination

Second  
nearest

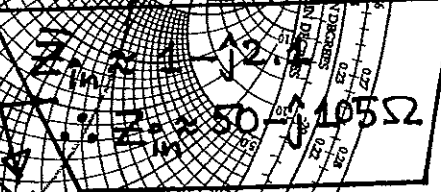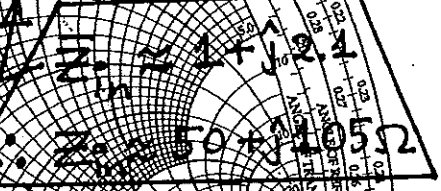

~0.311

~0.424

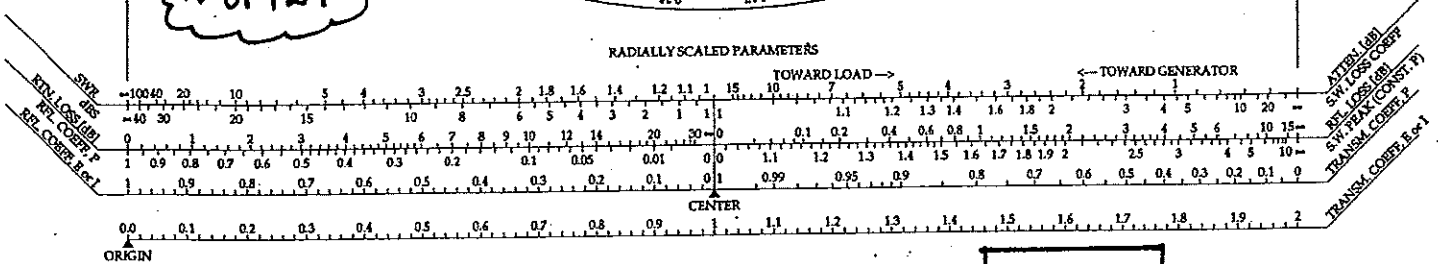


Nearest  $\rightarrow l_1 / \lambda \approx (0.5 - 0.424) + 0.19 = 0.266$

Second nearest  $\rightarrow l_2 / \lambda \approx (0.5 - 0.424) + 0.311 = 0.387$

# The Complete Smith Chart

Black Magic Design

Problem #9

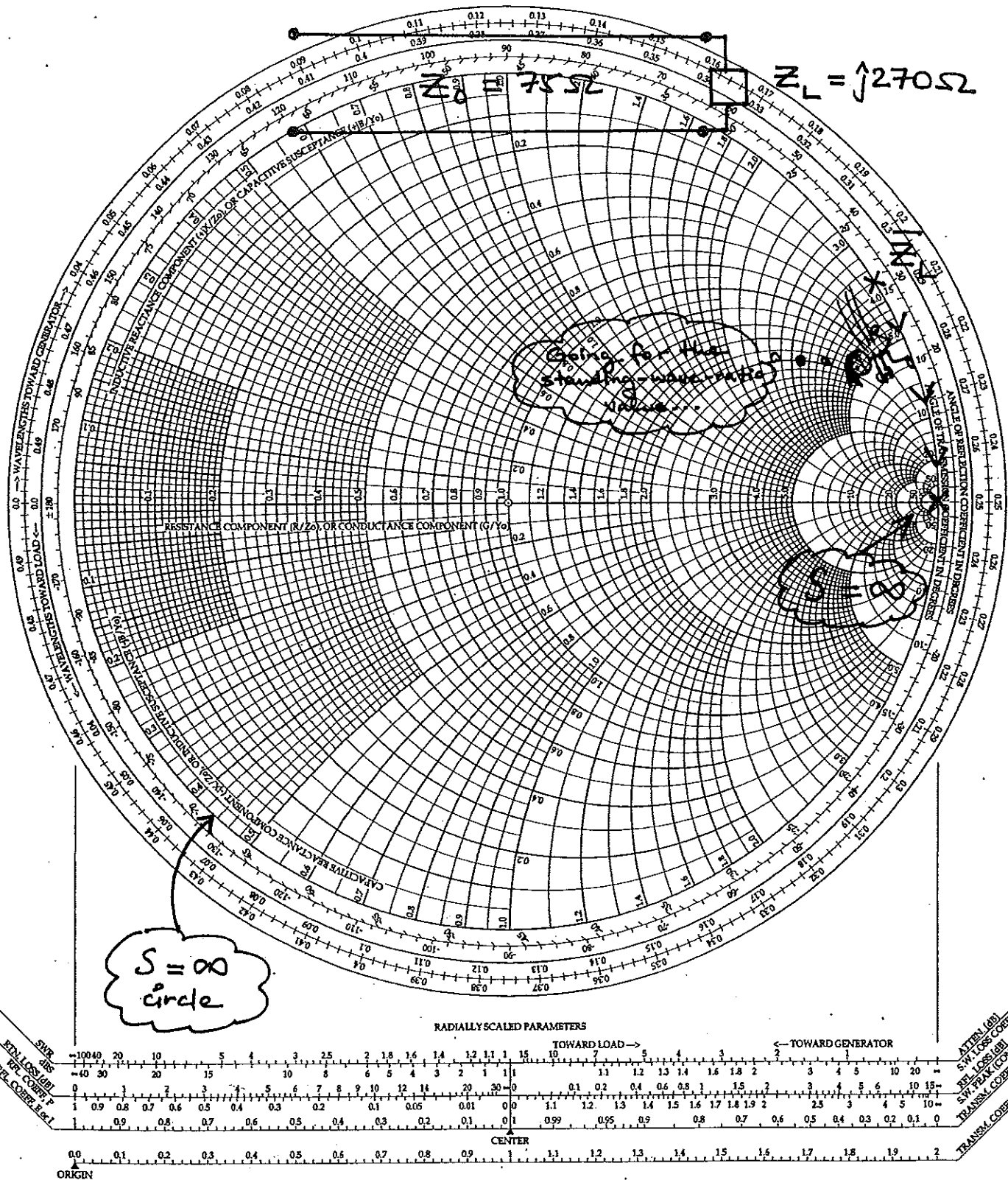


# The Complete Smith Chart


## Black Magic Design
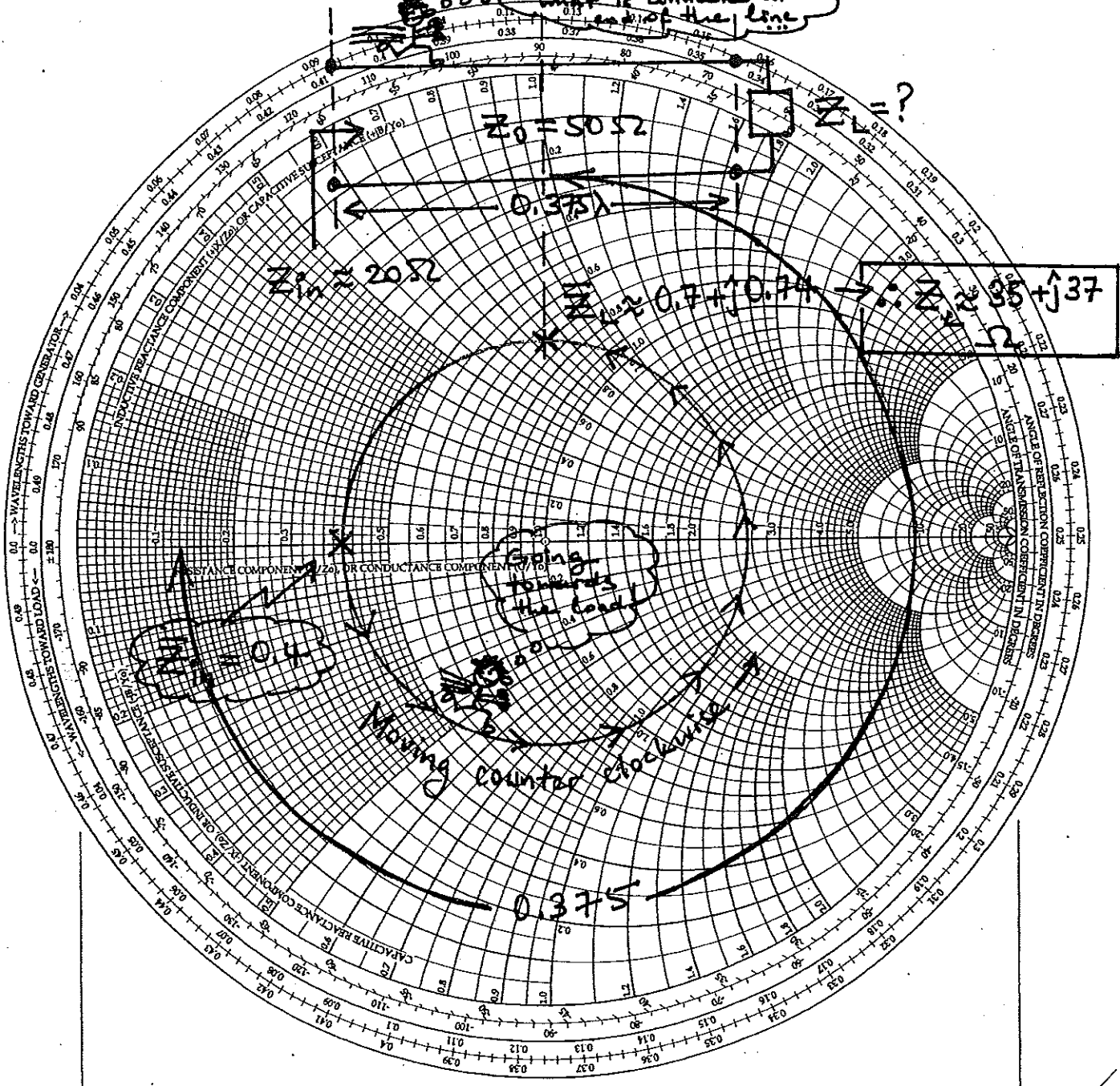
### Problem #10

I have to find out what is connected at the end of this line




#### RADIALLY SCALED PARAMETERS

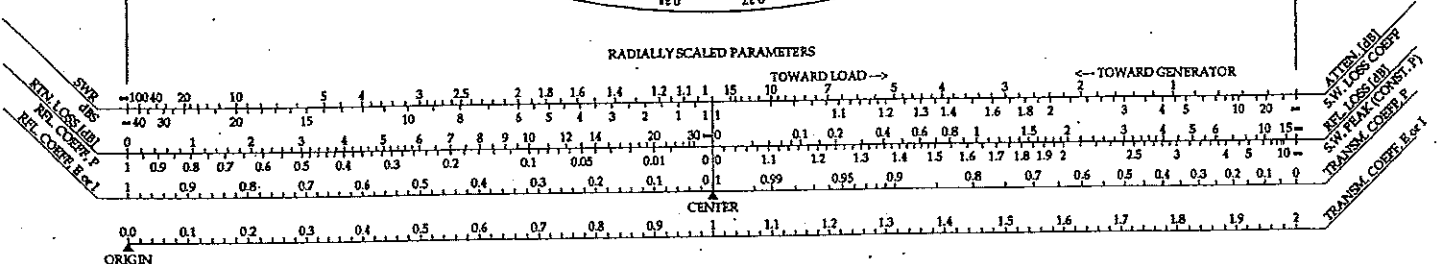

# The Complete Smith Chart

Black Magic Design

Problem #11

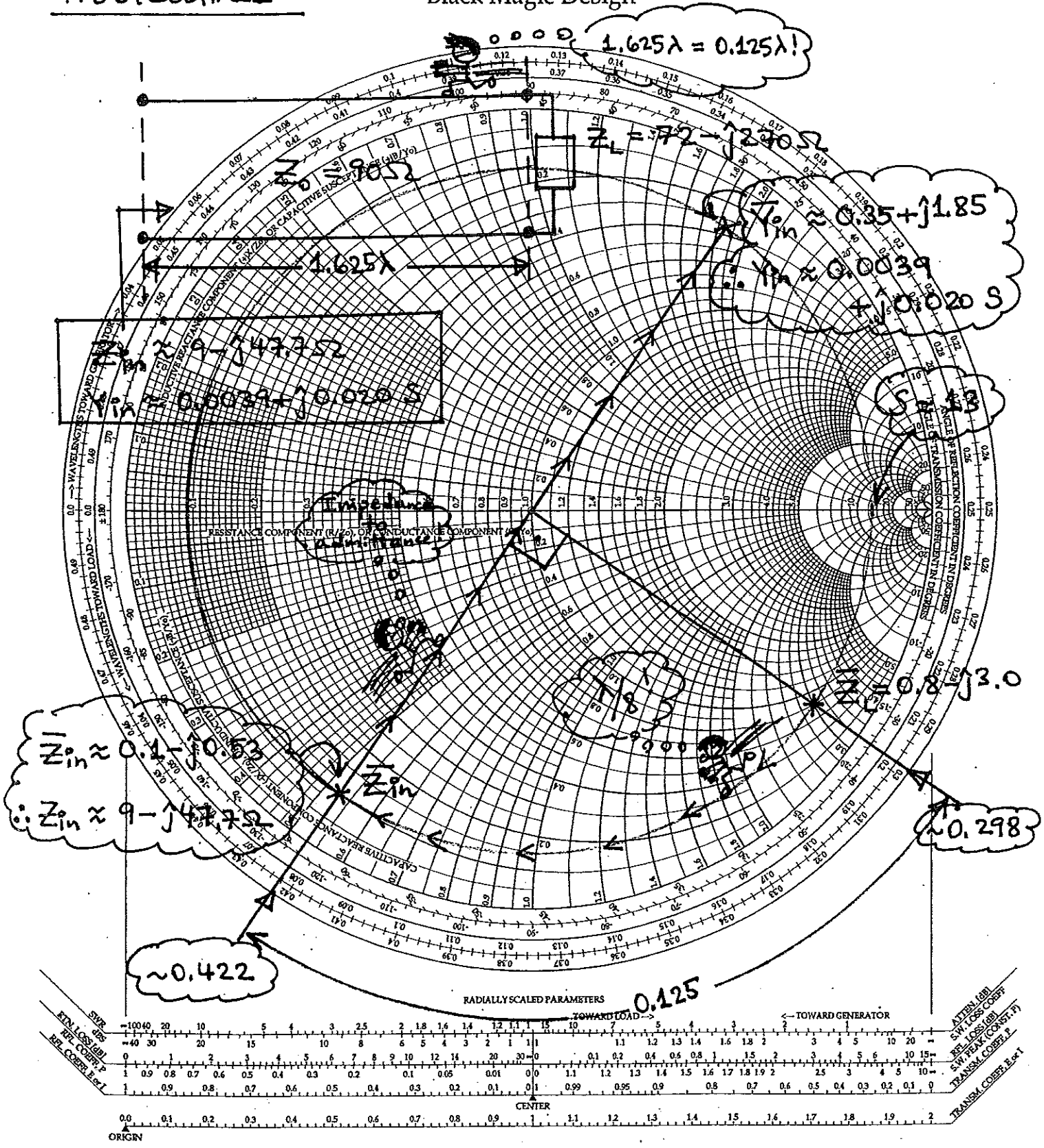





Problem # 12

The Complete Smith Chart  
Black Magic Design

$$\bar{Z} = \bar{R} + j\bar{X}$$

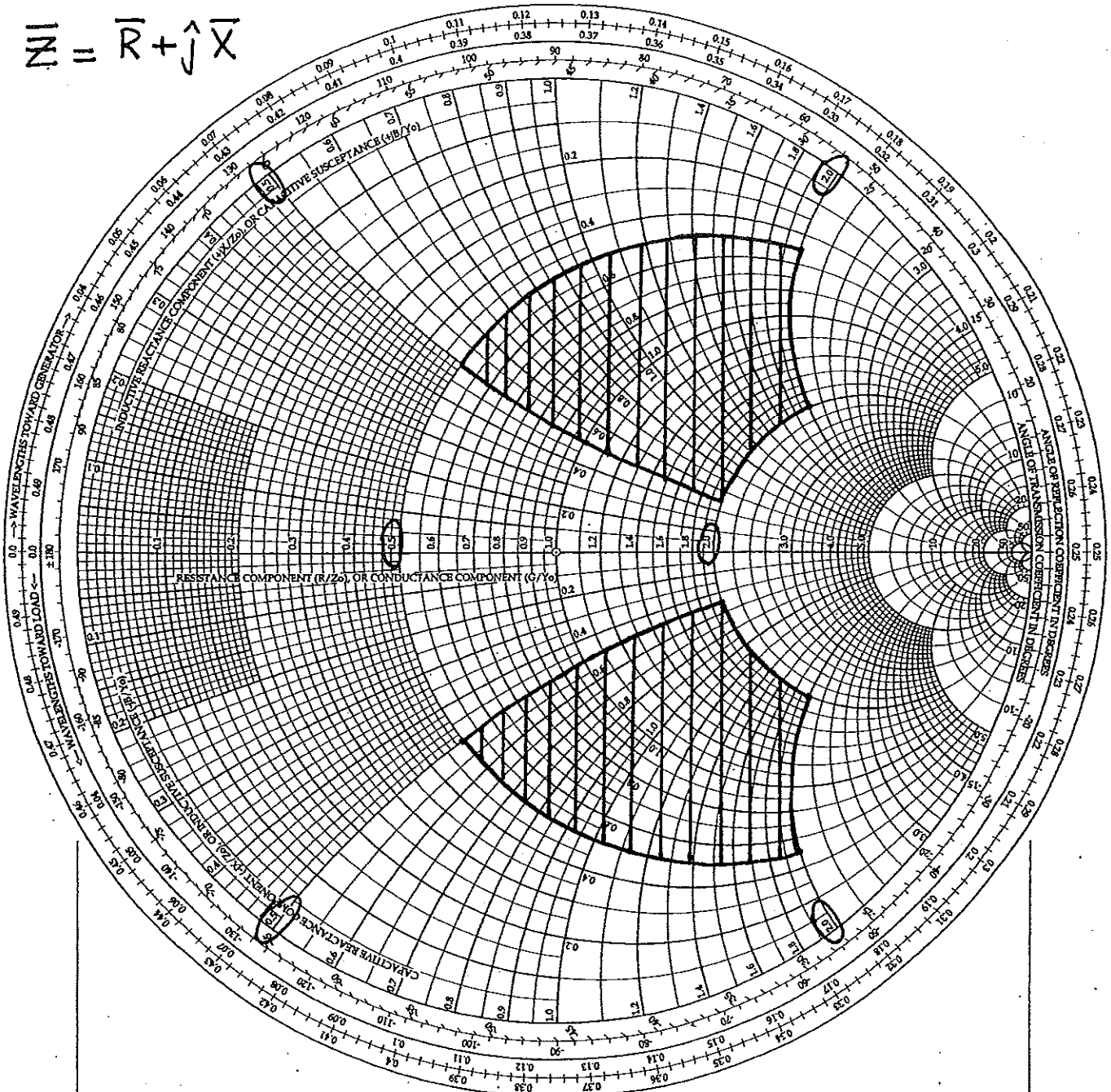

RADIALLY SCALED PARAMETERS

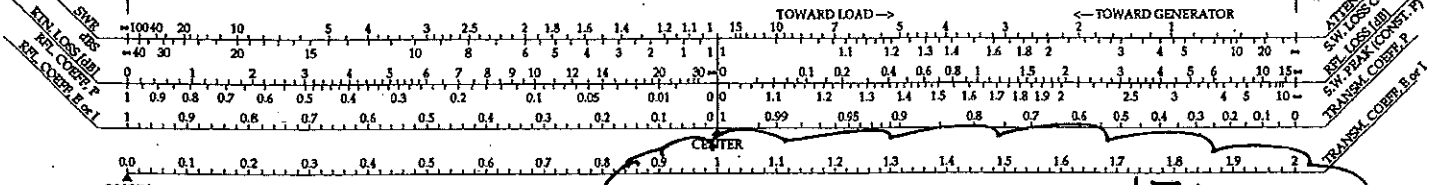

Shaded region  $\rightarrow 0.5 < \bar{R} < 2.0$  &  $0.5 < |\bar{X}| < 2.0$