

University of Portland School of Engineering

EE 301
Spring 2014
A.Inan

Homework # 4

(Monday, February 25, 2014)


Sinusoidal Steady-State (SSS) Waves on Transmission Lines

(Due Friday, March 7, 2014, 11:25a.m.)


(1) **Electrical length of transmission lines.** Find the electrical lengths of the following transmission lines:

- (a) 100-kilometer long air transmission line at 60 Hz;
- (b) 100-meter long coaxial line with a velocity factor of 0.67 at 300 MHz.

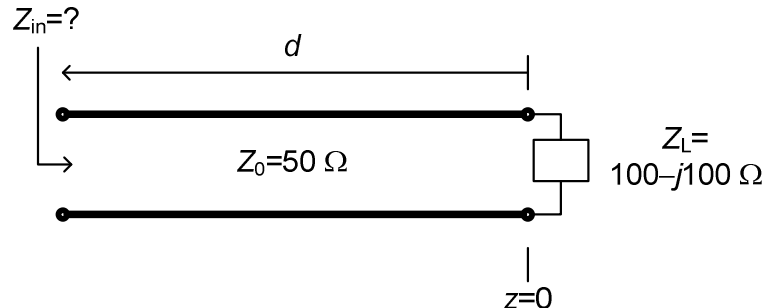
(2) **Load reflection coefficient, standing wave ratio, and input impedance.** A 50Ω transmission line is terminated with a capacitive load having a load impedance of $Z_L = 100 - j100 \Omega$, as shown. (a) Find the load reflection coefficient, i.e., Γ_L . (b) Find the standing wave ratio S on the line. (c) Find the input impedance of the line, Z_{in} , for four different line lengths: $d_1 = 0.125\lambda$, $d_2 = 0.25\lambda$, $d_3 = 0.375\lambda$, and $d_4 = 0.5\lambda$, respectively.



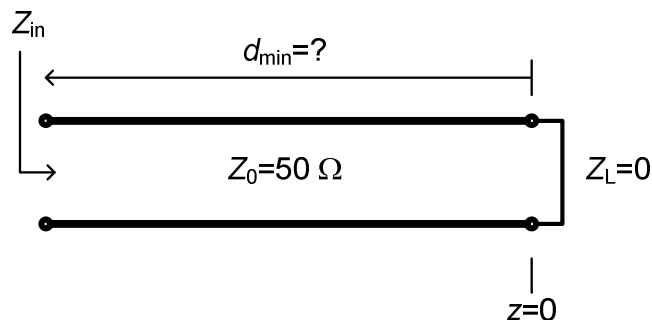
(3) **Input impedance of a transmission line.** Consider a short-circuited 50Ω transmission line (a short-circuited stub) as shown. Find the shortest electrical length of the line such that (a) $Z_{in} = j50 \Omega$; (b) $Z_{in} = -j150 \Omega$; (c) $Z_{in} = \infty$, and (d) $Z_{in} = 0$.



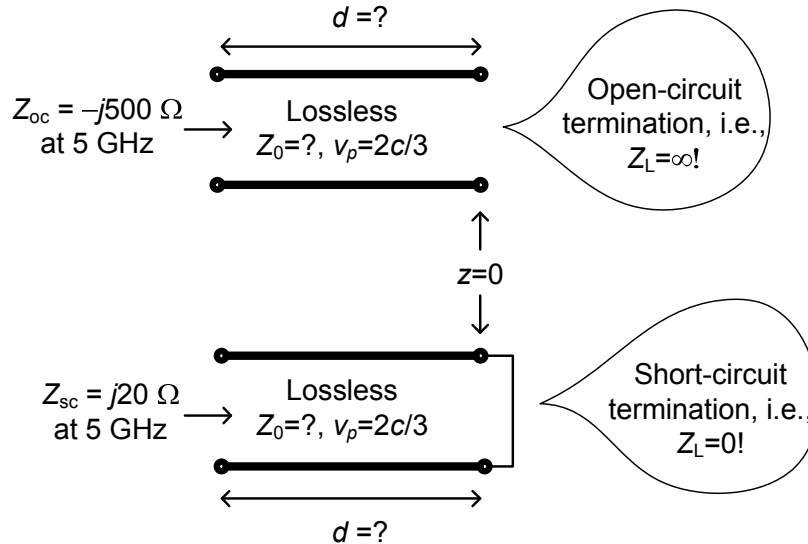
- (4) **Open- and short-circuit impedance measurements.** If the open- and short-circuit terminated input impedances of a lossless transmission line with characteristic impedance Z_0 , length d and phase velocity $v_p = 2c/3$ are measured at 5 GHz to be $Z_{oc} = -j500 \Omega$ and $Z_{sc} = j20 \Omega$ respectively, calculate Z_0 and the length d of this line. (Note that $c = 3 \times 10^8$ m/s.)




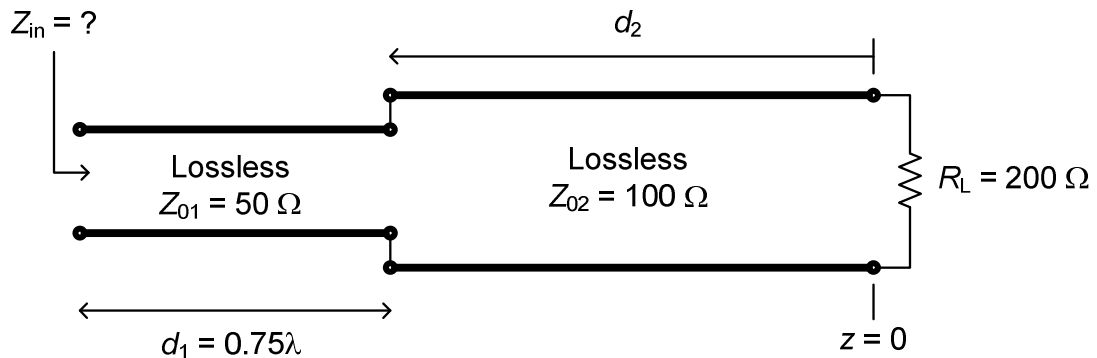
- (5) **Input impedance.** Find the input impedance Z_{in} of the transmission line system shown for (a) $d_2 = 0.25\lambda$; (b) $d_2 = 0.5\lambda$; and (c) $d_2 = 0.125\lambda$.



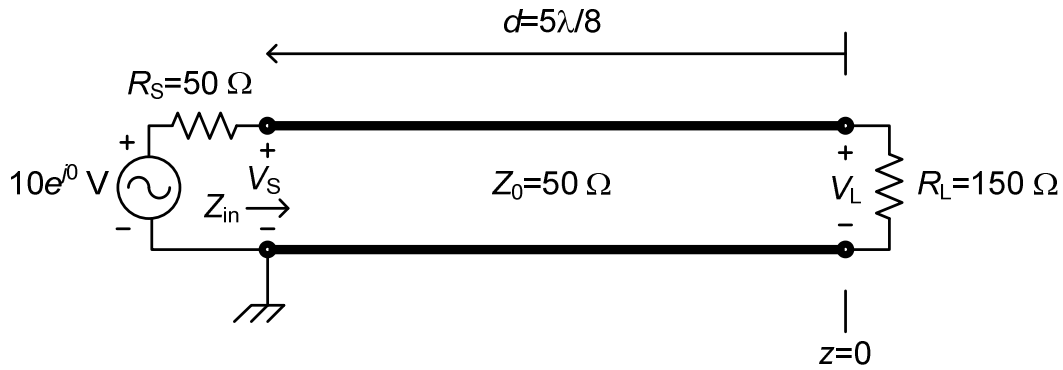- (6) **Source- and load-end voltages.** For the transmission line shown, assuming sinusoidal steady state, calculate the source-end and load-end voltages V_S and V_L in phasor form.



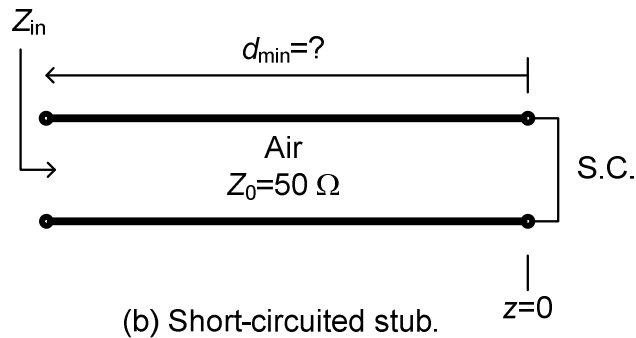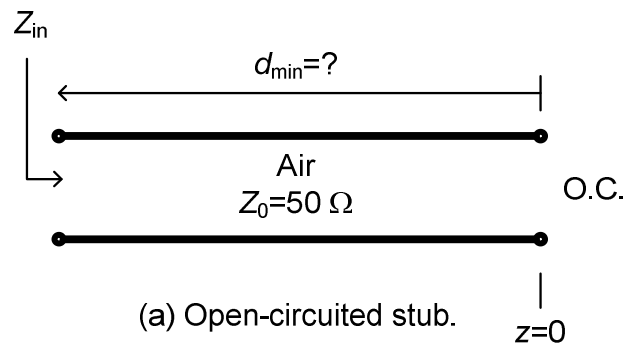- (7) **Designing a capacitor using a stub.** Capacitive and inductive circuit elements can be designed using short-circuit or open-circuited stubs. The lengths of these stubs are typically short with respect to the associated wavelength. (a) Design an open-circuited 50Ω air stub that will provide the impedance of a 4 nF capacitor at 10 GHz . Find the shortest length of the stub. (b) Redesign the capacitor in part (a) using a short-circuited 50Ω air stub. (c) Which design yields the shortest length and why?



- (8) **Designing an inductor using a stub.** (a) Design an open-circuited 50Ω microstrip transmission-line stub having an effective relative dielectric constant of $\epsilon_r \cong 6$ that will provide the impedance of a 5 nH inductor at 5 GHz . Find the shortest length of the stub. (b) Repeat the same design using a short-circuited 50Ω microstrip line stub having an effective relative dielectric constant of $\epsilon_r \cong 6$. (c) Which design resulted in a shorter stub and why?

Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #4-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 301/Spring 2014 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.

An Important Reminder Note:

EE 301-Midterm # 2 is scheduled to be given on Friday, April 4, 2014

(It will be in-class closed-book exam. Two formula sheets will be allowed.)