

University of Portland School of Engineering

EE 301
Spring 2014
A.Inan

Solutions to Homework # 4 (Wednesday, March 19, 2014)

(1) Electrical length of transmission lines. Find the electrical lengths of the following transmission lines:

- (a) 100-kilometer long air transmission line at 60 Hz;
- (b) 100-meter long coaxial line with a velocity factor of 0.67 at 300 MHz.

Solution:


(a) Since air line, $v_p = c \cong 3 \times 10^5 \text{ km} \cdot \text{s}^{-1}$. So, the electrical length of the 100-kilometer air line at 60 Hz is given by

$$\bar{d} = \frac{d}{\lambda} = \frac{d}{(v_p/f)} \cong \frac{(100 \text{ km})}{(3 \times 10^5 \text{ km} \cdot \text{s}^{-1})/(60 \text{ Hz})} \cong 0.02$$

(b) The electrical length of the 100-meter coaxial line with velocity factor 0.67 at 300 MHz can be calculated as

$$\bar{d} = \frac{d}{\lambda} = \frac{d}{(v_p/f)} \cong \frac{(100 \text{ m})}{(0.67 \times 3 \times 10^8 \text{ m} \cdot \text{s}^{-1})/(3 \times 10^8 \text{ Hz})} \cong 149.25$$

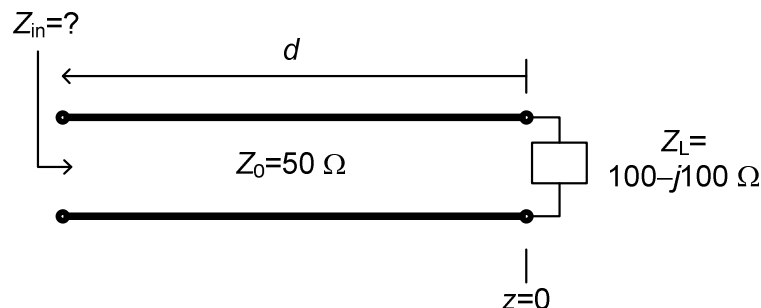(2) Load reflection coefficient, standing wave ratio, and input impedance. A 50Ω transmission line is terminated with a capacitive load having a load impedance of $Z_L = 100 - j100 \Omega$, as shown. (a) Find the load reflection coefficient, i.e., Γ_L . (b) Find the standing wave ratio S on the line. (c) Find the input impedance of the line, Z_{in} , for four different line lengths: $d_1 = 0.125\lambda$, $d_2 = 0.25\lambda$, $d_3 = 0.375\lambda$, and $d_4 = 0.5\lambda$, respectively.



Solution:

(a) The load reflection coefficient Γ_L is given by

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - j100 - 50}{100 - j100 + 50} = \frac{50 - j100}{150 - j100} = \frac{1 - j2}{3 - j2} \times \underbrace{\frac{3 + j2}{3 + j2}}_{\substack{\text{complex} \\ \text{conjugate} \\ \text{multiplication!}}} = \frac{7 - j4}{13} \cong \underbrace{0.620}_{|\Gamma_L|} e^{j\left(\frac{-29.7^\circ}{\theta_L}\right)}$$

(b) The standing wave ratio S on the line can be found as

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \cong \frac{1 + 0.620}{1 - 0.620} \cong 4.27$$

(c) For $d_1 = 0.125\lambda$, the input impedance Z_{in1} of the line is given by

$$\begin{aligned} Z_{in1} &= Z_0 \frac{Z_L + jZ_0 \tan(2\pi d_1/\lambda)}{Z_0 + jZ_L \tan(2\pi d_1/\lambda)} = 50 \frac{(100 - j100) + j50 \tan\left(\frac{2\pi \times 0.125}{\pi/4}\right)}{50 + j(100 - j100) \tan\left(\frac{2\pi \times 0.125}{\pi/4}\right)} \\ &= 50 \frac{100 - j100 + j50}{50 + j(100 - j100)} = 50 \frac{100 - j50}{150 + j100} = 50 \frac{2 - j}{3 + j2} \times \underbrace{\frac{3 - j2}{3 - j2}}_{\substack{\text{complex} \\ \text{conjugate} \\ \text{multiplication!}}} \\ &= 50 \frac{4 - j7}{13} \cong 15.38 - j26.92 \Omega \end{aligned}$$

For $d_2 = 0.25\lambda$ (i.e., quarter wavelength), the input impedance Z_{in2} is given by


$$Z_{in2} = \frac{Z_0^2}{Z_L} = \frac{50^2}{(100 - j100)} \times \underbrace{\frac{100 + j100}{100 + j100}}_{\substack{\text{complex} \\ \text{conjugate} \\ \text{multiplication!}}} = \frac{50^2(100 + j100)}{\underbrace{100^2 + 100^2}_{2 \times 10^4}} = 12.5 + j12.5 \Omega$$

For $d_3 = 0.375\lambda$, the input impedance Z_{in3} is given by

$$\begin{aligned}
Z_{in3} &= Z_0 \frac{Z_L + jZ_0 \tan(2\pi d_3/\lambda)}{Z_0 + jZ_L \tan(2\pi d_3/\lambda)} = 50 \frac{(100 - j100) + j50 \tan\left(\frac{2\pi \times 0.375}{3\pi/4}\right)}{50 + j(100 - j100) \tan\left(\frac{2\pi \times 0.375}{3\pi/4}\right)} \\
&= 50 \frac{100 - j100 - j50}{50 - j(100 - j100)} = 50 \frac{100 - j150}{-50 - j100} = 50 \frac{2 - j3}{-1 - j2} \times \underbrace{\frac{-1 + j2}{-1 + j2}}_{\text{complex conjugate multiplication!}} \\
&= 50 \frac{4 + j7}{5} = 40 + j70 \Omega
\end{aligned}$$

For $d_4 = 0.5\lambda$ (i.e., half wavelength), the input impedance Z_{in4} is given by $Z_{in4} = Z_L = 100 - j100 \Omega$.

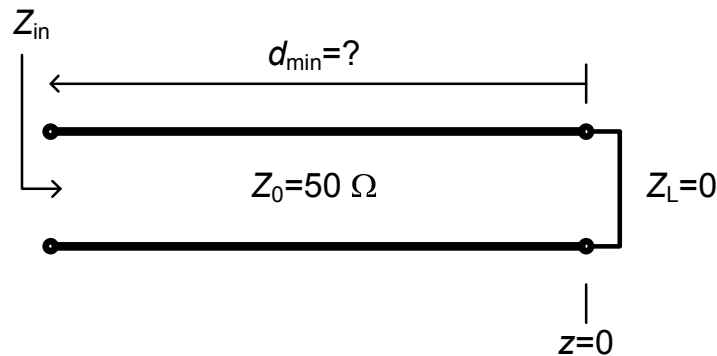- (3) Input impedance of a transmission line.** Consider a short-circuited 50Ω transmission line (a short-circuited stub) as shown. Find the shortest electrical length of the line such that (a) $Z_{in} = j50 \Omega$; (b) $Z_{in} = -j150 \Omega$; (c) $Z_{in} = \infty$, and (d) $Z_{in} = 0$.



Solution:

- (a) The input impedance of a short-circuited transmission line is given by

$$Z_{in.s.c.} = jZ_0 \tan\left(\frac{2\pi}{\lambda} d\right)$$

So, substituting the values $Z_{in} = j50 \Omega$ and $Z_0 = 50 \Omega$, we have

$$Z_{in.s.c.} = j50 \tan\left(\frac{2\pi}{\lambda} d\right) = j50 \Omega \rightarrow \bar{d} = \frac{d}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1} 1}_{\pi/4 \text{ rad}} = 0.125$$

- (b) Substituting the values $Z_{in} = -j150 \Omega$ and $Z_0 = 50 \Omega$, we have

$$Z_{\text{in.s.c.}} = j50 \tan\left(\frac{2\pi}{\lambda} d\right) = -j150 \Omega \rightarrow \bar{d} = \frac{d}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1}(-3)}_{\sim -1.249 \text{ rad}} \cong -0.1988 + 0.5 = 0.3012$$


(c) Substituting the values $Z_{\text{in}} = \infty$ and $Z_0 = 50 \Omega$, we have

$$Z_{\text{in.s.c.}} = j50 \tan\left(\frac{2\pi}{\lambda} d\right) = \infty \rightarrow \bar{d} = \frac{d}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1}(\infty)}_{(\pi/2) \text{ rad}} = \frac{1}{2\pi} \times \frac{\pi}{2} = 0.25$$

(d) Substituting the values $Z_{\text{in}} = 0$ and $Z_0 = 50 \Omega$, we have

$$Z_{\text{in.s.c.}} = j50 \tan\left(\frac{2\pi}{\lambda} d\right) = 0 \rightarrow \bar{d} = \frac{d}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1}(0)}_{\pi \text{ rad}} = \frac{1}{2\pi} \times \pi = 0.5$$

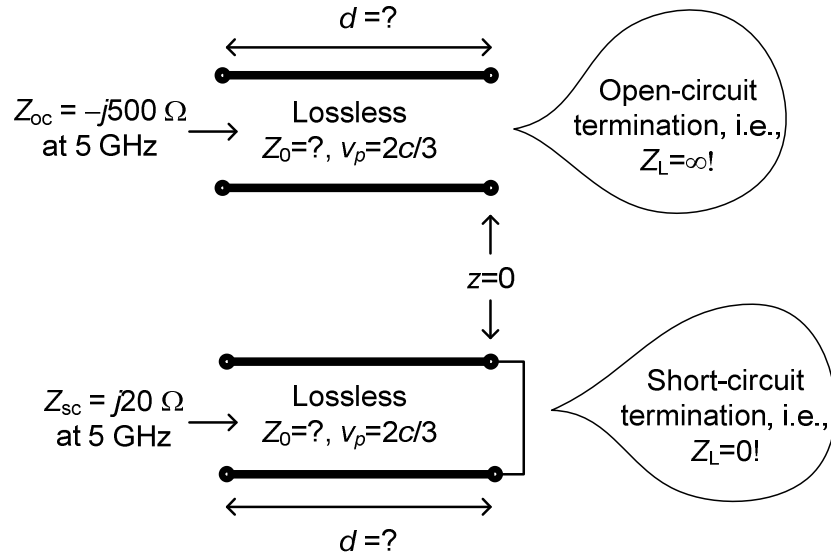(4) Open- and short-circuit impedance measurements. If the open- and short-circuit terminated input impedances of a lossless transmission line with characteristic impedance Z_0 , length d and phase velocity $v_p = 2c/3$ are measured at 5 GHz to be $Z_{\text{oc}} = -j500 \Omega$ and $Z_{\text{sc}} = j20 \Omega$ respectively, calculate Z_0 and the length d of this line. (Note that $c = 3 \times 10^8$ m/s.)



Solution:

The input impedances of the open-circuited and short-circuited lines are given by

$$Z_{\text{in.o.c.}} = \frac{-jZ_0}{\tan\left(\frac{2\pi}{\lambda} d\right)} = -j500 \Omega \quad \text{and} \quad Z_{\text{in.s.c.}} = jZ_0 \tan\left(\frac{2\pi}{\lambda} d\right) = j20 \Omega$$

So, by multiplying the above two equations yields


$$Z_{\text{in},s.c.} \times Z_{\text{in},o.c.} = jZ_0 \tan\left(\frac{2\pi}{\lambda}d\right) \times \frac{-jZ_0}{\tan(2\pi d/\lambda)} = Z_0^2 = (j20)(-j500) = 10^4 \Omega^2 \rightarrow Z_0 = 100 \Omega$$

The electrical length of the line can then be obtained by substituting the Z_0 value calculated in one of the above equations as

$$Z_{\text{in},s.c.} = j100 \tan\left(\frac{2\pi}{\lambda}d\right) = j20 \Omega \rightarrow \bar{d} = \frac{d}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1}(0.2)}_{\sim 0.1974 \text{ rad}} \cong 0.0314$$

Since $f = 5 \text{ GHz}$ and $v_p = 2c/3$, $\lambda = v_p / f = 2 \times 10^8 \text{ m}\cdot\text{s}^{-1} / 5 \times 10^9 \text{ Hz} = 0.04 \text{ m} = 4 \text{ cm}$. Therefore, the actual length of the line can be found from the electrical length as $d = (0.0314)(4 \text{ cm}) = 0.126 \text{ cm}$.

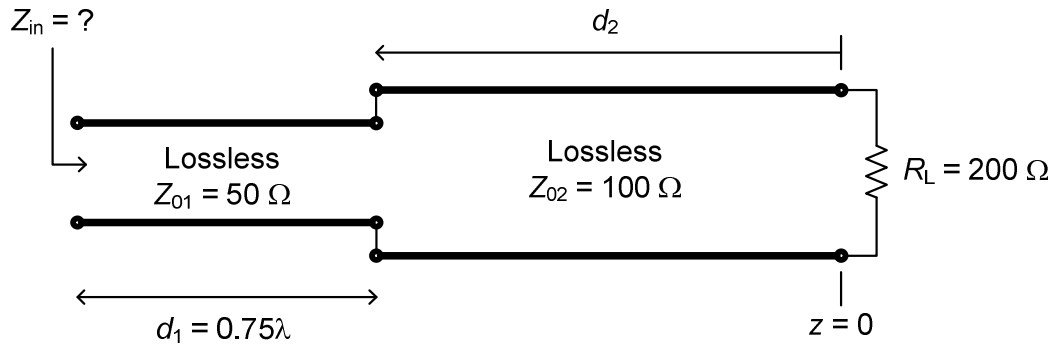- (5) **Input impedance.** Find the input impedance Z_{in} of the transmission line system shown for (a) $d_2 = 0.25\lambda$; (b) $d_2 = 0.5\lambda$; and (c) $d_2 = 0.125\lambda$.



Solution:

- (a) For $d_2 = 0.25\lambda$, the input impedance of the second line can be calculated as

$$Z_{\text{in}2} = \frac{Z_{02}^2}{Z_L} = \frac{(100)^2}{200} = 50 \Omega$$

The input impedance of the first line is then given by

$$Z_{\text{in}1} = \frac{Z_{01}^2}{Z_{\text{in}2}} = \frac{(50)^2}{50} = 50 \Omega$$

- (b) For $d_2 = 0.5\lambda$, the input impedance of the second line can be calculated as

$$Z_{\text{in}2} = Z_L = 200 \Omega$$

The input impedance of the first line is then given by

$$Z_{in1} = \frac{Z_{01}^2}{Z_{in2}} = \frac{(50)^2}{200} = 12.5 \Omega$$


(c) For $d_2=0.125\lambda$, the input impedance of the second line can be calculated as

$$\begin{aligned} Z_{in2} &= Z_{02} \frac{Z_L + jZ_{02} \tan(2\pi d_2/\lambda)}{Z_{02} + jZ_L \tan(2\pi d_2/\lambda)} = 100 \frac{200 + j100 \tan\left(\frac{2\pi \times 0.125}{\pi/4}\right)}{100 + j200 \tan\left(\frac{2\pi \times 0.125}{\pi/4}\right)} \\ &= 100 \frac{200 + j100}{100 + j200} = 100 \frac{2 + j}{1 + j2} \times \underbrace{\frac{1 - j2}{1 - j2}}_{\text{complex conjugate multiplication!}} = 100 \frac{2 + 2 + j - j4}{5} \Omega = 80 - j60 \Omega \end{aligned}$$

The input impedance of the first line is then given by

$$Z_{in1} = \frac{Z_{01}^2}{Z_{in2}} = \frac{(50)^2}{80 - j60} = \frac{125}{4 - j3} \times \underbrace{\frac{4 + j3}{4 + j3}}_{\text{complex conjugate multiplication!}} = \frac{125(4 + j3)}{25} = 20 + j15 \Omega$$

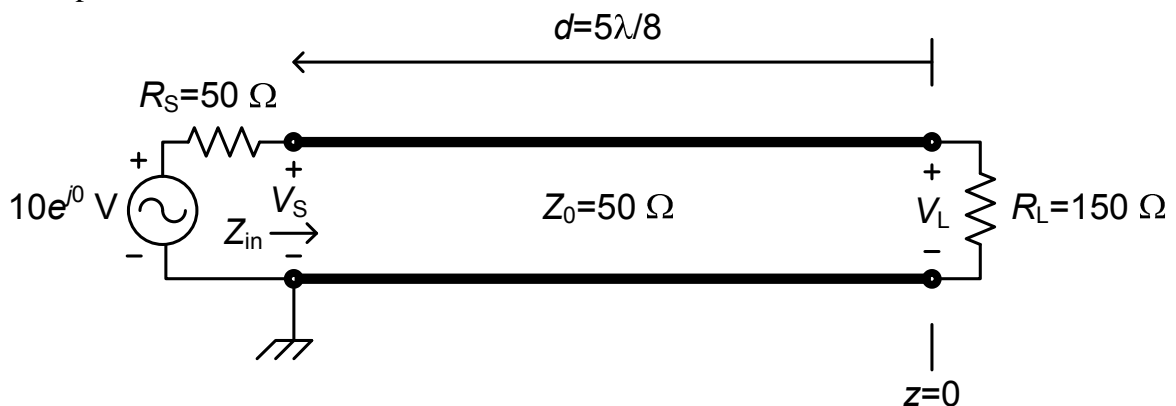
(6) Source- and load-end voltages. For the transmission line shown, assuming sinusoidal steady state, calculate the source-end and load-end voltages V_S and V_L in phasor form.



Solution:

The input impedance of a uniform lossless transmission line is given by

$$\begin{aligned}
Z_{in} &= Z_0 \frac{Z_L + jZ_0 \tan(2\pi d/\lambda)}{Z_0 + jZ_L \tan(2\pi d/\lambda)} = 50 \frac{150 + j50 \tan\left(\frac{2\pi \times 0.625}{5\pi/4}\right)}{50 + j150 \tan\left(\frac{2\pi \times 0.625}{5\pi/4}\right)} \\
&= 50 \frac{150 + j50}{50 + j150} = 50 \frac{3 + j}{1 + j3} \times \underbrace{\frac{1 - j3}{1 - j3}}_{\text{complex conjugate multiplication!}} = 50 \frac{3 + 3 + j - j9}{1 + 9} \\
&= 5(6 - j8) = 30 - j40 \Omega
\end{aligned}$$

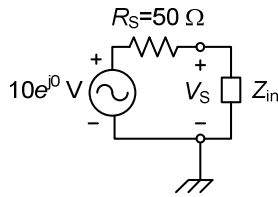

I'm a lumped impedance and I represent the transmission line seen from the source end. In fact I'm a Thevenin equivalent impedance and I absorb exactly the same power as R_L because the line is lossless!

Using the voltage divider principle, the source-end phasor voltage V_S is obtained as

$$V_S = \frac{Z_{in}}{R_S + Z_{in}} (10e^{j0}) = \frac{30 - j40}{\underbrace{50 + 30 - j40}_{80 - j40}} (10e^{j0}) \cong \frac{50e^{-j53.13^\circ}}{89.44e^{-j26.57^\circ}} (10e^{j0}) \cong 5.59e^{-j26.57^\circ} \Omega$$

Note that the total phasor voltage at any position along the transmission line is given by

$$V(z) = \underbrace{V^+ e^{-j\beta z}}_{\text{Incident voltage wave}} + \underbrace{V^- e^{+j\beta z}}_{\text{Reflected voltage wave}} = V^+ e^{-j\beta z} [1 + \Gamma_L e^{+j2\beta z}]$$

Note that the load reflection coefficient is given by

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 50}{150 + 50} = 0.5$$

Using the values of Γ_L and V_S , we can obtain the value of V^+ as follows:


$$V\left(\underbrace{z = -\frac{5\lambda}{8}}_{V_s}\right) = V^+ e^{j5\pi/4} \left[1 + \Gamma_L \underbrace{e^{-j5\pi/2}}_{-j} \right] = V^+ e^{j5\pi/4} [1 - j0.5] \cong 5.59 e^{-j26.57^\circ}$$

$$\rightarrow V^+ \cong 5e^{-j225^\circ} \quad V = 5e^{j135^\circ} \quad V$$

Next, the load-end phasor voltage can be calculated as

$$V_L = V(z=0) = V^+ \left[1 + \underbrace{\Gamma_L}_{0.5} \right] \cong 5e^{j135^\circ} \times 1.5 = 7.5e^{j135^\circ} \quad V$$

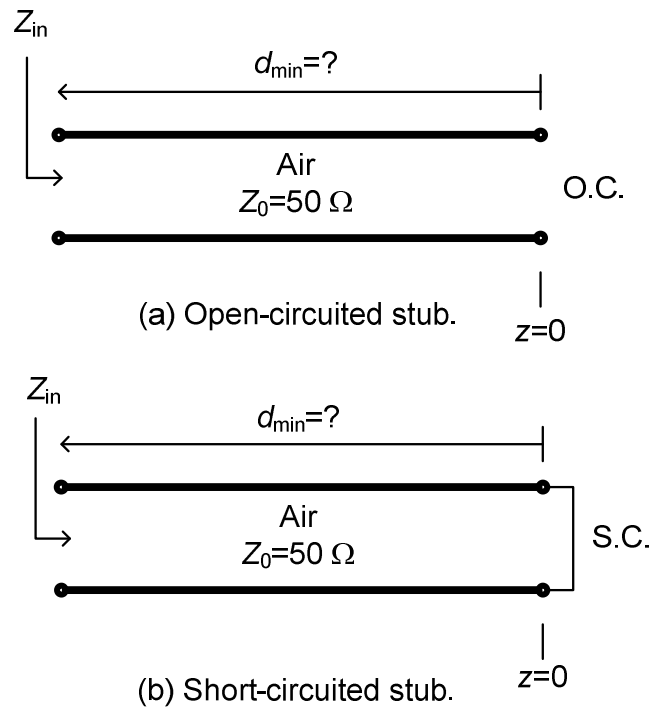- (7) Designing a capacitor using a stub.** Capacitive and inductive circuit elements can be designed using short-circuit or open-circuited stubs. The lengths of these stubs are typically short with respect to the associated wavelength. (a) Design an open-circuited $50 \, \Omega$ air stub that will provide the impedance of a $4 \, \text{nF}$ capacitor at $10 \, \text{GHz}$. Find the shortest length of the stub. (b) Redesign the capacitor in part (a) using a short-circuited $50 \, \Omega$ air stub. (c) Which design yields the shortest length and why?



Solution:

- (a) Note that $\lambda_{\text{air}} \cong (3 \times 10^{10} \text{ cm} \cdot \text{s}^{-1}) / (10^{10} \text{ Hz}) = 3 \text{ cm}$. Equating the input impedance expression of an open-circuited stub to the impedance of a lumped capacitor, we have

$$Z_{\text{in.o.c.}} = \frac{-jZ_0}{\tan\left(\frac{2\pi}{\lambda}d\right)} = Z_{\text{cap}} = \frac{-j}{\omega C} \rightarrow \frac{-j50}{\tan\left(\frac{2\pi}{\lambda}d\right)} = \frac{-j}{2\pi \times 10^{10} \times \underbrace{4 \times 10^{-9}}_{4 \text{ nF}}} = \frac{-j}{80\pi} \Omega$$

$$\rightarrow \frac{d_{\text{min}}}{\lambda} = \frac{1}{2\pi} \tan^{-1}(4000\pi) \cong 0.249987 \rightarrow d_{\text{min}} \cong 0.249987 \lambda_{\text{air}} \cong 0.74996 \text{ cm}$$

$\sim \pi/2 \text{ rad}$

(b) Using the input impedance expression of a short-circuited stub, we have

$$Z_{\text{in.s.c.}} = jZ_0 \tan\left(\frac{2\pi}{\lambda}d\right) = Z_{\text{cap}} = \frac{-j}{\omega C} \rightarrow j50 \tan\left(\frac{2\pi}{\lambda}d\right) = \frac{-j}{80\pi} \Omega$$

$$\rightarrow \frac{d_{\text{min}}}{\lambda} = \frac{1}{2\pi} \tan^{-1}\left(\frac{-1}{4000\pi}\right) \cong -1.2665 \times 10^{-5} + \underbrace{0.5}_{\substack{\text{adjustment} \\ \text{to obtain a} \\ \text{positive } d!}} = 0.499987$$

$\sim -0.000079577 \text{ rad}$

$$\rightarrow d_{\text{min}} \cong 0.499987 \lambda_{\text{air}} \cong 1.49996 \text{ cm}$$

(c) As expected, the open-circuited stub yields the shortest length since the input impedance of the open-circuited stub is capacitive when its electrical length falls in the range $0 < d/\lambda < 0.25$ whereas the input impedance of the short-circuited stub in the same range is inductive.

(8) Designing an inductor using a stub. (a) Design an open-circuited 50Ω microstrip transmission-line stub having an effective relative dielectric constant of $\epsilon_r \cong 6$ that will provide the impedance of a 5 nH inductor at 5 GHz . Find the shortest length of the stub. (b) Repeat the same design using a short-circuited 50Ω microstrip line stub having an effective relative dielectric constant of $\epsilon_r \cong 6$. (c) Which design resulted in a shorter stub and why?

Solution:

(a) Note that $\lambda \cong (3 \times 10^{10} \text{ cm} \cdot \text{s}^{-1} / \sqrt{6}) / (5 \times 10^9 \text{ Hz}) \cong 2.45 \text{ cm}$. Equating the input impedance expression of an open-circuited stub to the impedance of a lumped inductor, we have

$$Z_{\text{in.o.c.}} = \frac{-jZ_0}{\tan\left(\frac{2\pi}{\lambda}d\right)} = \underbrace{j\omega L}_{Z_{\text{coil}}} \rightarrow \frac{-j50}{\tan\left(\frac{2\pi}{\lambda}d\right)} = \underbrace{j2\pi \times 5 \times 10^9 \times 5 \times 10^{-9}}_{j50\pi}$$

$$\rightarrow \frac{d_{\text{min}}}{\lambda} = \frac{1}{2\pi} \tan^{-1}\left(-\frac{1}{2\pi}\right) \cong -0.02512 + 0.5 = 0.4749 \rightarrow d_{\text{min}} \cong 0.4749 \lambda \cong 1.163 \text{ cm}$$

$\sim -0.1578 \text{ rad}$

(d) Using the input impedance expression of a short-circuited stub, we have

$$Z_{\text{in,s.c.}} = jZ_0 \tan\left(\frac{2\pi}{\lambda} d\right) = \underbrace{j\omega L}_{Z_{\text{coil}}} \rightarrow j50 \tan\left(\frac{2\pi}{\lambda} d\right) = j50\pi$$
$$\rightarrow \frac{d_{\text{min}}}{\lambda} = \frac{1}{2\pi} \underbrace{\tan^{-1} \pi}_{\sim 1.2626 \text{ rad}} \cong 0.20095 \rightarrow d_{\text{min}} \cong 0.20095\lambda \cong 0.4922 \text{ cm}$$

(e) As expected, the short-circuited stub yields the shortest length since the input impedance of the short-circuited stub is inductive when its electrical length falls in the range $0 < d/\lambda < 0.25$ whereas the input impedance of the open-circuited stub in the same range is capacitive.