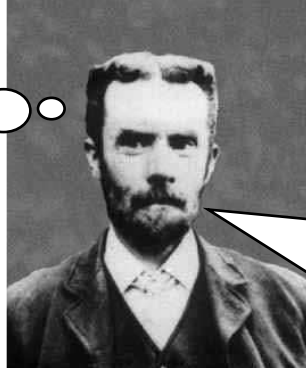


University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.

Spring 2014

You will pay a heavy price for giving these students such tough tests and scaring them to death Inaaan!
@*\$*#&XΘχ@*§ξ!



Best of luck to you EE 301 students and please, demonstrate to Inan that unlike what everyone might think, his tests are nothing but simply a piece of cake! (Bring his fame down about giving challenging exams!)

Midterm Exam # 1

(Prepared by Professor A. S. Inan)

(Friday, February 21, 2014)

(Closed Book Exam; 1 Formula Sheet Allowed)

(Total Time: 55 mins.)

Name: _____ 😊

Signature: _____ 😊

“Honesty is the best policy.”

Aesop (~ 620B.C. -?)

“An honest mind possesses a kingdom.”


Lucius Annaeus Seneca (4B.C.–65A.D.)

“Honest people are the true winners of the universe.”

Anonymous

(1) (20 mins., Total: 50 points) **Step excitation of a lossless line.** A uniform, lossless transmission line is excited with a step source as shown.

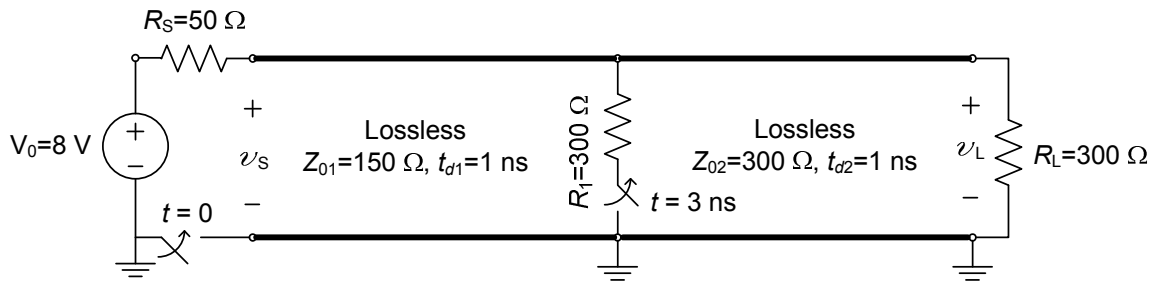(a) (30 points) Draw a bounce diagram showing all the voltage waves including their values on each line, for a time period of $0 \leq t \leq 6$ ns.



(b)(20 points) Using the data in your bounce diagram, calculate the values of the source-end voltage v_S and the load-end voltage v_L at the specific times indicated in the table below and enter these values in the table. Show your work.

t (ns)	$v_S(t)$ (v)	$v_L(t)$ (v)
1^+		
2^+		
3^+		
4^+		
5^+		
6^+		

- (2) (20 mins., 50 points) **Reactive element at the junction.** In the transmission-line circuit shown, find the complete mathematical expressions and sketch both the source-end voltage v_s and the load-end voltage v_L as a function of time. Sketch the two waveforms separately. Provide all the pertinent values on each sketch.

