

University of Portland
School of Engineering

EE 301-Electromagnetic Fields-3 cr. hrs.
Spring 2014

Midterm Exam # 2
Sinusoidal Steady-State Waves on Transmission Lines
(Prepared by Professor A. S. Inan)

(Monday, April 4, 2014)
(Closed Book Exam; 3 Formula Sheets Allowed)
(Total Time: 55 mins.)

Name: SOLUTIONS ☺

Signature:

SOLUTIONS ☺

"Honesty is the best policy."
Aesop (~ 620B.C. -?)

"An honest mind possesses a kingdom."
Lucius Annaeus Seneca (4B.C.-65A.D.)


"Honest people are the true winners of the universe."
Anonymous

This table will be used by Inan for grading!

Problem #	Points gained
#1	
#2	
#3	
#4	
Total	

We are both odd integer multiples of quarter wavelength!

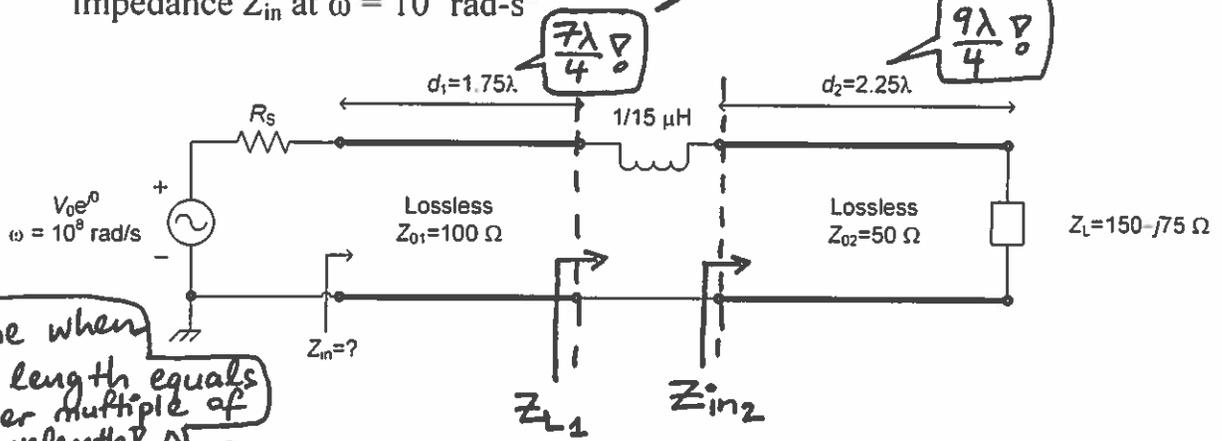(1)(10 mins., 20 points) Input impedance of a transmission-line circuit. For the double transmission-line circuit shown, find the input impedance Z_{in} at $\omega = 10^8 \text{ rad}\cdot\text{s}^{-1}$



$7\lambda/4$

$9\lambda/4$

Apply me when the line length equals odd integer multiple of quarter wavelength!

$$Z_{in2} = \frac{Z_{02}^2}{Z_L} = \frac{(50)^2}{150 - j75} = \frac{100}{6 - j3} = \frac{100}{3(2 - j)} \times \frac{2 + j}{2 + j}$$

$$= \frac{20(2 + j)}{3} \Omega \approx 13.3 + j6.67 \Omega$$


I'm the impedance of the inductor!

$$Z_{L1} = Z_{ind} + Z_{in2} = j(10^8) \left(\frac{10^{-6}}{15} \right) + \frac{20(2 + j)}{3} = \frac{40(1 + j)}{3} \Omega \approx 13.3(1 + j) \Omega$$

$$Z_{in} = \frac{Z_{01}^2}{Z_{L1}} = \frac{3(100)^2}{40(1 + j)} = \frac{750}{1 + j} \times \frac{1 - j}{1 - j} = \frac{750}{2} (1 - j) = 375(1 - j) \Omega$$

Just like $9\lambda/4$, $7\lambda/4$ is also an odd integer multiple of quarter wavelength!

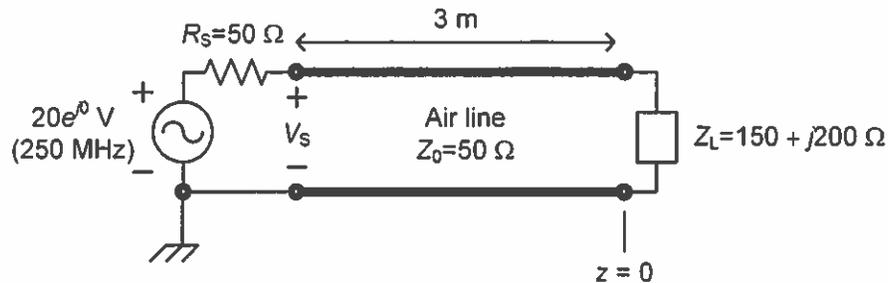- (2)(15 mins., Total: 40 points) A lossless transmission line terminated with a complex impedance. A $50\ \Omega$ air transmission line is terminated with an inductive load impedance given by $Z_L = 150 + j200\ \Omega$ and excited by a sinusoidal voltage source as shown.



- (a) (10 points) Calculate the load reflection coefficient Γ_L . (Provide your answer in polar form.) Show your work!

$$\begin{aligned}\Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 + j200 - 50}{150 + j200 + 50} = \frac{100(1 + j2)}{200(1 + j)} \times \frac{1 - j}{1 - j} \\ &= \frac{3 + j}{4} = \frac{\sqrt{10}}{4} e^{j \tan^{-1}(1/3)} \approx \boxed{0.791 e^{j 18.4^\circ}}\end{aligned}$$

We are the magnitude of Γ_L !

- (b) (5 points) What is the value of the standing wave ratio S on the line?

$$\begin{aligned}S &= \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + \frac{\sqrt{10}}{4}}{1 - \frac{\sqrt{10}}{4}} = \frac{4 + \sqrt{10}}{4 - \sqrt{10}} \\ &\approx \boxed{8.55}\end{aligned}$$


(c) (15 points) Calculate the time-average power delivered to the load.

$$\lambda_{\text{air}} = \frac{c}{f} \approx \frac{3 \times 10^8 \text{ m-s}^{-1}}{250 \times 10^6 \text{ Hz}} = 1.2 \text{ m} \rightarrow \bar{l} = \frac{l}{\lambda} = \frac{3 \text{ m}}{1.2 \text{ m}}$$

I'm the electrical length of the transmission line

$$= 2.5$$
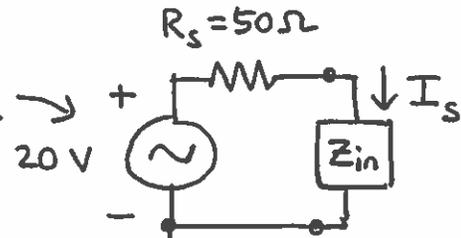
$$Z_{\text{in}} = Z_L = 150 + j200 \Omega$$



$$I_s = \frac{20 e^{j0}}{50 + 150 + j200} = \frac{1}{10(1+j)} \times \frac{1-j}{1-j} = \frac{1-j}{20} = \frac{\sqrt{2}}{20} e^{-j45^\circ} \text{ A}$$

$$P_L = P_{Z_{\text{in}}} = \frac{1}{2} |I_s|^2 R_{\text{in}} = \frac{1}{2} \left(\frac{\sqrt{2}}{20}\right)^2 (150) = \boxed{0.375 \text{ W}}$$

Since the line is lossless...

(d) (10 points) Find the first two V_{max} and the first two V_{min} positions nearest to the position of the load on this transmission line. Provide your answers in units of distance.

Since the load is inductive, V_{max} is closer to the load.


$$\phi_L + 2\beta z_{\text{max}_1} = 0 \rightarrow z_{\text{max}_1} = -\frac{\phi_L}{2\beta} \approx \frac{-0.322 \text{ rad}}{\frac{2\pi}{1.2}} \approx \boxed{-0.0307 \text{ m}} = -3.07 \text{ cm}$$

$$z_{\text{max}_2} = z_{\text{max}_1} - \frac{\lambda_{\text{air}}}{2} \approx -0.0307 - 0.6 = \boxed{-0.6307 \text{ m}}$$

$$z_{\text{min}_1} = z_{\text{max}_1} - \frac{\lambda_{\text{air}}}{4} \approx -0.0307 - 0.3 = \boxed{-0.3307 \text{ m}}$$

$$z_{\text{min}_2} = z_{\text{min}_1} - \frac{\lambda_{\text{air}}}{2} \approx \boxed{-0.9307 \text{ m}}$$

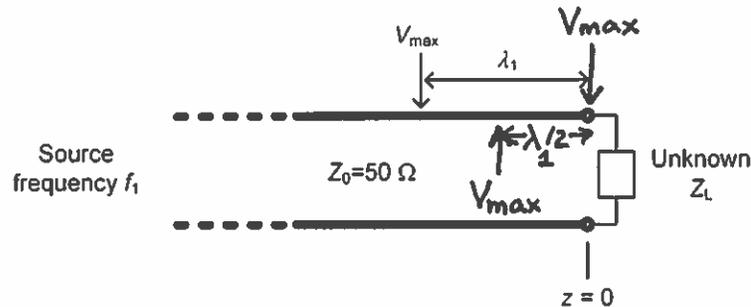- (3)(10 mins., 20 points) **Unknown load.** The standing wave ratio on a 50Ω transmission line excited at f_1 frequency and terminated with an unknown load Z_L is measured to be 5. If a voltage maximum position on the line is located at λ_1 distance away from the load position, determine the value of the load impedance Z_L . (Note that λ_1 is the wavelength at source frequency f_1 .)



$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \rightarrow |\Gamma_L| = \frac{S - 1}{S + 1} = \frac{5 - 1}{5 + 1} = \frac{2}{3}$$

If a voltage maximum position on the line is located at λ_1 distance away from the load, since V_{max} positions alternate every $\lambda_1/2$, the load position must also be a voltage maximum position. This means


$$\phi_L = 0 \rightarrow \therefore \Gamma_L = \frac{2}{3} e^{j0} = \frac{2}{3}$$

$$\text{Using } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow \frac{2}{3} = \frac{Z_L - 50}{Z_L + 50}$$

$$\rightarrow 2Z_L + 100 = 3Z_L - 150 \rightarrow Z_L = \boxed{250 \Omega}$$

As expected, I'm purely resistive and my value is greater than Z_0

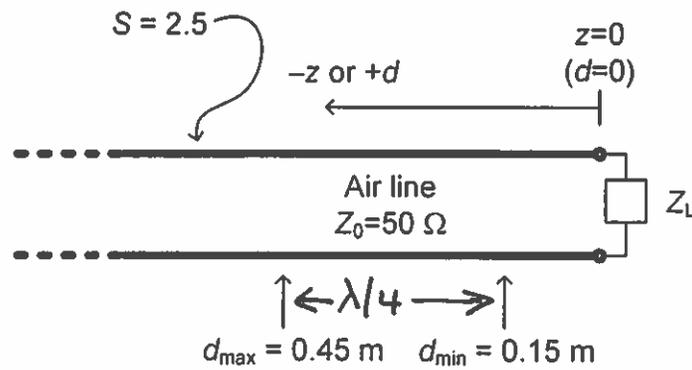- (4)(10 mins., 20 points) **Unknown load.** A 50Ω air transmission line with a standing wave ratio of $S = 2.5$ has its first voltage minimum and maximum positions on the line nearest to the load at 0.15 m and 0.45 m respectively. Calculate (a) the operating frequency f ; and (b) the load impedance Z_L .



$$(a) \quad \frac{\lambda_{\text{air}}}{4} = 0.45 - 0.15 = 0.3 \text{ m} \rightarrow \lambda_{\text{air}} = 1.2 \text{ m}$$

$$f = \frac{c}{\lambda_{\text{air}}} \approx \frac{3 \times 10^8 \text{ m} \cdot \text{s}^{-1}}{1.2 \text{ m}} = \boxed{250 \text{ MHz}}$$

$$(b) \quad S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \rightarrow |\Gamma_L| = \frac{S - 1}{S + 1} = \frac{2.5 - 1}{2.5 + 1} = \frac{3}{7}$$

$$\phi_L + 2\beta z_{\text{min}_1} = -\pi$$

I represent a capacitive load?

$$\rightarrow \phi_L = -\pi - 2\left(\frac{2\pi}{1.2}\right)(-0.15) = -\pi + \frac{\pi}{2} = -\frac{\pi}{2}$$

$$\therefore \Gamma_L = \frac{3}{7} e^{-j\frac{\pi}{2}} = -j\frac{3}{7}$$

$$\text{Using } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \rightarrow Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$\rightarrow Z_L = 50 \frac{1 - j\frac{3}{7}}{1 + j\frac{3}{7}} = 50 \frac{7 - j3}{7 + j3} \times \frac{7 - j3}{7 - j3}$$

$$= 50 \frac{40 - j42}{49 + 9} \approx \boxed{34.5 - j36.2 \Omega}$$

Indeed I'm capacitive!