

University of Portland School of Engineering

EE 301
Spring 2018
A. Inan

Homework # 3


(Assigned: Wednesday, February 7, 2018)
(Due: Friday, February 16, 2018, 11:25a.m.)

These problems are assigned from Engineering Electromagnetics and Waves (Second Edition, 2015) by Inan² Said (pages 80-98):

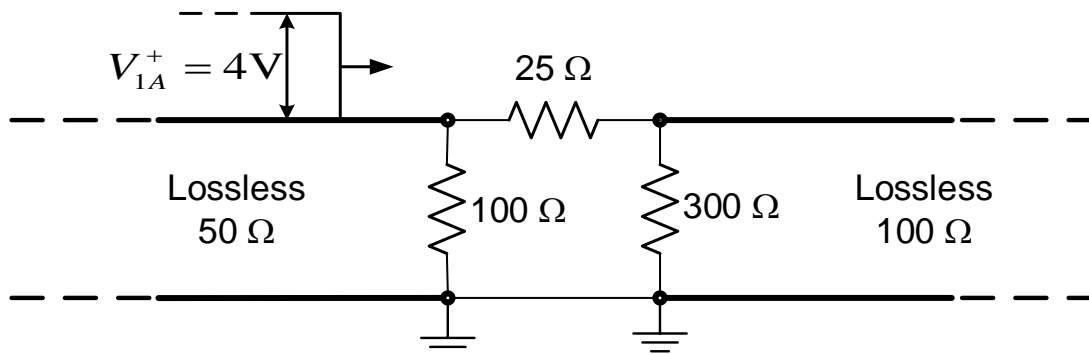- 2.13. Time-domain reflectometry (TDR).
- 2.15. Time-domain reflectometry (TDR).
- 2.19. Parallel multiple lines.
- 2.24. Digital IC interconnect.
- 2.25. Terminated IC interconnects.

Inan Problem # 1: Reflected & transmitted voltage waves.


Two lossless transmission lines A & B are connected via a lumped Π resistive network as shown.




If a step-type voltage wave $V_{1A}^+ = 4V$ traveling on the $50\ \Omega$ line is approaching towards the junction from the left side, find the reflected and transmitted voltage waves V_{1A}^- and V_{1B}^+ .

Inan Problem # 2: Reflected & transmitted voltage waves.

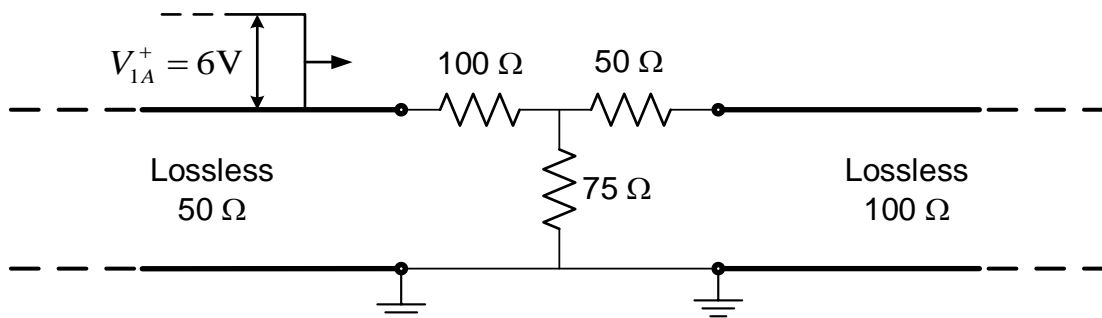(a) Two lossless transmission lines A & B are connected via a lumped T resistive network as shown.



- If a step-type voltage wave $V_{1A}^+ = 6\text{ V}$ traveling on the $50\ \Omega$ line is approaching towards the junction from the left side, find the reflected and transmitted voltage waves V_{1A}^- and V_{1B}^+ .
- (b) Repeat part (a) if the step-type voltage is approaching the junction from the right side, as shown. If the step-type voltage wave traveling on the $100\ \Omega$ line is given as $V_{1B}^- = 6\text{ V}$, find the reflected and transmitted voltage waves V_{1B}^+ and V_{1A}^- .

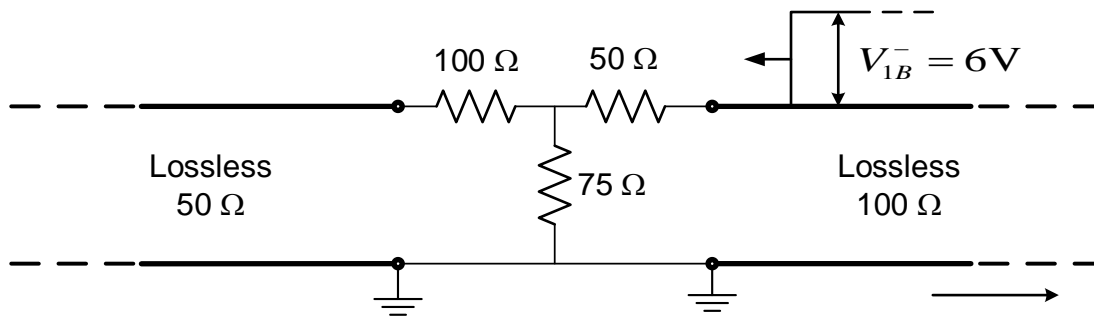

Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #3-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 301/Spring 2018 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.

Happy Double Consecutive *e* Days!
February 7, 2018 (2/7/18) & February 8, 2018 (2/8/18)
 $e \approx 2.7182818$