

University of Portland School of Engineering


EE 301
Spring 2018
A. Inan

Homework # 6

(Assigned: Monday, March 26, 2018)
(Due: Wednesday, April 4, 2018, 11:25a.m.)


Inan problem # 9: Sinusoidal Steady-State Waves on Transmission Lines.

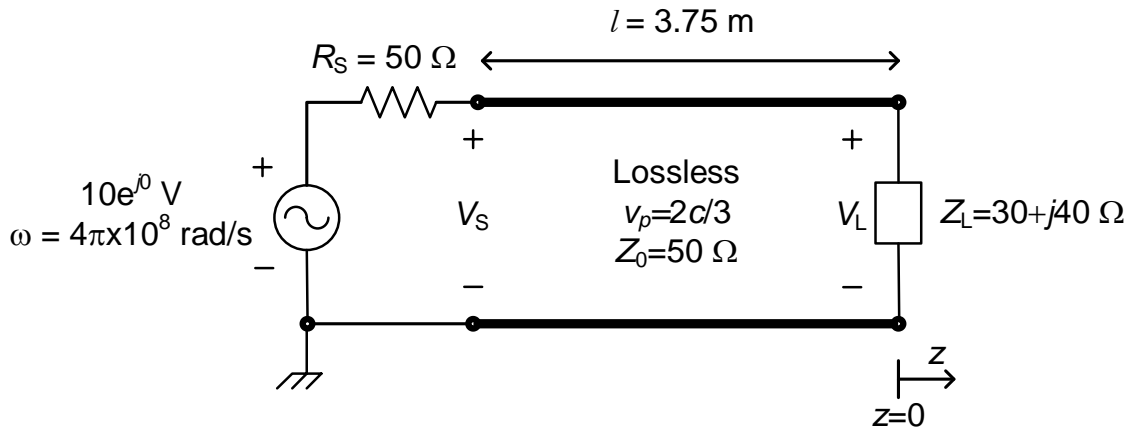For the uniform lossless 50Ω transmission line circuit shown, find : (a) the load reflection coefficient Γ_L ; (b) the standing wave ratio S ; (c) all the V_{\max} and V_{\min} positions (provided in a table); (d) the V_S and V_L phasor voltages; and (e) the time-average power P_L delivered to the load.




Inan problem # 10: Two lossless transmission lines.

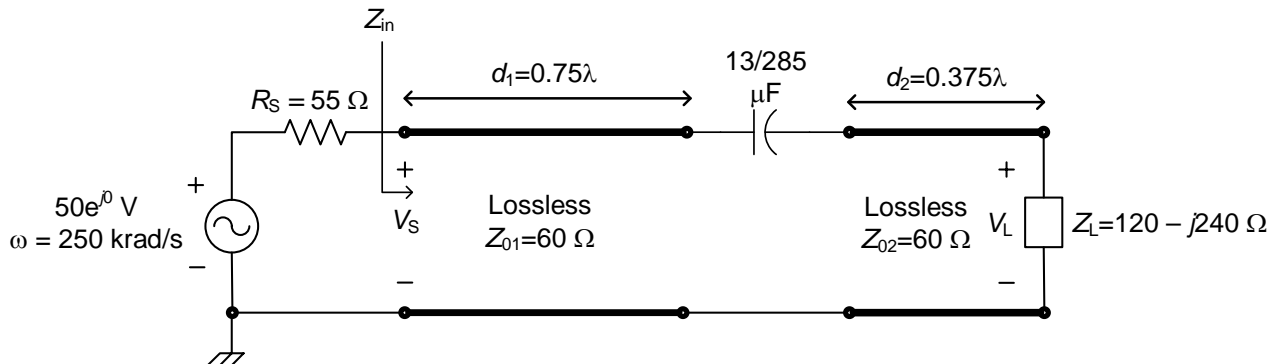For the double transmission line circuit shown, find (a) the standing wave ratio on each line (S_1 and S_2); (b) the input impedance Z_{in} ; and (c) time-average power P_L delivered to the load impedance Z_L .




Inan problem # 11: Two lossless transmission lines.

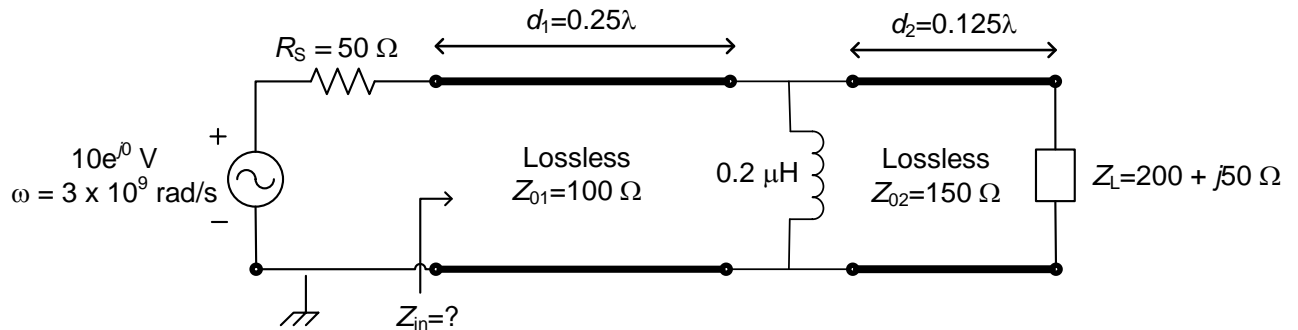Repeat Inan problem # 10 for the transmission line circuit shown.



Inan problem # 12: Unknown load.

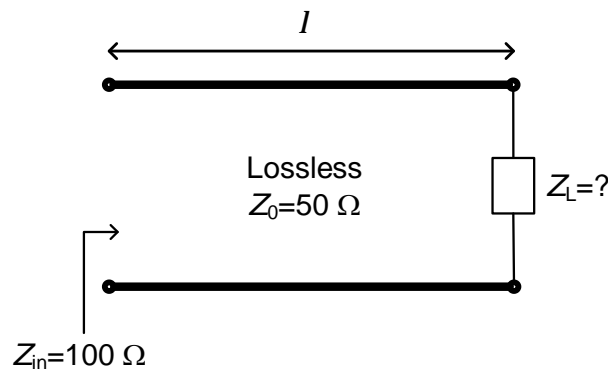For the 50 Ω lossless transmission line shown, find the unknown load impedance Z_L for the following cases: (a) $l = 0.25\lambda$; (b) $l = 0.375\lambda$; (c) $l = 0.5\lambda$; and (d) $l = 1.75\lambda$.



Please use the following guidelines for your homework solutions:

- 1) On the first sheet, at the top center, write: Homework #6-Solutions.
- 2) Provide your full name on the upper right corner of the first sheet.
- 3) Also write: EE 301/Spring 2018 on the upper left corner of the first sheet.
- 4) Solve each problem on a separate sheet unless your solution is very short.
- 5) Box all of your answers.
- 6) Staple your solutions in the above order before you turn them in.

Please turn in your homework on time.