

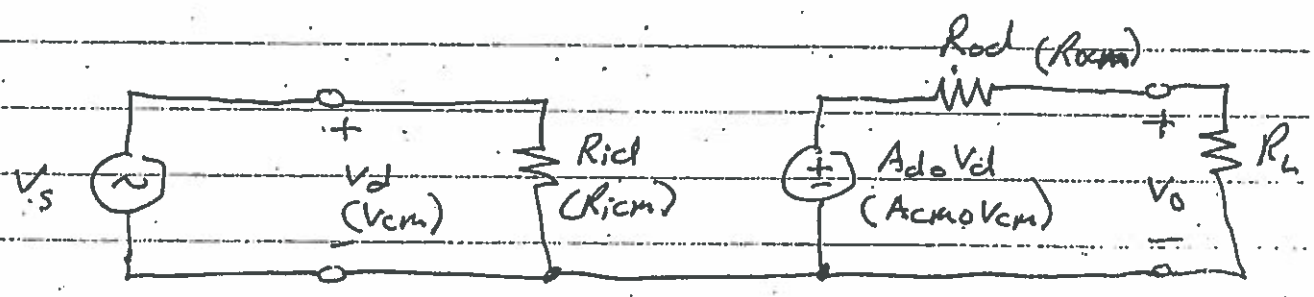
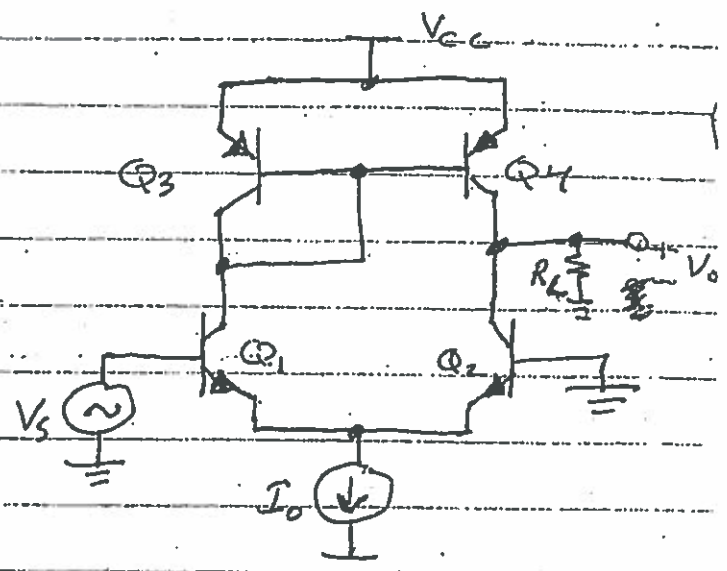
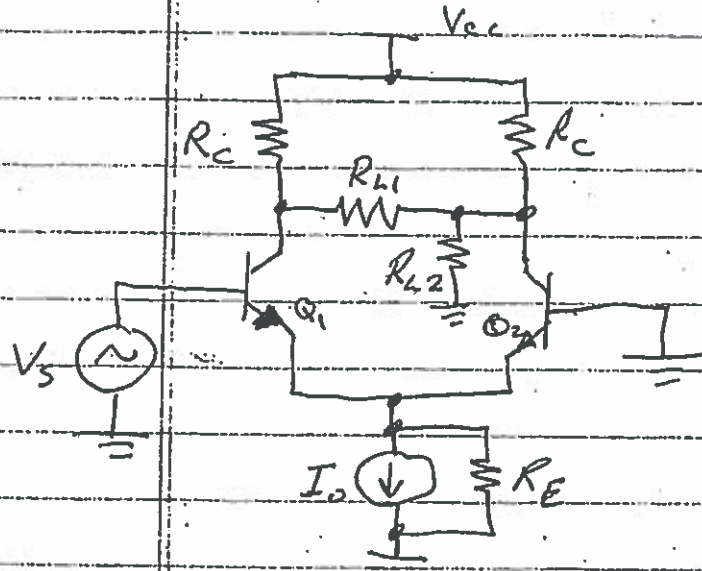


EE352
 BJT Diff Amp Summary

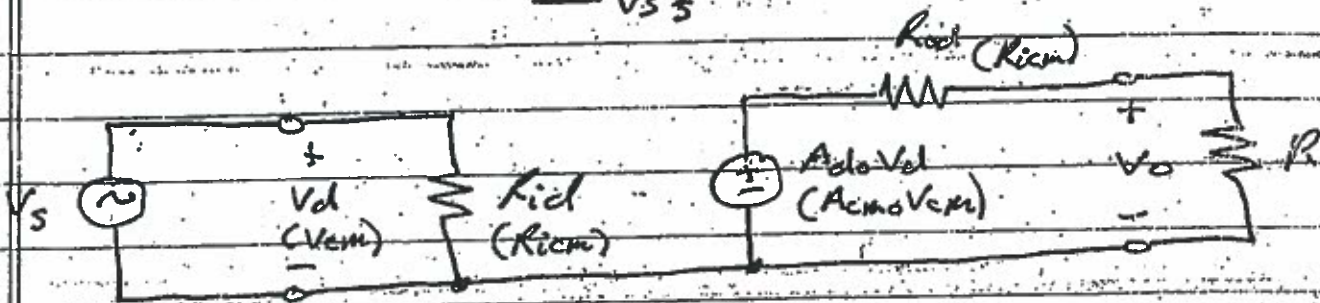

	P/L DOM ($R_{L2} = \infty$)	P/L SEOM ($R_{L1} = \infty$)	A/L SEOM
A_{do}	$-\frac{g_m}{2} R_{od}$	$+\frac{g_m}{2} R_{od}$	$+g_m R_{od}$
A_d	$-\frac{g_m}{2} [R_{od} R_{L1}]$	$+\frac{g_m}{2} [R_{od} R_{L2}]$	$+g_m [R_{od} R_L]$
R_{icl}	$2r_{\pi}$	$2r_{\pi}$	$2r_{\pi}$
R_{od}	$2R_c$	R_c	$r_{o2} r_{o4}$
A_{cmo}	0	$-\frac{\alpha R_{ocm}}{2R_E}$	0
A_{cm}	0	$-\frac{\alpha [R_{ocm} R_{L2}]}{2R_E}$	0
R_{icm}	$R_E(1+\beta)$	$R_E(1+\beta)$	N/A $R_E(1+\beta)$
R_{ocm}	$2R_c$	R_c	N/A $r_{o2} r_{o4}$
CMRR	∞	$20 \log \left[\frac{g_m R_E}{\alpha} \right]$	∞
R_E	V_A / I_0	V_A / I_0	N/A V_A / I_0

MOS Diff Amp Summary

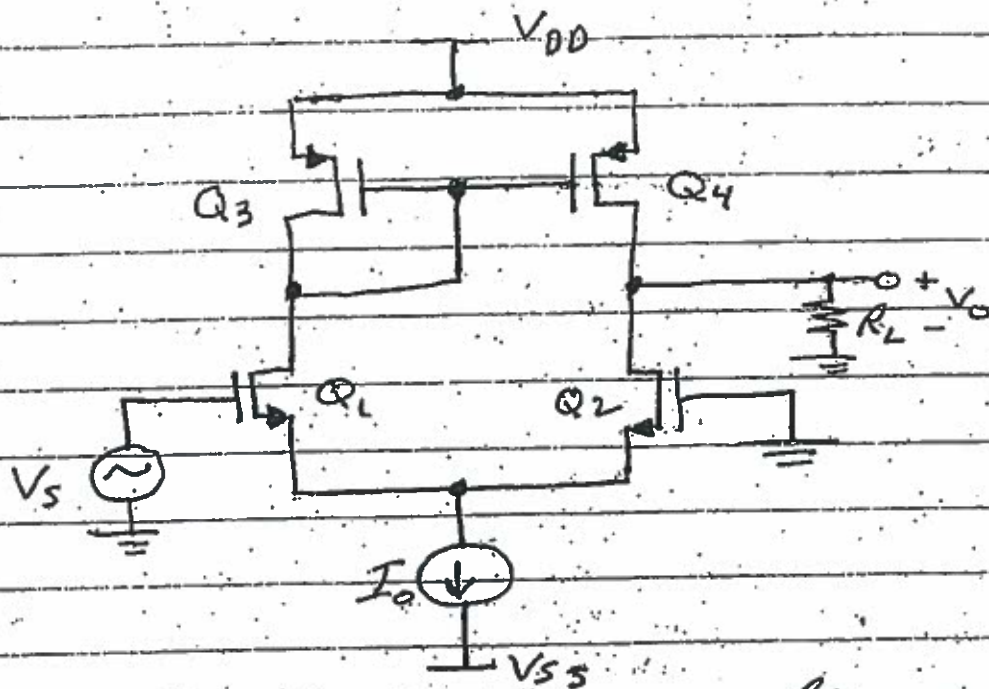

	A/L SEOM
A_{do}	$+g_m R_{od}$
A_d	$+g_m [R_{od} \parallel R_L]$
R_{id}	∞
R_{od}	$r_{o2} \parallel r_{o4}$
A_{cmo}	0
A_{cm}	0
R_{icm}	N/A ∞
R_{ocm}	N/A $r_{o2} \parallel r_{o4}$
CMRR	∞
R_E	N/A $1/I_0$