
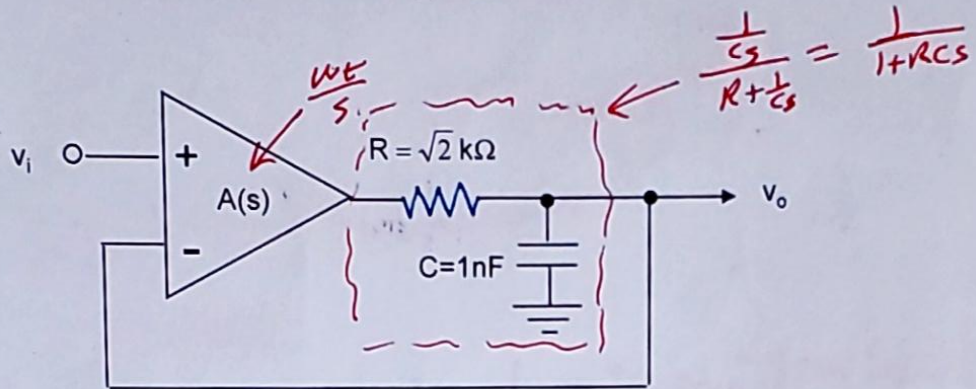


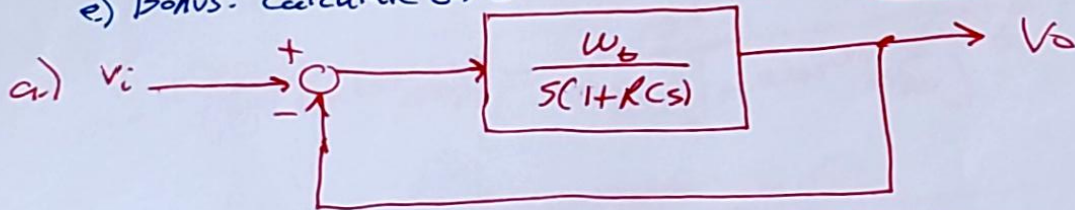Problem 1 (50 points):

Consider the following closed-loop negative feedback opamp circuit. Assume the opamp has an open-loop transfer function, $A(s) \approx \omega_p/s = 10^6/s$.



- Sketch the equivalent classic negative feedback block diagram of this closed-loop system.
- Calculate the closed-loop transfer function, $A_f(s) = V_o/V_i(s)$.
- Calculate the Loop Gain, $LG(s)$.
- Calculate ω_1 and the PM.
- Bonus: Calculate GM.



b.)
$$A_f(s) = \frac{\frac{\omega_p}{s(1+RCs)}}{1 + \frac{\omega_p}{s(1+RCs)}} = \frac{1}{\sqrt{2} \times 10^{-6} s^2 + 10^{-6} s + 1}$$

c.)
$$LG(s) = \frac{\omega_p}{s(1+RCs)} = \frac{10^6}{s(1 + \sqrt{2} \times 10^{-6} s)}$$

d.)
$$PM = 180^\circ - |LG(j\omega)|$$

$$\angle LG(j\omega) = -90^\circ - \tan^{-1}(\sqrt{2} \times 10^{-6} \omega)$$

$$|LG(j\omega)| = 1 = \frac{10^6}{\omega \sqrt{1 + 2 \times 10^{-12} \omega^2}} \Rightarrow \omega_1 = \frac{\sqrt{2}}{2} \times 10^6 \text{ rad/sec}$$

$$\Rightarrow \angle LG(j\omega) = -90^\circ - \tan^{-1}(1) = -135^\circ \Rightarrow PM = 45^\circ$$

e.) Bonus: Calculate GM

$$GM = 20 \log \left[\frac{1}{|LG(j\omega_{180})|} \right]$$

~~$|LG(j\omega_{180})| = 180$~~

~~$LG(j\omega_{180})$~~

$$|*LG(j\omega_{180})| = 180 = |-90^\circ - \tan^{-1}(\sqrt{2} \times 10^6 \omega_{180})|$$

$$\tan^{-1}(\sqrt{2} \times 10^6 \omega_{180}) = 180^\circ - 90^\circ = 90^\circ$$

$$\sqrt{2} \times 10^6 \omega_{180} = \tan 90^\circ = \infty$$

$$\boxed{\therefore \omega_{180} = \infty}$$


$$|LG(j\omega_{180})| = \frac{10^6}{\omega_{180} [1 + 2 \times 10^{-12} \omega_{180}^2]^{1/2}}$$

~~180~~ = 0

$$\boxed{\therefore GM = 20 \log \left[\frac{1}{\infty} \right] = \infty \text{ dB}}$$

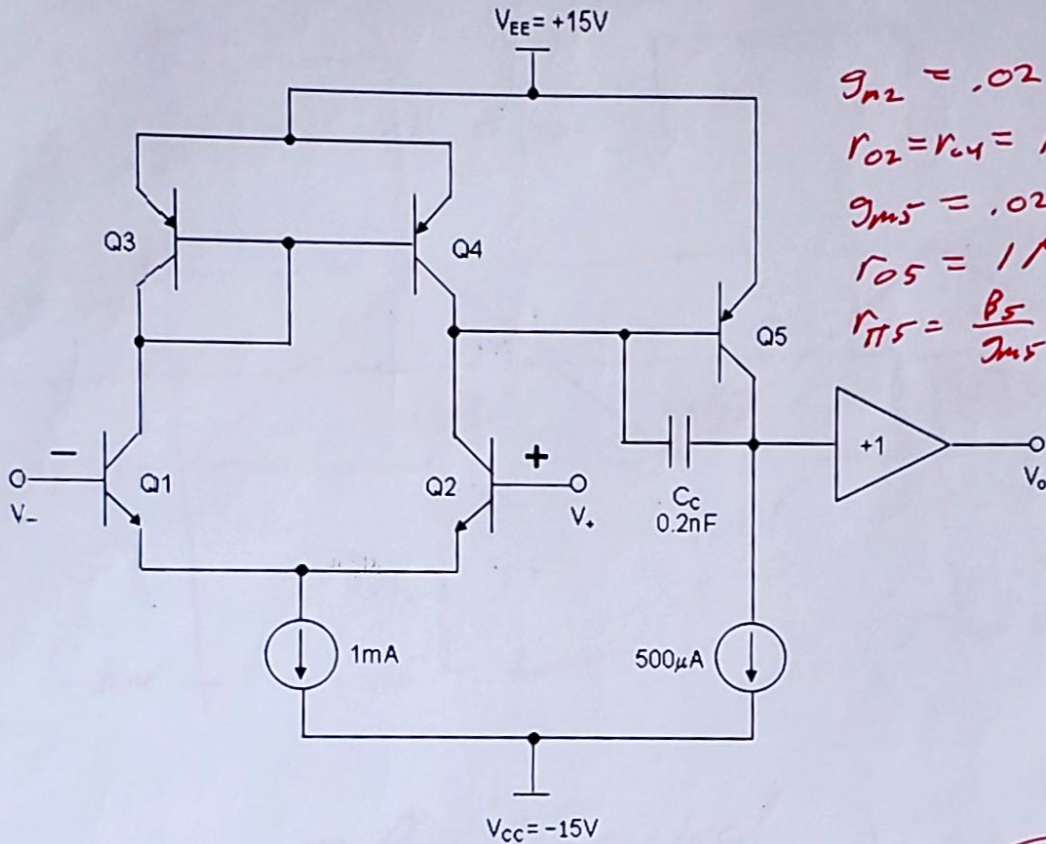Problem 2 (50 points)

Consider the following open-loop opamp circuit. Assume the unity-gain output buffer is ideal. Assume $V_T=25\text{mV}$, $\beta_n=\beta_p=100$ and $V_{An}=V_{Ap}=500\text{V}$. You may make reasonable approximations, as usual.



Handwritten notes:

$$g_{m2} = .02 \text{ A/V}$$

$$r_{o2} = r_{o4} = 1 \text{ M}\Omega$$

$$g_{m5} = .02 \text{ A/V}$$


$$r_{o5} = 1 \text{ M}\Omega$$

$$r_{\pi5} = \frac{\beta_5}{g_{m5}} = 5 \text{ k}\Omega$$

- Calculate A_o of the opamp. $\Rightarrow A_o = g_{m2} [r_{o2} || r_{o4} || r_{\pi5}] g_{m5} r_{o5} = 2 \times 10^6 \text{ V/V}$
- Calculate ω_H of the opamp. $\Rightarrow \omega_H = \frac{g_{m5} r_{o5}}{(g_{m5} r_{o5}) [r_{o2} || r_{o4} || r_{\pi5}] C_c} = 50 \text{ rad/sec}$
- Calculate ω_t of the opamp. $\Rightarrow \omega_t = A_o \omega_H = g_{m2} / C_c = 10^8 \text{ rad/sec}$
- Calculate the SR of the opamp. $\Rightarrow \text{SR} = \frac{I_{o1}}{C_c} = 5 \text{ V}/\mu\text{s}$
- Now, connect the opamp in its unity-gain configuration. Determine the closed-loop transfer function, $A_f(s)$. (Please assume $A(s) \approx \omega_t/s$). $A_f(s) = \frac{1}{1 + s/\omega_t} = \frac{1}{1 + s/10^8}$
- For the circuit in Part e), if $v_i(t)$ is a square wave of amplitude $\pm 10\text{V}$ and frequency 500kHz , qualitatively sketch and annotate the output voltage, $v_o(t)$. (Hint: $v_o(t)$ will be Slew Rate limited and have no dc offset).

See Next Page

f.)

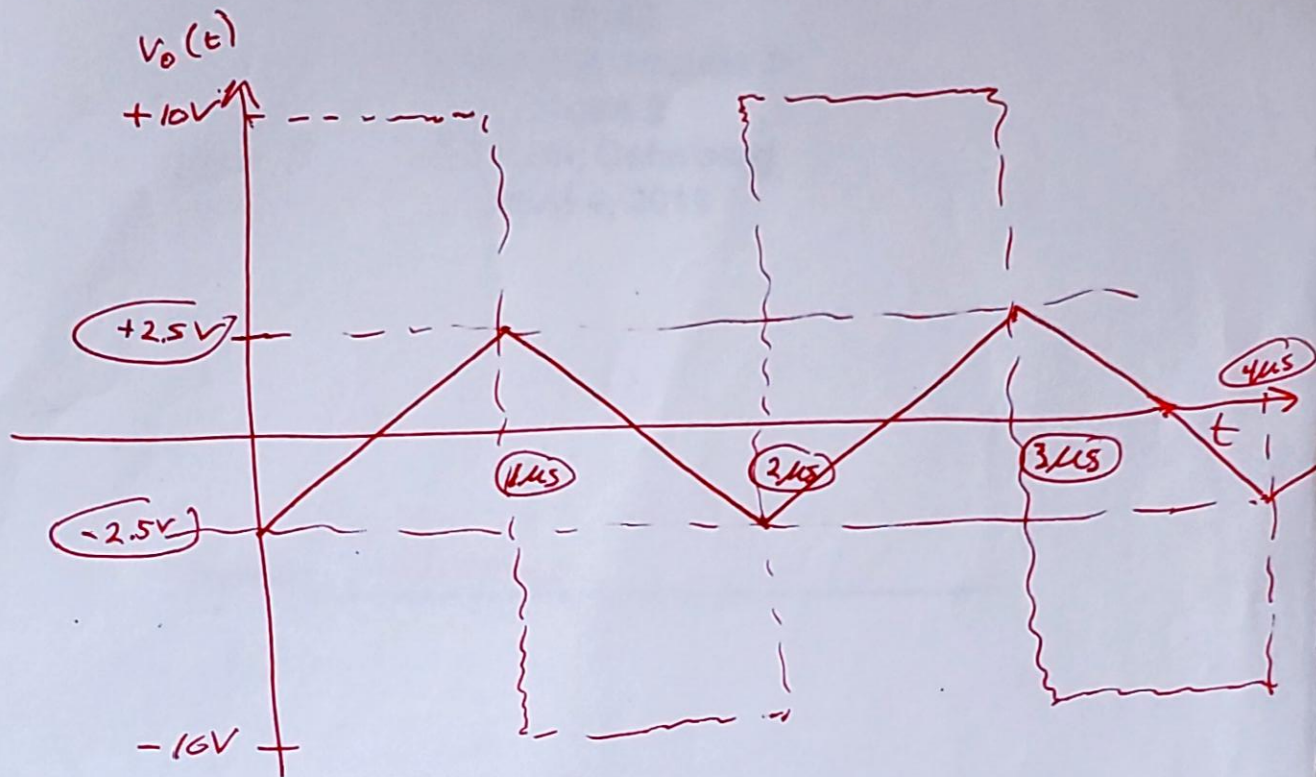

S_R-Limited

$$S_R = \left. \frac{dv_o}{dt} \right|_{\max} = 5 \text{ V}/\mu\text{s}$$