
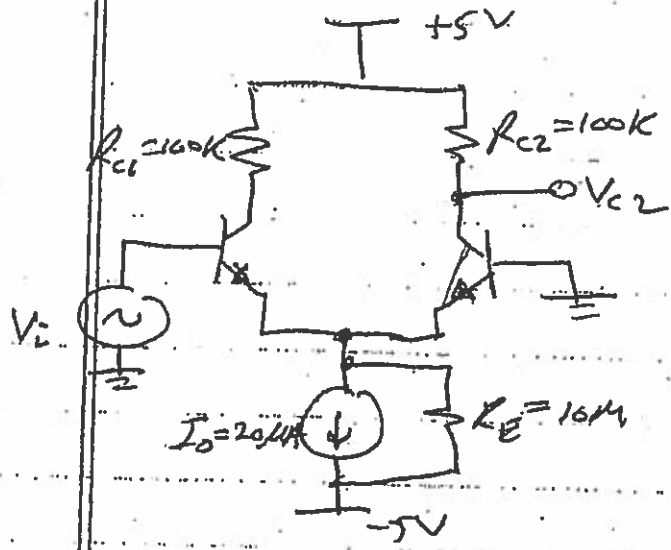


EE 352 HW1 Solutions

1- SEOM - Case
"D:SS Config"

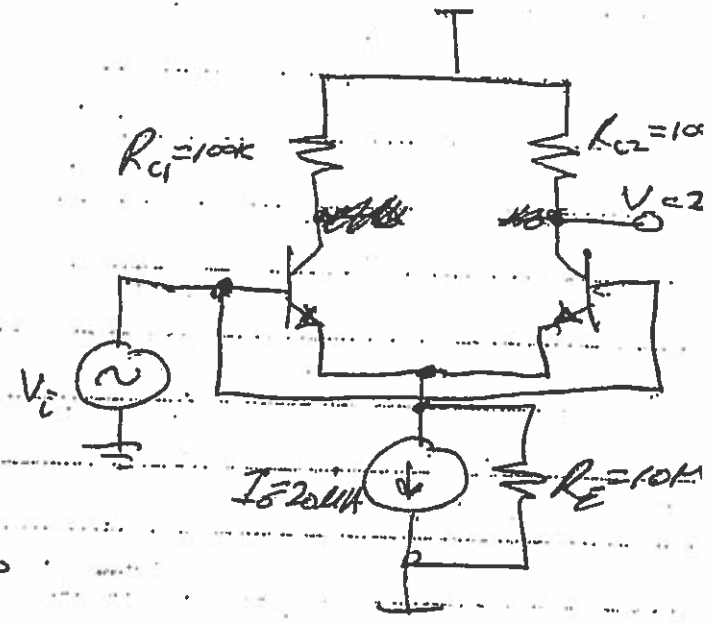

SEOM Case
"CM Config"



$\beta = 100$

$R_B = 0$

$g_m = \frac{I_0/2}{R_T/2} = 4 \text{ mS}$

$r_\pi = \frac{\beta}{g_m} = 250 \text{ k}$

From your Class Notes:

$A_d = \frac{g_m R_c}{2} = 20$

$A_{cm} = -\frac{2R_c}{2R_E} = -0.05$

$R_{id} = 2r_\pi = 500 \text{ k}$


$R_{icm} = R_E(1+\beta) = 1010 \text{ k}$

$R_{od} = R_c = 100 \text{ k}$

$R_{ocm} = R_c = 100 \text{ k}$

$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| = 72 \text{ dB}$

2 See PSpice output files

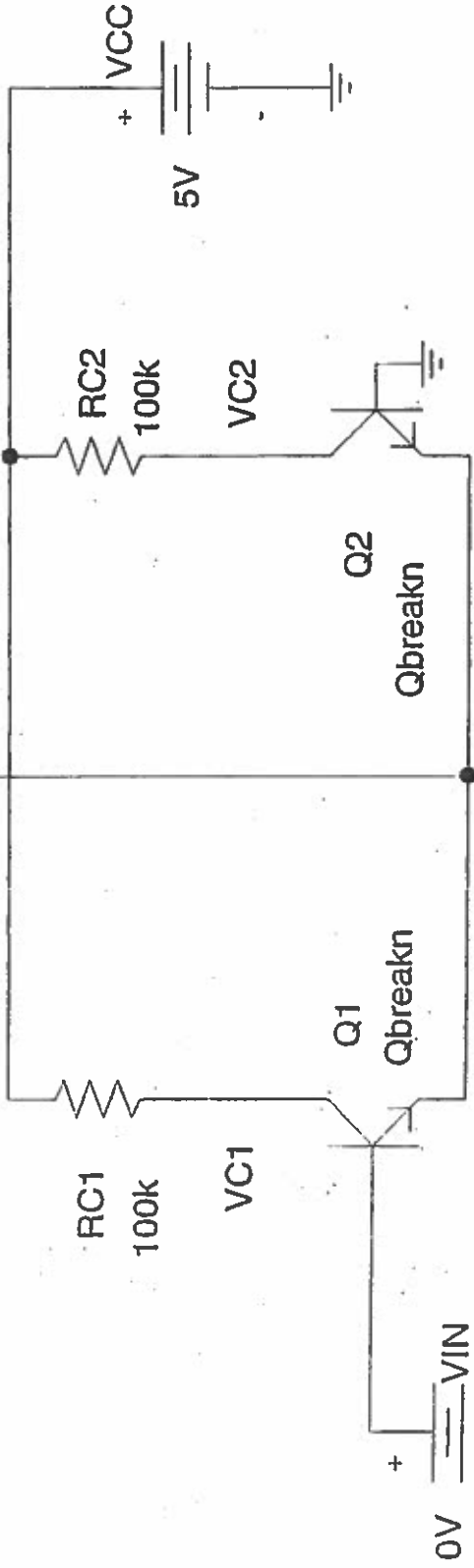

PS PKE Schematic

~~XXXXXXXXXX~~
~~XXXXXXXXXX~~

SKOM case

"Disg carbis"

```

****      CIRCUIT DESCRIPTION
*****
* Schematics Version 9.1 - Web Update 1
* Mon Jan 21 10:50:56 2019
** Analysis setup **
.TF V([VC2]) V_VIN
.OP
.LIB hwl.lib"
V_VCC      $N_0001 0 5V
V_VIN      $N_0002 0 0V
V_VEE      $N_0003 0 -5V
Q_Q1       VC1 $N_0002 VE Qbreakn
R_RC1      VC1 $N_0001 100k
R_RC2      VC2 $N_0001 100k
I_I        VE $N_0003 DC 20uA
Q_Q2       VC2 0 VE Qbreakn
.probe
.END

```

*PSPICE
xxx.out file
SEOM Case
"Diff Config"*

```

****      BJT MODEL PARAMETERS
          Qbreakn
          NPN
BF 100

```

```

****      SMALL SIGNAL BIAS SOLUTION      TEMPERATURE = 27.000 DEG C
*****
NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE NODE VOLTAGE
(VE) -.6548 (VC1) 4.0099 (VC2) 4.0099
($N_0001) 5.0000 ($N_0002) 0.0000 ($N_0003) -5.0000

```

```

****      BIPOLAR JUNCTION TRANSISTORS
NAME      Q_Q1      Q_Q2
MODEL     Qbreakn  Qbreakn
IB        9.90E-08  9.90E-08
IC        9.90E-06  9.90E-06 ← Hand = 10 uA
VBE       6.55E-01  6.55E-01
VBC       -4.01E+00 -4.01E+00
VCE       4.66E+00  4.66E+00
BETADC    1.00E+02  1.00E+02
GM        3.83E-04  3.83E-04 ← Hand = 0.4 mA/V
RPI       2.61E+05  2.61E+05 ← Hand = 250 kΩ
RO        1.00E+12  1.00E+12


```

```

****      SMALL-SIGNAL CHARACTERISTICS
V(VC2)/V_VIN = 1.914E+01 ← Hand Ad = 20V/V
INPUT RESISTANCE AT V_VIN = 5.225E+05 ← Hand Rid = 500kΩ
OUTPUT RESISTANCE AT V(VC2) = 1.000E+05 ← Hand Rod = 100kΩ

```

All values compare favorably !!

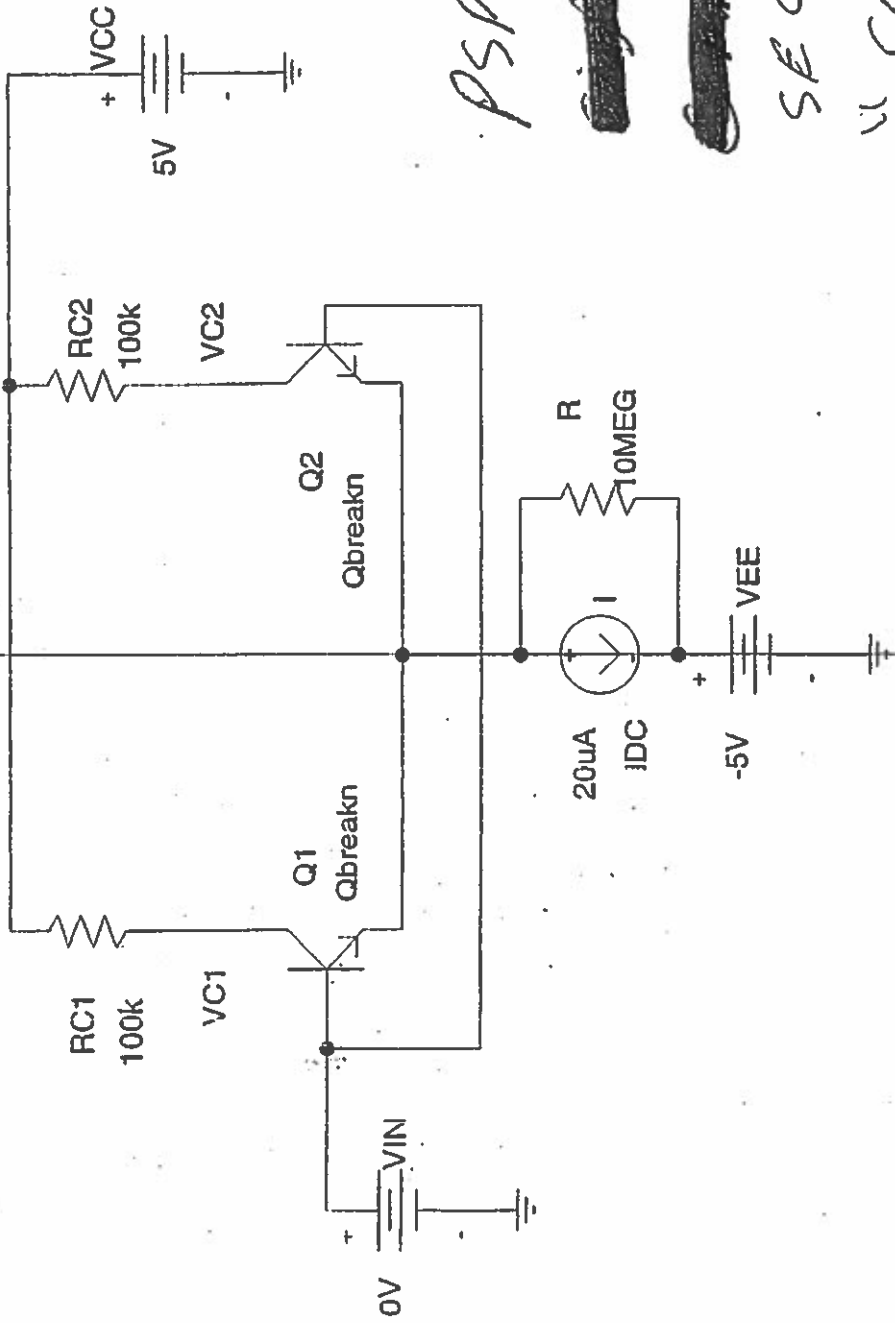

PSPICE Schematic

~~XXXXXXXXXX~~

~~XXXXXXXXXX~~

SEE OHM CASE

“CM Config”


```

  *****
  * Schematics Version 6.2 - April 1995
  * Fri Jan 28 11:01:52 2000
  ** Analysis setup **
  .TF V([VC2]) V_VIN
  .OP
  .LIB hw1.lib
  R_RC1      VC1 $N_0001 100k
  R_RC2      VC2 $N_0001 100k
  V_VCC      $N_0001 0 5V
  I_I        $N_0002 $N_0003 DC 20uA
  V_VIN      $N_0004 0 0V
  V_VEE      $N_0003 0 -5V
  R_R        $N_0003 $N_0002 10MEG
  Q_Q1       VC1 $N_0004 $N_0002 QbreakN
  Q_Q2       VC2 $N_0004 $N_0002 QbreakN
  .probe
  .END
  
```

PSPICE
 txt. out
 file
 SECM case
 "CM config"

**** BJT MODEL PARAMETERS *****

```

  QbreakN
  NPN
  BF 100
  RB 0
  
```

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C *****

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(VC1)	3.9884	(VC2)	3.9884	(\$N_0001)	5.0000		
(\$N_0002)	-0.6554			(\$N_0003)	-5.0000		
(\$N_0004)	0.0000						

**** BIPOLAR JUNCTION TRANSISTORS

NAME	Q_Q1	Q_Q2
MODEL	QbreakN	QbreakN
IB	1.01E-07	1.01E-07
IC	1.01E-05	1.01E-05
VBE	6.55E-01	6.55E-01
VBC	-3.99E+00	-3.99E+00
VCE	4.64E+00	4.64E+00
BETADC	1.00E+02	1.00E+02
GM	3.91E-04	3.91E-04
RPI	2.56E+05	2.56E+05
RX	0.00E+00	0.00E+00
RO	1.00E+12	1.00E+12
CBE	0.00E+00	0.00E+00
CBC	0.00E+00	0.00E+00
CBX	0.00E+00	0.00E+00
CJS	0.00E+00	0.00E+00
BETAAC	1.00E+02	1.00E+02
FT	6.22E+15	6.22E+15

Hand = 10 uA ✓
 Hand = 0.4 mA/V ✓
 Hand = 250 kΩ ✓

**** SMALL-SIGNAL CHARACTERISTICS

V(VC2)/V_VIN = -4.950E-03
 INPUT RESISTANCE AT V_VIN = 1.008E+09
 OUTPUT RESISTANCE AT V(VC2) = 1.000E+05

A_{cm} Hand = -0.005 V/V ✓
 R_{icm} Hand = 1010 MΩ ✓
 R_{ocm} Hand = 100K ✓

All values compare favorably !!

$CMRR = 20 \log |A_d| = 71.9 \text{ dB } \checkmark$